

276

276

8

-: HAND WRITTEN NOTES:-

OF

④

ELECTRICAL ENGINEERING

-: SUBJECT:-

ANALOG ELECTRONICS

2

Topic →

1) Semi conductor physics. ③

2) P N jⁿ diode.

Special diodes

✓ Zener diode

✓ Tunnel diode

→ Schottky diode

→ Photo diode

Applications →

- Rectifiers

- filters

Diode CKTs →

- Ideal diode problems.

- Practical diode problems

- clippers

- clampers.

BIT -

- BIT device analysis

- BIT biasing (DC)

Analog CKTs -

- Small signal analysis

- low freq Analysis

- High freq Analysis

- freq response of an amplifier.

- large signal Amplifiers. (power amplifiers)

- multistage amplifiers

Feedback -

- Feedback amplifiers

- Oscillators

BET / MOSFET :-

- Fet biasing
- Small signal analysis
- low freq analysis
- High freq analysis

④

Problems.

OP - Amps -

- Differential amplifiers.
- Op amp applications.
- 555 timer.
- Active filters


Semi conductor physics

Introduction : →

$1s^2 2s^2 2p^6$


Cu - 29

(3)

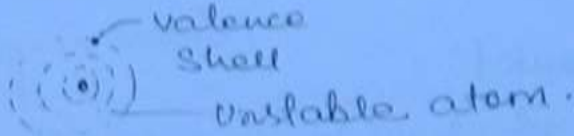

Mg - $1s^2 2s^2 2p^6 3s^2$

Conductors.

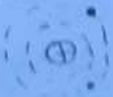

Al - 13



t - 10

f - 14.

Q: The max no. of e^- that can be filled in the valence shell of an atom will be

a) $4e^-$, b) $6e^-$ c) $18e^-$ d) None [8e-]

Ans: Acc. to Aufbau principle, s, p, d, s, p

Si - 14

Ge - 32



$T = 0K \rightarrow$ Insulators
 $T \neq 0K \rightarrow$ conductors } \rightarrow s.c.

As - 33



Br - 35



Ne - 10

$1s^2 2s^2 2p^6$



Stable atom

Insulators

∴ the no. of e⁻ that can be fixed in the valence shell of a semiconductor will be —

$$\frac{4}{3} \pi \cdot 4 e^-$$


6

Examples of Semiconductors :-

Si, Ge, GaAs [Gallium Arsenic]
Single crystalline compound
Semi conductors

Q. Why Si and Ge are generally preferred compare to Gallium Arsenide (~~GA~~ GaAs)?

44

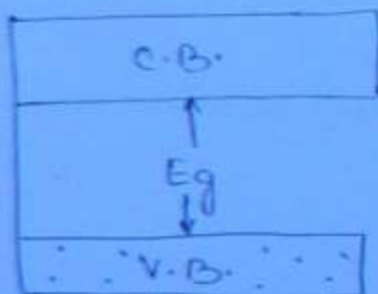

c.b. \rightarrow conduction band

$Eg \rightarrow en. \text{zap}$

V.B. \rightarrow Valence band.

* At $t=0$ K.,


Ego

$$I_{se} = 0.785 \text{ eV}$$
 $\delta_i = 1.2 \text{ eV}$

GeAs - 1.58 eV

As the en. gap value for Silicon and Germanium is less compare to galli GaAs, we expect more conduction is possible in case of Silicon and Germanium.

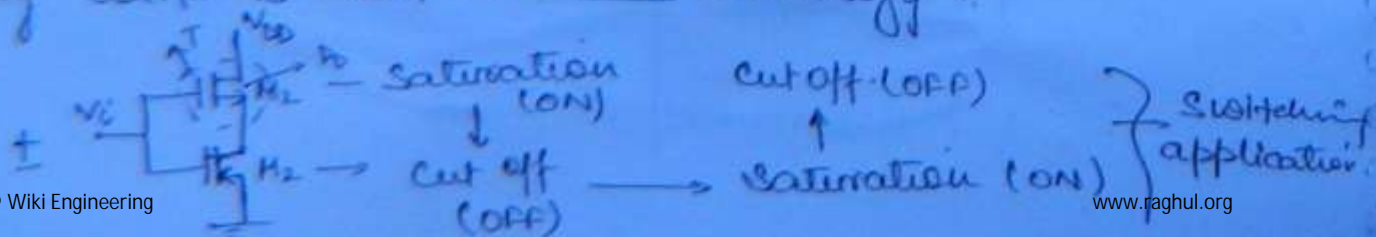2. Why GaAs is used in 'CMOS' technology?



movement of carrier (majority) is called mobility. -

1) The mobility of charge ^(μ) carriers in case of GaAs > Si and Ge. (7)

2) The temp with standing capability is more for GaAs (E_g is more)

→ Typical Values of temp. for which the device can withstand with: -

Ge → 100°C

Si → 200°C

GaAs > 200°C

Q. Why $\mu_e > \mu_h$

$\mu \rightarrow$ mobility


a) The traffic level in CB < in V.B.

b) The traffic level in CB > VB

c) The traffic level in CB = VB


d) None

Ans.

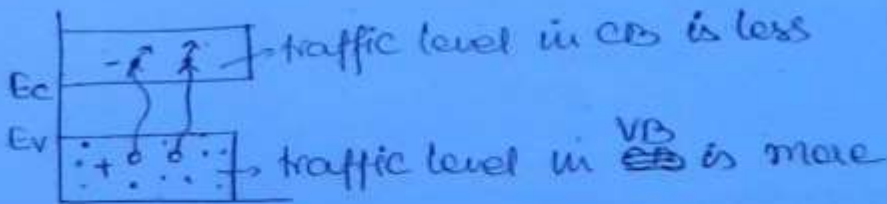

2nd reason, When things are in motion

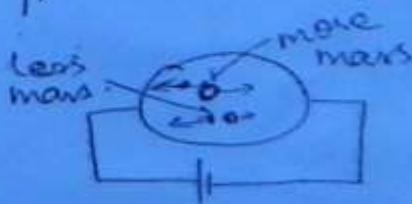The effective mass of a hole is always greater than effective mass of an e^- .




Traffic level is more in Ge, Si compare to GaAs.
mobility of Ge, Si < mobility of GaAs.

Atomic structure of an atom :-

(8)

Q. What is the relation b/w E_1, E_2, E_3 .

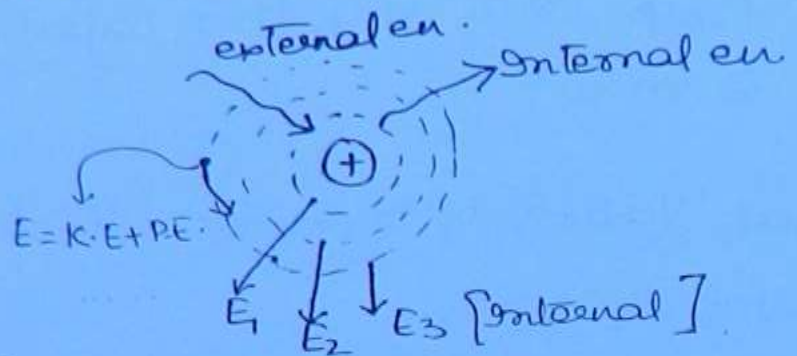- a) $E_1 < E_2 < E_3$
- b) $E_1 > E_2 > E_3$
- c) $E_1 = E_2 = E_3$
- d) none.



Ans. E_1, E_2 and E_3 are internal orbit energies.

Int. en.

$E_n \rightarrow e^-$ revolving around the ~~nucleus~~ ^{nucleus}

$$= \frac{-13.56}{n^2} \text{ eV}$$

$$E_1 = \frac{-13.56}{1^2} = -13.56 \text{ eV}$$

$$E_2 = \frac{-13.56}{2^2} = -3.5 \text{ eV}$$

⋮

$$E_\infty = \frac{-13.56}{\infty^2} = 0 \text{ eV.}$$

$n = \infty$	-----	0 eV
$n = 3$	-----	-1.5 eV
$n = 2$	-----	-3.5 eV
$n = 1$	-----	-13.56 eV

en. diagram for an isolated atom

* The balance cell of an atom will have the highest en. level.

(9)

Ions →

There are two types of ions :-

- 1) +ve ions
- 2) -ve ions

+ve ions →

When the atom loses an e^- , the atom is characterised as +ve ion.

-ve ion :-


When the atom gains an e^- , the atom is characterised as -ve ion.

NOTE -


Ions are indirectly atoms which are immobile in nature.

Energy band diagram concept :-

Ex:- Si material

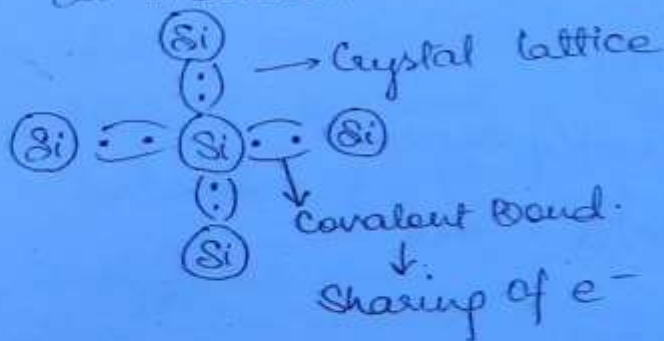

Interatomic Spacing
(ooo)

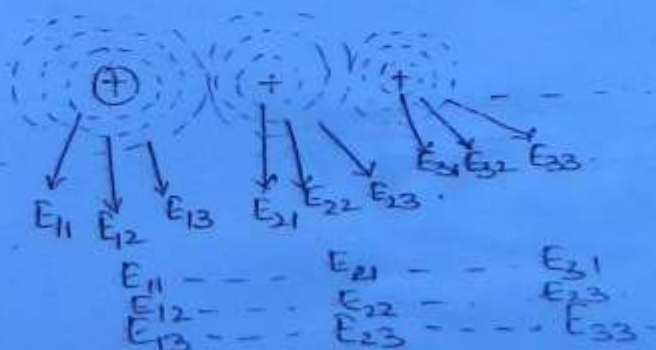

ignore E_{11}, E_{21}, E_{31}

E_{12}, E_{22}, E_{32}



because outer levels interact with each other.

conclusions: -

- 1) The above en. diagram is valid for isolated atoms.
- 2) This type of diagram is not valid for material concept because the interatomic spacing b/w the atoms is very less.


(10)

Si = 14.


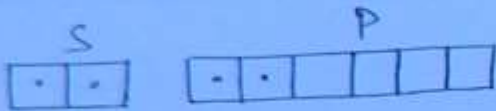
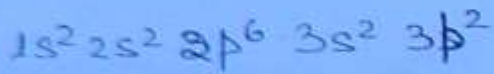


2N States $\rightarrow 2N e^-$
(S Shell)

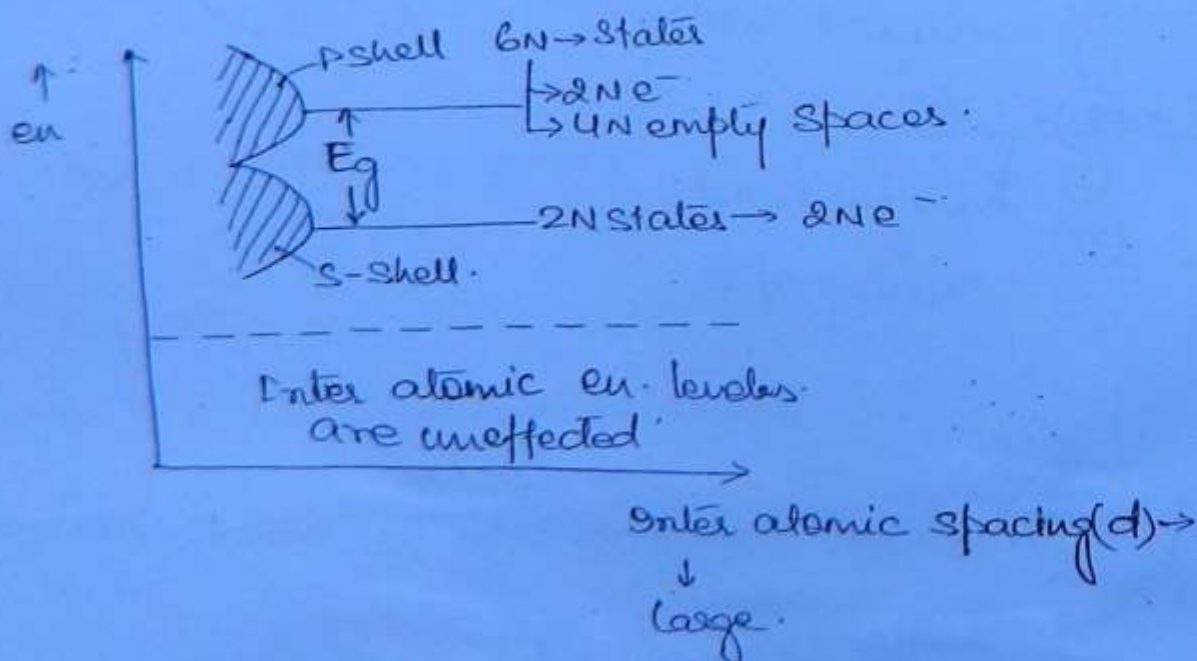6N States $\left\{ \begin{array}{l} 2N e^- \\ 4N \text{ empty states} \end{array} \right.$
(P Shell)



(11)

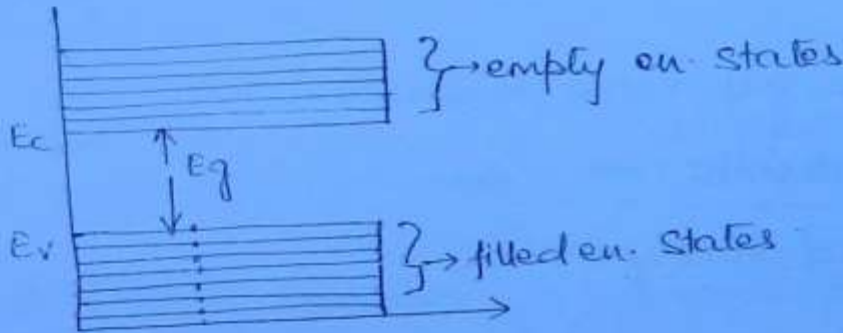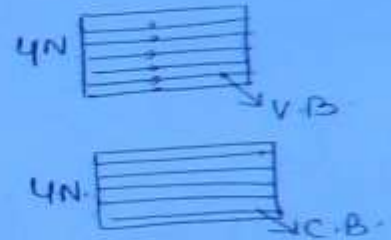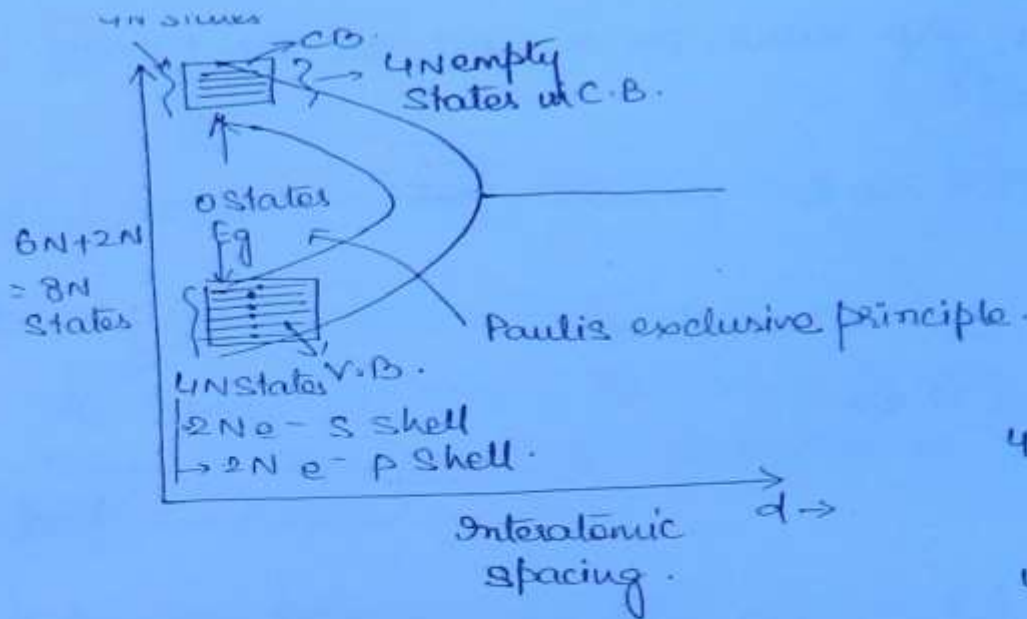

$E_c \rightarrow$ lowest en. level in C.B.
 $E_v \rightarrow$ highest en. level in V.B.
 $E_g \rightarrow$ forbidden gap or en. gap.

energy gap vs temp :-

$$* E_g (\text{at any temp in } K) = E_{g0} - \beta T$$

\downarrow
 en. gap at any temp in
 K .

\downarrow
 en. gap
 at $0K$.

$\beta \rightarrow$ const for a material

$Gc - 0.78 \text{ eV}$
 $\& - 1.21 \text{ eV}$

$\beta (Si) = 3.6 \times 10^{-4}$
 $\beta (Ge) = 2.23 \times 10^{-4}$

$T \rightarrow$ temp in K .

Q. Cal. the en. gap value for Si and Ge at room temp. $[T = 27^\circ\text{C}]$

(12)

Ans. $T = 273 + 27 = 300\text{ K}$.

$$\begin{aligned} \text{Si} \\ E_g(300\text{K}) &= 1.21 - 3.6 \times 10^{-4} \times 300 \\ &= 1.12\text{ eV} \end{aligned}$$


$$\begin{aligned} \text{Ge} \\ E_g(300\text{K}) &= 0.785 - 2.23 \times 10^{-4} \times 300 \\ &= 0.72\text{ eV} \end{aligned}$$

NOTE \rightarrow


As temp increases, en. gap value decreases.

Classification of materials \rightarrow


- Based on en. band theory.

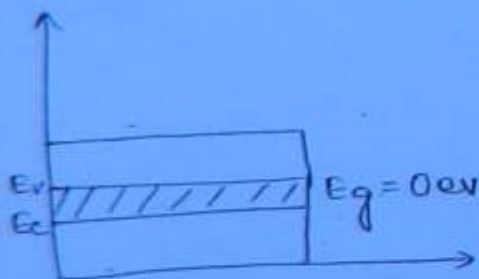

Conductor.

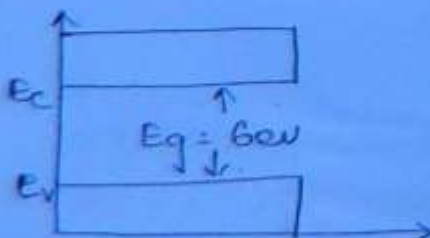


Insulator.

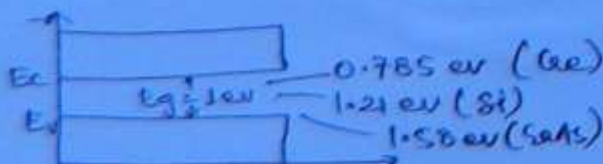

Semiconductor.

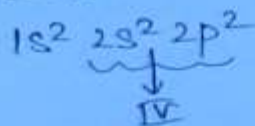$C \rightarrow 2\text{ eV}$ going toward Insulator.



$$E_g = 2\text{eV}$$

(13)

Q. Why Carbon is not behaving like a semiconductor?

Ans: E_g for carbon = 2eV.


As energy gap value for carbon is more than the typical value of semiconductors. Sometimes it is behaving like a perfect insulator.

* Differences between conductors, insulators and semiconductors

Property	Conductors	Insulators	Semi-conductors.
1) Resistivity	less $10^{-8} \Omega\text{cm}$	Highest $10^{12} \Omega\text{cm}$	10^{-4} to $10^3 \Omega\text{cm}$
2) type of bonding	Metallic (free)	ionic & covalent	covalent
3) Energy gap	0eV	6eV	1eV
4) temp coeff. of resistance	positive	—	negative.
5) Charge Carriers	e^-	—	electron & holes

Properties of Semiconductors →

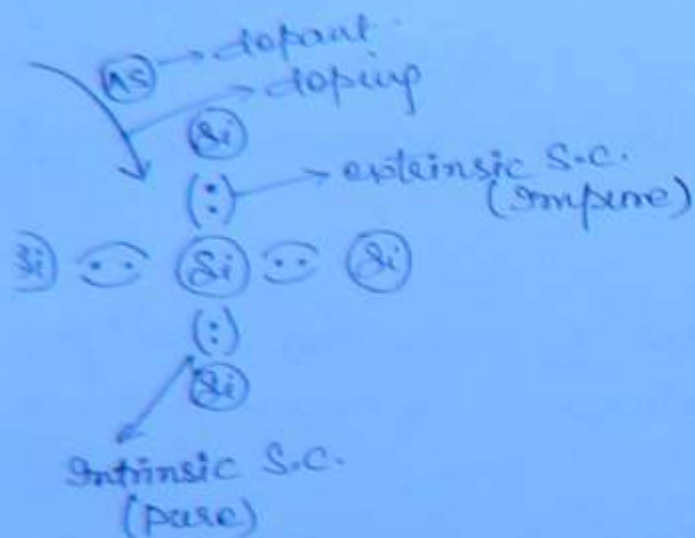- 1) Resistivity of a semiconductor is more than that of a conductor but less than of an insulator.
- 2) It is having -ve temp co-eff. of Resistance property.
- 3) Doping is possible in it.



When an impurity is added to an intrinsic S.C., its conducting property changes.

Note → Doping is a process which improves the conductivity of a semiconductor.

Unit of eu: —


$$1 \text{ ev} = 1.6 \times 10^{-19} \text{ J.C.} \times 1 \text{ V.}$$

$$= 1.6 \times 10^{-19} \text{ J.}$$




The amount of eu. required for an e^- to fall through a diff. of 1V is called as '1 ev'


Semiconductors →

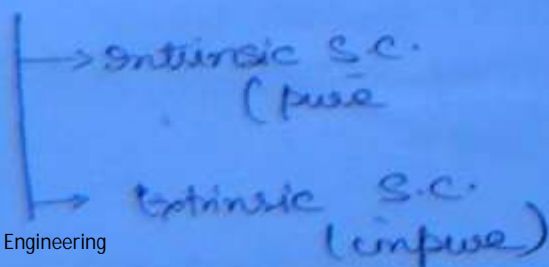

Intrinsic S.C. (pure)

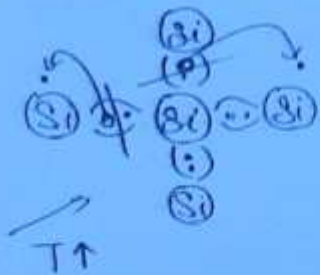

(15)

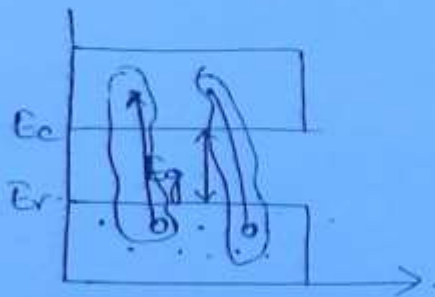

$$n = p$$

$$n = \text{conc. of } e^- / \text{cm}^3$$

$$p = \text{conc. of } e^- \text{ holes} / \text{cm}^3$$

$$n = p = n_i$$

$$n_i \rightarrow \text{intrinsic conc. } (e-h) / \text{cm}^3$$


Extrinsic S.C. (Impure)

Intrinsic S.C. + Other material = Extrinsic S.C.

Other material \rightarrow dopants


- \rightarrow Pentavalent impurity -
Arsenic, Antimony, Bismuth, Phosphorus etc.
- \rightarrow Trivalent impurity -
eg - Gallium, Boron, Al, Indium.

Pentavalent

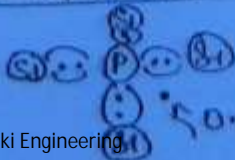

major carriers $\rightarrow e^-$
minority carriers \rightarrow holes.
 n type S.C.

Trivalent -

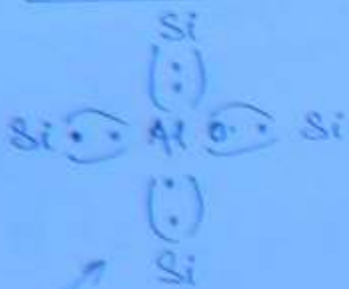




(16)

major. carriers - holes

min. carriers - e^-

P type S.C.

28/12/11

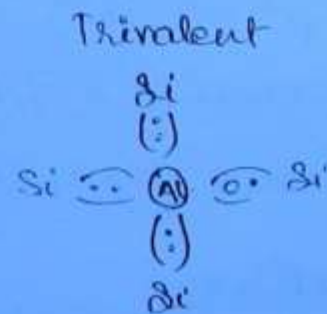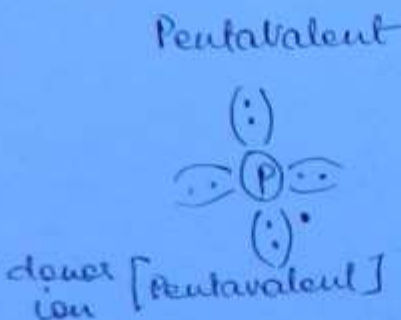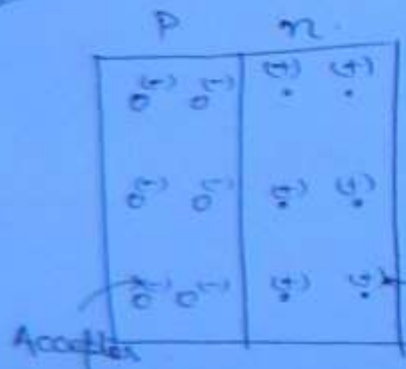

[Trivalent]


En. band diagram in a semiconductor \rightarrow

Fermi Dirac probability $f^{\circ} \rightarrow$

"In energy band diagram, the probability that the en. level of e^- is given by a f° called as fermi f° defined as

$$F(E) = \frac{1}{1 + e^{(E-E_f)/KT}}$$

At $t = 0K$,

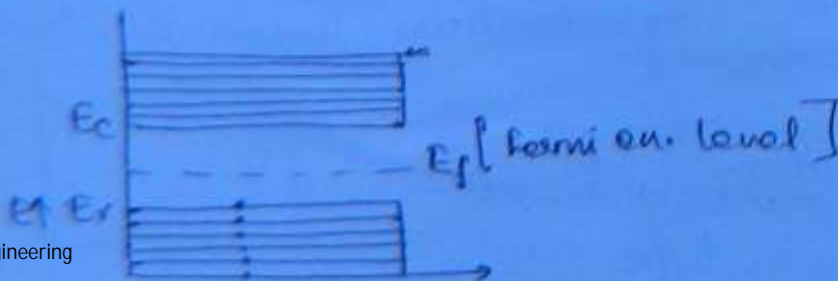

$T = 0K,$

$$F(E) = 1 \quad E < E_f$$

$$= 0 \quad E > E_f$$

$$= X \downarrow \quad E = E_f$$

indeterminate


(12)

$$F(E) = \frac{1}{1 + e^{(E - E_f)/KT}}$$

At $E = E_f,$

$T = 0K.$
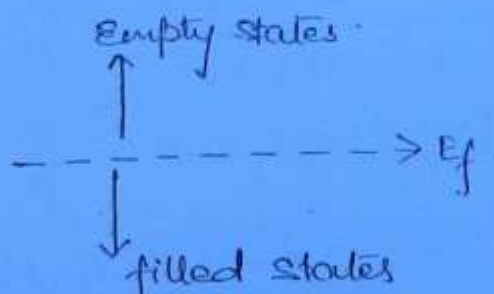
$$F(E) = \frac{1}{1 + e^{0/0}} \rightarrow \text{Indeterminate}$$



Fermi level \rightarrow

It is the ref. en. level which separates filled states and empty states ~~at 0K.~~

Ex. Q.


$T \neq 0K,$

$$F(E) = 0.5 \quad E = E_f$$

$$F(E) = \frac{1}{1 + e^{(E - E_f)/KT}}$$

$$= \frac{1}{1 + 1}$$

$$= 0.5$$

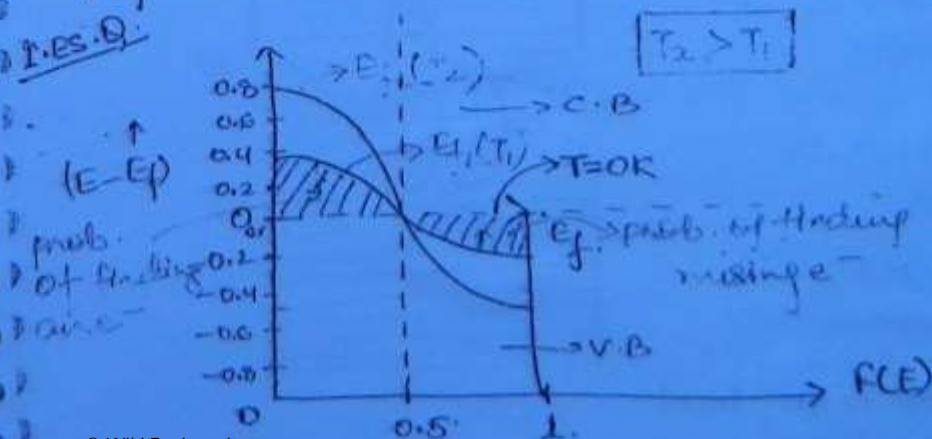

1) At $t=0K$, the fermi level line will be shown like a flat line.


(18)

2) At $t \neq 0K$, the fermi level will be represented like a curvative nature.


* Fermi level is not a const level and depends on doping.

Energy band diagrams:-


Intrinsic S.C. \rightarrow

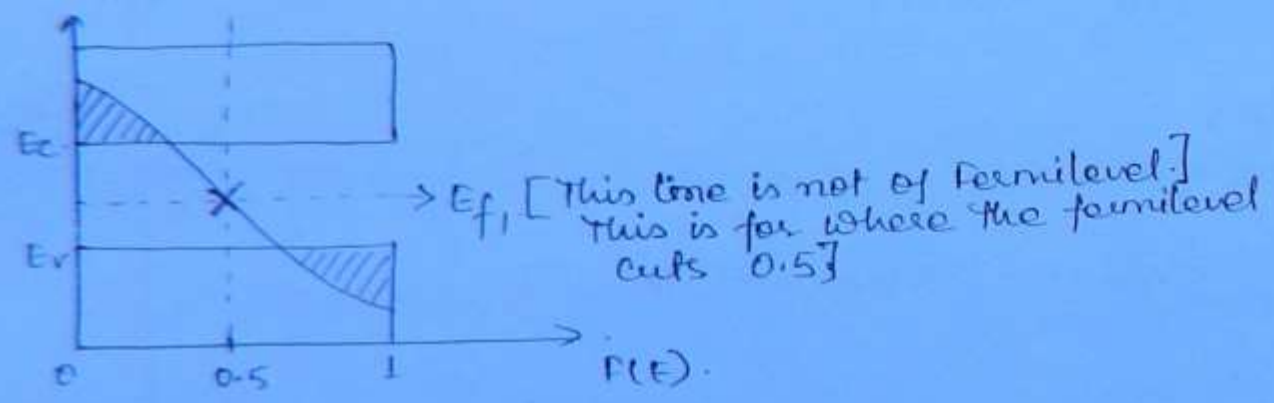

N-type

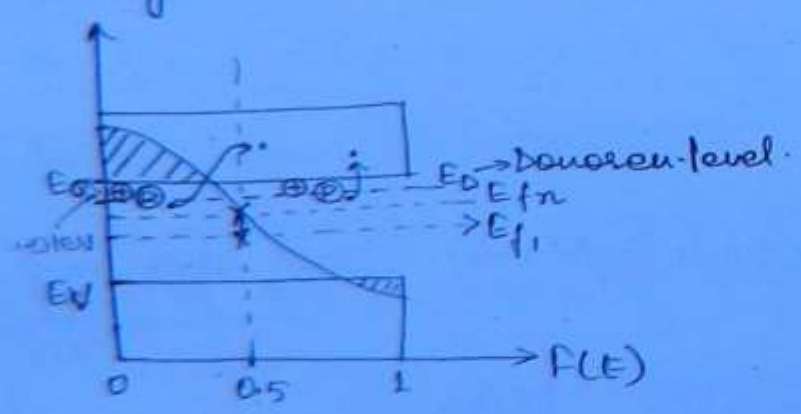

P-type \rightarrow

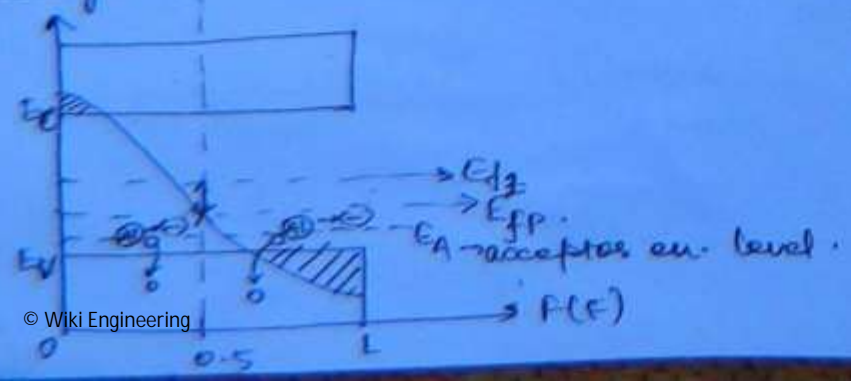

Mathematical Analysis →

$$\begin{aligned} n &= N_c e^{-(E_c - E_f)/KT} \\ p &= N_v e^{-(E_f - E_v)/KT} \end{aligned} \left. \vphantom{\begin{aligned} n &= N_c e^{-(E_c - E_f)/KT} \\ p &= N_v e^{-(E_f - E_v)/KT} \end{aligned}} \right\} \text{Fermi Dirac prob. f.d.}$$

(19)

n → conc. of e^-

p → conc. of holes

N_c → effective density of states in C.B.

N_v → Eff. density of states in V.B.

E_c → lowest en. level in C.B.

E_v → highest en. level in V.B.

E_f → Fermi level

K → Boltzmann const = $1.38 \times 10^{-23} \text{ J/K}$


T → Temp in Kelvin.

$$\frac{K}{q} = \frac{1.38 \times 10^{-23} \text{ J/K}}{1.6 \times 10^{-19} \text{ C}}$$

$$\frac{K}{q} = 8.65 \times 10^{-5} \text{ eV/K}$$

N_c & N_v →

$T \neq 0K$

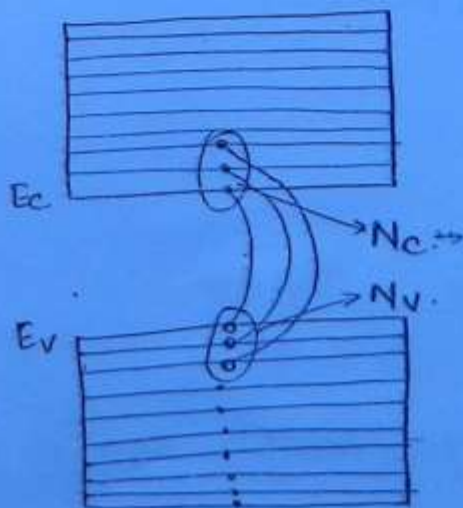

N_c → The density of en. states where the e^- are filled.

N_v → The density of en. states where the e^- are missing

$N_c \approx N_v$ → intrinsic s.c.
[material perfect]

$N_c \neq N_v$ → intrinsic s.c.
[material imperfect]

$N_c = N_v$ → ideal condition

$$N_c = 4.82 \times 10^{15} \left(\frac{m_n}{m} \right)^{3/2} T^{3/2} / \text{cm}^3$$

$$N_v = 4.82 \times 10^{15} \left(\frac{m_p}{m} \right)^{3/2} T^{3/2} / \text{cm}^3.$$

(20)

If $m_n = m_p \Rightarrow N_c = N_v$.

$m_n \rightarrow$ Effective mass of e^- in c.B.

$m_p \rightarrow$ Effective mass of proton [i.e holes]

$m \rightarrow$ Rest mass of an e^-
 $= 9.18 \times 10^{-31} \text{ kg}.$

Expression for fermi level in case of intrinsic semiconductor:

$$n = p$$

$$+ N_c e^{-(E_c - E_f)/KT} = N_v e^{-(E_f - E_v)/KT}$$

$$\Rightarrow K_T \ln \frac{N_c}{N_v} = E_c + E_v - 2E_f$$

$$\Rightarrow E_f = \frac{E_c + E_v}{2} - K_T \ln \left(\frac{N_c}{N_v} \right) \Rightarrow N_c \neq N_v \text{ [Imperfect]}$$

$$E_f = \frac{E_c + E_v}{2} \Rightarrow N_c \approx N_v \text{ [perfect]}$$

if $N_c > N_v$, $E_f' < E_f [0.5]$.

if $N_c < N_v$, $E_f' > 0.5$.

Expression for fermi level in Extrinsic S.C.: \rightarrow


N type \rightarrow

$$n \approx N_D \text{ [Donor conc]}$$




P type \rightarrow

$$n - p = N_A \text{ [Acceptor conc]}.$$

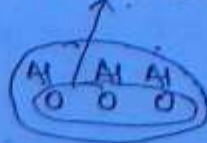

minor conc. level in S.C. = $n = p = n_i$ (intrinsic S.C.).

(21)

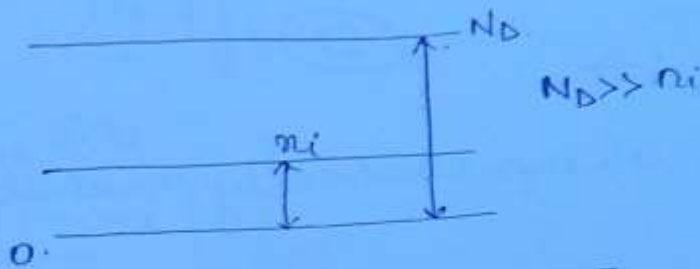

Law of mass Action : \rightarrow [Applied for all type of S.C.]

$$n \cdot p = \text{const.}$$


$$n = N_c e^{-(E_c - E_f)/KT}$$

$$p = N_v e^{-(E_f - E_v)/KT}$$

$$n_0 p_0 = N_c N_v e^{-(E_c - E_v)/KT}$$

$$= N_c N_v e^{-E_g/KT}$$

$$= n_i^2$$

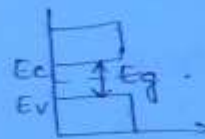

$$N_c N_v e^{-E_g/KT} = \underbrace{4.82 \times 10^{15} \left(\frac{m_p}{m} \right)^{3/2}}_{N_c} T^{3/2} \underbrace{4.82 \times 10^{15} \left(\frac{m_p}{m} \right)^{3/2}}_{N_v} T^{3/2} e^{-E_g/KT}$$

$$= A_0 T^3 e^{-E_g/KT}$$

$$= n_i^2$$

Intrinsic S.C. :-

$$n \cdot p = n_i^2$$

$$n = p$$

n type \rightarrow

$$n \cdot p = n_i^2$$

majority minority

p type

$$n \cdot p = n_i^2$$

minority \rightarrow majority



law of mass action is valid for all types of semiconductors

[Intrinsic, n-type, p-type]

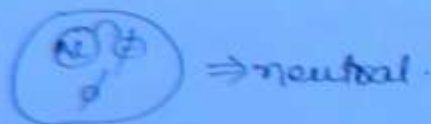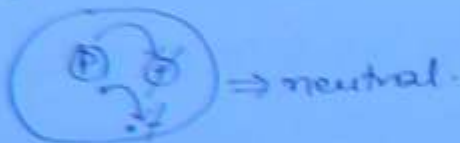(22)

Charge neutrality equation : \rightarrow

"Any part of a s.c. bar is always electrically neutral"



Net charge density = 0.

Total +ve charge density = total -ve charge densities

$$\begin{array}{cccc} n & p & N_D & N_A \\ - & + & \oplus & \ominus \end{array}$$

$$\boxed{p + N_D = n + N_A}$$

N-type \rightarrow

$$p + N_D = n + N_A$$

$$n \gg p; N_A \approx 0$$

$$\frac{n_i^2}{n} + N_D = n + 0$$

$$\Rightarrow n^2 - N_D n - n_i^2 = 0$$

$$\Rightarrow n = \frac{N_D}{2} \pm \sqrt{\left(\frac{N_D}{2}\right)^2 + n_i^2}$$

$$n = \frac{N_D}{2} + \sqrt{\left(\frac{N_D}{2}\right)^2 + n_i^2}$$

$$N_D \gg n_i \Rightarrow \boxed{n \approx N_D}$$

Similarly, for P-type \rightarrow

$$P = \frac{N_A}{2} + \sqrt{\left(\frac{N_A}{2}\right)^2 + n_i^2}$$

$$N_A \gg n_i$$

$$P \approx N_A$$

N-type

$$n = N_c e^{-(E_c - E_f)/KT}$$

$$\downarrow$$

$$N_D$$

$$KT \ln \frac{N_c}{N_D} = E_c - E_{fn}$$

$$E_{fn} = E_c - KT \ln \left(\frac{N_c}{N_D} \right)$$

P-type

$$P = N_v e^{-(E_f - E_v)/KT}$$


$$\downarrow$$

$$N_A$$

$$N_A = N_v e^{-(E_f - E_v)/KT}$$

$$KT \ln \left(\frac{N_v}{N_A} \right) = E_{fp} - E_v$$

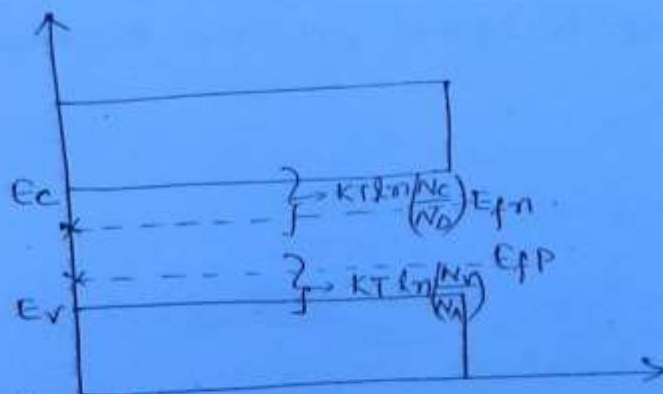
$$E_{fp} = E_v + KT \ln \frac{N_v}{N_A}$$




Questions \rightarrow

Q1. As temp inc. ϕ in an extrinsic S.C. what happens to the position of fermi level?

Ans.

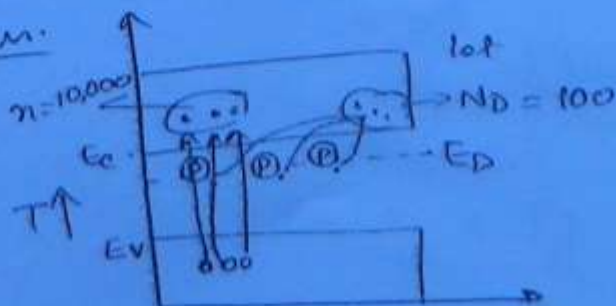

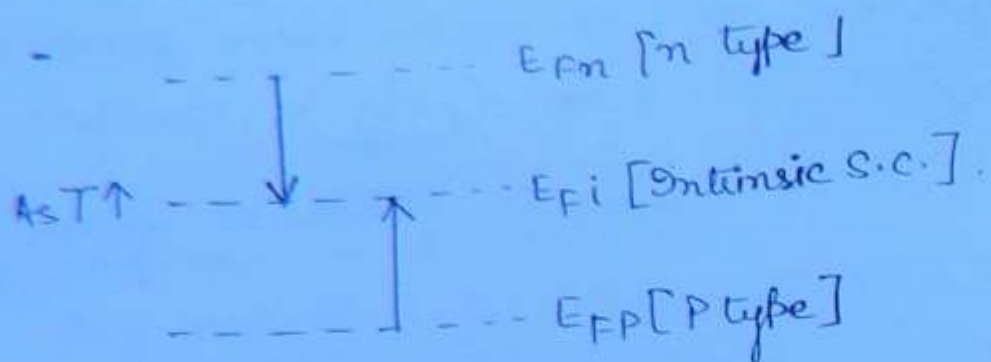As temp inc, n also increases but on N_D , temp has no effect. So, at high temp, extrinsic S.C. behaves as intrinsic S.C.



The fermi level moves toward the intrinsic S.C. in case of n type and P-type.

* At very very high temp, extrinsic S.C. will behave like an intrinsic S.C.

Q2 As doping conc. increases, in an extrinsic S.C. what happens to fermi level?


Ans Fermi level moves towards the CB in case of n-type and moves towards the V.B. in case of P-type.

Q3 If $N_D \gg N_C$ in n type what happens to the position of fermi level?

$$\underline{\text{w.}} \quad E_{Fn} = E_C - KT \ln \left(\frac{N_C}{N_D} \right)$$

$$N_D \gg N_C$$

$$E_{Fn} = E_C + KT \ln N_D$$

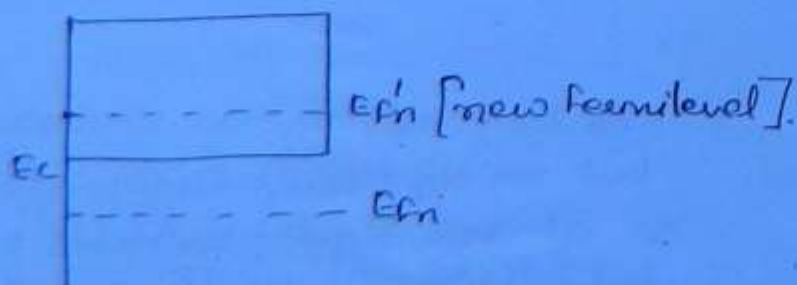


if $N_A \gg N_V$ in p-type, under happens in the Fermi level 9

(25)


Ans. $E_{FP} = E_V \pm KT \ln \left(\frac{N_V}{N_A} \right)$

$N_A \gg N_V$

$E_{FP} = E_V - KT \ln N_A$

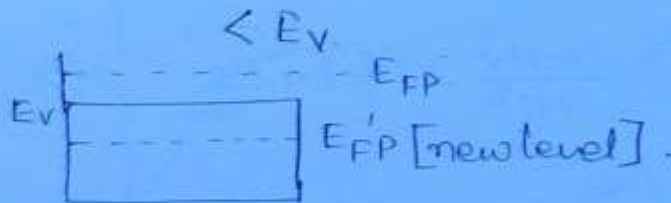

Conclusion \rightarrow

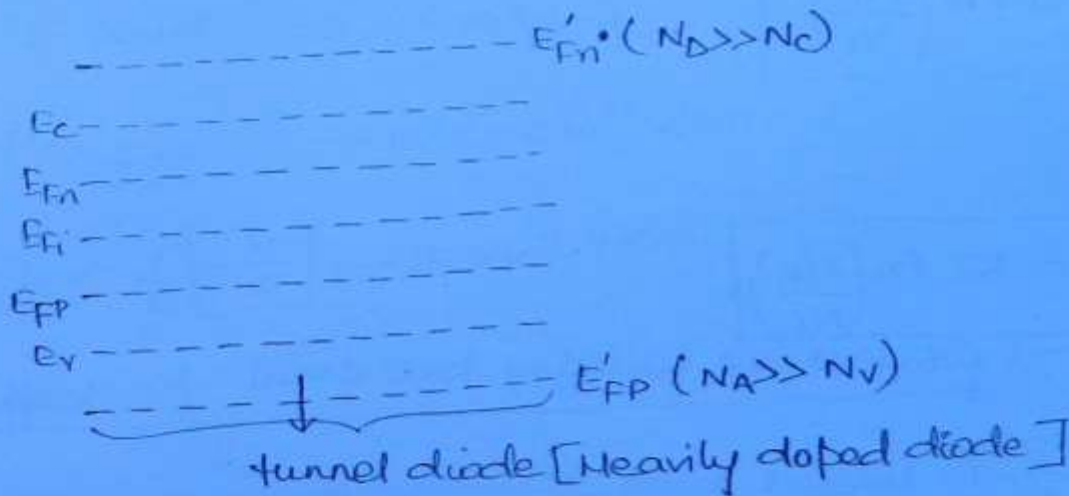

Shift in the fermi level in case of n-type :—
w.r.t. intrinsic fermi level.

$\{ E_{Fn} - E_{fi} \}$

$= E_c - KT \ln \left(\frac{N_c}{N_D} \right) - \left\{ \frac{E_c + E_v}{2} - \frac{KT}{2} \ln \frac{N_c}{N_v} \right\}$

$= E_c - KT \ln \left(\frac{N_c}{N_D} \right) - \left\{ \frac{E_c + E_c - E_g}{2} - \frac{KT}{2} \ln \frac{N_c}{N_v} \right\}$

$= -KT \ln \frac{N_c}{N_D} + \frac{E_g}{2} + \frac{KT}{2} \ln \left(\frac{N_c}{N_v} \right) \quad \text{---(1)}$

$$n \cdot p = n_i^2$$

$$n_i^2 = N_c N_v e^{-\frac{(E_c - E_v)/KT}{E_g}}$$

(26)

$$E_g = KT \ln \frac{N_c N_v}{n_i^2}$$

From (1)

$$= -KT \ln \frac{N_c}{N_D} + \frac{KT}{2} \ln \frac{N_c N_v}{n_i^2} + \frac{KT}{2} \ln \frac{N_c}{N_v}$$

$$= KT \ln \frac{N_D}{N_c} \frac{\sqrt{N_c N_v}}{n_i} \frac{\sqrt{N_c}}{\sqrt{N_v}}$$

$$E_{Fn} - E_{Fi} = KT \ln \left(\frac{N_D}{N_i} \right)$$

Similarly,

$$E_{Fi} - E_{Fp} = KT \ln \left(\frac{N_A}{N_i} \right)$$

For P-type

Drift current →

It occurs in metals and S.C.

eg.



$$V \propto E$$

$$V = \mu E$$

$$\text{Mobility} = \frac{\text{Drift velo}}{\text{Electric fld}} = \frac{m/\text{Sec}}{V/m}$$


$$= m^2/V\text{-sec.}$$

The current is produced due to the drifting of free e^- is called as drift current [drifting means movement]

Mobility →

(27)

Effect of E-field on mobility : —

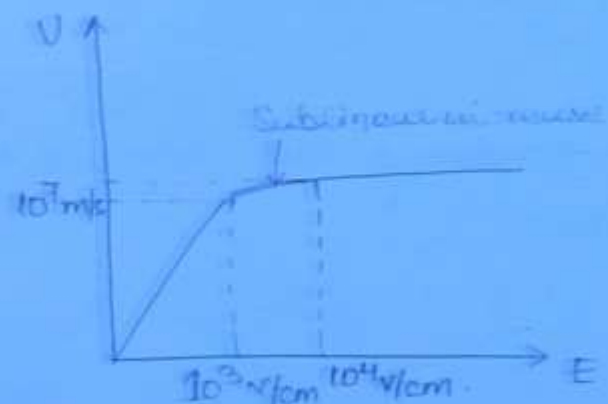


$$\mu = \text{const} \rightarrow E < 10^3 \text{ V/cm}$$

$$\mu \propto \frac{1}{\sqrt{E}} \rightarrow 10^3 < E < 10^4 \text{ V/cm}$$

$$\mu \propto \frac{1}{E} \left[= \frac{V}{E} \right] \rightarrow E > 10^4 \text{ V/cm}$$

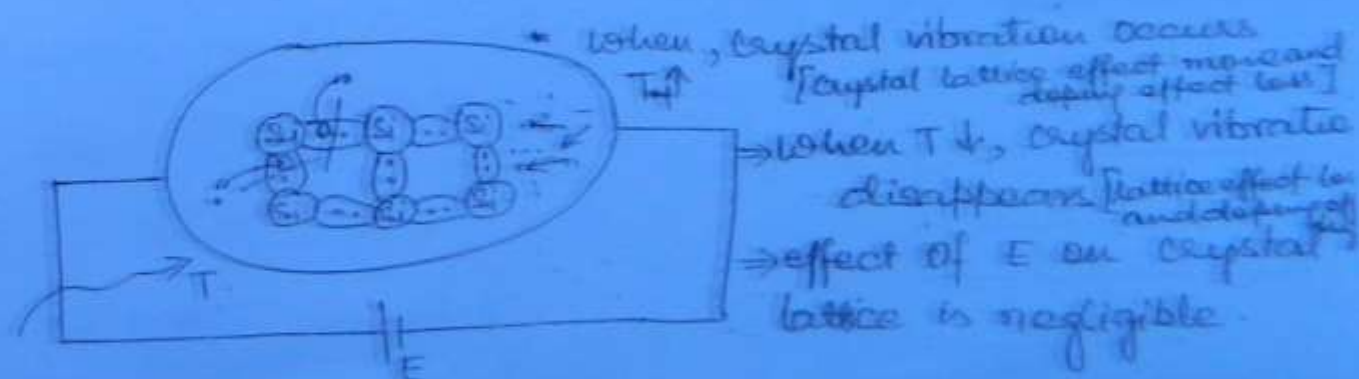Effect of temp and impurity on mobility : —



The e^- and hole mobility are influenced by two scattering phenomena. One is lattice scattering effect and other is impurity scattering.

Lattice scattering : \rightarrow

As temp increases, there will be vibration in the crystal lattice which produces the mobility. (28)

$$\mu \propto T^{-m}$$

Impurity scattering \rightarrow

As temp decreases, impurity scattering will become more dominant then mobility reduces.

$$\mu \propto T^m$$

Current density : \rightarrow

$$J = \frac{I}{A}$$

$$I = \frac{N \cdot e}{T}$$

$T \rightarrow$ time

$$I = \frac{N \cdot e}{T \cdot A}$$

$$\text{Time} = \frac{\text{dist}}{\text{Velo}}$$

$$T = \frac{L}{v}$$



$N \rightarrow$ no. of e^-

$$I = \frac{N e v}{L A}$$

$$\eta = \frac{N}{L A}$$

$$I = \eta e v$$

\downarrow
 $f = \eta x e = \text{charge density}$

$$I = f v$$

metals

$$I = n e v$$

$$v = \mu E$$

(29)

$$I = n e \mu E$$

$$I = \sigma E \quad \left[\sigma \rightarrow \text{conductivity} \right]$$

$$\sigma = n e \mu$$

S.C.

$$I_{sc} = I_n + I_p$$

$$I_n = n q \mu_n E$$

$$I_p = p q \mu_p E$$

$$I_{sc} = n q \mu_n E + p q \mu_p E$$

$$I_{sc} = \underbrace{(n \mu_n + p \mu_p) q E}_{\sigma_{sc}}$$

$$\text{where } \sigma_{sc} = (n \mu_n + p \mu_p) q$$

Expression for conductivity in case of extrinsic S.C. :-

$$\sigma_{sc} = (n \mu_n + p \mu_p) q$$

$$n = p = n_i$$

$$\sigma_{sc} = n_i (\mu_n + \mu_p) q$$

$$\text{where } n_i^2 = A_0 T^3 e^{-E_g / kT}$$

$$n_i \propto T^{3/2}$$

For n-type :-

$$\sigma_{sc} = (n \mu_n + p \mu_p) q = n \mu_n q$$

$p \mu_p q \rightarrow \text{can be neglected}$

$$\sigma_{N\text{-type}} \approx n k T q$$

$$\approx N_D k T q$$

(30)

For P-type \rightarrow

$$\sigma_{P\text{-type}} \approx n k T q$$

$$\approx N_A k T q$$



9/12/11


Parameter	Ge	Si
1) E_g at 0K	0.785 eV	1.21 eV
2) E_g at 300K	0.72 eV	1.12 eV
3) n_i/cm^3 at 300K	$2.5 \times 10^{13} / \text{cm}^3$	$1.5 \times 10^{10} / \text{cm}^3$
4) $\mu_n \text{ cm}^2/\text{Vsec}$	3,800	1300
5) $\mu_p \text{ cm}^2/\text{Vsec}$	1800	500
6) no. of atoms/ cm^3	$4.4 \times 10^{22} / \text{cm}^3$	$5.0 \times 10^{22} / \text{cm}^3$

Diffusion current : \rightarrow

It occurs in a non uniformly doped S.C.

eg.

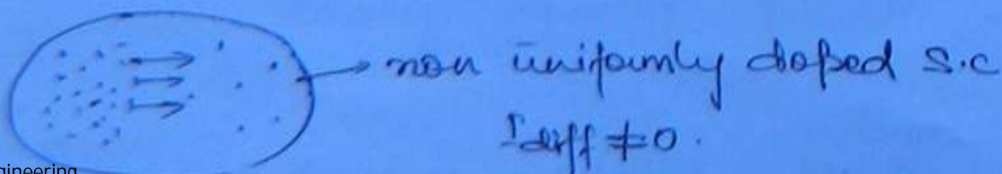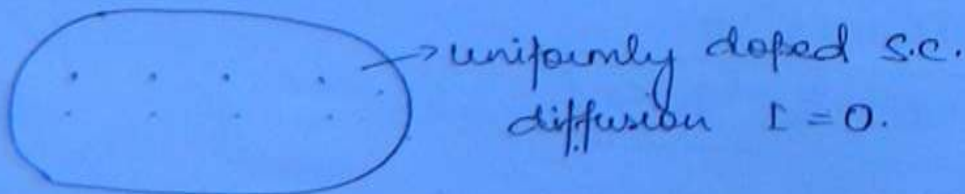

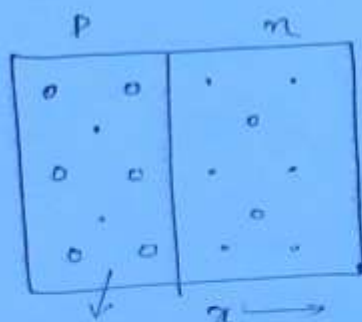

(31)

The best eg of non uniformly doped S.C. is p-n jⁿ.

The rate of change of conc. w.r.t. dist. x is called as diffusion current.

NOTE →

Diffusion current mechanism can also be called as conc. gradient $\left[\frac{dn}{dx} \right]$.

Drift current mechanism can also be called as pot. gradient $\left[\frac{dV}{dx} \right]$.

$$I_n \propto q D_n \frac{dn}{dx}$$

$$I_n = q D_n \frac{dn}{dx}$$

D_n → diffusion const of e^-




$$I_n = A q D_n \frac{dn}{dx}$$

$$I_p \propto q D_p \frac{dp}{dx}$$

$$I_p = q D_p \frac{dp}{dx} \rightarrow X$$

D_p → Diffusion const of holes
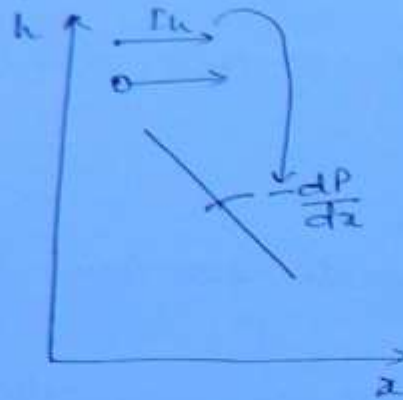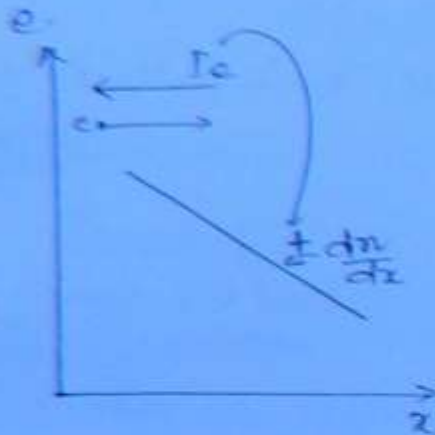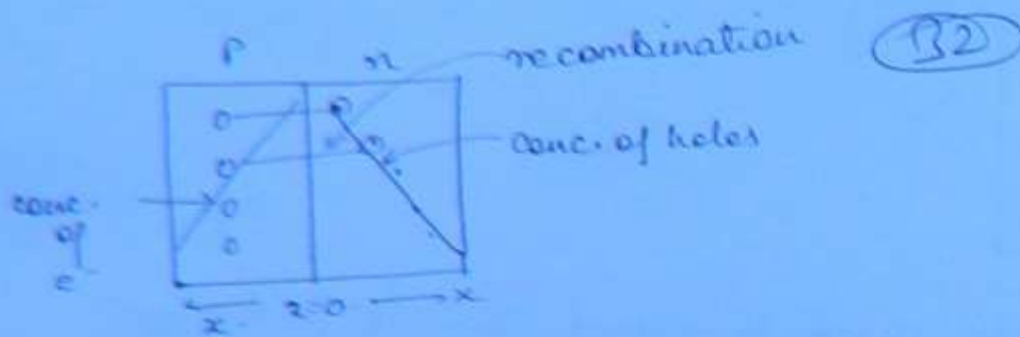
$$I_p = A q D_p \frac{dp}{dx} \rightarrow X$$



$$\Rightarrow J_p = -qD_p \frac{dp}{dx}$$

$$\Rightarrow I_p = -AqD_p \frac{dp}{dx}$$

Total current in a S.C. \Rightarrow

$$I_{sc} = I_{drift} + I_{diff.}$$

$$= nq\mu_n EA + p q \mu_p EA + AqD_n \frac{dn}{dx} - AqD_p \frac{dp}{dx}$$

There is an imp. relation b/w diffusion const. and mobility.

$$D \propto \mu$$

$$D = V_T \mu$$

$V_T \rightarrow$ volt equivalent temp 'or' Thermal voltage.

$$V_T = \frac{KT}{q} = \frac{K}{q} T = \frac{T}{11600}$$

$$1.38 \times 10^{-23} \text{ J/K}$$

$$8.65 \times 10^{-5} \text{ eV/K}$$

g. can the vol. - 1. temp at in room temp.

Ans. $T = 27^{\circ}\text{C}$
 $= 300\text{K}$

(33)

$$V_T = \frac{T}{11600}$$

$$= 0.026\text{V}$$

or

$$V_T = 26\text{mV}$$

Units


$$\mu \rightarrow \text{m}^2/\text{V-sec.}$$

$$V_T \rightarrow \text{V.}$$

$$D \rightarrow \text{m}^2/\text{sec}$$

$$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = V_T \rightarrow \text{Einstein relation.}$$


Problems based on diffusion current :-

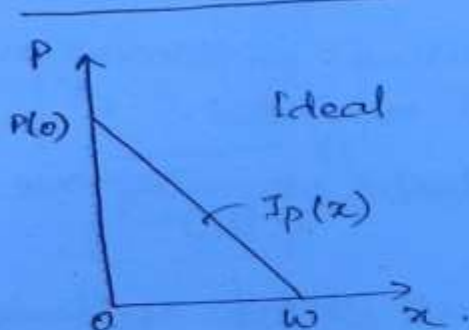

$$I_p(x) = -qD_p \frac{dP(x)}{dx}$$

$$= -qD_p \left(\frac{P(0) - 0}{0 - w} \right)$$

$$= qD_p \frac{P(0)}{w}$$

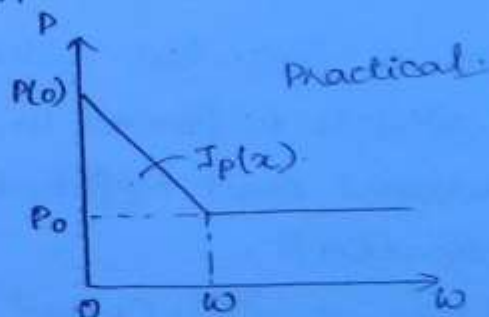

$$I_p(x) = -qD_p \frac{dP(x)}{dx}$$


$$= -qD_p \left(\frac{P(0) - P_0}{0 - w} \right)$$

$$= \frac{qD_p (P(0) - P_0)}{w}$$


$$J_p(x) = \frac{qD_p \{P(0) - P_0\}}{W} \quad 0 < x < W.$$

(34)

= 0 else

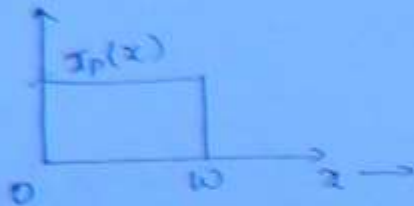

Hall effect →

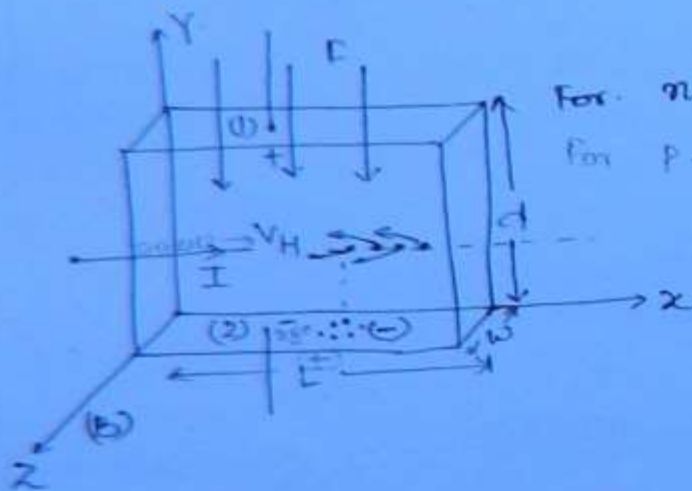

For n-type, Side 2 (-).

For p-type, Side 2 (+).

- 1) let us consider a S.C. bar whose current is flowing in the x -dirⁿ which is placed in a I^z mag. fld.
- 2) Due to the current and M-fld, an Electro magnetic force (EMF) exist in the y -dirⁿ.
- 3) Due to the EMF, a P.d. called as hall voltage is developed in the y -dirⁿ.

The main application of hall effect is to find the S.C. bar whether it is n -type or p -type.

Side (2) "-" → n type

"+" → p type.

Other application of Hall effect: —

(25)

- 1) We can determine the mobility of charge carriers in a S.C. bar.
- 2) We can also determine the conductivity of charge carriers.
- 3) It can be used as a voltage multiplier $[V_H \propto B \times I]$.

Expression for hall voltage (V_H), hall coefficient (R_H), mobility (μ), conductivity (σ): —

$$F_E = F_B$$

$F_E \rightarrow$ force due to E field.

$F_B \rightarrow$ " " " " M-field.

$$qE = Bqv$$

$v \rightarrow$ velo.

$$\frac{V'}{d} = Bv$$

$V' \rightarrow$ volt. = V_H .

$$V' = Bvd$$

$$= \frac{BI}{f} d \quad [I = fV]$$

$$= \frac{BI}{A f} d$$

$$= \frac{BI}{wf} d$$

$$V_H = \frac{BI}{wf}$$

$$R_H = \frac{1}{f} \quad f \rightarrow \text{charge density}$$

$$V_H = \frac{BI}{w} R_H$$


$$R_H = \frac{V_H w}{BI}$$

$$\sigma = \frac{n \times e \times \mu}{f}$$

$$\sigma = f \mu$$



$$\mu = \frac{\sigma}{f} = \sigma R_H$$

Generation and Recombination of charge carriers :-

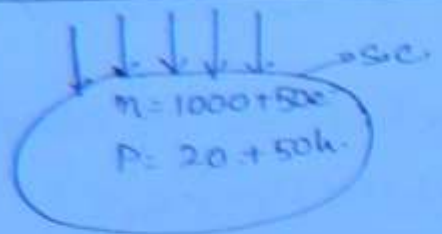eg.  rate of incⁿ of e^- is less as compared to rate of incⁿ of holes. $\Rightarrow 250\%$

For the analysis of S.C. bar, we have to conc. on minority carriers but not majority carrier.

(36)

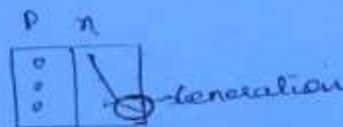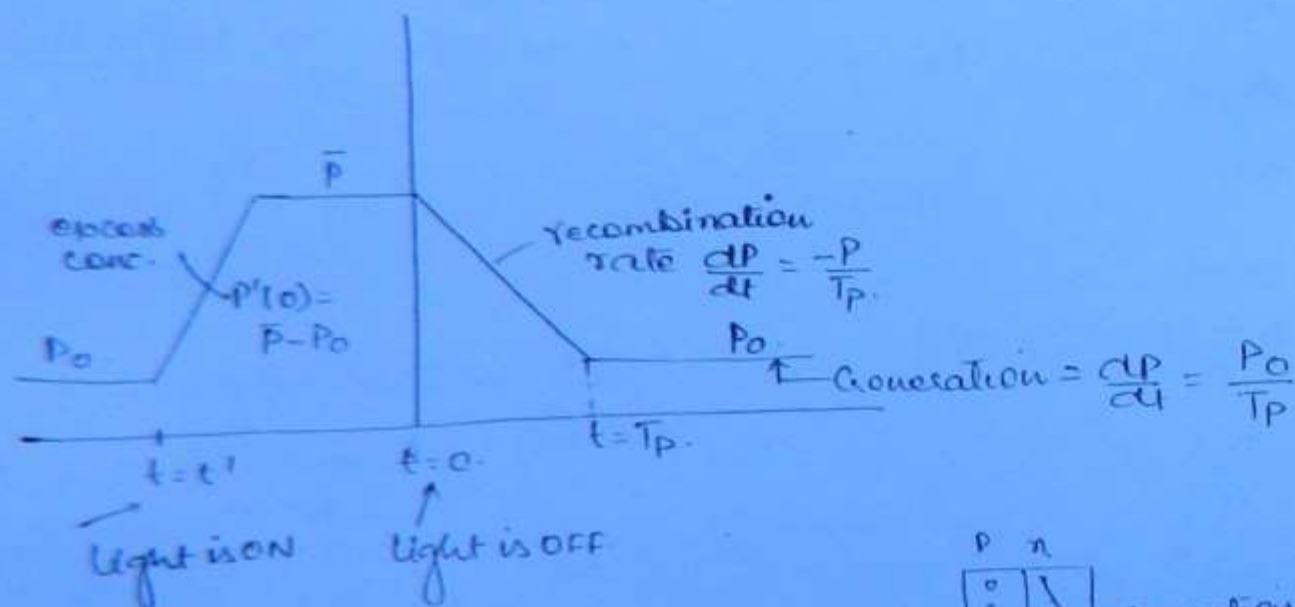

T_p [Carrier life time]

$T_p \rightarrow$ Carrier life time for holes.

It is a time taken for a hole to exist before recombination is called as carrier life time for holes.

1) When light radiation is applied to a S.C. bar, two mechanism will be happen.

Recombination rate \rightarrow

$$\frac{dP}{dt} = -\frac{P}{T_p}$$


Generation rate \rightarrow

$$\frac{dP}{dt} = \frac{P_0}{T_p}$$


2) Generation rate T_p always occurs after recombination rate.

continuity equation →

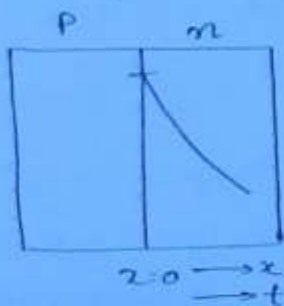- 1) For the analysis of a diode or a transistor we have to determine the conc. of charge carriers w.r.t. time and space
- 2) For such analysis, we have a mathematical eqⁿ called as continuity eqⁿ



(37)

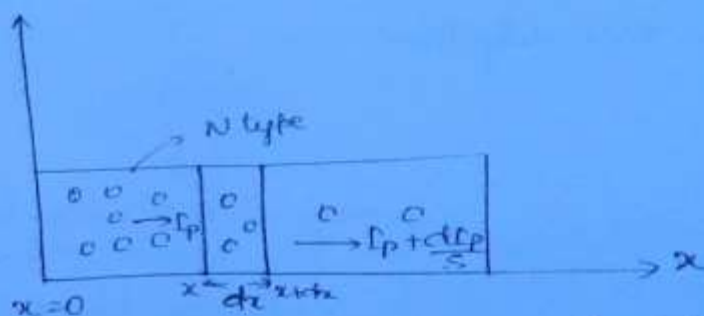

Factors affecting the conc. P of thin slice of thickness dx and area of x sec A is

1) Diffusion →

$$\frac{dP}{dt} = \frac{\text{charge taken away}}{\text{Unit charge} \times \text{Vol.}}$$

$$= -\frac{dI_p}{q \times A \times dx} \quad \text{--- (1)}$$

2) when light radiation is applied →

$$G = \frac{dP}{dt} = \frac{P_0}{T_p} \quad \text{--- (2)}$$

$$R = \frac{dP}{dt} = -\frac{P}{T_p} \quad \text{--- (3)}$$

① + ② + ③ ⇒


$$\boxed{\frac{dP}{dt} = -\frac{dI_p}{q \times A \times dx} + \frac{P_0}{T_p} - \frac{P}{T_p}}$$

Case 1. →

w.r.t. time →

P_{n0} → thermal equilibrium

$P'_n(0)$ → excess charge carriers.

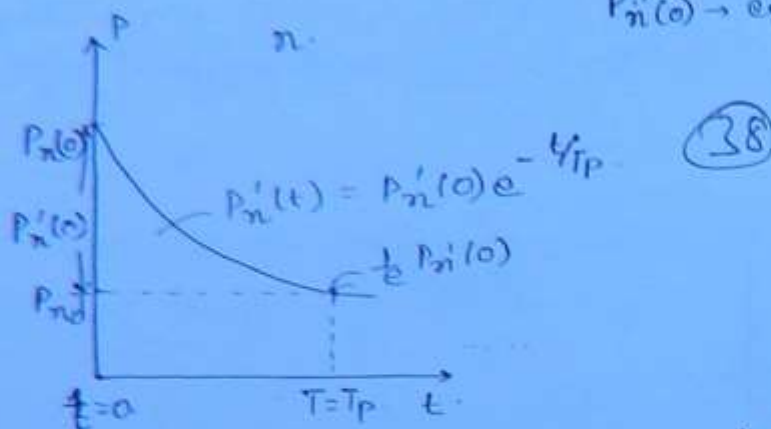

$P_n(0)$ → Injected minority carrier conc. [on the j^n always e^- or hole → minority]


P_{n0} → Thermal equilibrium minority conc.

$P'_n(0)$ → excess conc.

Case 2 →

w.r.t. Space →

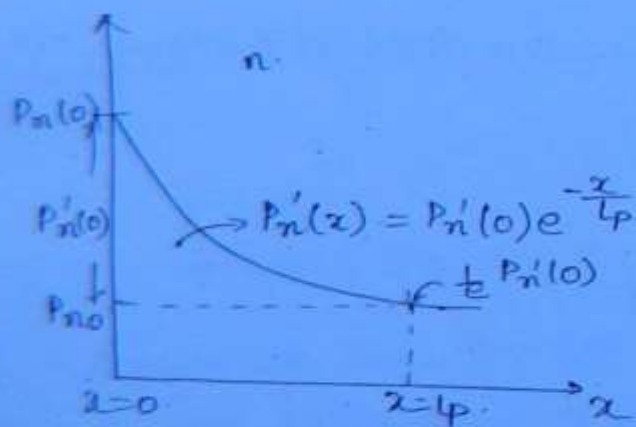L_p → mini dist traveled by hole before recombination
= diffusion length for holes.




L_p →

It is the mini distance travelled by a hole before recombination is called as diffusion length for a hole. $[L_p]$

$$L_p^2 = D_p \tau_p$$

9.

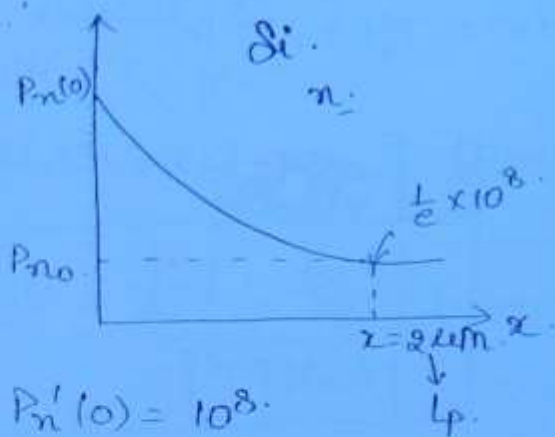

Q9

$$P_n'(0) = 10^8$$

$$P_n(0) = 1 \times 10^8$$

$$P_n(0) = 2 \times 10^8$$

Cal.

a) e^- conc.

$$b) L_p = 2 \mu m$$

$$c) T_p = \frac{L_p^2}{D_p} = 9$$


$$4m. a) \eta = \frac{n_i^2}{P_{n0}} = \frac{(1.5 \times 10^{10})^2}{1 \times 10^8}$$

$$b) L_p = 2 \mu m = 2 \times 10^{-6} m$$

$$c) T_p = \frac{L_p^2}{D_p} =$$

$$D_p = L_p V_T = 0.05 \times 0.026$$

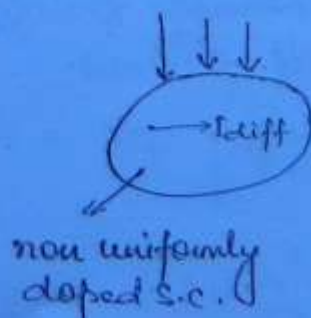Total current in an illuminated O.C. S.C. bar:—



non uniformly doped S.C.

$$I_{sciff} = I_n(x) + I_p(x)$$

$$I_p(x) = -AqD_p \frac{dP(x)}{dx}$$

$$P(x) = P_n'(0) e^{-x/L_p}$$

$$= \frac{+AqD_p P_n'(0) e^{-x/L_p}}{+L_p} \quad \text{---(I)} \quad (40)$$

$$I_n(x) = \frac{-AqD_n P_n'(0) e^{-x/L_n}}{L_n} \quad \text{---(II)}$$

When light is ON.

$$1) P_n'(0) = n_p'(0)$$

$$2) L_p = L_n$$

$$\therefore I_n(x) = \frac{-AqD_n P_n'(0) e^{-x/L_p}}{L_p} \quad \text{---(3)}$$

$$\textcircled{1} + \textcircled{3} \Rightarrow$$

$$I_{diff} = \frac{AqD_p \left(1 - \frac{D_n}{D_p}\right) P_n'(0) e^{-x/L_p}}{L_p}$$


$$= I_p \left[1 - \frac{D_n}{D_p}\right]$$

$$\text{As } D_n > D_p$$

$$I_{diff} = -ve$$

Conclusion: →

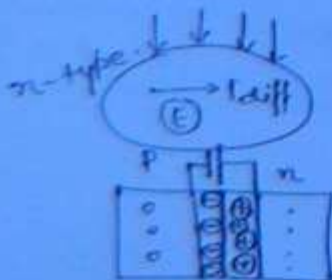In a O.C. S.C. bar, net current should be equal to 0 that means there is an E-field generated which produces drift current that cancels the diff. current




$$\text{net current} = 0.$$

$$I_{\text{drift}} + I_{\text{diff}} = 0.$$

$$nq\mu_n EA + I_p \left[1 - \frac{D_n}{D_p} \right] = 0. \quad (41)$$

$$E = \frac{\left| I_p \left[1 - \frac{D_n}{D_p} \right] \right|}{\left| nq\mu_n A \right|}$$

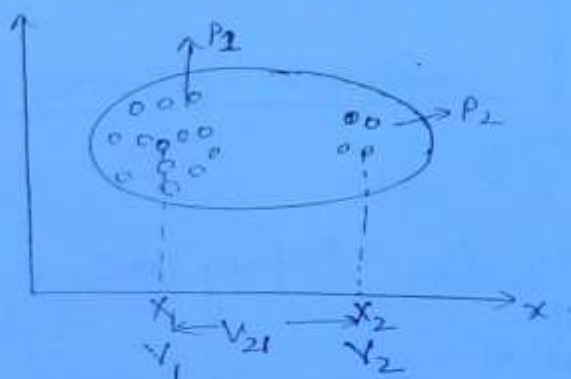Potential variation in a o.c. s.c. bar :-



$$I = 0$$

$$I_{\text{drift}} + I_{\text{diff}} = 0.$$

$$I_n + I_p + I_n + I_p = 0$$

$$I_p = 0. \quad \text{we are taking about holes, so, ignore } I_n.$$

$$I_{p\text{drift}} + I_{p\text{diff}} = 0.$$

$$p q \mu_p E - q D_p \frac{dp}{dx} = 0.$$

$$E = \frac{D_p}{\mu_p} \frac{1}{p} \frac{dp}{dx}.$$

$$\int_{V_1}^{V_2} \frac{dv}{dx} dx = V_T \int_{P_1}^{P_2} \frac{1}{p} \frac{dp}{dx} dx$$


$$V_2 - V_1 = V_T (-\ln p) \Big|_{P_1}^{P_2}.$$

$$V = V_T \ln \left(\frac{P_1}{P_2} \right)$$

$$\left. \begin{aligned} P_1 &= P_2 e^{-v_{x1}/V_T} \\ P_2 &= P_1 e^{-v_{x2}/V_T} \end{aligned} \right\} \begin{array}{l} \text{Boltzmann} \\ \text{relation} \\ \text{Kinetic gas theory.} \end{array}$$

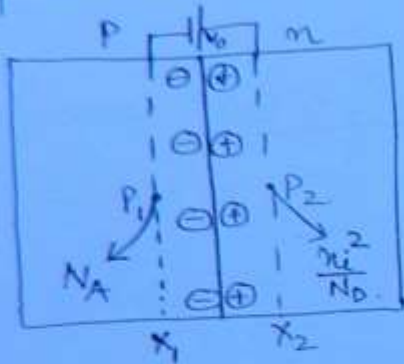(42)

20/12/11
Applying the Boltzmann relation in a o.c. pn jⁿ to find the barrier potential V_0



$$V_0 = V_T \ln \left[\frac{N_A N_D}{n_i^2} \right]$$

$N_A, N_D \rightarrow$ Doping conc.

$$V_0(\text{Ge}) = 0.1 \text{ to } 0.3 \text{ V}$$


$$V_0(\text{Si}) = 0.5 \text{ to } 0.7 \text{ V}$$


$$n_i(\text{Ge}) = 2.5 \times 10^{13} / \text{cm}^3$$

$$n_i(\text{Si}) = 1.5 \times 10^{10} / \text{cm}^3$$

P-N Junction Diode \rightarrow

open ckt P-n jⁿ \rightarrow

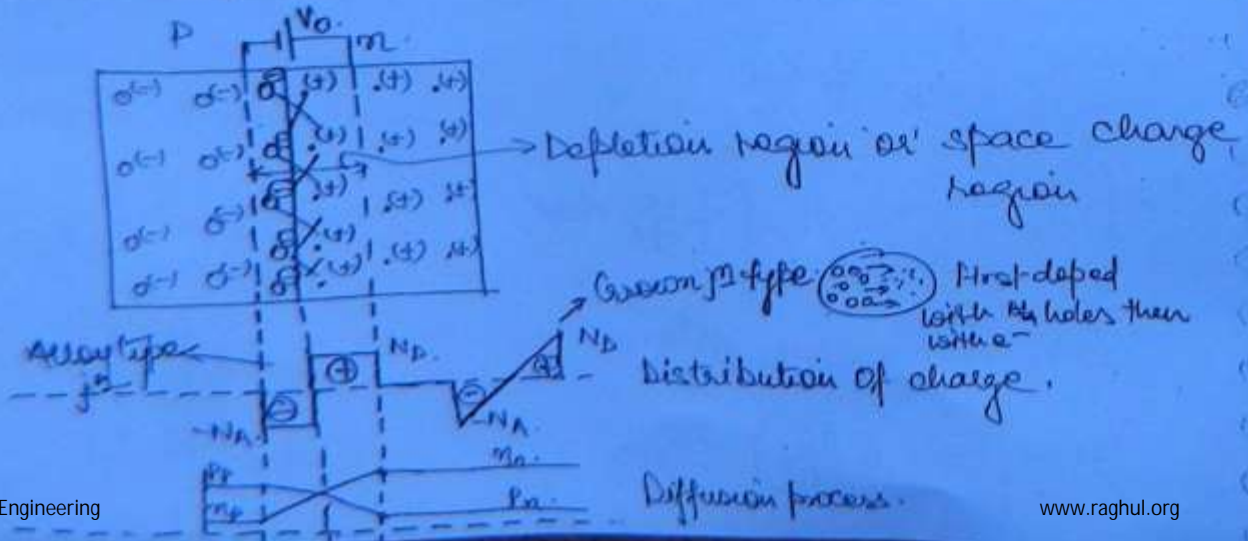

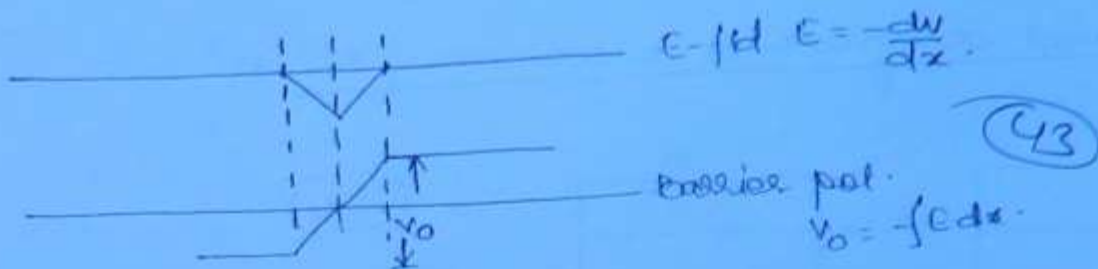

Mobile charge carriers

e^- holes

Immobile charge carriers

donor ions acceptor ions

Pn junction formation techniques

$$W \propto \sqrt{V_j}$$

Alloy type j^n

↓
Step graded j^n

↓
Sudden change or abrupt change.

$$W \propto \sqrt[3]{V_j}$$

Conc. j^n type

↓
to linearly graded j^n

↓
diffused type.

V_0 or V_j or $V_T \rightarrow$

Barrier potential
or

Built in voltage
or

Cut in voltage
or

Contact potential.


or
Depletion voltage

or
Space charge voltage



or
Transition voltage.

* Electric fld will be more conc. on the j^n .

Energy band diagram in a p-n junction

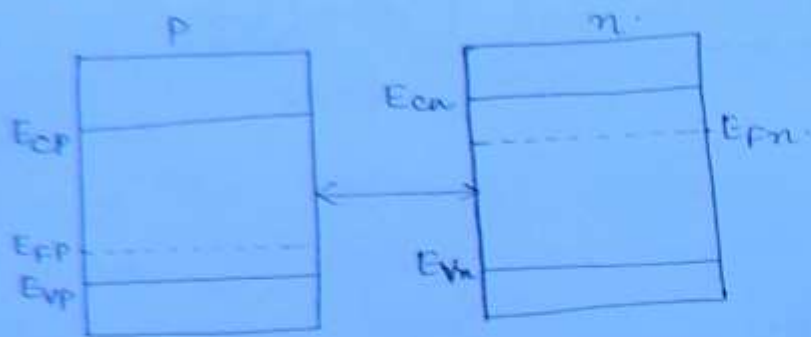

(44)

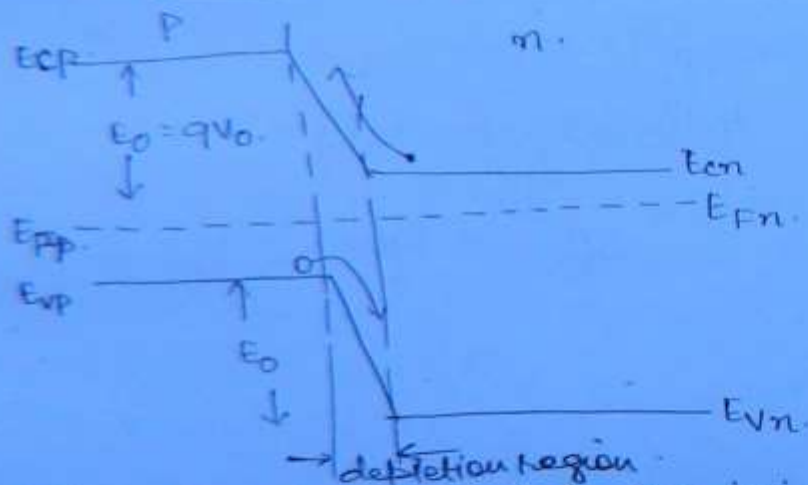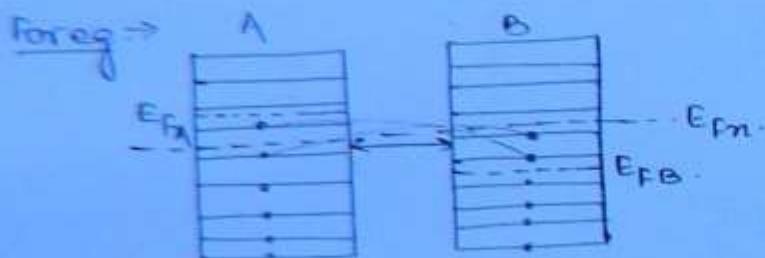


$E_0 \rightarrow$ potential en/for an e^-

$V_0 \rightarrow$ barrier pot.

Note \rightarrow Any two materials are joined fermi levels will be in aligned position.

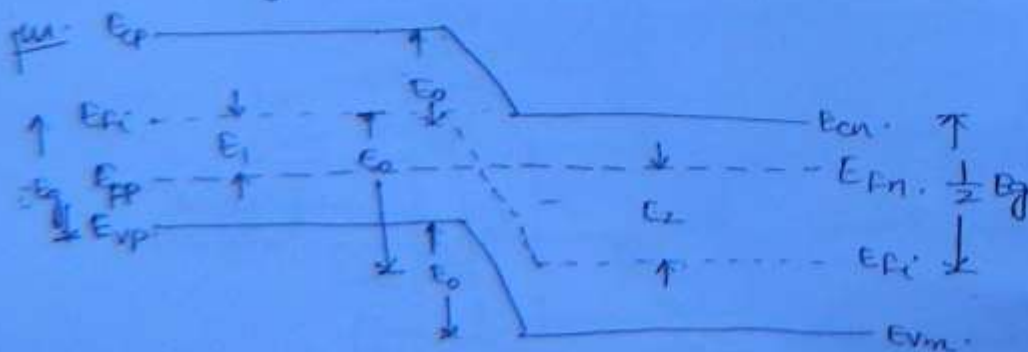Derive an expression for pot. en/for an e^- , E_0 from En. band theory concept.



$$E_0 = E_{cp} - E_{cn}$$

or

$$= E_{vp} - E_{vn}$$

or

$$= E_1 + E_2$$

(45)

$$E_{FP} - E_{VP} = \frac{1}{2} E_g - E_1 \quad (1)$$

$$E_{cn} - E_{fn} = \frac{1}{2} E_g - E_2 \quad (2)$$

$$E_0 = E_1 + E_2$$

$$= E_g - \{E_{FP} - E_{VP}\} - \{E_{cn} - E_{fn}\}$$


$$= KT \ln \left(\frac{N_c N_v}{n_i^2} \right) - KT \ln \left(\frac{N_v}{N_A} \right) - KT \ln \left(\frac{N_c}{N_D} \right)$$

$$= KT \ln \left(\frac{N_c N_v}{n_i^2} \frac{N_A}{N_v} \frac{N_D}{N_c} \right)$$

$$E_0 = KT \ln \left(\frac{N_A N_D}{n_i^2} \right) \text{ eV.}$$

$$V_0 = \frac{KT}{q} \ln \left(\frac{N_A N_D}{n_i^2} \right) \text{ eV.}$$

Formulas based on O.C. P-N j2.

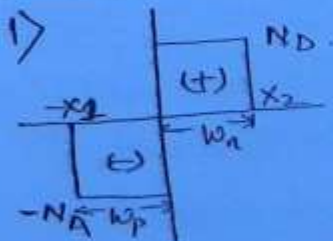

Net charge densities = 0.

Positive charge densities = -ve charge densities.

$$q N_D w_n = q N_A w_p$$

$$\left[\frac{N_D}{N_A} = \frac{w_p}{w_n} \right] \rightarrow \text{neutrality concept}$$

$$2) \frac{\partial^2 V}{\partial x^2} = -\frac{f}{\epsilon}$$

$$3) f: \begin{array}{ll} qN_D & 0 < x < x_2 \\ -qN_A & -x_1 < x < 0 \\ 0 & \text{else.} \end{array}$$


(16)

$$4) E = \left| \frac{qN_D w}{\epsilon} \right| = \left| \frac{qN_A w}{\epsilon} \right|$$

$$V_0 = \left| \frac{qN_D w^2}{2\epsilon} \right| = \left| \frac{qN_A w^2}{2\epsilon} \right|$$

$$w \propto \sqrt{V_0}$$

5) P⁺N.

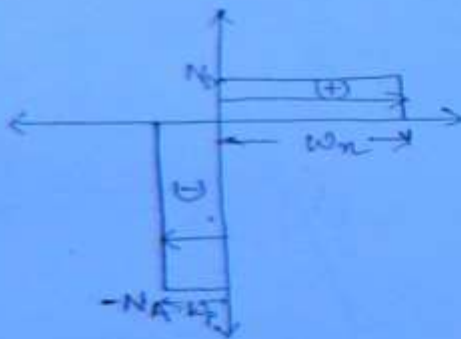


$$w_n + w_p = w$$

$$w \approx w_n$$

$$E = \left| \frac{qN_D w}{\epsilon} \right|$$

$$V_0 = \left| \frac{qN_D w^2}{2\epsilon} \right|$$

6) P⁺N⁺

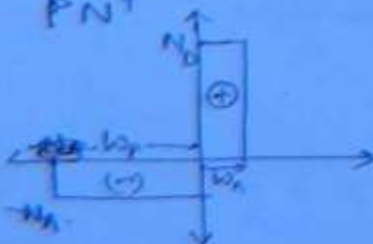

$$w \approx w_p$$

$$E = \left| \frac{qN_A w_p}{\epsilon} \right|$$

$$V_0 = \left| \frac{qN_A w_p^2}{2\epsilon} \right|$$

Note →


- 1) When the material is lightly doped one, the penetration of the depletion region will be more.
- 2) When material is heavily doped, the penetration of the depletion region will be narrower. (7)

$$w = \left[\frac{2\epsilon_0 \epsilon_r V_j}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) \right]^{1/2}$$

$$w_n = \left\{ \frac{2\epsilon_0 \epsilon_r V_j}{q} \frac{1}{N_D} \right\}^{1/2}$$

$$w_p = \left\{ \frac{2\epsilon_0 \epsilon_r V_j}{q} \frac{1}{N_A} \right\}^{1/2}$$

Bias →

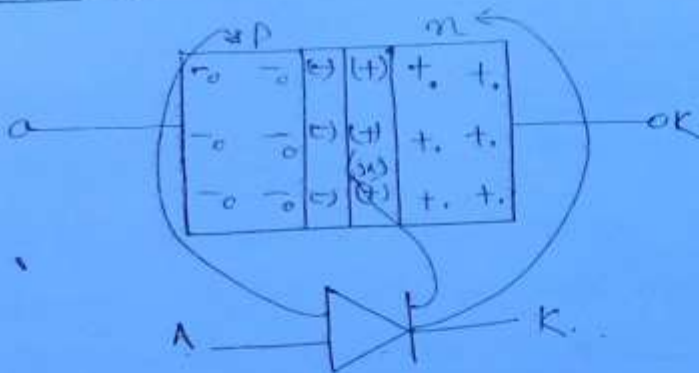


→ Adding an ext. dc voltage to a P-n jⁿ diode is called 'Bias'

→ There are two types of Bias -

1) Forward bias

2) Reverse bias.

Forward Bias →

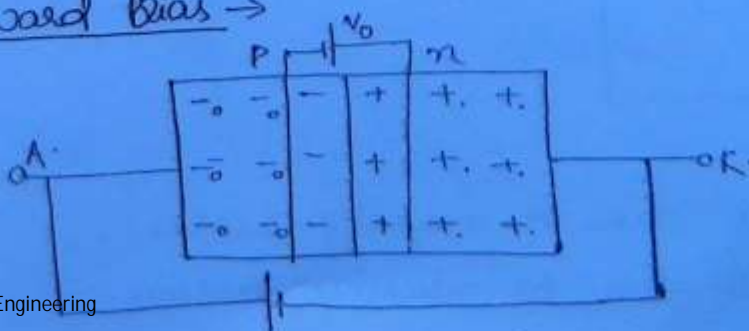

1) If $V_f > V_0$, current conduction is possible. (48)

2) The current is possible due to majority carriers.
and that majority current is represented by

$$I_f \rightarrow mA$$


3) The current will be zero due to minority carriers.

4) The depletion region becomes narrower or negligible.


5) In en. band diagram, barrier height decreases.

6) Resistance offered by the diode is very less.

Energy band diagram in forward bias :-

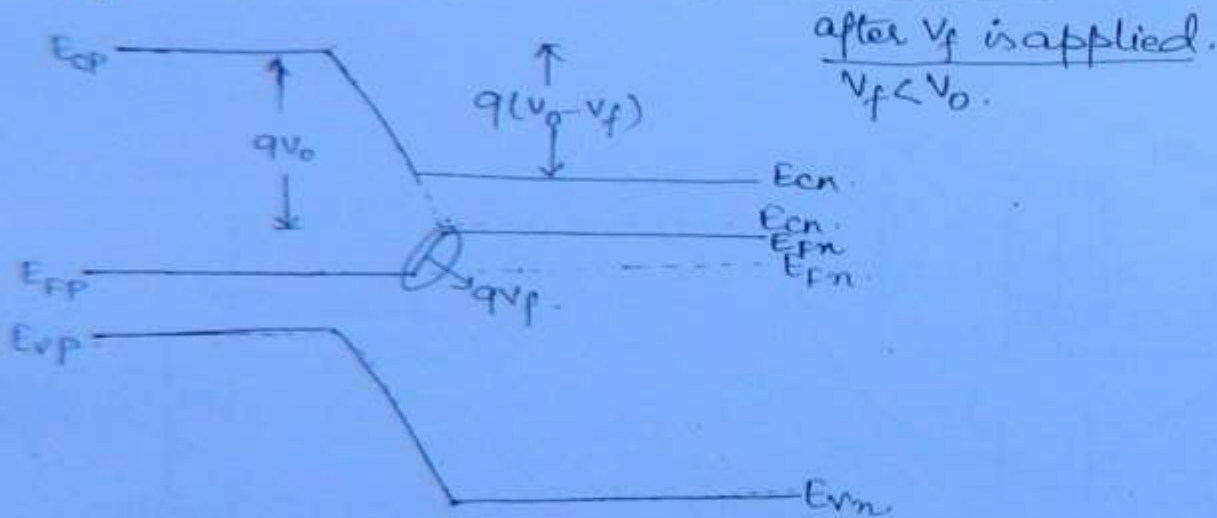

Reverse bias →

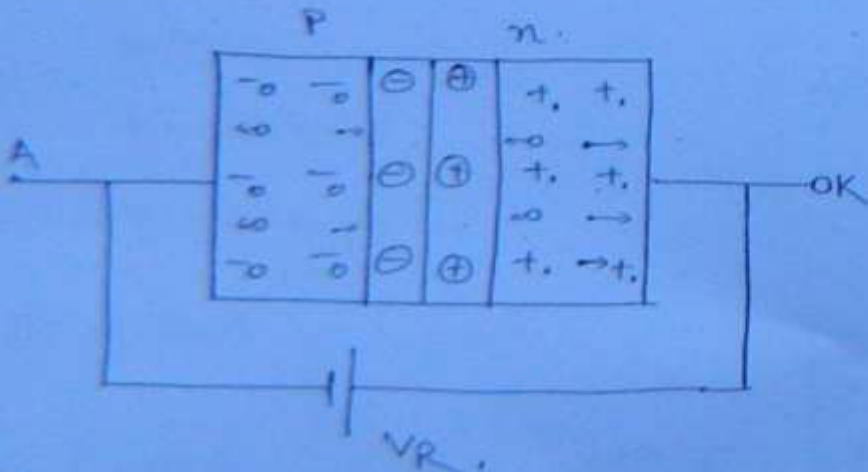

1) The current will be 0 due to majority carriers.

2) The current is possible due to minority carriers.


3) Minority current can also be called as reverse saturation current. [I_0 or I_s]

\swarrow \searrow
 μA nA
 (Ge) (Si)

(49)

Q. Why the reverse saturation current for Ge is in ' μA ' and for Si it is in ' nA '?

Ans.

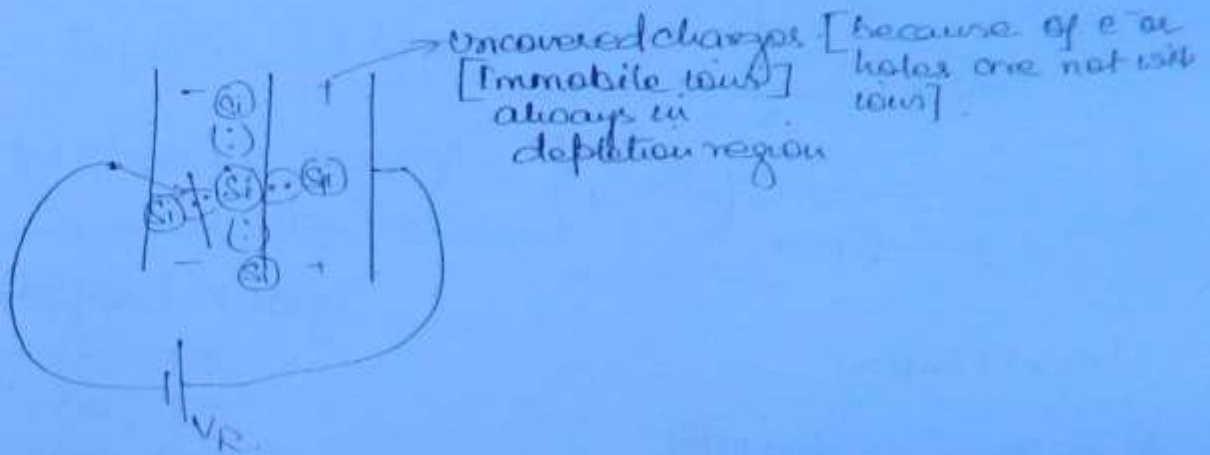

→ In the depletion region, there will be some stable atoms along with uncovered charges.


→ As the reverse bias voltage inc, the velo. of the minority charge carrier increases which collides with the stable atom in the depletion region.

→ As the en. gap value for Ge is less compare to Silicon we expect I_0 to be in μA for Ge and nano amp. in Silicon.


→ Depletion region becomes wider in reverse bias.

→ In en. band diagram, barrier height increases.

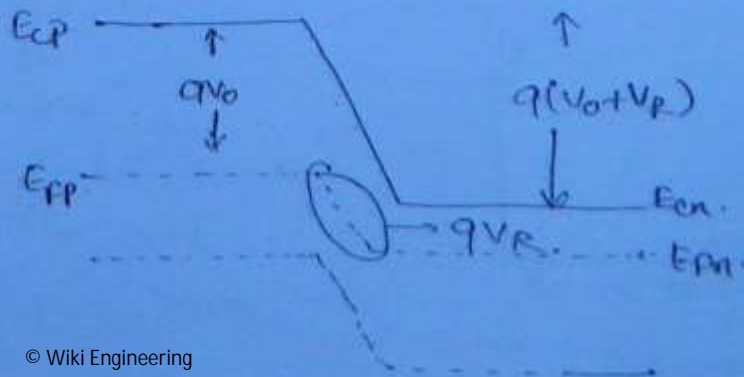→ Resistance offered is very high in the order of $M\Omega$.



Current components in p-n diode :-

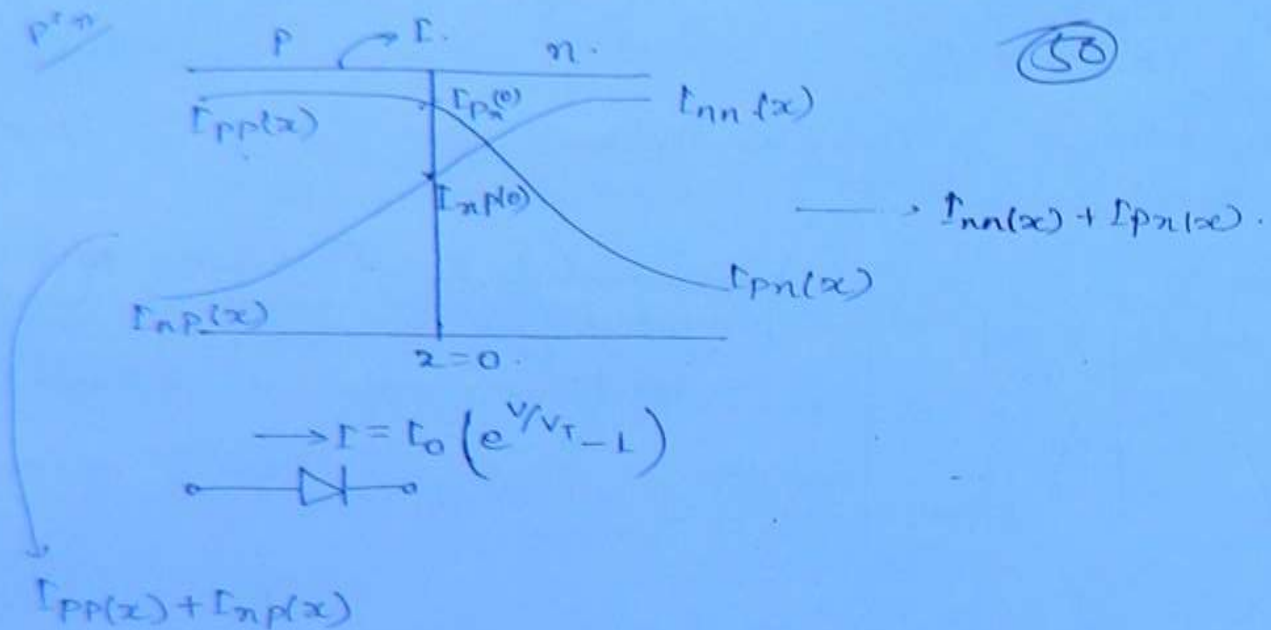


At $x=0$, minority \rightarrow minority
 $I = I_{pn}(0) + I_{np}(0)$

$$I_{pn}(x) = -AqD_p \frac{dp(x)}{dx} \rightarrow p_n'(0) e^{-x/L_p}$$

$$= \frac{-AqD_p p_n'(0) e^{-x/L_p}}{-L_p}$$

at $x=0$,
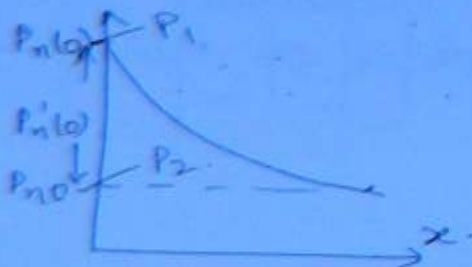
$$I_{pn}(0) = \frac{AqD_p p_n'(0)}{L_p} = AqD_p p_{n0} (e^{V/V_T} - 1)$$



$$p_n(0) = p_{n0} e^{V/V_T} \rightarrow \text{Law of } j^2$$

$$p_n'(0) = p_n(0) - p_{n0}$$

$$= p_{n0} (e^{V/V_T} - 1)$$

$$p_1 = p_2 e^{x_2/x_1}$$

$$I = \left[\frac{AqD_pP_n(0)}{L_p} + \frac{AqD_nn_p(0)}{L_n} \right] (e^{\frac{V}{V_T}} - 1)$$

↓
 I_0

(5)

31/12/11

Diode current equation : \rightarrow

$$I = I_0 \left(e^{\frac{V}{\eta V_T}} - 1 \right)$$

$I \rightarrow$ Total current through diode

$I_0 \rightarrow$ Reverse saturation current

$V \rightarrow$ Applied Voltage.

\rightarrow +ve FB

\rightarrow -ve RB

$\eta \rightarrow$ Idealised factor

= 1 (Ge)

= 2 (Si).

$V_T \rightarrow$ Volt eq temp.

$$= \frac{T}{11,600}$$

At 300K, $V_T \rightarrow 26\text{mV}$.

Diode current eqⁿ can also be called as v-i char. eqⁿ.

VI characteristics of P-n diode : \rightarrow

$$I = I_0 \left(e^{\frac{V}{\eta V_T}} - 1 \right)$$

Case 1. \rightarrow


FB.

$V \rightarrow$ +ve

$$I = I_0 \left(e^{\frac{V}{\eta V_T}} - 1 \right)$$

$$e^{\frac{V}{\eta V_T}} \gg 1$$

$$I = I_0 e^{\frac{V}{\eta V_T}}$$

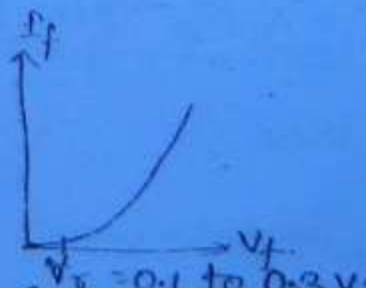

Cut-in voltage = 0.5 to 0.7 V (Si)

Case 2:

RB.

$V \rightarrow -\infty$

$$I = I_0 \left(e^{-V/nV_T} - 1 \right)$$

$$e^{-V/nV_T} \ll 1$$

$$I = -I_0$$



(S2)

Temp dependence on VI char. of P-n diode \rightarrow


$$I = I_0 \left(e^{\frac{V}{nV_T}} - 1 \right)$$

I_0 vs $T \rightarrow$

$$I_0 = \left[\frac{AqD_p p_{n0}}{L_p} + \frac{AqD_n n_{p0}}{L_n} \right]$$

$$= \left[\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right] Aq n_i^2$$
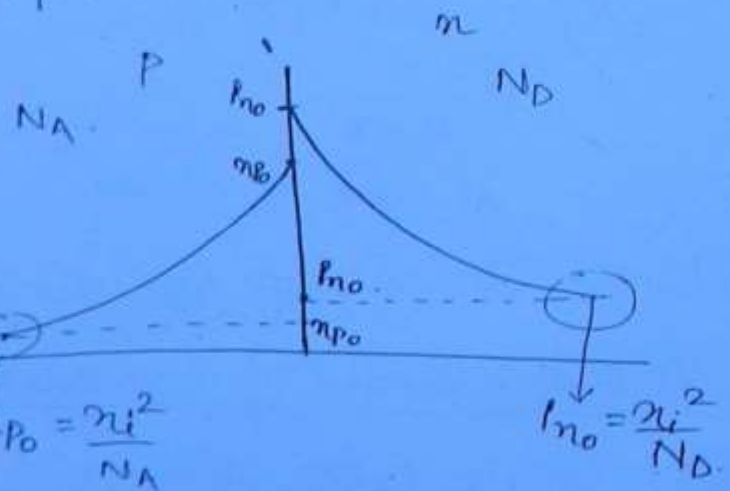
$$= \frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A}$$



Property \rightarrow

Si

$$I_0 \propto n_i$$

Ge

$$I_0 \propto \frac{1}{T}$$

$$n_i^2 = A_0 T^3 e^{-E_g/KT}$$

For Si \rightarrow

$$I_0 = K_1 T^{3/2} e^{-\frac{E_g}{2KT}}$$

For Ge,

$$I_0 = K_2 T^2 e^{-\frac{E_{g0}}{kT}}$$

(S3)

$$I_0 = K' T^m e^{-\frac{E_{g0}}{\eta kT}}$$

	m.	E_{g0}	η .
Si	1.5	1.21	2
Ge	2	0.785	1

Relative temp co-eff of I_0

$$\frac{\partial I_0}{I_0} / \partial T$$

$$\ln I_0 = \ln K' + m \ln T - \frac{E_{g0}}{\eta kT}$$

diff w.r.t T

$$\frac{1}{I_0} \frac{dI_0}{dT} = 0 + \frac{m}{T} + \frac{E_{g0}}{\eta kT^2}$$

Ge.

$$\frac{\partial I_0}{I_0} / \partial T = \left[\frac{2}{300} + \frac{0.785}{k \times 1.0.026 \times 300} \right] = 10.7 \% / ^\circ C$$

Si,

$$\frac{\partial I_0}{I_0} / \partial T = \frac{1.5}{300} + \frac{1.21}{2 \times 0.026 \times 300} = 8.2 \% / ^\circ C$$

} $7 \% / ^\circ C$

$$(1.07)^{10} = 2$$

→ For every $10^\circ C$ rise in temp, I_0 will be double

→ For every $1^\circ C$ " " " , I_0 will be 7%.

1) I_0 increases by 7% for every degree centigrade rise in temp. I_0 doubles for every $10^\circ C$ rise in temp.

Applied Voltage V/s Temp: \rightarrow

$$\frac{dv}{dT} = -2.5 \text{ mV}/^{\circ}\text{C}$$

(54)

$$I = I_0 \left(e^{\frac{V}{\eta V_T}} - 1 \right)$$

F.B.

$$I = I_0 e^{\frac{V}{\eta V_T}}$$


$$\Rightarrow V = \eta V_T \ln\left(\frac{I}{I_0}\right)$$

diff. w.r.t T.

$$\begin{aligned} \frac{dV}{dT} &= -0.0019 \text{ V} ; -0.0017 \text{ V} \rightarrow (-2 \text{ mV}/^{\circ}\text{C}) \\ &= -1.9 \text{ mV} ; -1.7 \text{ mV} \rightarrow 0.5 \text{ mV} \\ &\quad \downarrow \quad \quad \downarrow \\ &\quad \text{Si} \quad \quad \text{Ge} \end{aligned}$$

$$\begin{aligned} \frac{dV_D}{dT} &= \left[\frac{I_0}{I} \right] \cdot \left[-2.5 \text{ mV}/^{\circ}\text{C} \right] , \quad \left[-2 \text{ mV}/^{\circ}\text{C} \right] \\ &\quad \downarrow \quad \quad \downarrow \\ &\quad \text{on } 0.7 \text{ mV} \quad , \quad \text{on } 0.5 \text{ mV} \end{aligned}$$

eg.

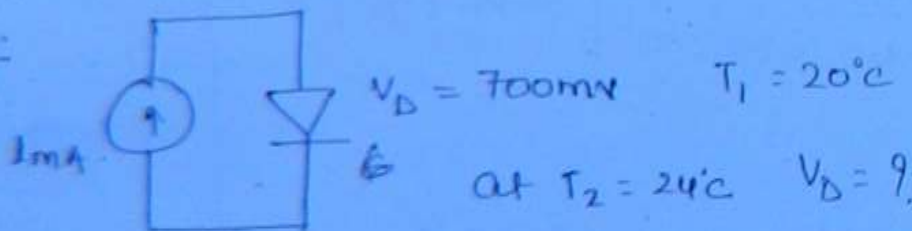

4m.

$$\frac{dv}{dT} = -2.5 \text{ mV}$$


$$\begin{aligned} \therefore V_D &= 0.7 \text{ V} - 4 \times 2.5 \\ &= 0.700 \text{ mV} - 10 \text{ mV} \\ &= 690 \text{ mV} \end{aligned}$$

As $T \uparrow$, $I_0 \uparrow$ and $V_D \downarrow$
 V_T v/s Temp \rightarrow
 $V_T = \frac{T}{11600}$

(SS)

$T \uparrow, V_T \uparrow$

Q.

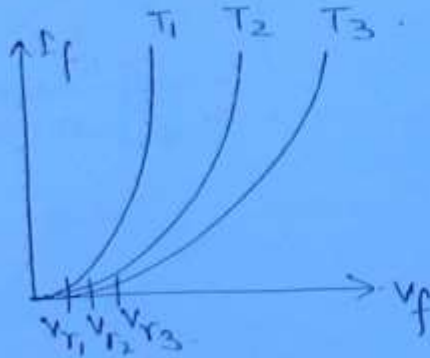

$T \uparrow, V_f \downarrow$


a) $T_1 < T_2 < T_3$

☒ b) $T_1 > T_2 > T_3$

c) $T_1 = T_2 = T_3$

d) None.


Q.

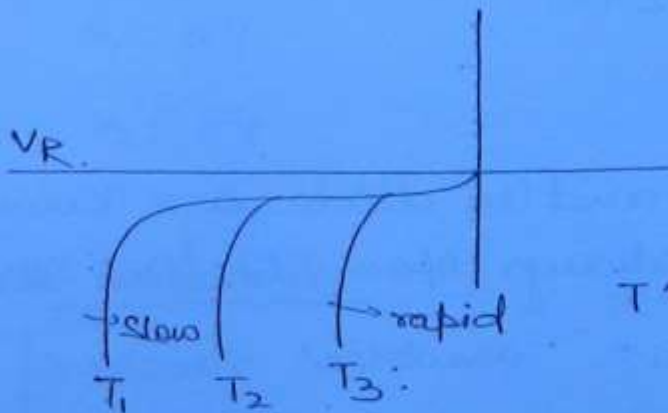

$T \uparrow, I_0 \uparrow$

$T_3 > T_2 > T_1$

Q.

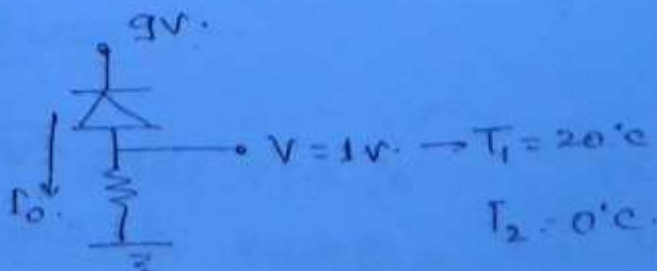


0°C I_0 10°C 20°C 30°C 40°C
 $\frac{I_0}{4}$ $\frac{I_0}{2}$ I_0 $2I_0$ $4I_0$


(56)

at $T_2 = 0^\circ\text{C}$, $V_k = 0.25\text{V}$

Q.

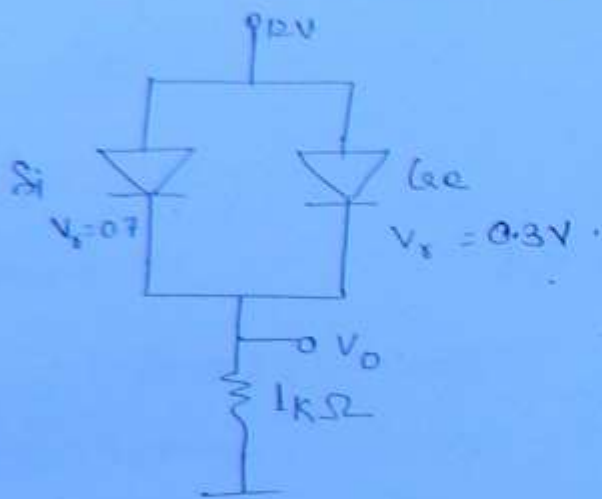


Ans.

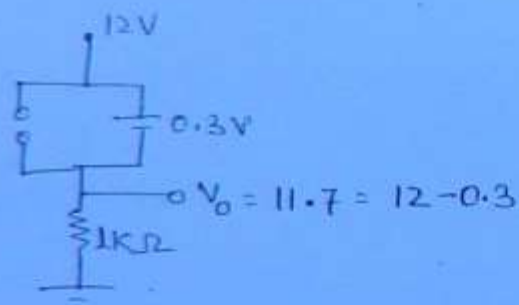

- When a practical Silicon and Ge diode are connected in parallel, Silicon will be always open ckt (OFF state)

Q.

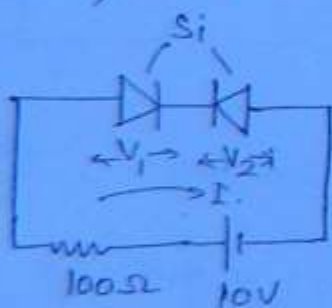

$V_1 =$

- ~~a) 0.7~~ b) 9.3V
 c) 8.6V d) 2.6V

$V_2 =$

- a) 0.7V ~~b) 9.3V~~
 c) 8.6V d) 2.6V


$$I =$$

a) 3mA b) $\frac{3}{2}\text{mA}$

c) 6.2mA d) I_0

(57)

2)

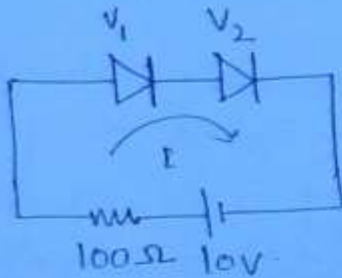


$$V_1 = 0.7$$

$$V_2 = 0.7$$

$$I = 86\text{mA} = \frac{10 - 0.7 - 0.7}{100} = 86 \times 10^{-3}\text{A}$$

3)

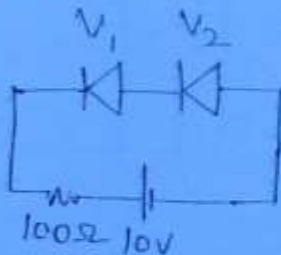

$$V_1 = 5\text{V}$$


$$V_2 = 5\text{V}$$

$$I = I_0$$

Diode resistance →


→ Static Resistance

$$R = \frac{V}{I}$$

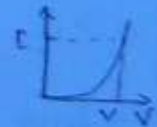

→ Dynamic Resistance

$$r = \frac{\partial V}{\partial I}$$

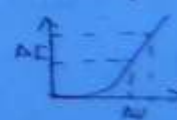

Static resistance : →

$$R = \frac{V}{I}$$

F.B.

$$R = \frac{V}{I} = \frac{0.7\text{V}}{100\text{mA}} = 7\Omega$$

R.B. →

$$R = \frac{V}{I} = \frac{10V}{1 \mu A} = 10 M\Omega$$

Dynamic Resistance →

(58)

$$r = \frac{\partial V}{\partial I}$$

$$g = \frac{\partial I}{\partial V}$$

$$= \frac{\partial I_0 \left(e^{\frac{V}{\eta V_T}} - 1 \right)}{\partial V}$$

$$= \frac{I_0 e^{\frac{V}{\eta V_T}}}{\eta V_T}$$

$$I = I_0 \left(e^{\frac{V}{\eta V_T}} - 1 \right)$$

$$\frac{V_T}{V/s \text{ temp}}$$

$$V_T = \frac{T}{11600}$$

#

$$g = \frac{I + I_0}{\eta V_T}$$

For F.B. →

$$g = \frac{I}{\eta V_T}$$

Typically

$$\eta = 1, I = 100 \mu A, V_T = 26 mV$$

$$g \gg 1$$

$\gamma \rightarrow \text{loss}$

For R.B. →

$$g = \frac{2 I_0}{\eta V_T} < 1$$

$\gamma \rightarrow \text{high}$

Transition Capacitance : \rightarrow

\rightarrow transition capacitance \rightarrow R.B.


\rightarrow Diffusion capacitance \rightarrow F.B.

(59)

Transition means depletion region. Depletion region exist only in R.B.

Diffusion is a process occurs in Forward Bias because of negligible depletion region.

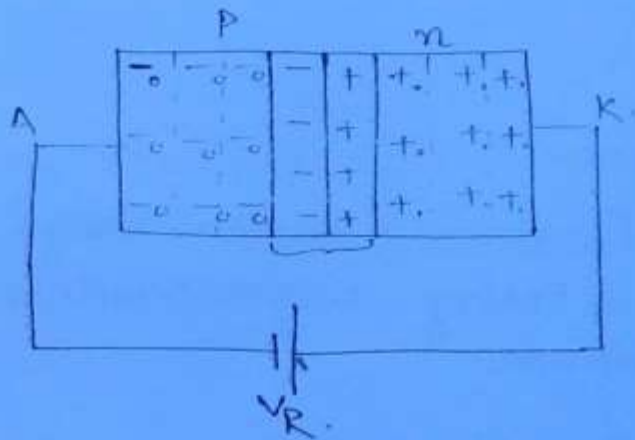Transition capacitance : — $C_S \rightarrow$ space charge.
(C_T)



The rate of change of charge with the applied voltage — capacitance

The rate of change of immobile charge in the depletion region with the applied R.B. Voltage is a capacitive effect called as transition capacitance.

$$C = \frac{\epsilon A}{d}$$

$$C_T = \frac{\epsilon A}{W}$$

$$W \propto \sqrt{V_j} \quad W \propto \sqrt[3]{V} \quad \left. \vphantom{W \propto \sqrt{V_j}} \right\} \rightarrow \text{open ckt}$$


↓ ↓
(Alloy type) (Crown Jⁿ)

$$W \propto \sqrt{V_j + V_R} \quad W \propto \sqrt[3]{V_j + V_R} \quad \left. \vphantom{W \propto \sqrt{V_j + V_R}} \right\} \rightarrow \text{R.B.}$$

$$C_T \propto \frac{1}{\sqrt{V_R}} \rightarrow \text{away type}$$

$$C_T \propto \frac{1}{\sqrt[3]{V_R}} \rightarrow \text{known type} \quad (68)$$

Diffusion Capacitance \rightarrow

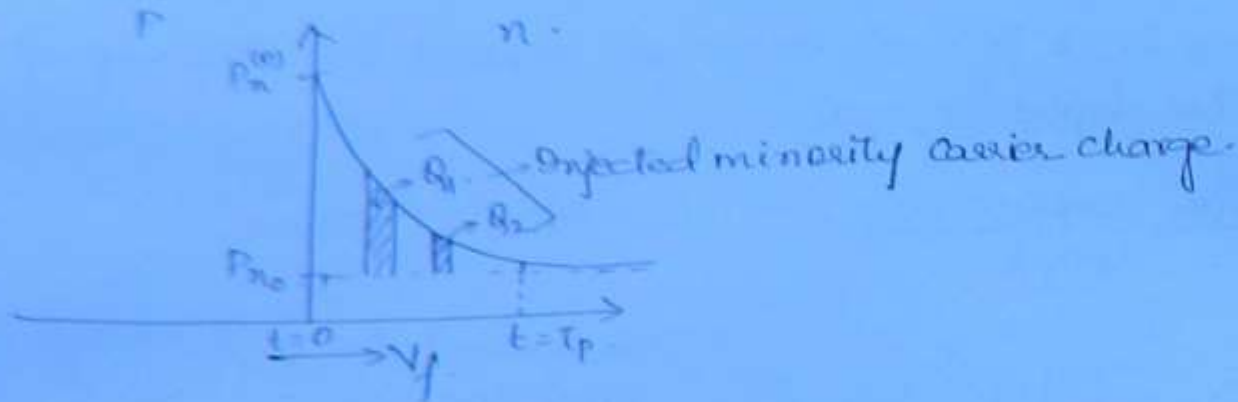

$p_n^{(i)}$ — injected minority carrier conc.

The rate of change of injected minority carrier charge with the applied forward bias voltage is a capacitive effect called as diffusion capacitance.

$$Q = I_p \times \tau_p$$

$$C_D = \frac{dQ}{dV} = \tau_p \frac{\partial I_p}{\partial V} \rightarrow \frac{I_p + V_0}{\eta V_T}$$


$$C_D = \frac{\tau_p \partial I_p}{V_T}$$

2/01/12 Diode equivalent models \rightarrow


$$V_f \geq V_r + I_f R_f$$

Case 1 \rightarrow

$$R_f = \text{const.}$$

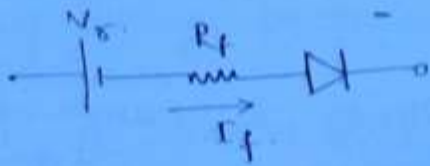


(61)

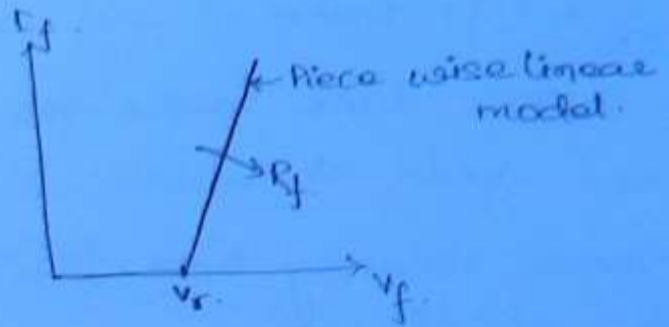

Case 2 →


$$R_f = 0$$

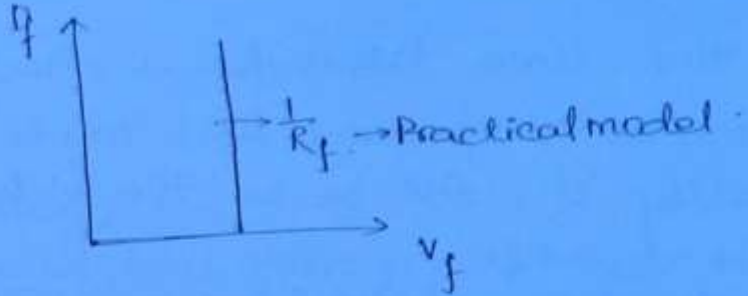


Case 3 →

Ideal model

$$V_s = 0, R_f = 0$$

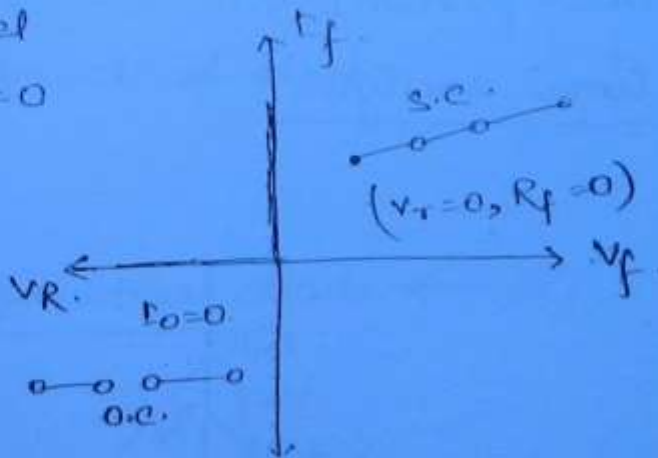

Diode Switching times : →

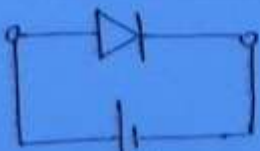

Reverse Recovery time
"t_{rr}"



Forward Recovery time
"t_{fr}"

t_{rr} :-

It is the time taken for a diode to change forward biased mode to reverse biased mode.

Reverse recovery time practically, it will be in the order of μs. (62)




t_{fr} :-

It is the time taken for a diode to change reverse bias mode to forward bias mode.

Practically it will be in the order of Pico secs.

In high freq. applications, forward recovery time is neglected in the analysis (Pico secs) but reverse recovery time becomes a serious problem (μs)

Reverse Recovery time analysis :- →

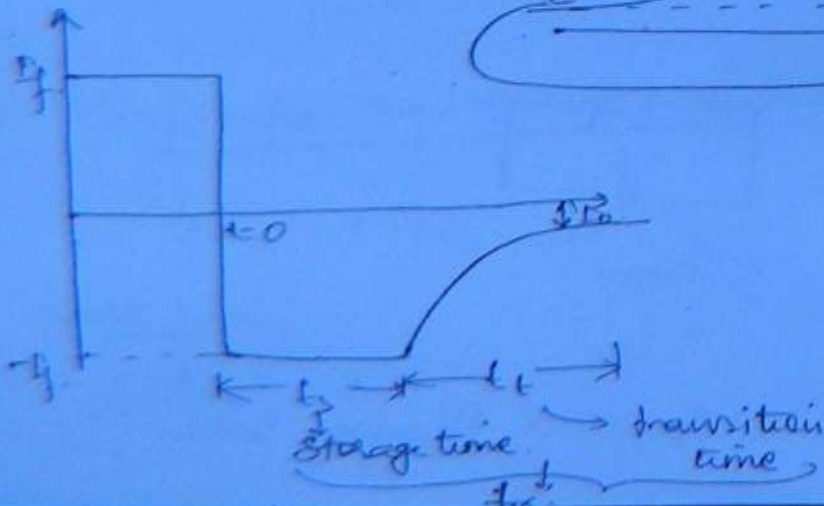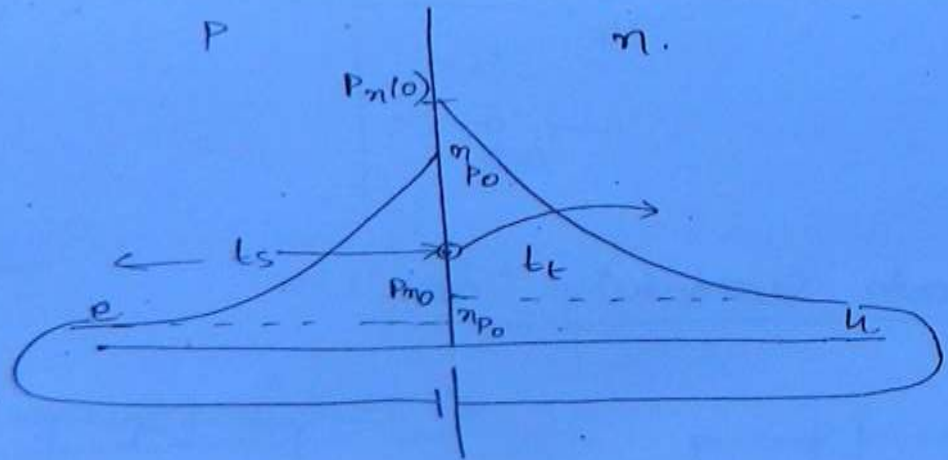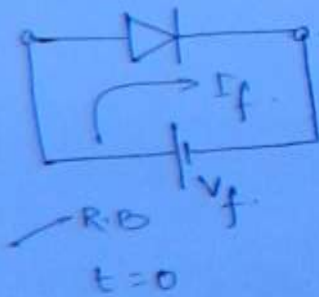

Q Why Si is preferred over Ge in most of the applications?

Ans. 1) Temp $\begin{cases} 200^\circ\text{C} (\text{Si}) \\ 100^\circ\text{C} (\text{Ge}) \end{cases}$

2) PIV $\begin{cases} 400\text{V} (\text{Ge}) \\ 1000\text{V} (\text{Si}) \end{cases}$

(63)

PIV (Peak Inverse Voltage) \rightarrow

It is the max reverse bias voltage applied to a diode.

The main drawback of Silicon is cut-in voltage.

Diode problems \rightarrow


\rightarrow Ideal and practical diode.

\rightarrow Clippers.

\rightarrow Clampers.


Ideal and practical diode:—

Model 1.

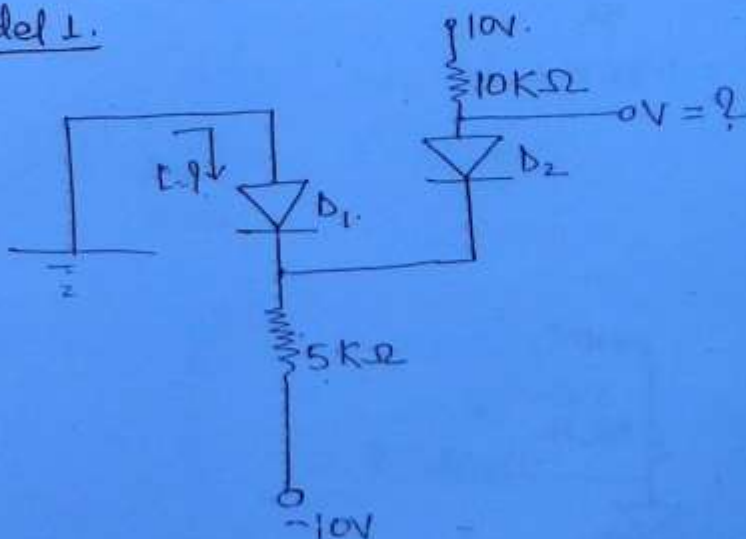


Assume D_1 and D_2 DB.

(64)

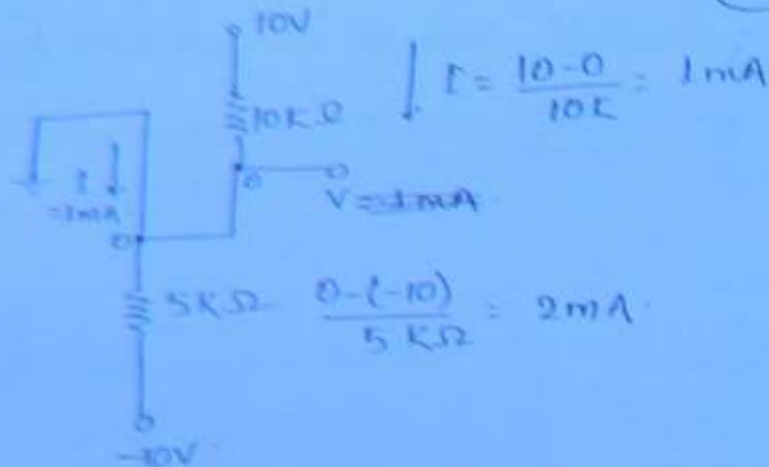


$V = 0V$
 $I = 1mA$

Practical \rightarrow

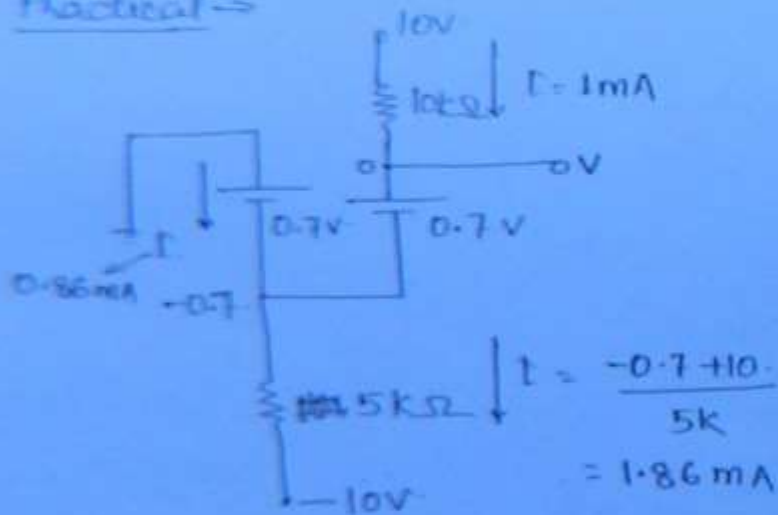


$V = 0V$
 $I = 0.86mA$

model 2

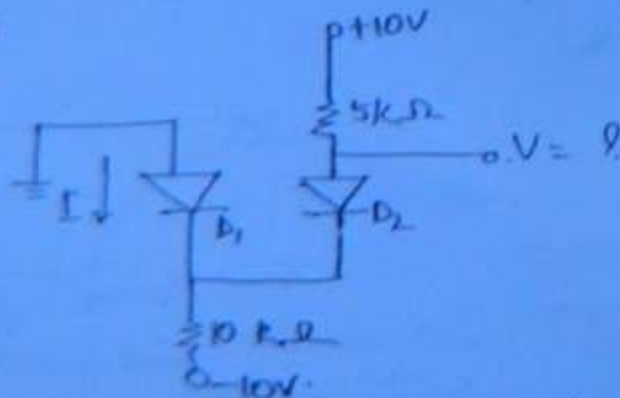


Single branch problem. → MODEL-2.


I.

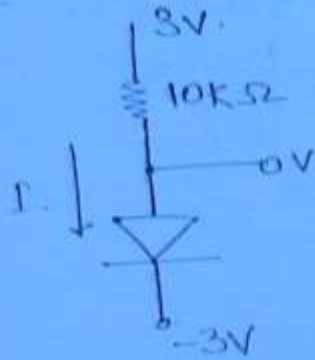


II.

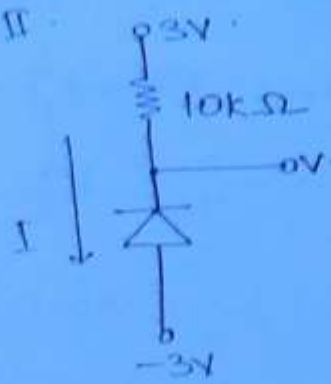


III.

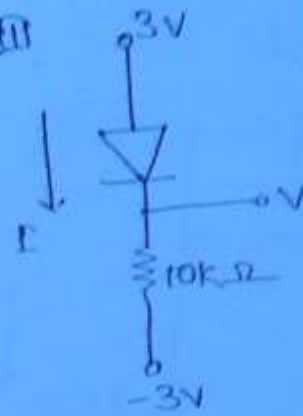

IV.

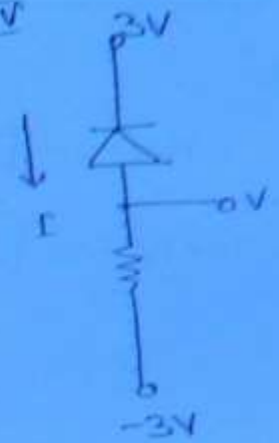

I.

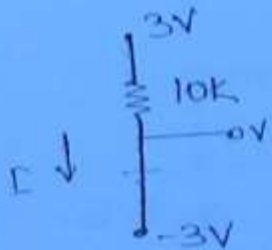


$$I = \frac{3 - (-3) \text{ V}}{10\text{K}}$$

$$= 0.6 \text{ mA}$$

$$V = -3 \text{ V}$$

(65)


II.

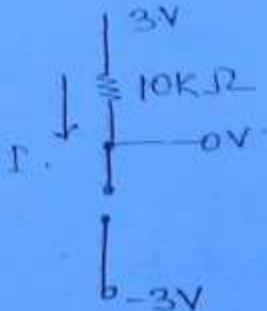

$$I = 0$$

$$V = 3 \text{ V}$$

III.

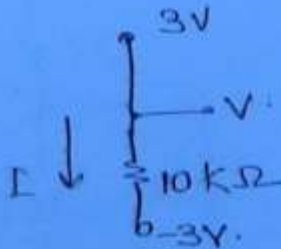

$$V = 3 \text{ V}$$

$$I = 0.6 \text{ mA}$$

IV.



$$V = -3 \text{ V}$$



$$I = 0$$

model - 3. →


I.

(66)

II.

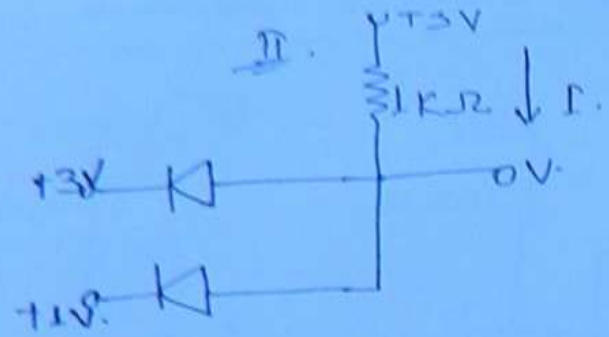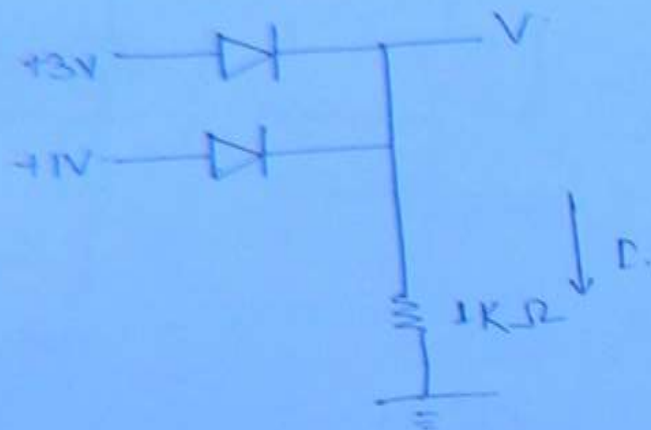

OR - logic.

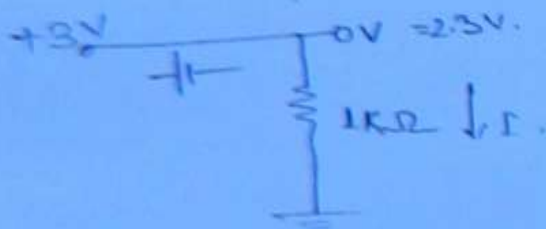


highest voltage is F.B.

$$V = 3V$$

$$I = 3mA$$

AND logic.

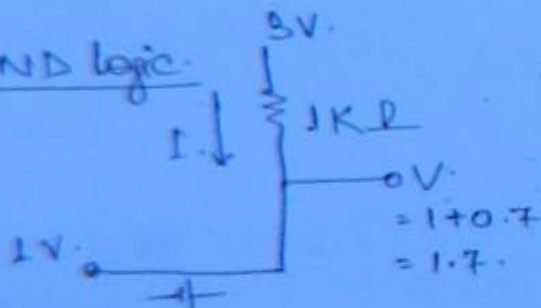

lowest voltage is F.B.



$$I = 2mA$$

$$V = 1V$$

- In OR logic problems highest I/P voltage applied to the diode will be the O/P.
- In AND logic problems, lowest I/P voltage applied to the diode will be the O/P.

ideal →

Assume D_1 and D_2 are F.B.

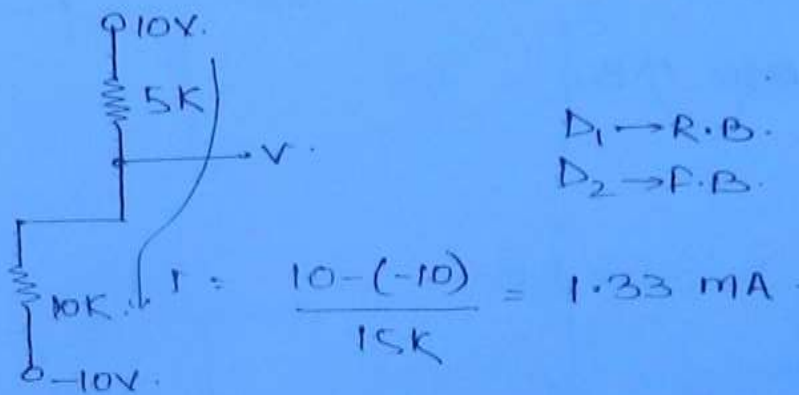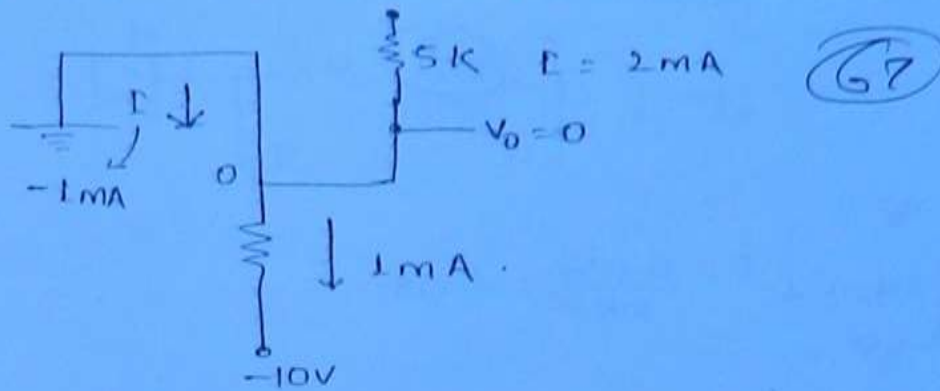


$D_1 \rightarrow \text{R.B.}$
 $D_2 \rightarrow \text{F.B.}$

$$V = 10\text{K} \times 1.33\text{mA} - 10$$


$$= 13.3 - 10$$

$$= 3.3\text{V}$$

Ckt-1

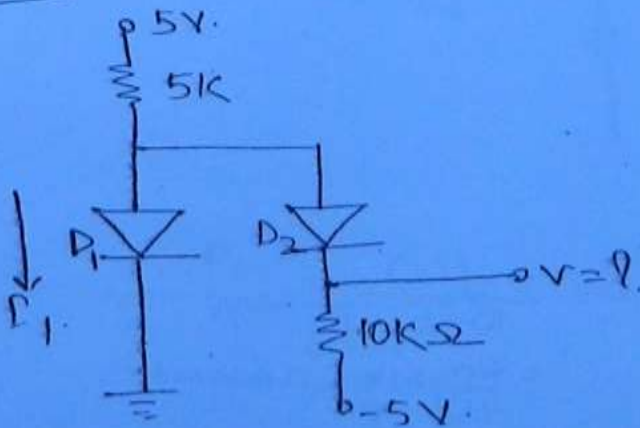


Ckt-2

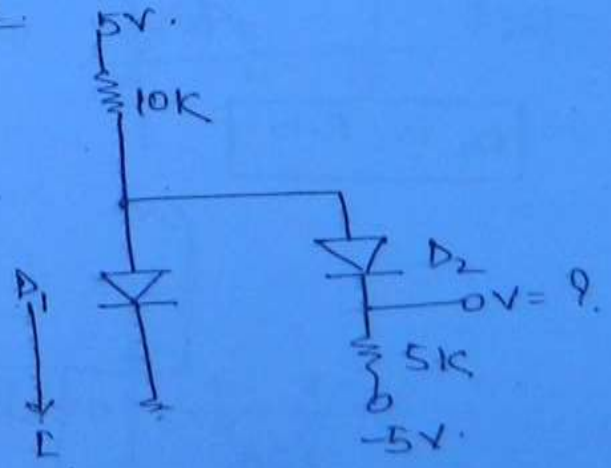

Ckt 1. Assume D_1 and D_2 are F.B.

(68)


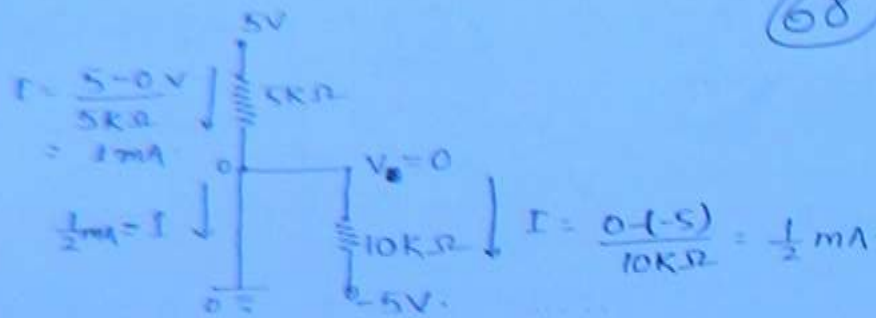


Assumption is true

$\therefore D_1$ and D_2 are F.B.

Ckt 2.

Assume D_1 and D_2 are F.B.

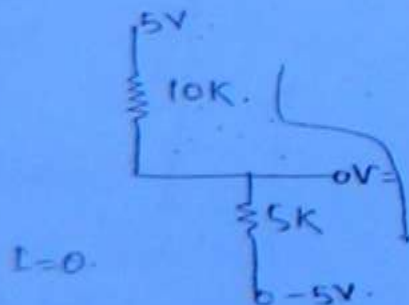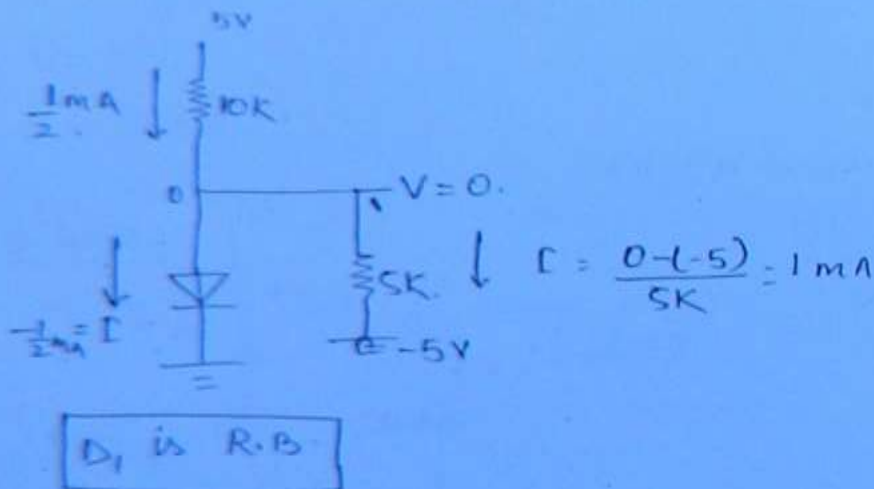







$$I = \frac{5-(-5)}{10+5} = \frac{10}{15} mA = 0.666 mA$$


$$V = 5 - 10K \times 0.666 mA = -1.67 V$$

Model 4:


AC Analysis.

(69)

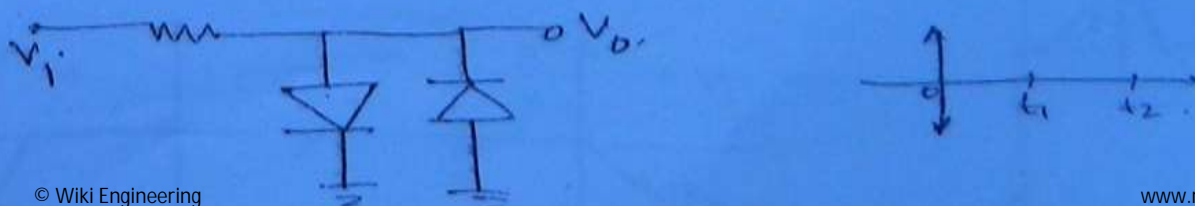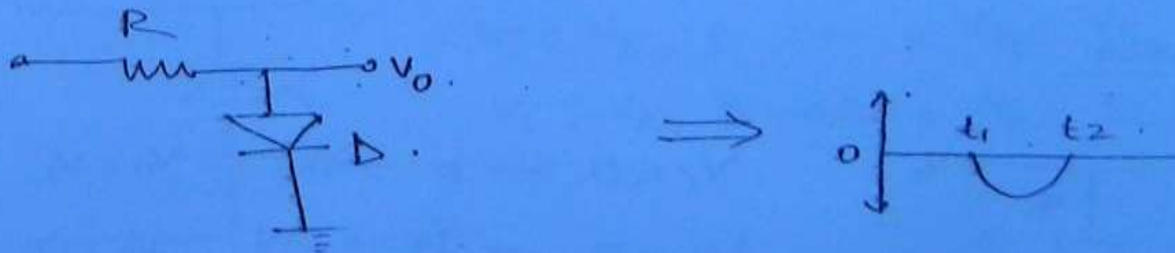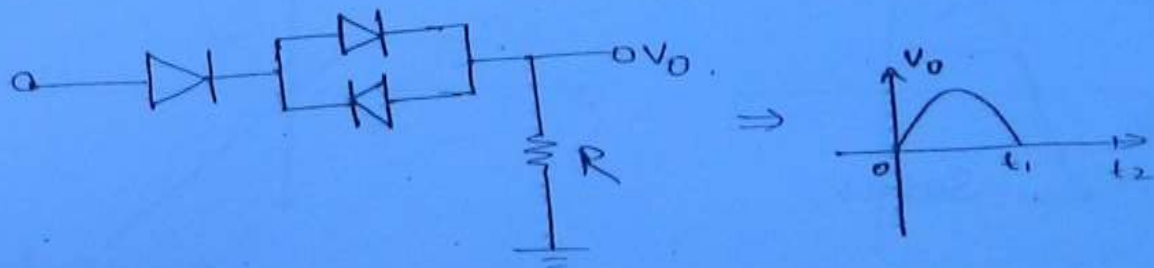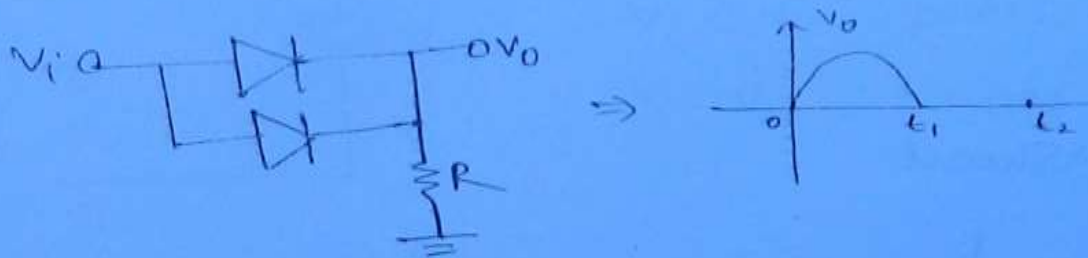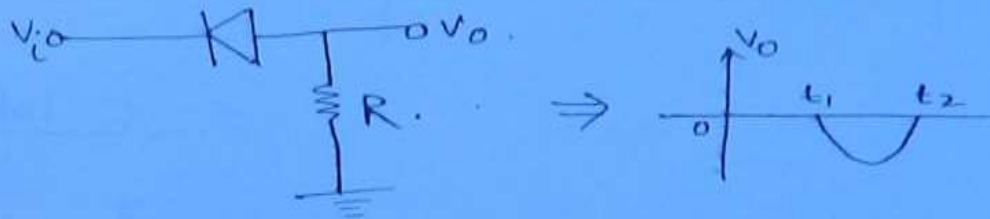
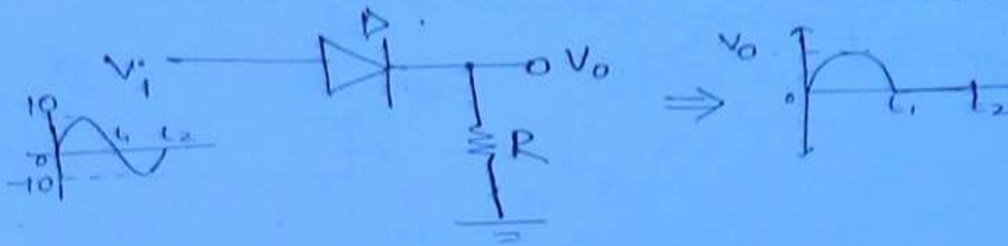


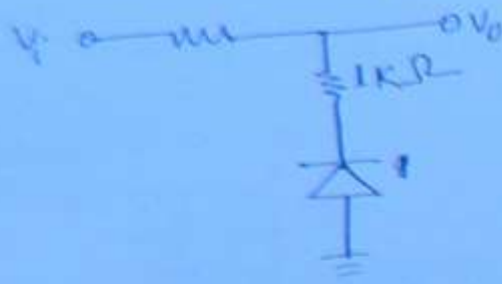



⇒ Approximate

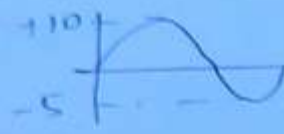


(70)

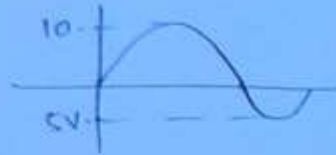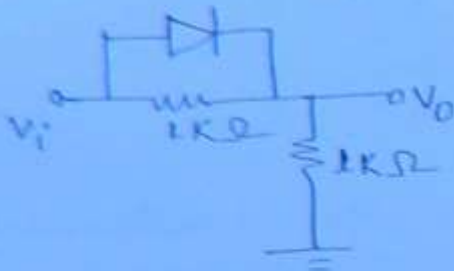

Clippers →

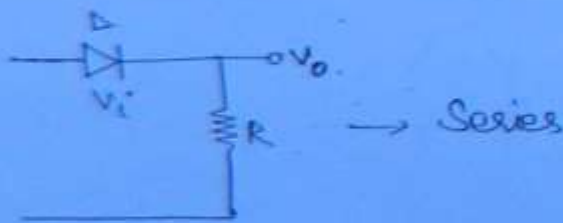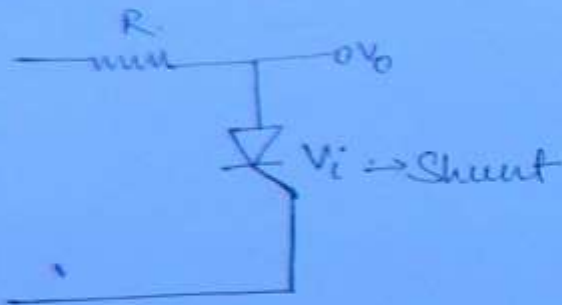


Shunt clippers →

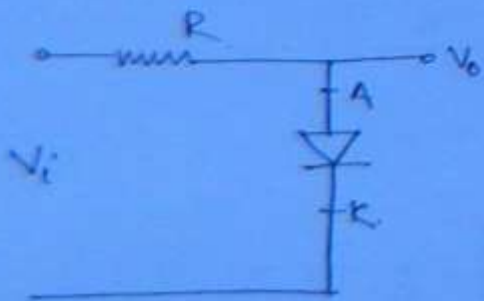


$$V_i < 0 \rightarrow D \rightarrow \text{OFF} \quad V_o = V_i$$

$$V_i > 0 \rightarrow D \rightarrow \text{ON} \quad V_o = 0$$

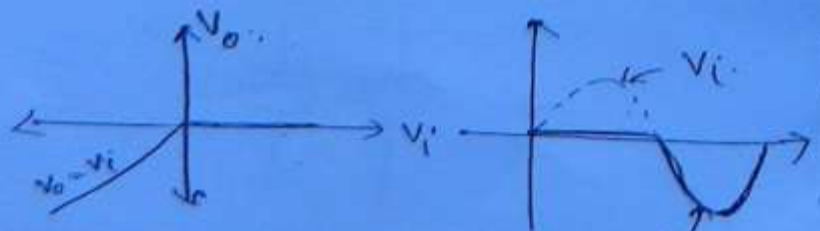



Model 1. →

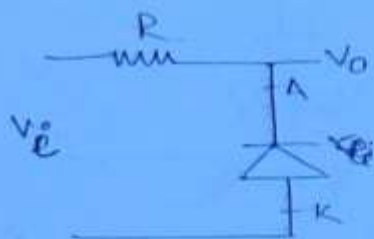


$V_i < 0$, D-ON $V_o \rightarrow 0$.

$V_i > 0$, D-OFF $V_o = V_i$

(21)

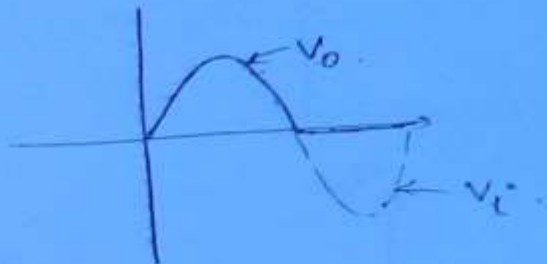
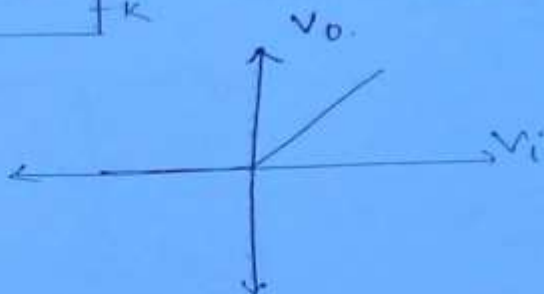


Model-3. →

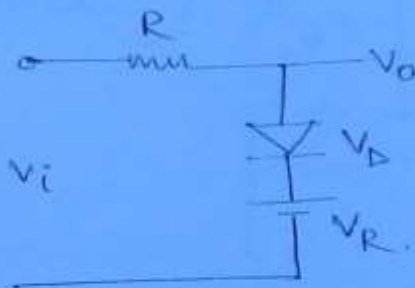


$V_i < V_R$, D-OFF, $V_o = V_i$

$V_i > V_R$, D-ON, $V_o = V_i + V_R$

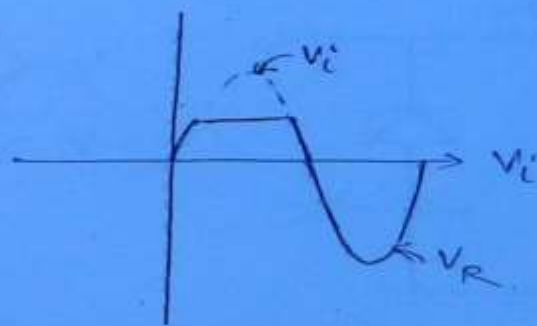
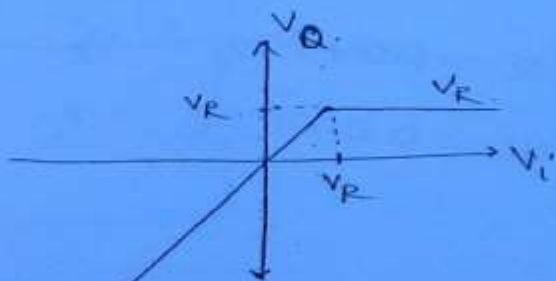


model-4. →

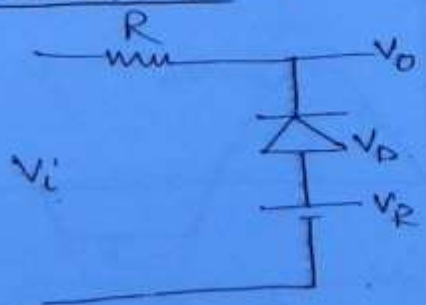


$V_i < V_R$, D-ON, $V_o = V_R$

$V_i > V_R$, D-OFF, $V_o = V_i$

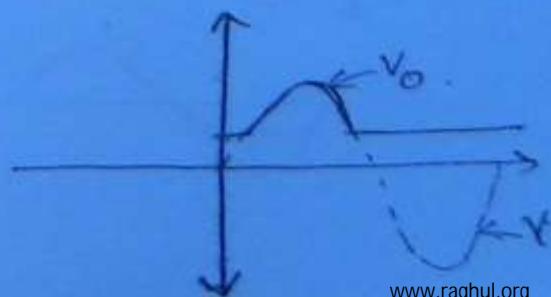
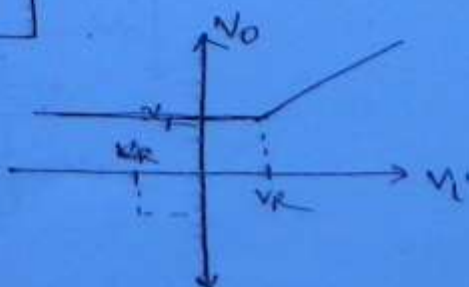


model 5 →

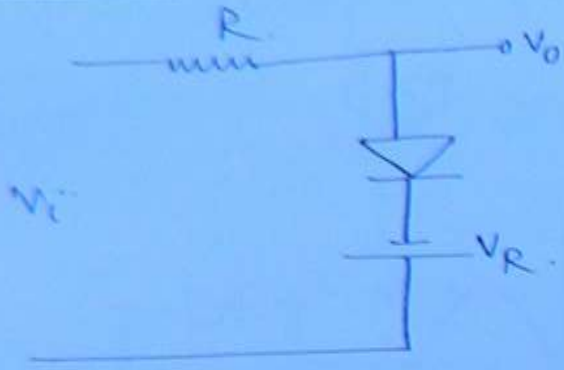


(22)



$V_i < -V_R \rightarrow \text{DOFF} \quad V_o = V_i$
 $V_i \geq -V_R \rightarrow \text{DON} \quad V_o = -V_R$



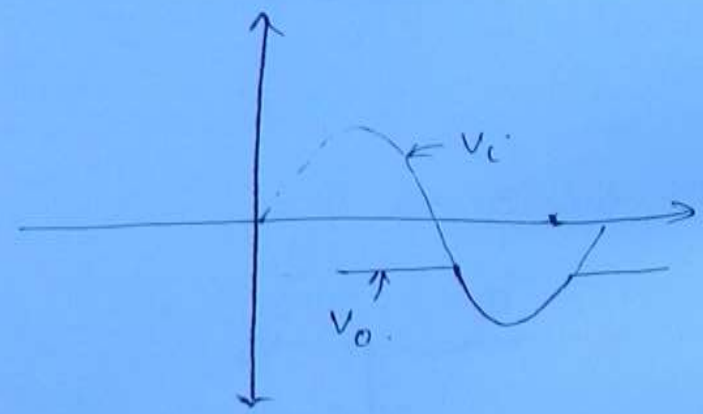
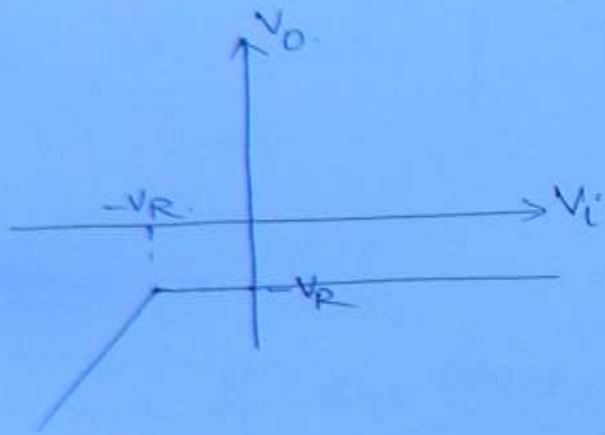


model 6 —

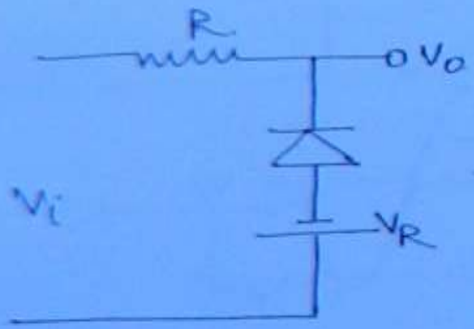

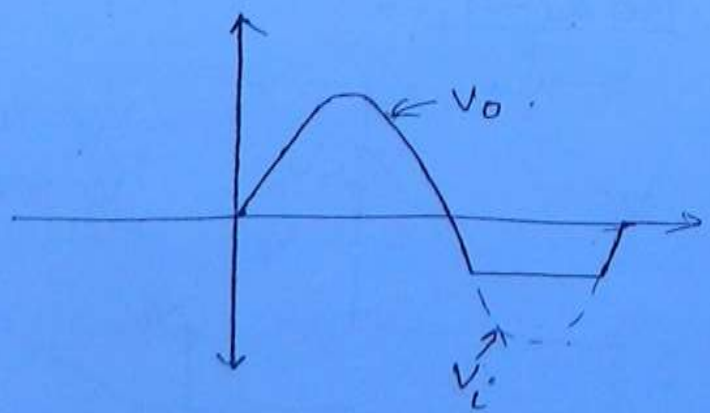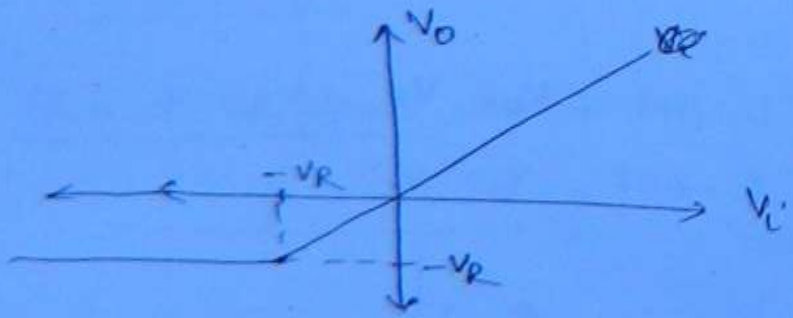$V_i < -V_R \rightarrow \text{DON} \quad V_o = -V_R$
 $V_i \geq -V_R \rightarrow \text{DOFF} \quad V_o = V_i$





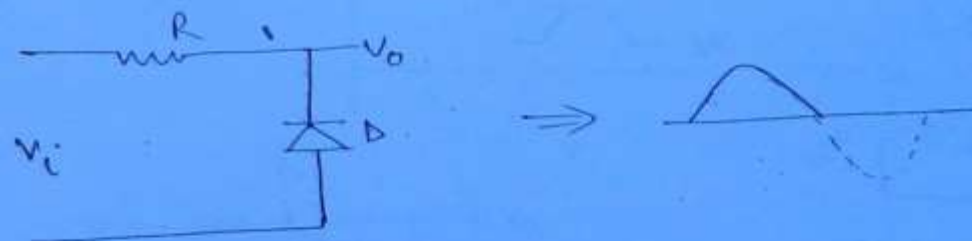
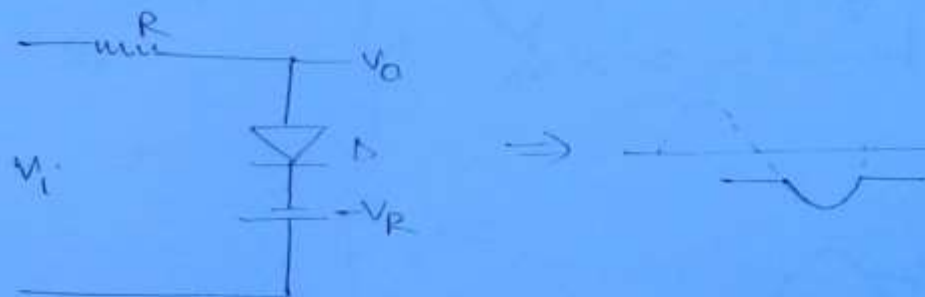
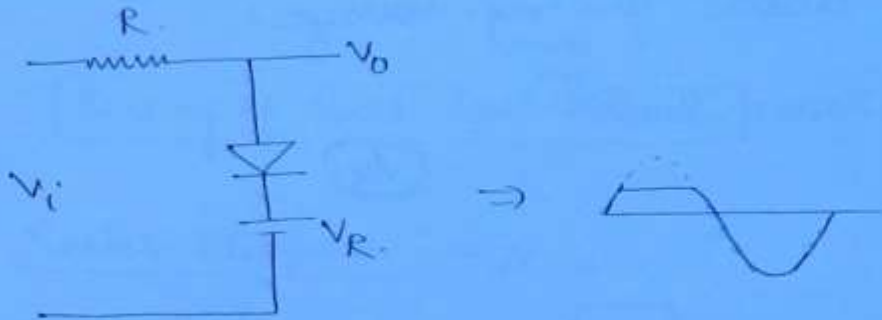
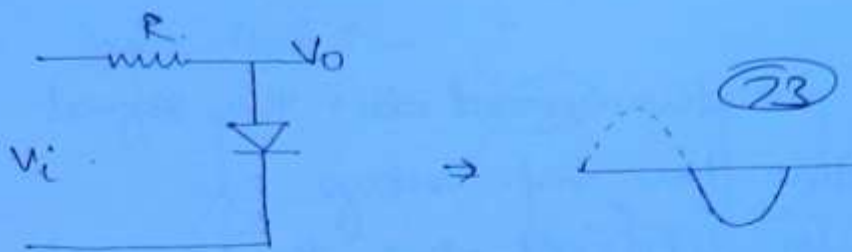


Conclusion . —

- 1) When the diode is in downward dirⁿ the signal will be transmitted below the ref. voltage.
- 2) When the diode is in upward dirⁿ the signal will be transmitted above the ref. voltage.

Typical models → • Zener is ON.


(74)

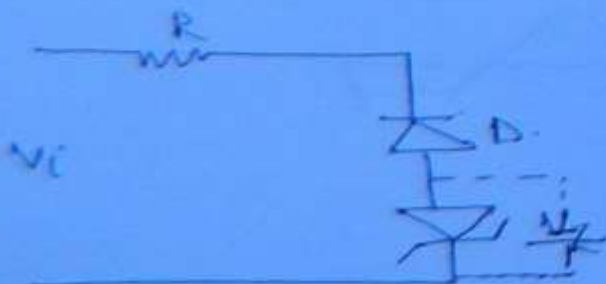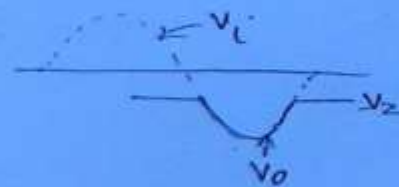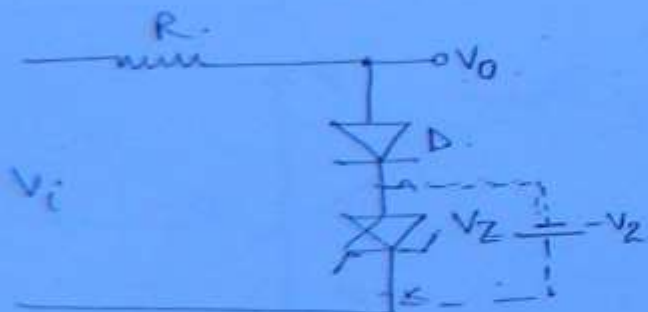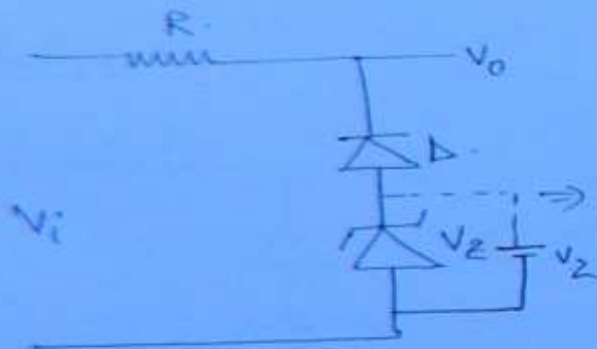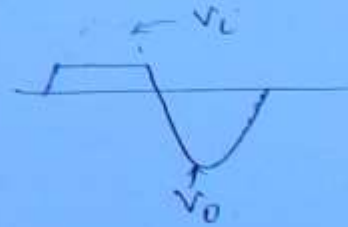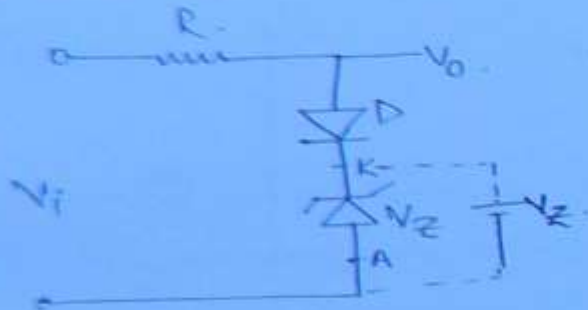

Zener diode →




(28)

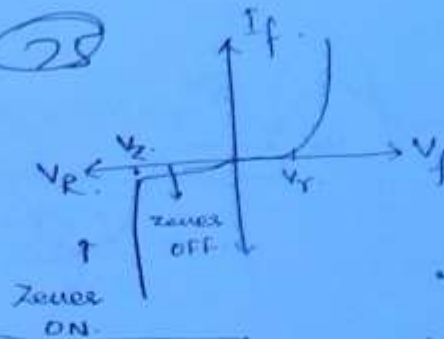

Best eg of const Volt. Source

$V > V_Z \rightarrow \text{ON}$
 $V < V_Z \rightarrow \text{OFF}$
 $V \rightarrow V_f \rightarrow \text{FB}$







Series Clippers →






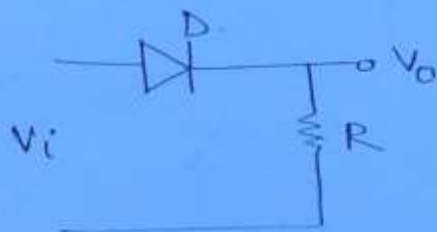


$V_i < 0 \rightarrow D - \text{OFF} \Rightarrow V_o = 0$

$V_i > 0 \rightarrow D \rightarrow \text{ON}$

$V_o = V_i$

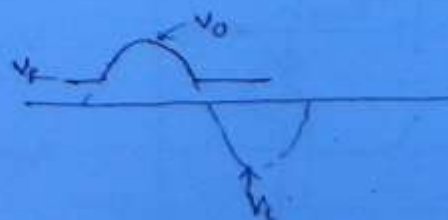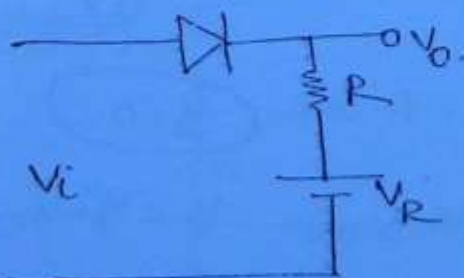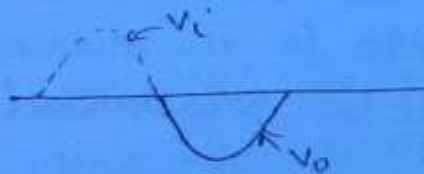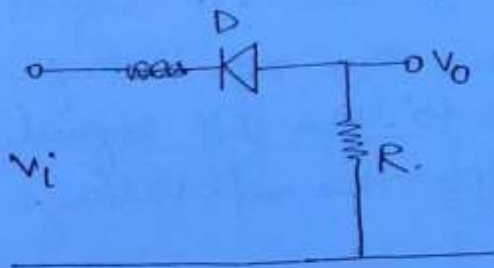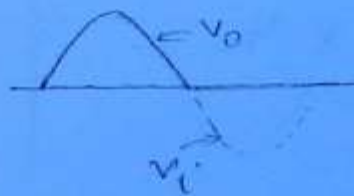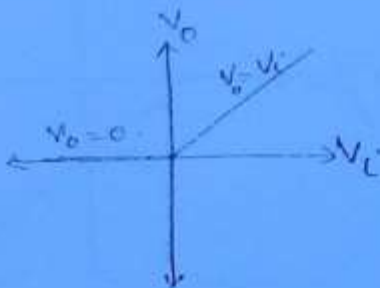


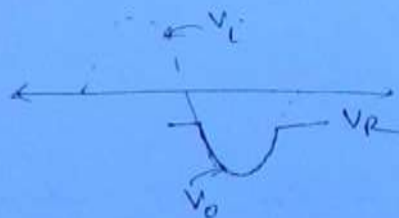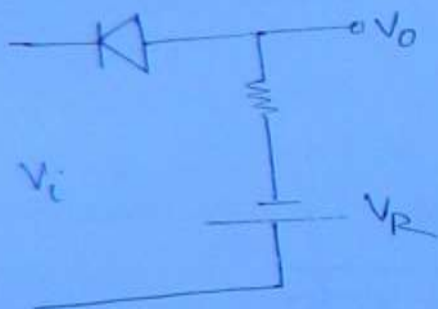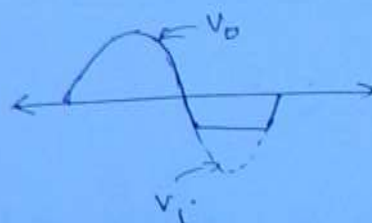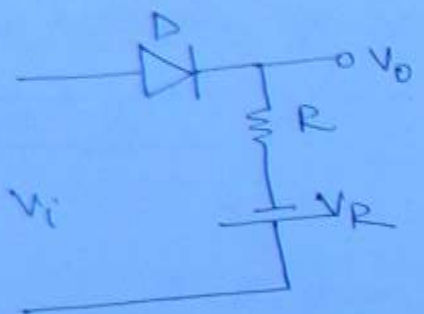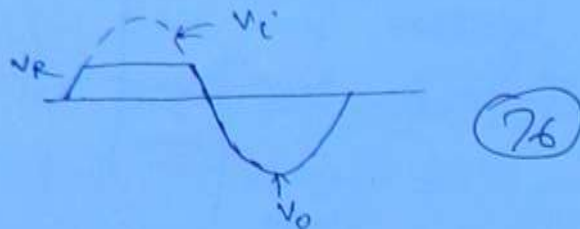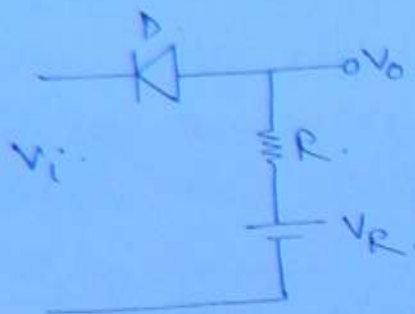

conclusions →



- When the diode is in forward dirⁿ to the I/P signal, the signal will be transmitted above the ref. voltage.
- When the diode is in reversed dirⁿ to the I/P signal, the signal will be transmitted below the ref. voltage.

Output following I/P CKTS →

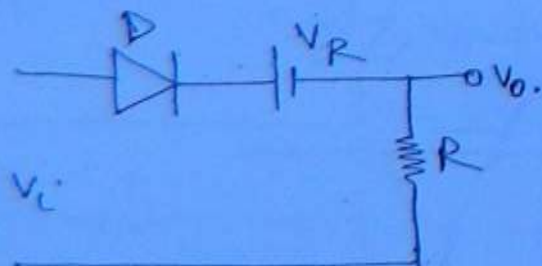


$$V_i < V_R \quad D \text{ OFF} \quad V_o = 0$$
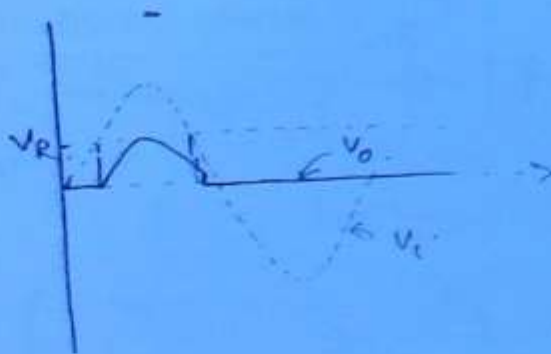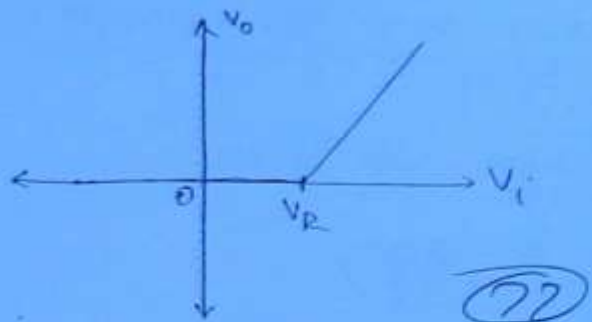
$$V_i > V_R \quad D \text{ ON} \quad V_o = V_i - V_R$$





#

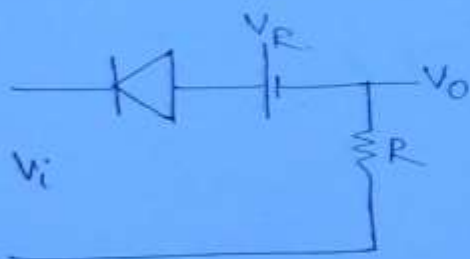


$V_i < V_R$, D-ON, $V_o = V_i - V_R$

$V_i > V_R$, D-OFF, $V_o = 0$

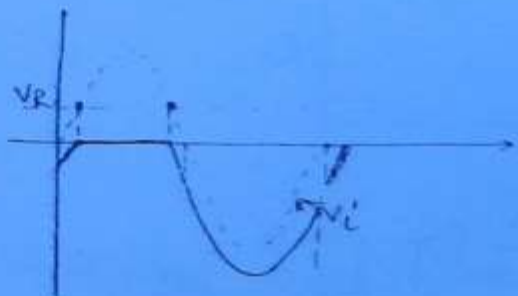
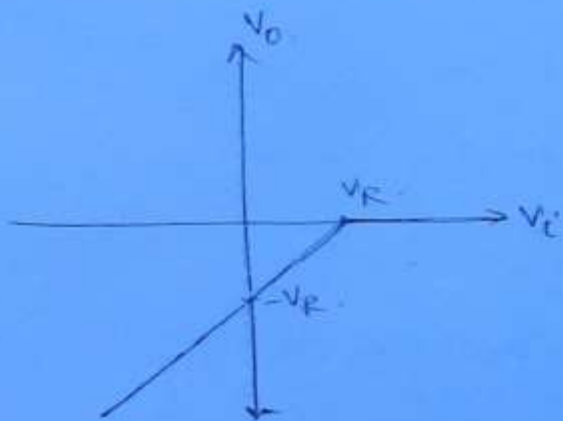



#

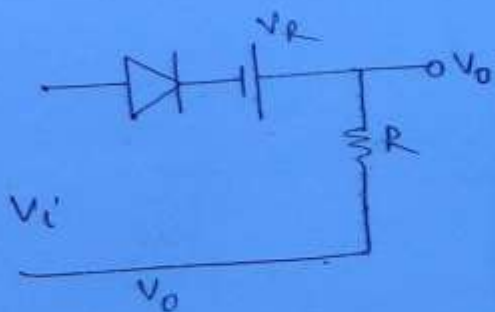

$V_i > V_R$ D ON $V_o = V_i + V_R$

$V_i < -V_R$ D OFF $V_o = 0$


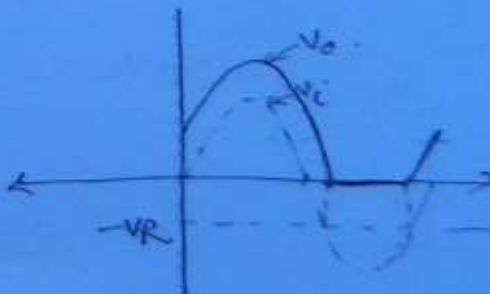
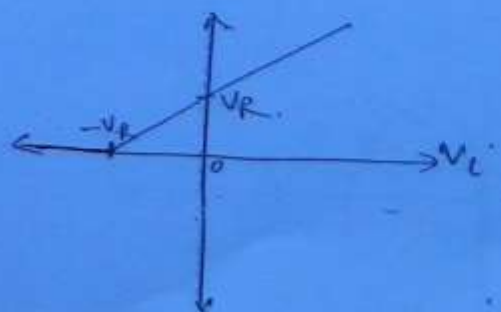


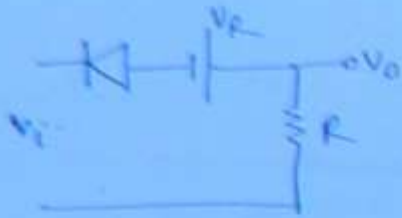

$V_i > -V_R$ D OFF. $V_o = 0$


$V_i < -V_R$ D ON $V_o = V_i + V_R$

(78)

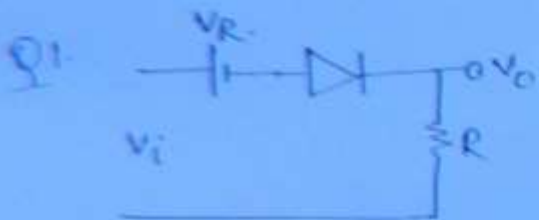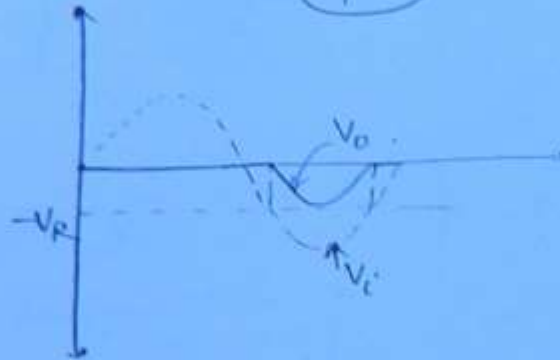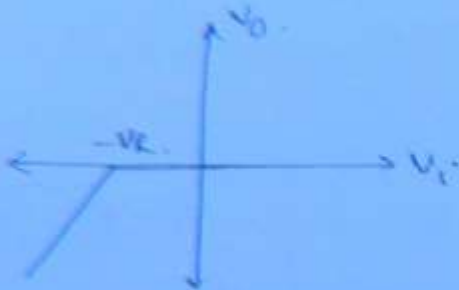

$V_i > V_R$ D ON $V_o = V_i - V_R$



$V_i < V_R$ D OFF $V_o = 0$

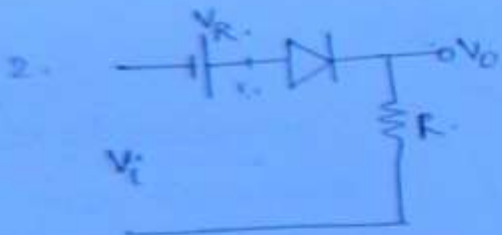



$V_i > -V_R$ D ON $V_o = V_i + V_R$

$V_i < -V_R$ D OFF $V_o = 0$

Sol(1)


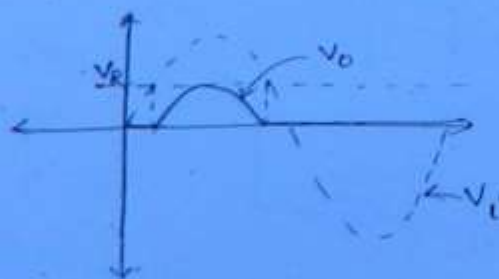
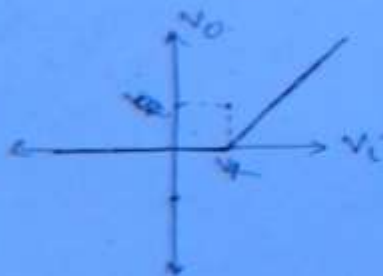


Sol(2)

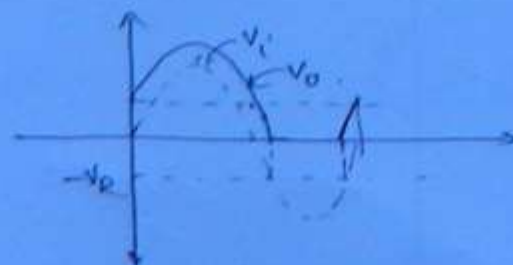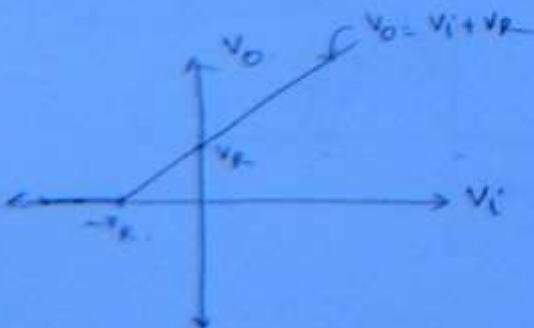

Clipping at two independent levels: \rightarrow

$V_{R1} > V_{R2}$ ← always.

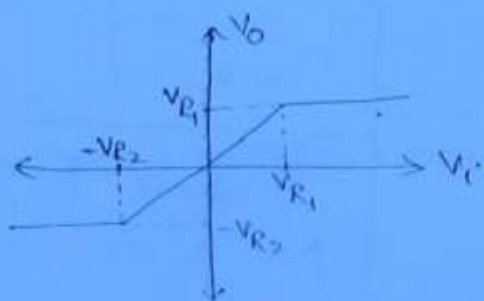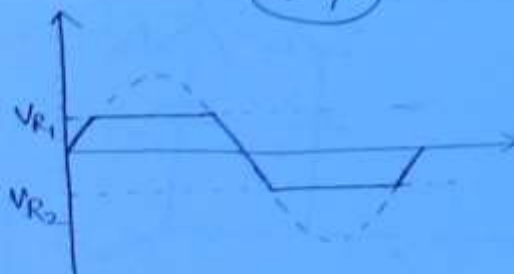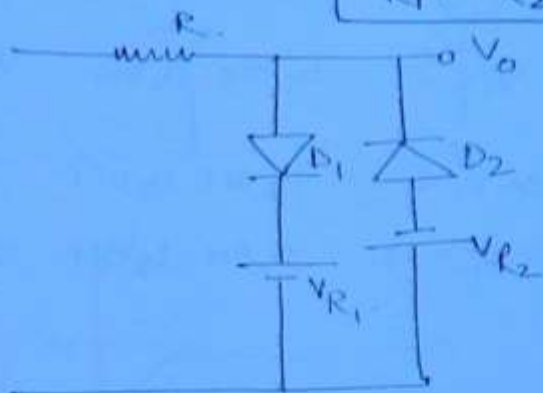


$V_i < -V_{R2}$ D_1 OFF D_2 ON $V_o = -V_{R2}$

$-V_{R2} < V_i < V_{R1}$ D_1 OFF D_2 OFF $V_o = V_i$

$V_i > V_{R1}$ D_1 ON D_2 OFF $V_o = V_{R1}$

3/03/12



$V_{R1} > V_{R2}$

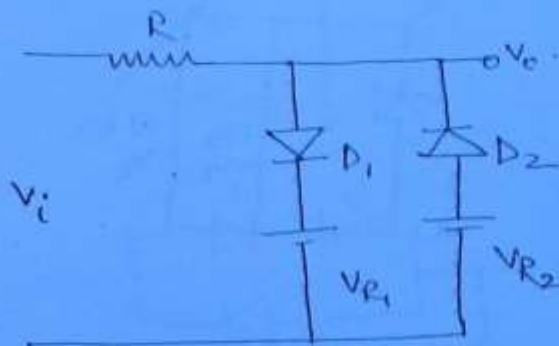


$V_i < V_{R2}$ D_1 OFF D_2 ON $V_o = V_{R2}$

$V_{R2} < V_i < V_{R1}$ D_1 OFF D_2 OFF $V_o = V_i$



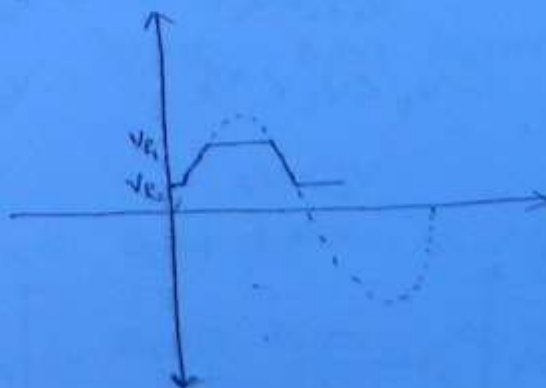
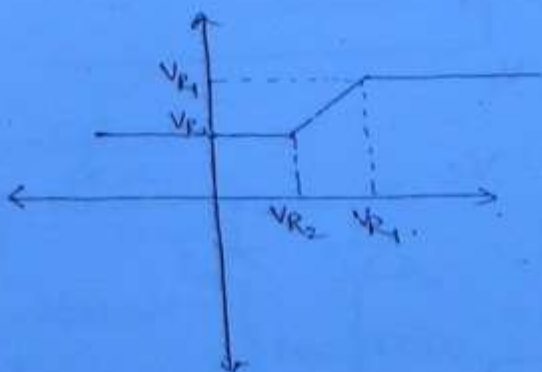
$V_i > V_{R1}$ D_1 ON D_2 OFF $V_o = V_{R1}$





(80)

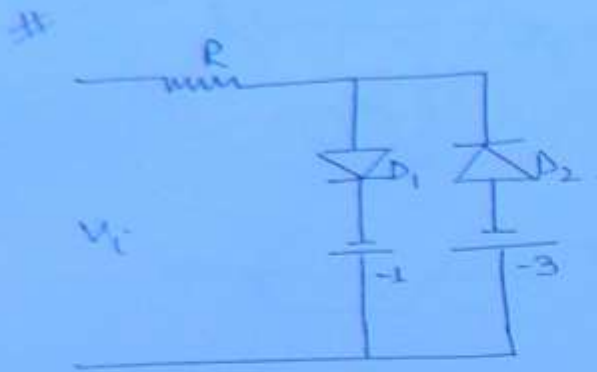

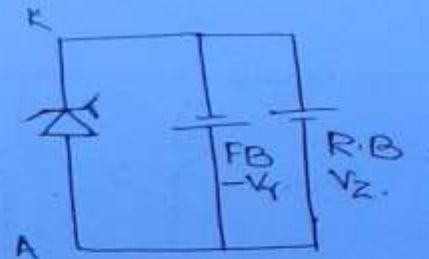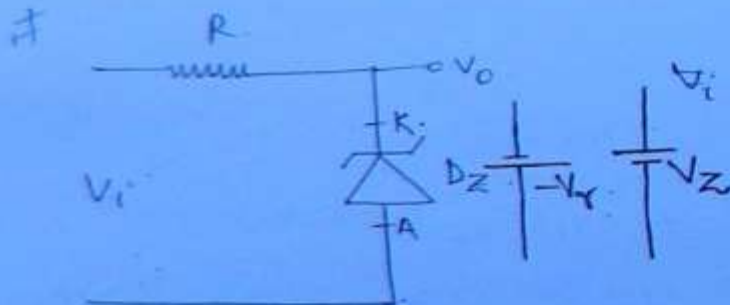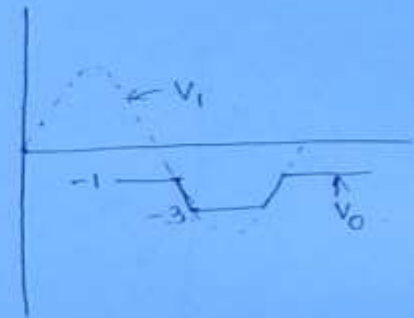
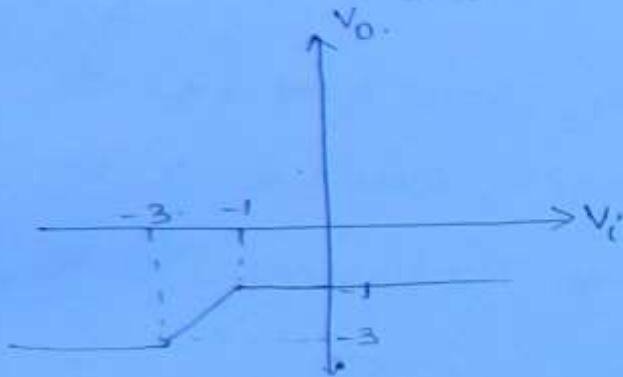
$V_i < -3$ D_1 OFF D_2 ON $V_o = -3V$
 $-3 < V_i < -1$ D_1 OFF D_2 OFF $V_o = V_i$
 $V_i > -1$ D_1 ON D_2 OFF $V_o = -1V$



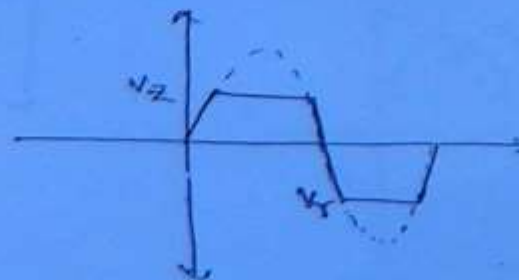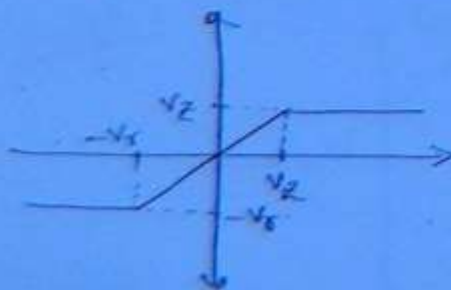
$V_i < -V_Y$ $V_o = -V_Y$
 $-V_Y < V_i < V_Z$ $V_o = V_i$
 $V_i > V_Z$ $V_o = V_Z$




#

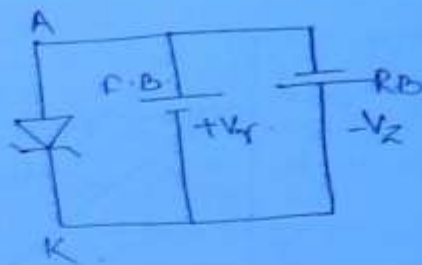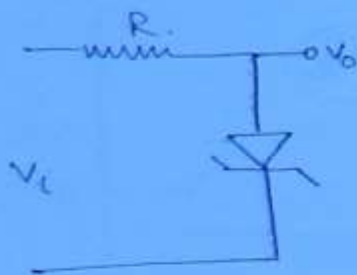


(81)

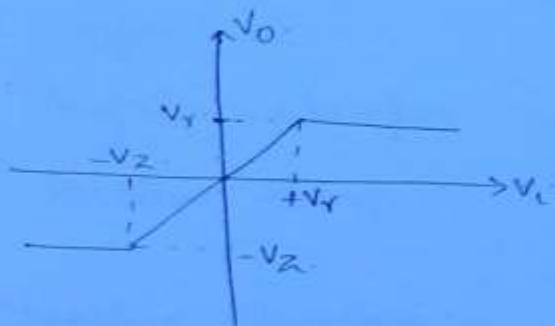

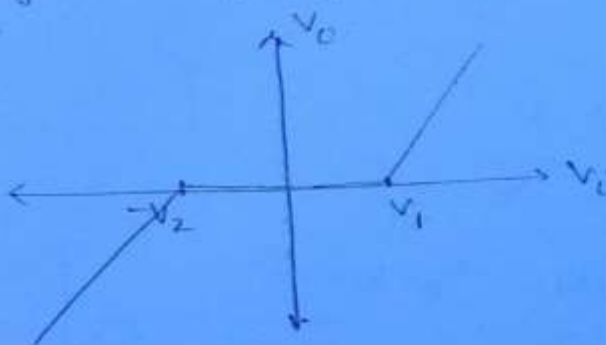Design a clipping ckt for the transfer char. shown below.



Ans.

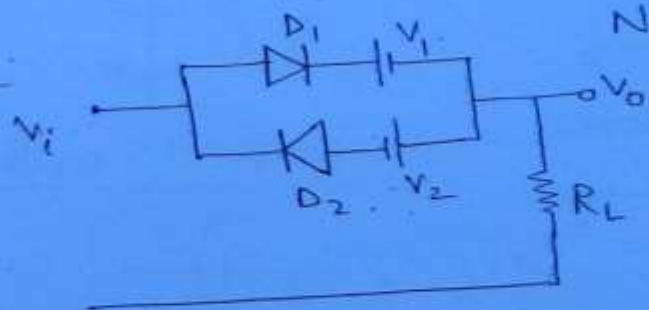


Noise clippers design.

$$V_i < -V_2 \quad D_1 \text{ OFF} \quad D_2 \text{ ON} \quad V_o = V_i + V_1$$

$$-V_2 < V_i < V_1 \quad D_1 \text{ OFF} \quad D_2 \text{ OFF} \quad V_o = 0$$



$$V_i > V_1 \quad D_1 \text{ ON} \quad D_2 \text{ OFF} \quad V_o = V_i - V_2$$

Attenuated ckt

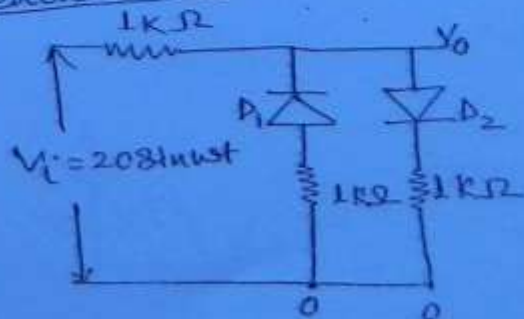


$$V_i < 0 \quad D_1 \text{ ON} \quad D_2 \text{ OFF} \quad V_o = \frac{V_i}{2}$$
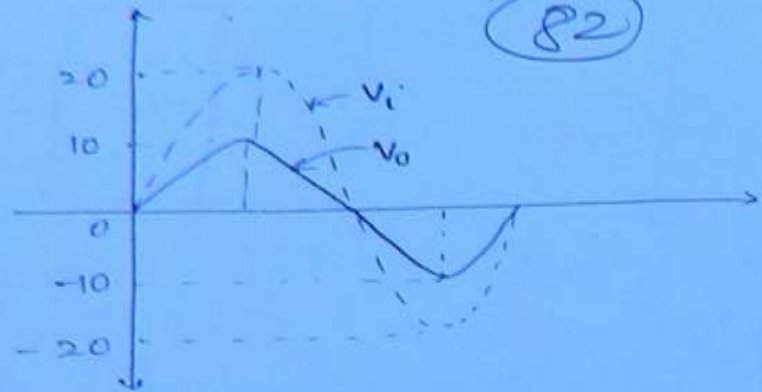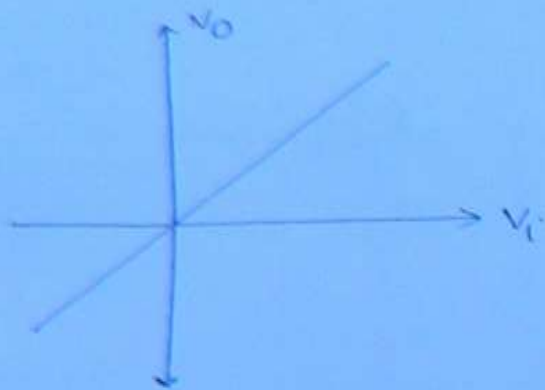
$$V_i > 0 \quad D_1 \text{ OFF} \quad D_2 \text{ ON} \quad V_o = \frac{V_i}{2}$$




82

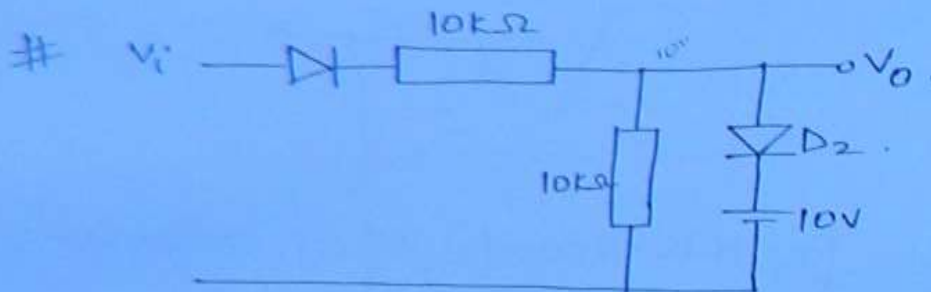


$$V_i < 0 \quad D_1 \text{ OFF} \quad V_o = 0$$

$$0 < V_i < 20V \quad D_1 \text{ ON} \quad D_2 \text{ OFF} \quad V_o = \frac{V_i}{2}$$

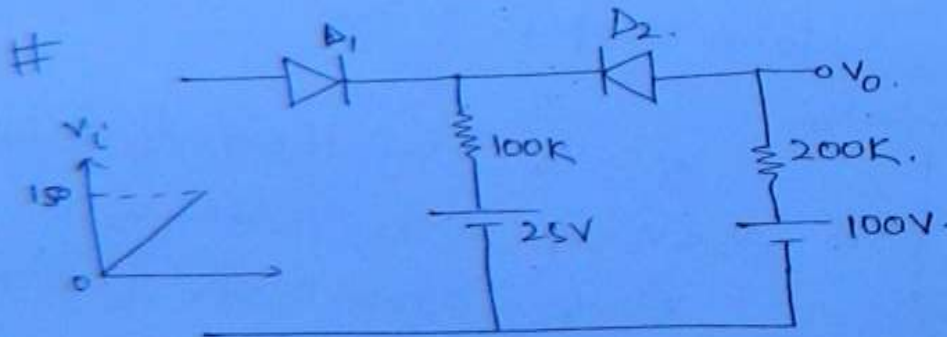
$$V_i > 20V \quad D_1 \text{ ON} \quad D_2 \text{ ON} \quad V_o = 10V$$


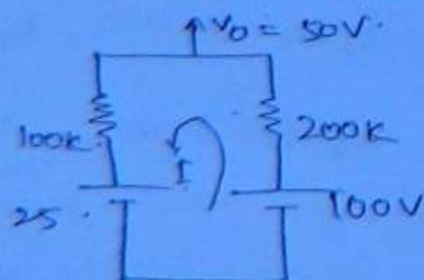
$$\text{At } V_i = 0V, \quad D_1 \text{ OFF} \quad D_2 \text{ ON}$$



$$I = \frac{75}{300} = 0.25V$$

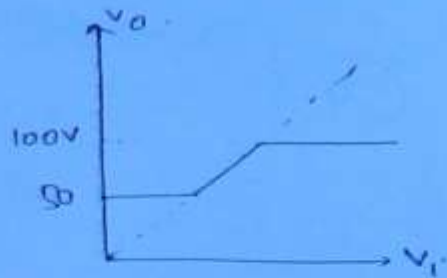

$$V_i = 0 \quad D_1 \text{ OFF} \quad D_2 \text{ ON} \quad V_o = 50V$$

$$50 < V_i < 100$$

$$V_o = V_i$$

$$V_i > 100V$$

$$V_o = 100V$$


83

Clampers →

Negative clamper

Positive clamper.

Negative clampers :-

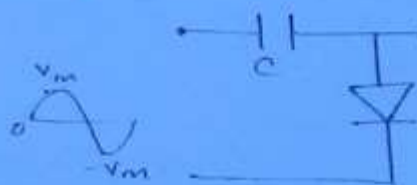

$$V_o = V_i - V_m$$


$$V_o = 0$$

$$V_i = 0$$


$$V_o = -V_m$$

$$V_i = -V_m$$

$$V_o = -2V_m$$

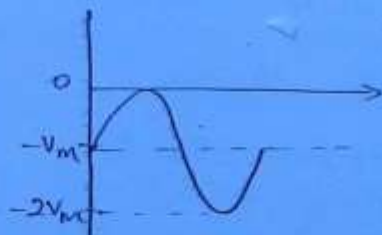

Positive clampers -

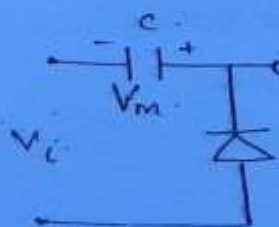

$$V_o = V_i + V_m$$

$$V_i = V_m$$


$$V_o = 2V_m$$

$$= 0$$



$$V_o = V_m$$

$$= -V_m$$

$$V_o = 0$$

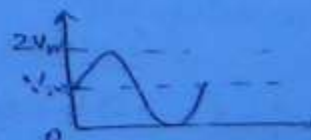

Ques
8-3

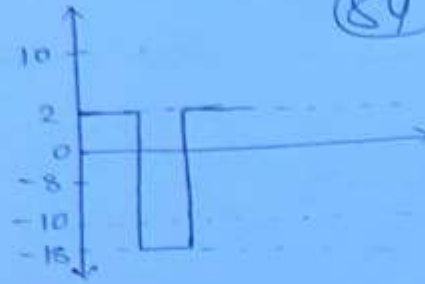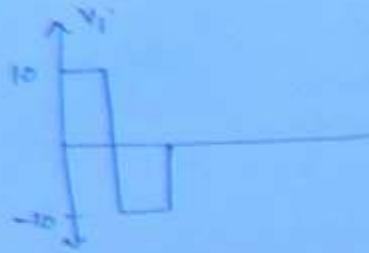

(d)

Conclusions →

- 1) When the diode is in downward dirⁿ, the total signal will be clamped below the ref. voltage.
- 2) When the diode is in upward dirⁿ, the total signal will be clamped above the ref. voltage.


Special diodes →

Zener diode →

- 10^8 s.c. atoms → 1 impurity → ordinary diode.
- 10^6 s.c. atoms → 1 impurity → Zener diode
- 10^3 s.c. atoms → 1 impurity → Tunnel diode.


Breakdown mechanism →

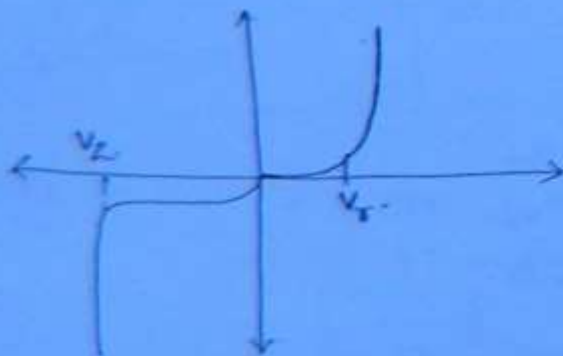- two types of breakdown.
- Avalanche breakdown
- Zener breakdown.



Avalanche breakdown.


It occurs in a lightly doped

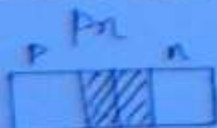

$V_Z > 6$

Zener breakdown.


It occurs in a heavily doped

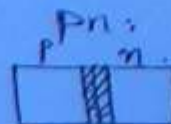

$V_Z < 6V$


Mechanism →

(88)

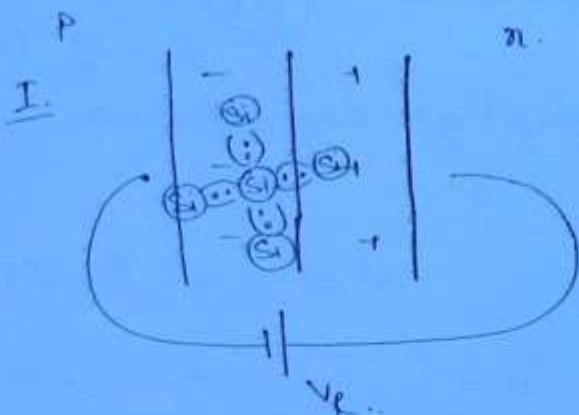

Linear breakdown

Avalanche breakdown

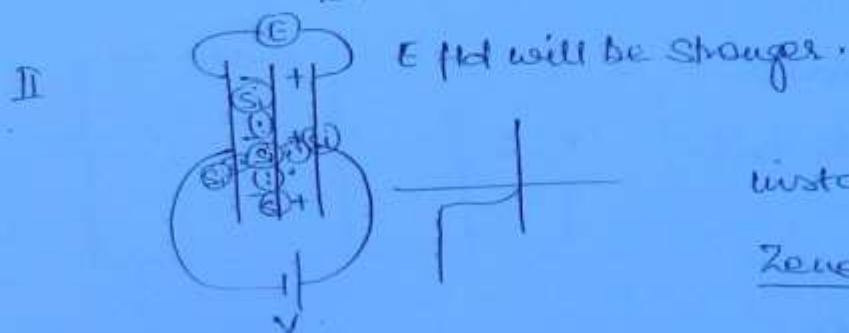

instant breakdown

Zener breakdown

I This type of breakdown occurs because of the velocity of minority charge carriers colliding with the stable atom in the depletion region.

II Due to heavily doped P-n jⁿ depletion region becomes narrower. When small reverse bias voltage is applied, strong int. E-fld will be generated bcoz of immobile ions.

Temp coeff. of V_{BR}

Zener breakdown →

$T \uparrow, V_{BR} \downarrow \therefore$ negative temp coeff.


Avalanche breakdown: —

$T \uparrow, V_{BR} \uparrow \therefore$ +ve Temp coeff.

As T inc, vibrational effect inc, so we require more en.

Zener diode as a voltage regulator. →


(86)

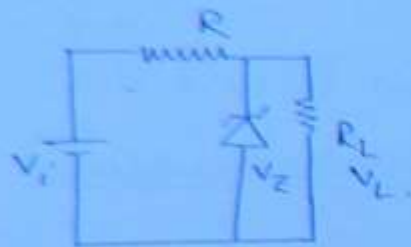


$V_Z = V_L$ (always) at any condition.

- 1) V_i & R_L fixed.
- 2) V_i fixed and R_L Variable
- 3) V_i variable and R_L fixed.
- 4) V_i & R_L Variable

I V_i & R_L fixed problem.

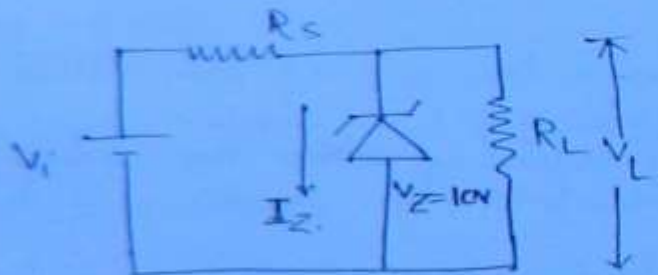


cal. V_L , I_Z , P_Z .

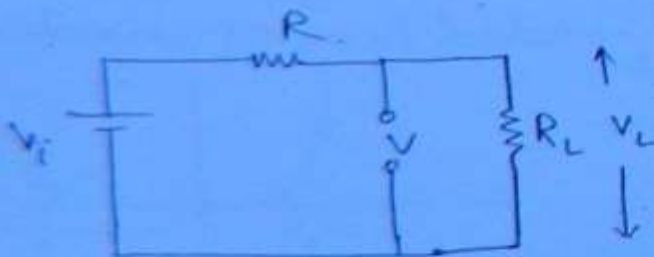

$$V = V_L = \frac{V_i \times R_L}{R + R_L}$$

if $V > V_Z$,

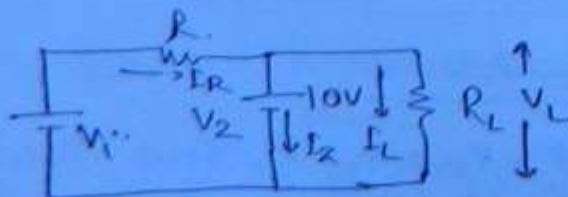


$$1) V_Z = V_L = 10V$$

$$(2) I_Z = I_R - I_L$$

$$= \frac{V_i - V_Z}{R} - \frac{V_Z}{R_L}$$

$$(3) P_Z = V_Z I_Z$$

When $V < V_Z$:

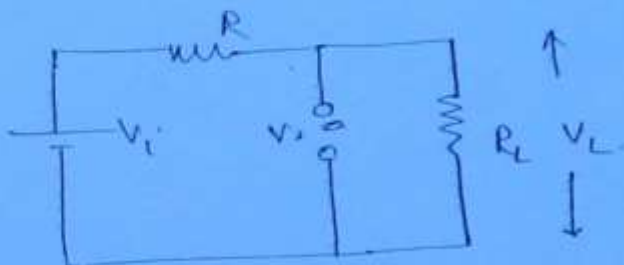


$$1) V_L = V$$

$$2) I_Z = 0$$


$$3) P_Z = 0$$

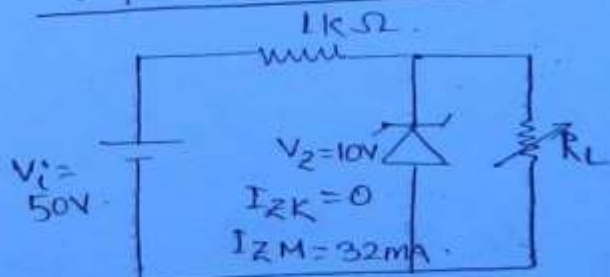II V_i fixed and R_L variable \rightarrow



btw R_{min} and R_{Lmax} ,
Zener diode is ON.

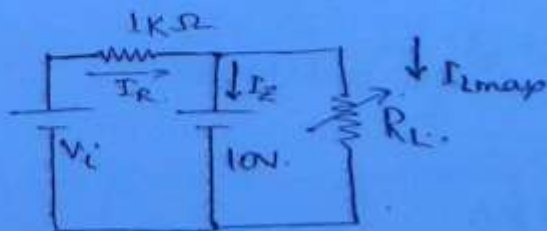Cal. R_{Lmin} , R_{Lmax} , I_{Lmin} , I_{Lmax} .



$$I_{Lmax} = I_R - I_{ZK}$$

$$= \frac{50 - 10}{1k} - 0$$

$$= 40mA$$


$$R_{Lmin} = \frac{V_Z}{I_{Lmax}} = \frac{10}{40mA} = 250\Omega$$

$$\begin{aligned}
 I_{Lmin} &= I_R - I_{ZM} \\
 &= 40 \text{ mA} - 32 \text{ mA} \\
 &= 8 \text{ mA}
 \end{aligned}$$


(88)

$$\begin{aligned}
 R_{Lmax} &= \frac{V_Z}{I_{Lmin}} \\
 &= \frac{10}{8 \text{ mA}} \\
 &= 1.25 \text{ k}\Omega
 \end{aligned}$$

Ex V_i variable and R_L fixed! —

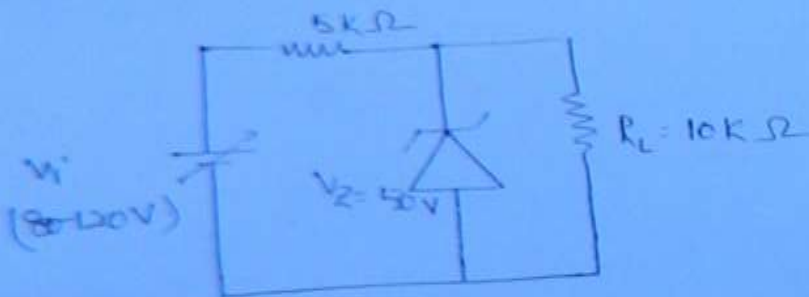

Cal. I_{Zmin} and I_{Zmax} .

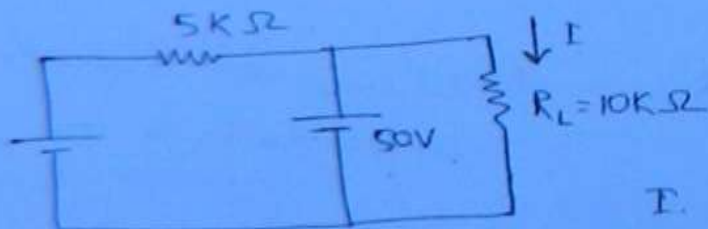

$$I = \frac{50 \text{ V}}{10 \text{ k}\Omega} = 5 \text{ mA}$$

I_{Zmax} ;

$$I_{Rmax} = \frac{120 - 50}{5 \text{ k}\Omega} = \frac{70}{5} = 14 \text{ mA}$$

$$\begin{aligned}
 I_{Zmax} &= (14 - 5) \text{ mA} \\
 &= 9 \text{ mA}
 \end{aligned}$$


I_{Zmin} ;

$$I_{Rmin} = \frac{80 - 50}{5 \text{ k}\Omega} = \frac{30}{5} = 6 \text{ mA}$$


$$\begin{aligned}
 I_{Zmin} &= (6 - 5) \text{ mA} \\
 &= 1 \text{ mA}
 \end{aligned}$$

IV V_i and R_L variable \rightarrow

(89)

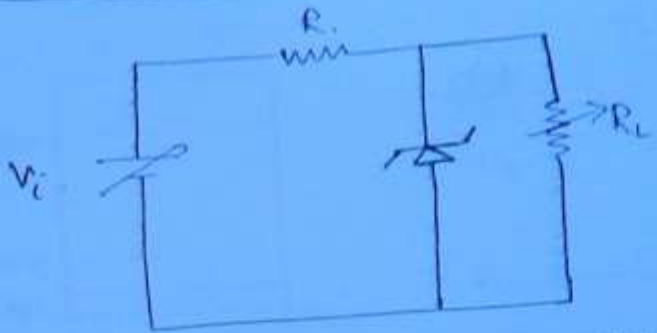

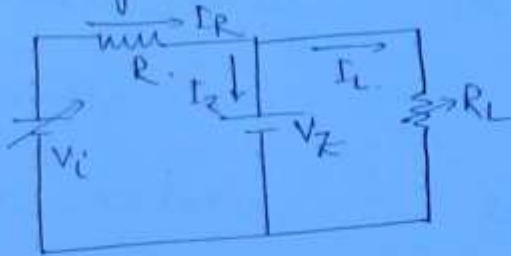Cal. the dynamic range of series resistance R .



$$R_{\min} = \frac{V_{i\max} - V_Z}{(I_R)_{\max}}$$

$$R_{\max} = \frac{V_{i\min} - V_Z}{(I_R)_{\min}}$$

$$I_R = I_Z + I_L$$


$$\frac{V_i - V_Z}{R} = I_Z + I_L$$

NOTE \rightarrow

For variable problems in zener diode, we can have an eq.

$$\frac{V_i - V_Z}{R} \geq I_Z + I_L$$

Q-15.
Ch-1.

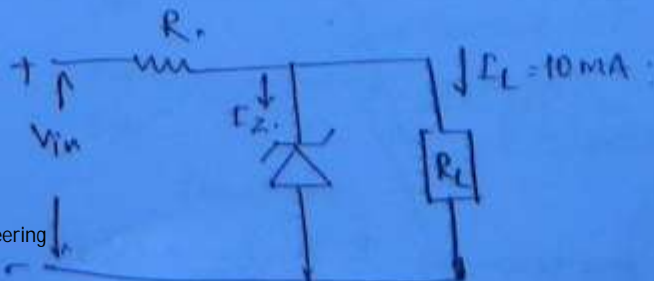

Given

$$V_{in} = 30V \text{ to } 50V.$$

(90)

$$I_L = 10mA$$

$$V_0 = V_Z = 10V.$$

$$I_{ZK} = 1mA.$$

$$I_R \geq I_Z + I_L.$$

$$\frac{V_i - V_Z}{R} \geq I_Z + I_L.$$

$$\underline{V_{in} = 30V.}$$

$$\frac{30 - 10}{R} \geq 1mA + 10mA.$$

$$\boxed{R \leq \frac{20}{11mA} = 1818\Omega} \rightarrow A_{in}$$

$$\underline{V_{in} = 50V.}$$

$$\frac{50 - 10}{R} \geq 11mA.$$

$$R \leq \frac{40}{11mA} = 3636\Omega$$

16).

$$\frac{V_i - V_Z}{R} \geq I_Z + I_L.$$

$$\cancel{I_L = 10mA}$$

$$\underline{I_L = 100mA.}$$

$$\frac{12 - 5}{R} \geq 0 + 100.$$



$$R \leq \frac{7}{100mA} = 70\Omega$$

$$I_L = 500mA.$$

$$\frac{12 - 5}{R} \geq 0 + 500 \Rightarrow R \leq \frac{7}{500} = 14\Omega.$$

Tunnel diode →

(91)

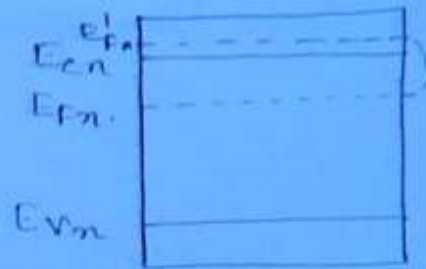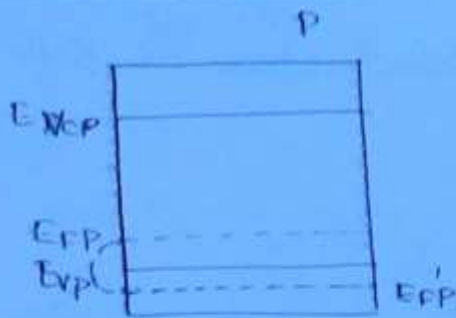

$$E_{FP} = E_V + KT \ln \frac{N_V}{N_A}$$



$$E_{Fn} = E_C - KT \ln \frac{N_C}{N_D}$$

$$N_A \gg N_V$$

$$N_D \gg N_C$$

$$E_{FP} = E_V - KT \ln N_A$$

$$E_{Fn} = E_C + KT \ln N_D$$

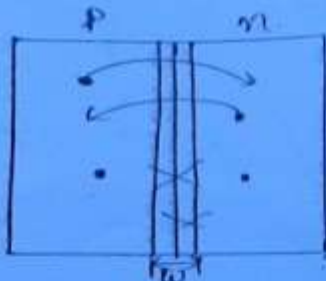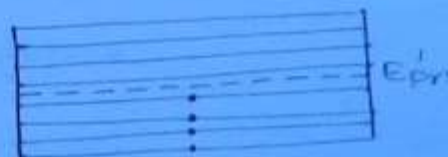


$$w = 100 \text{ \AA}$$

$$1 \text{ \AA} = 10^{-8} \text{ cm}$$

↙
1/15th wavelength of light.

Case 1. →

① open ckt P-n j'n.

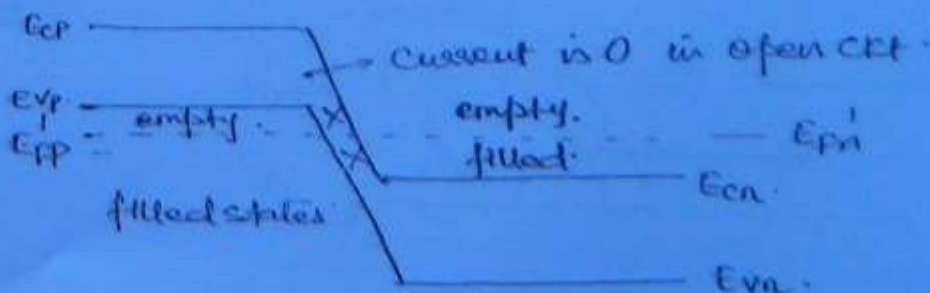

Reverse bias

(92)



It acts like good conductor in R.B.



Case 3:

Small FB (mv)

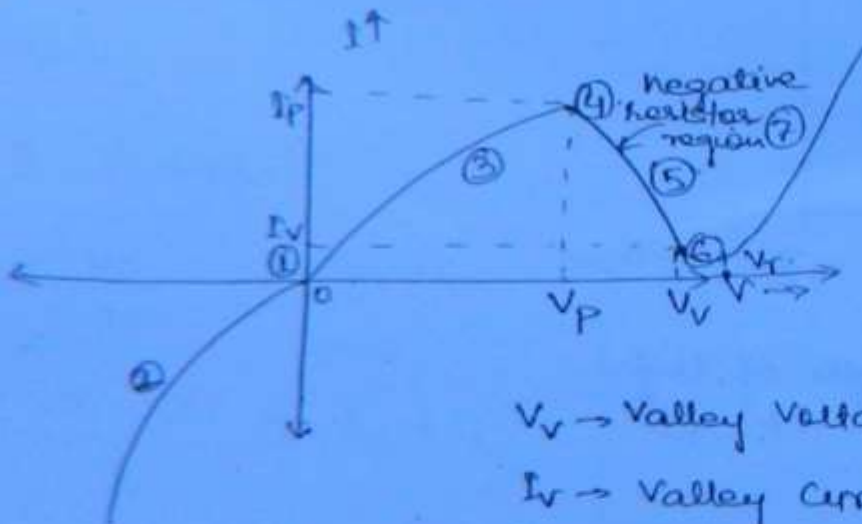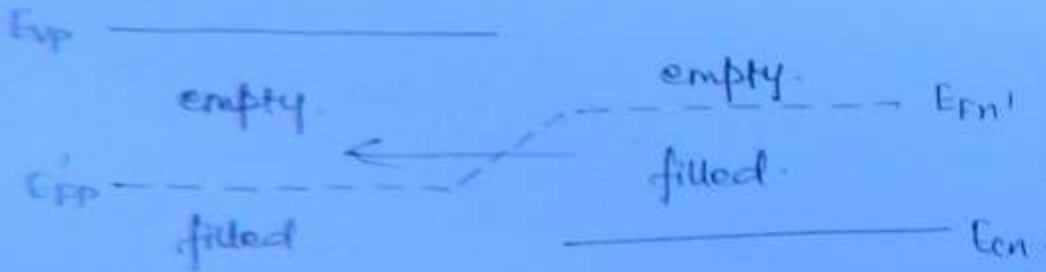zener \rightarrow Si
tunnel \rightarrow Ge




$V_v \rightarrow$ Valley Voltage

$I_v \rightarrow$ Valley Current

$V_r \rightarrow$ Cut in Voltage
 $\approx 0.3V$

Case 4:

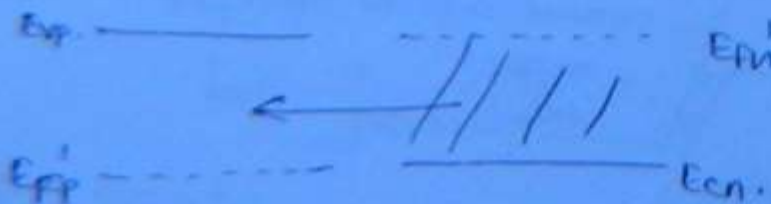


Case 5 \rightarrow

$$V_f > V_p$$

(93)




Case 6 \rightarrow

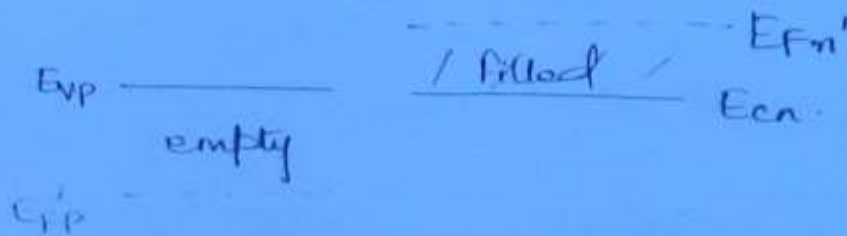

Case 7 \rightarrow

$$V_f > V_v$$

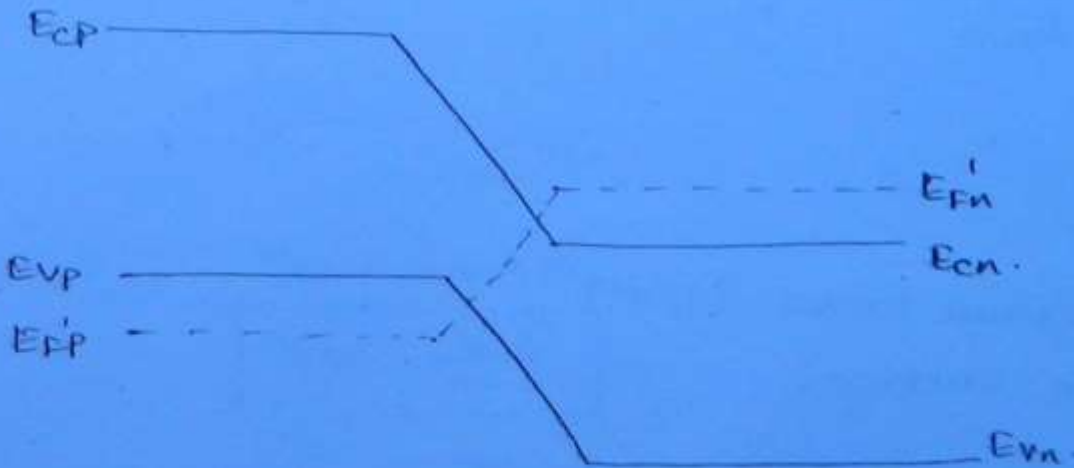


$$\begin{aligned} \frac{I_p}{I_v} \text{ ratio} &= 15 \quad (\text{GaAs}) \\ &= 8 \quad (\text{Ge}) \\ &= 3 \quad (\text{Si}) \end{aligned}$$

4/1/22 Rectifiers → Ac

(94)

Block diagram

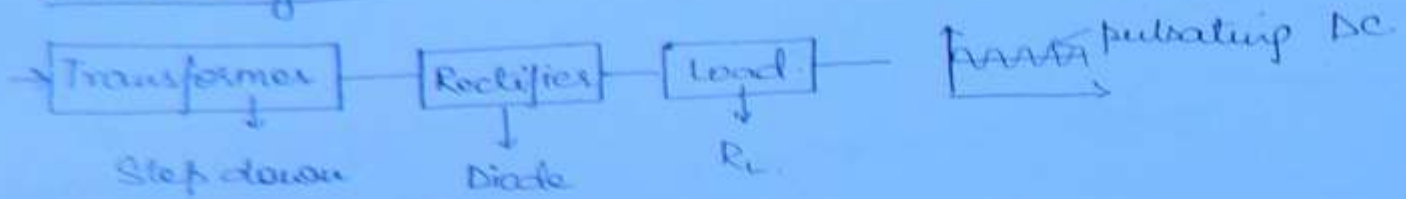

It is a ckt which converts Ac to pulsating DC.

Practical rectifiers designs :-

- 1) half wave rectifier →
- 2) full wave rectifier →
- 3) Bridge rectifiers -

Rectifier parameters →

i) Av current I_{DC}

ii) DC output voltage V_{DC}

iii) Rms load current I_{RMS}

iv) Ripple factor

v) voltage regulation

vi) Rectification η


vii) transformer utilisation factor (TUF)


viii) PIV (Peak inverse Voltage)

ix) F.F.

x) Peak factor

half wave Rectifier →

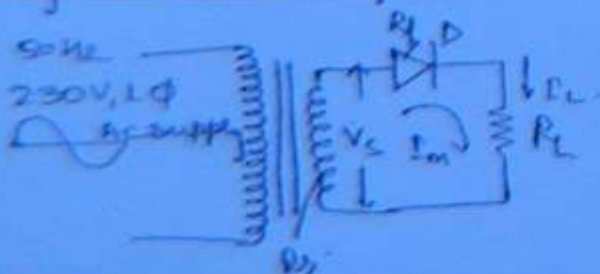

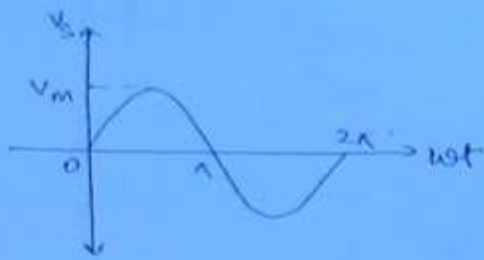

$$V_s = V_m \sin \omega t$$

(95)



$$i_L = I_m \sin \omega t$$

$$0 \leq \omega t < \pi$$

$$= 0$$

$$\pi \leq \omega t < 2\pi$$

Rectifier parameters :-

1) Av. current I_{dc} :-

$$I_{dc} = \frac{\text{area under the curve}}{2\pi}$$

$$\frac{1}{2\pi} \int_0^{2\pi} i_L(\omega t) d(\omega t)$$

$$= \frac{I_m}{2\pi} \int_0^{\pi} \sin \omega t d(\omega t)$$

$$\boxed{I_{dc} = \frac{I_m}{\pi}}$$

2) DC O/P voltage V_{dc} :-

$$V_{dc} = I_{dc} \times R_L$$

$$\boxed{V_{dc} = \frac{I_m}{\pi} R_L}$$

$$= \frac{V_m}{\pi (R_f + R_s + R_L)} \cdot R_L$$

$$= \frac{V_m}{\pi} \cdot \frac{1}{\frac{R_f + R_s}{R_L} + 1}$$

When $R_L \rightarrow \infty$

$$\boxed{(V_{dc}) = \frac{V_m}{\pi} \text{ No load.}}$$

3) RMS value current (I_{rms}) →

RMS ←


(96)

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int I^2 d(\omega t)}$$

$$= \frac{I_m}{\sqrt{2}} = \frac{I_m}{2}$$

$$V_{rms} = \frac{V_m}{2}$$

$$= \frac{V_m}{\sqrt{2}}$$

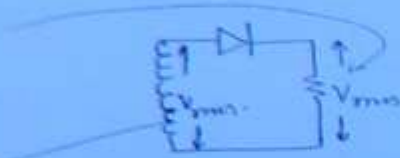

4) Ripple factor →

$$= \frac{\text{RMS of alternating component}}{\text{Av. Value}} = \frac{I'_{rms}}{I_{dc}}$$

Assume →

I' = Ac current

I_{dc} = dc current

I → total current

I'_{rms} = rms value of ac current

$$I'_{rms} = \left[\frac{1}{2\pi} \int_0^{2\pi} I'^2 d\alpha \right]^{1/2}$$

$$I' = I - I_{dc}$$

$$I'_{rms} = \left[\frac{1}{2\pi} \int_0^{2\pi} (I - I_{dc})^2 d\alpha \right]^{1/2}$$

$$I'^2_{rms} = \frac{1}{2\pi} \int_0^{2\pi} I^2 d\alpha - 2 I_{dc} \frac{1}{2\pi} \int_0^{2\pi} I d\alpha + I_{dc}^2 \frac{1}{2\pi} \int_0^{2\pi} d\alpha$$

$$= I_{rms}^2 - 2 I_{dc}^2 + I_{dc}^2$$

$$r.f. = \frac{I_{rms}}{I_{dc}} = \frac{\sqrt{I_{rms}^2 - I_{dc}^2}}{I_{dc}}$$

$$R.f. = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}$$

(9)

HWR

$$R.f. = \sqrt{\left(\frac{I_m/2}{I_m/\pi}\right)^2 - 1}$$

$$= \sqrt{\left(\frac{\pi}{2}\right)^2 - 1}$$


$$= 1.21$$

$$= 121\%$$

Conclusion →

Ripple v factor value is 1.21 for half wave rectifier i.e 121% of ac comp. is present in dc value.

5) Voltage Regulation →

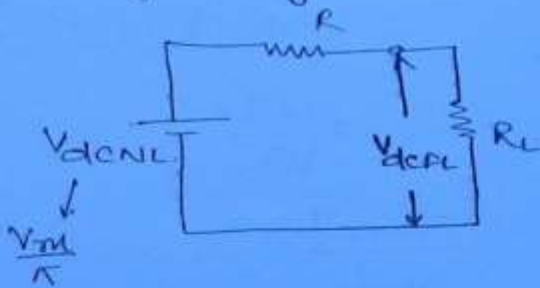

$$\%VR = \frac{V_{dcNL} - V_{dcFL}}{V_{dcFL}} \times 100\%$$

HWR.

$$I_{dc} = \frac{I_m}{\pi}$$

$$I_{dc} = \frac{V_m}{\pi(R_d + R_s + R_L)}$$

$$I_{dc}(R_d + R_s) + I_{dc}R_L = \frac{V_m}{\pi}$$

\downarrow \uparrow
 V_{dcFL} V_{dcNL}

$$\%VR = \frac{I_{dc}(R_d + R_s)}{\frac{V_m}{\pi} - I_{dc}(R_d + R_s)} \times 100\%$$

Ideally the v.r. should be 0. Practically it should be min. in value.

6) Rectification η :-

(98)

$$\eta = \frac{\text{DC power delivered to the load.}}{\text{ac I/P power.}}$$

$$= \frac{I_{dc}^2 R_L}{I_{rms}^2 (R_f + R_s + R_L)}$$

$$= \frac{I_{dc}^2}{I_{rms}^2} \frac{1}{\frac{R_f + R_s}{R_L} + 1}$$

$$\frac{R_f + R_s}{R_L} \ll 1.$$


$$\eta = \frac{I_{dc}^2}{I_{rms}^2}$$

$$= \frac{(I_m/\pi)^2}{(I_m/2)^2}$$

$$= \frac{4}{\pi^2} = 0.406.$$

$$= 40.6\%$$

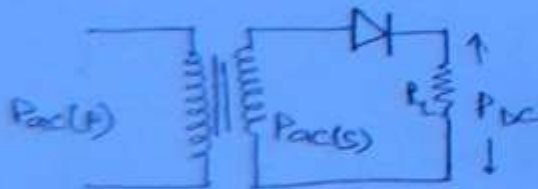7) Transformer utilisation factor : \rightarrow



$$TUF = \frac{(TUF)_p + (TUF)_s}{2}$$

for Full wave.

$$(TUF)_p = \frac{P_{dc}}{(P_{ac})_p}$$

for utilisation of 360°

$$(TUF)_s = \frac{P_{dc}}{(P_{ac})_s}$$

$$IUF = (IUF)_S.$$

$$= \frac{\text{DC power delivered to load}}{P_{ac \text{ rated } goe.}}$$

$$= \frac{I_{dc}^2 R_L}{V_{rms} \times I_{rms}}$$


$$\downarrow \qquad \qquad \downarrow$$

$$\frac{V_m}{\sqrt{2}} \qquad \frac{I_m}{2}$$

(99)

$$TUF = 28\%$$

8) PIV (Peak Inverse Voltage) →

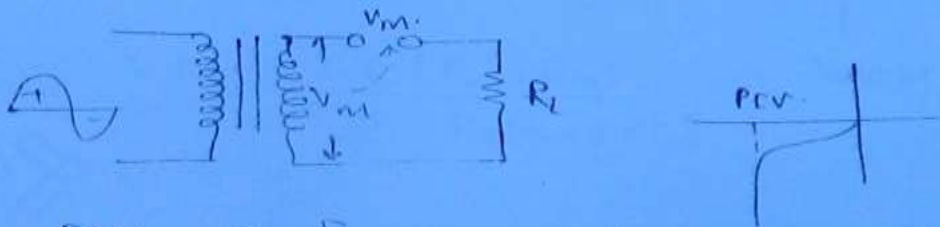

$$PIV = V_m [\text{negative half cycle}]$$

9) Form factor →

$$\frac{RMS}{AV.}$$

$$= \frac{I_{rms}}{I_{dc}}$$

$$= \frac{I_m/2}{I_m/\pi} =$$

$$= \sqrt{2}$$

10) Peak factor →



$$\frac{\text{Peak}}{RMS}$$

$$= \frac{I_m}{I_m/2}$$

$$= 2$$

Full wave Rectifier →

100

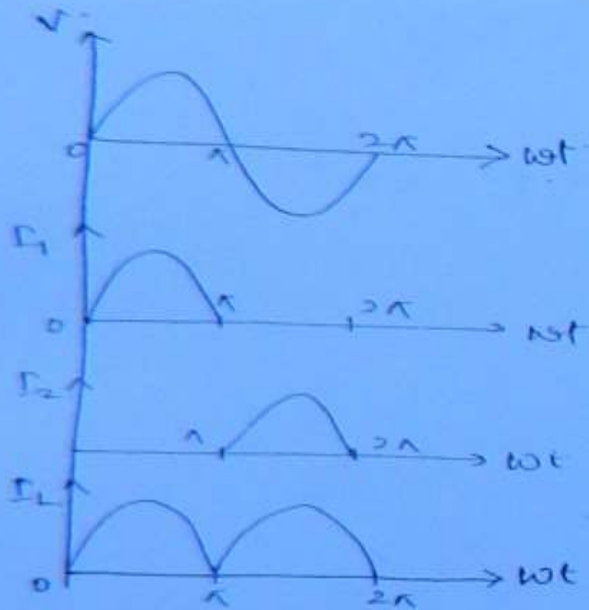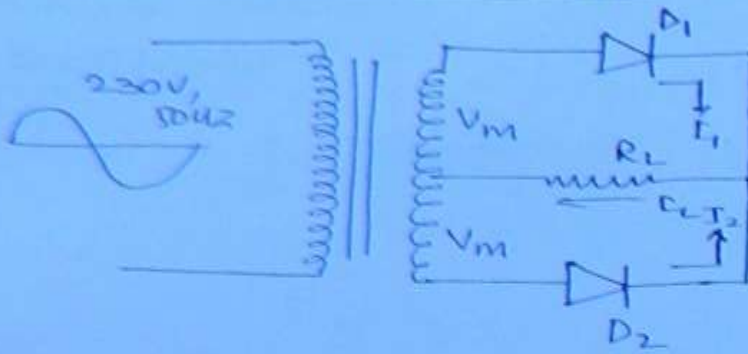

Rectifier parameters →

1) Avg. current I_{DC} →

$$I_{DC} = \frac{2I_m}{\pi}$$

2) Dc Output Voltage V_{DC} →

$$V_{DC} = \frac{2V_m}{\pi}$$

3) rms I_{rms} →

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\begin{aligned}
 4) R.f. &= \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1} \\
 &= \sqrt{\left(\frac{\frac{I_m/\sqrt{2}}{\frac{2I_m}{\pi}} \right)^2 - 1} \\
 &= \sqrt{\frac{\pi^2}{48} - 1} \\
 &= 48\%
 \end{aligned}$$

(0)

5) Voltage Regulation :—

$$I_{dc}(R_d + R_s) + I_{dc}R_L = V_{dc}NL$$

$$\begin{array}{ccc}
 \downarrow & & \downarrow \\
 V_{dcFL} & & \frac{2V_m}{\pi}
 \end{array}$$

$$V.R. = \frac{I_{dc}(R_d + R_s)}{\frac{2V_m}{\pi} - I_{dc}(R_d + R_s)}$$

$$\begin{aligned}
 \eta &= \frac{P_{DC}}{P_{ac}} \\
 &= \frac{I_{dc}^2}{I_{rms}^2} \\
 &= \frac{(2I_m/\pi)^2}{(I_m/\sqrt{2})^2} \\
 &= \frac{8}{\pi^2} \\
 &= 81.2\%
 \end{aligned}$$

7) TUF →

$$= \frac{(TUF)_P + (TUF)_S}{2}$$

$$(TUF)_S = \frac{P_{DC}}{P_{ac \text{ rated sec one half}}}$$

$$\begin{aligned}
 &P_{ac \text{ rated sec one half}} \rightarrow V_{rms} I_{rms} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{2} \\
 &+ P_{ac \text{ rated sec other half}} \rightarrow V_{rms} I_{rms} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{2} \\
 &= 57.3\%
 \end{aligned}$$

$$(TUF)_P = \eta = 81.2\%$$

102

$$TUF = \frac{81.2 + 57.3}{2}$$

$$= 69.3\%$$

8) PIV \rightarrow

$$2V_m$$

9) I.F. = $\frac{R_{ms}}{A_v}$

$$= \frac{I_{rms}}{I_{dc}}$$

$$= \frac{I_m/\sqrt{2}}{2I_m/\pi}$$

$$= \frac{\pi}{2\sqrt{2}}$$


10) Peak factor =

$$\frac{\text{Peak}}{\text{RMS}}$$

$$= \frac{I_m}{I_m/\sqrt{2}}$$

$$= \sqrt{2}$$

Bridge Rectifier \rightarrow

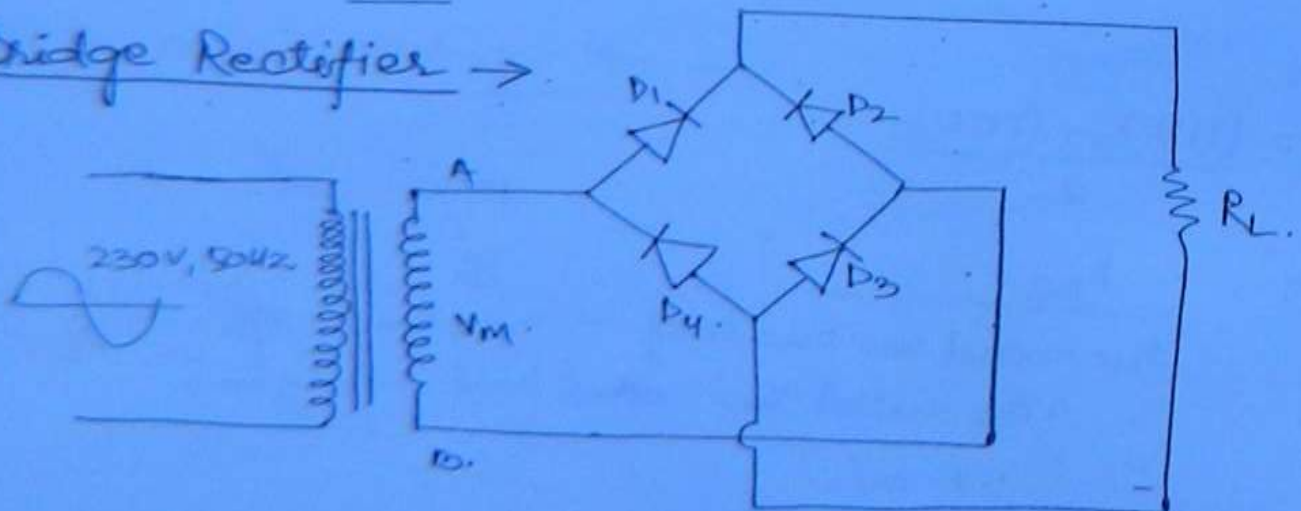

the half cycle →

A D₁ R_L D₃ B

D₁ D₃ → F.B.

D₂ D₄ → R.B.

-ive half cycle

B D₂ R_L D₄ A.

D₂ D₄ → F.B.

D₁ D₃ → R.B.

(103)

Common parameters as full wave Rectifier:—

$$I_{DC} = \frac{2 I_m}{\pi}$$

$$V_{DC} = \frac{2 V_m}{\pi}$$


$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$R.f. = 48\%$$

~~W.R.~~

$$\eta = 81.2\%$$

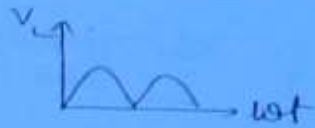

Other parameters →

Voltage Regulation =

$$I_{dc} (2R_d + R_s) + \underset{\substack{\downarrow \\ R_L}}{I_{dc} R_L} = \underset{\substack{\downarrow \\ N.L.}}{\frac{2V_m}{\pi}}$$

$$TUF = \frac{(TUF)_P + (TUF)_S}{2}$$

$$= 81.2\%$$

$$PIV = V_m$$

Filters →

R.f. (HWR) → 1.21.


(FWR) → 0.48.

(BR) → 0.48.


104

Filters →

→ Capacitive filter

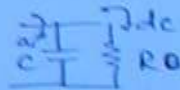


→ Inductor filter

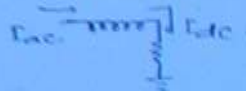


→ L Section filter




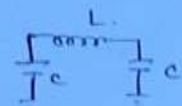
→ π Section filter [not for heavier loads]



→ RC filter

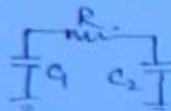


Capacitive filter →

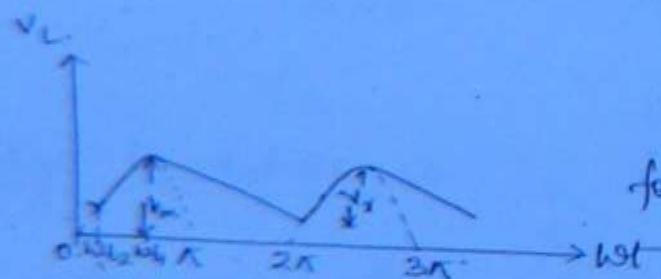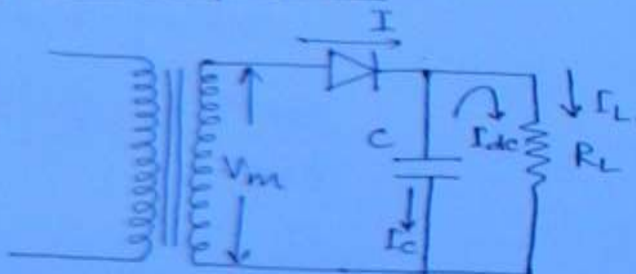


ωt_2 → cut in angle.

ωt_1 → cut out angle.

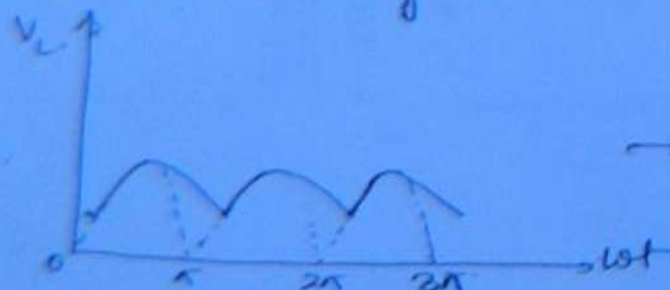

Expression for ripple voltage for full wave \rightarrow

(105)

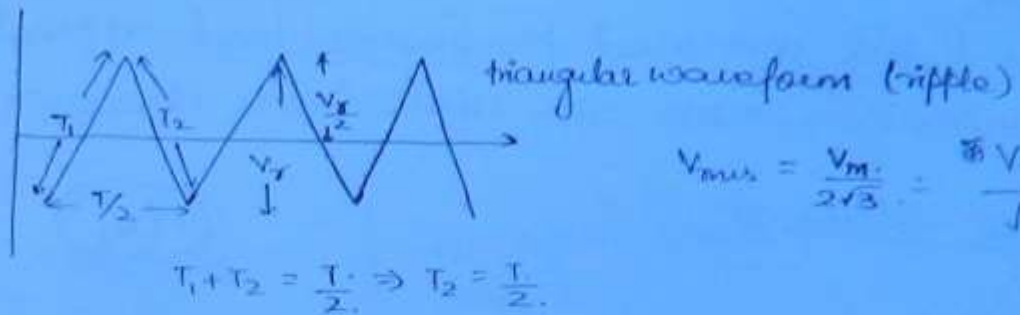

charge lost at time T_2 = charge lost by the capacitor.

$$I_{dc} \times T_2 = C \times V_r$$

$$V_r = \frac{I_{dc} \times T}{2C}$$

$$= \frac{I_{dc}}{2fC}$$

$$= \frac{V_{dc}}{2fCR_L}$$

$$R_{if} = \frac{V_{rms}}{V_{dc}}$$

$$= \frac{V_r}{2\sqrt{3}} / V_{dc}$$

$$= \frac{V_{dc}}{4\sqrt{3}fCR_L} / V_{dc}$$

$$R_{if} = \frac{1}{4\sqrt{3}fCR_L}$$

\rightarrow for high load.

and capacitive value must be high for low R_{if} .

$\omega t_2 \rightarrow$ Cut in angle \rightarrow

It is the angle at which the diode starts conducting or capacitor gets charged.

$\omega t_1 \rightarrow$ Cut Out angle \rightarrow





It is the angle at which the diode stops conducting or the capacitor gets discharged.

- common...
- Capacitive filters are used for heavier load application.
 - As the capacitive value inc, ripple factor decreases.

Inductive filters \Rightarrow

(106)

HWR.

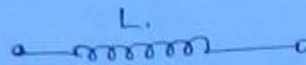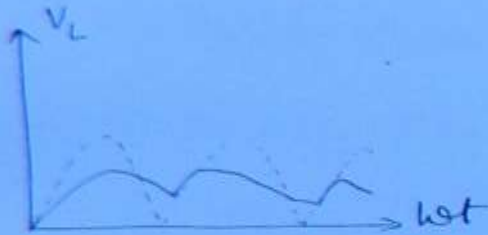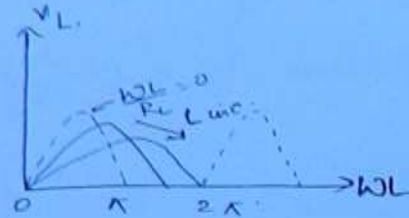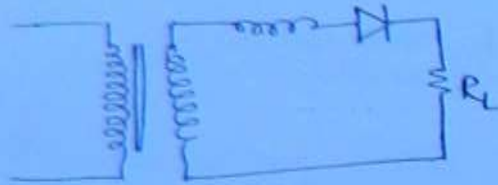

It can not block 2nd harmonics.

It block all the harmonic components except 2nd.

because in 2nd, $X_L = 2\pi f' L$

$$f' = 2 \times 50 \\ = 100 \text{ Hz}$$

not very high, unable to block.

$$I(t) = \frac{I_m}{\pi} - \frac{2I_m}{3\pi} \cos 2\omega t$$

\downarrow dc \downarrow 2nd harmonic

FWR.

$$I(t) = \frac{2I_m}{\pi} - \left(\frac{4I_m}{3\pi} \right) \cos 2\omega t$$

\uparrow I_m'

$$I_{dc} = \frac{2I_m}{\pi} = \frac{2V_m}{\pi R_L}$$

$$(I_{rms})_{2nd} = \frac{I_m'}{\sqrt{2}} = \frac{4I_m}{3\pi\sqrt{2}}$$

$$= \frac{4V_m}{3\pi\sqrt{2} (R_L + j2\omega L)}$$

$$= \frac{4V_m}{3\pi\sqrt{2}\sqrt{R_L^2 + 4\omega^2 L^2}}$$

$$R.f. = \frac{I_{rms}}{I_{dc}}$$

$$= \frac{\frac{\sqrt{2}}{3}}{\frac{R_L}{2\omega L}} \quad \left. \vphantom{\frac{\sqrt{2}}{3}} \right\} \begin{array}{l} \text{for lighter loads (} R_L \downarrow \text{)} \\ \text{high } L. \end{array}$$


(107)

Conclusion →

1) Inductor filter designs are used for lighter load application $[R_L]$

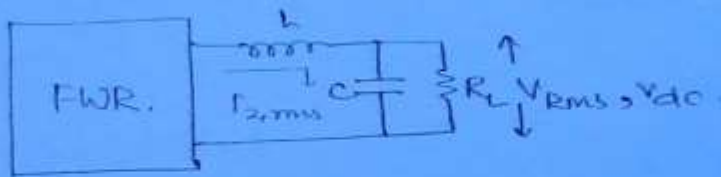2) If the inductor value is more, ripple factor will be less.

L-Section filter → [for varying load application]



$$(I_{rms})_{ind} = \frac{4V_m}{3\pi\sqrt{2}} \cdot \frac{1}{X_L} \quad (X_L = 2\omega L)$$

$$= \frac{2}{3\sqrt{2}} \left(\frac{2V_m}{\pi} \right)^{V_{dc}} \cdot \frac{1}{X_L}$$

$$= \frac{\sqrt{2}}{3} \frac{V_{dc}}{X_L}$$


$$V_{rms} = \frac{\sqrt{2}}{3} \frac{V_{dc}}{X_L} X_C \quad X_C = \frac{1}{j2\omega C}$$

$$R.f. = \frac{V_{rms}}{V_{dc}} = \frac{\frac{\sqrt{2}}{3} \frac{V_{dc}}{X_L} X_C}{V_{dc}}$$

$$R.f. = \frac{\sqrt{2}}{3} \frac{X_C}{X_L} \quad \left\{ \begin{array}{l} \text{free from load.} \\ X_L > X_C \end{array} \right.$$

L-section filters are used for varying load applications

π Section filter \rightarrow

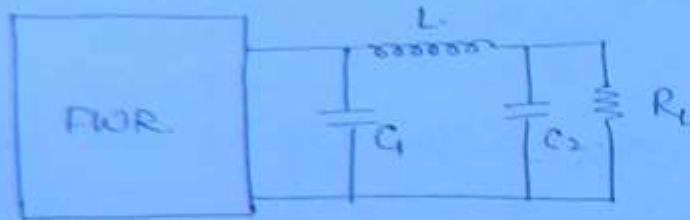

(168)

$$r.f. = \frac{\sqrt{2} X_{C1} X_{C2}}{X_L \cdot R_L}$$

$$\frac{2}{3} \frac{X_C}{X_L}$$

Parameters

L section

π section

V_{dc}

better

r.f.


better

f.V.R.

better

P.I.V.

RC filter \rightarrow

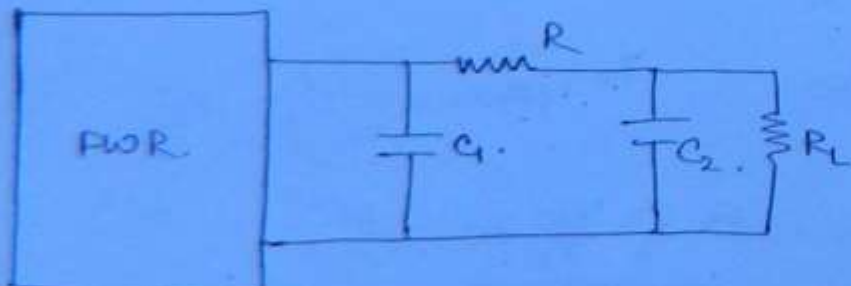

$$R \leq 10 X_{C2}$$

$$r.f. = \frac{\sqrt{2} X_{C1} X_{C2}}{R R_L}$$


- The main drawback of π section filter is it can not be used for heavier load application because of ind. properly.

(109)

In practical applications, ind. is becoming more costlier. To reduce that cost effectiveness, we replace inductor by resistor.

Voltage
5/1/12

Voltage multiplier : \rightarrow

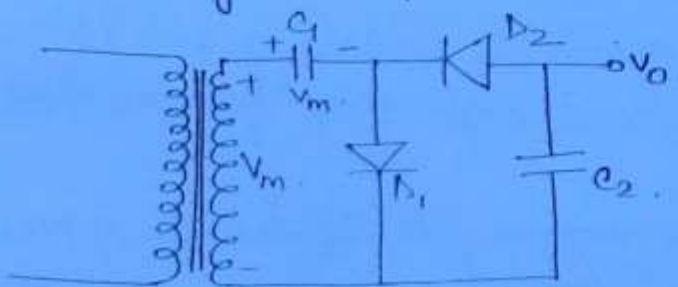


\rightarrow Half wave Voltage doubler


First half cycle,
 D_1 ON D_2 OFF

Second half cycle,
 D_1 OFF D_2 ON.

$V_0 = -2V_m$

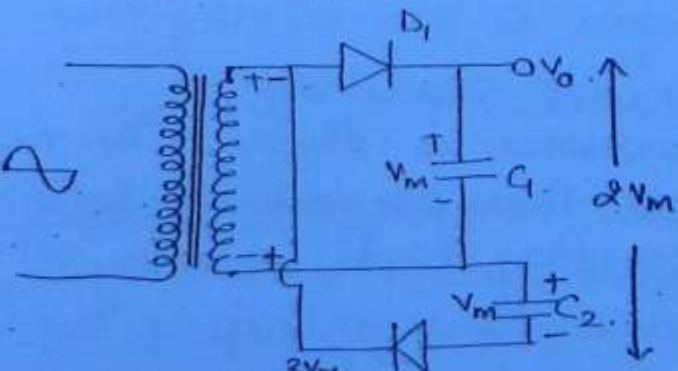

\rightarrow Full wave Voltage doubler

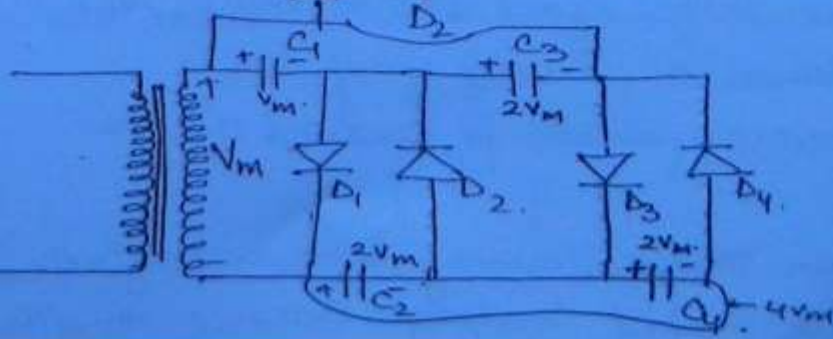


special name —

Schottky diode →

$f > 10\text{MHz}$

(1/0)

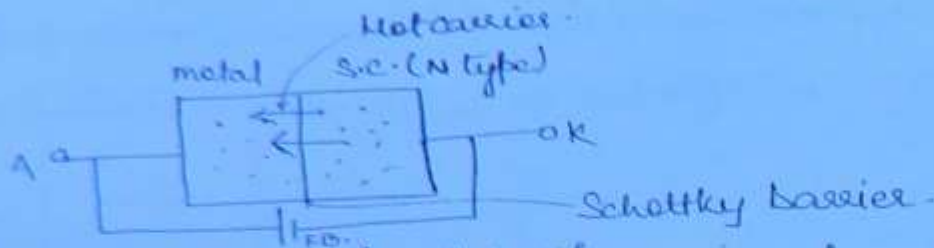


holes are not present. depletion region is not present.

Conclusions →

- Reverse recovery time is a problem in ordinary P-N junction diode which cannot be operated for high freq greater than 10MHz .
- To reduce the effect of reverse recovery time above 10MHz range special diode called as Schottky diode was implemented.
- Schottky diode construction details are diff. from ordinary diode.
- Schottky diode is a unipolar device where as ordinary diode is a bipolar device.
- There will be no depletion region in the Schottky diode because of missing of immobile ions and holes.
- As the e^- en. levels in semiconductor is always less than e^- en. levels in metal side. Therefore current is not possible in open ckt for Schottky diode [Schottky barrier]
- As the contact area b/w metal and S.C. is more, the forward and reverse resistance is very very less.
- A cut in voltage of Schottky diode is around 0.2 to 0.25V .
- In reverse bias condition, reverse recovery time is neglected. Therefore there will be rapid leakage current and less

breakdown curve -

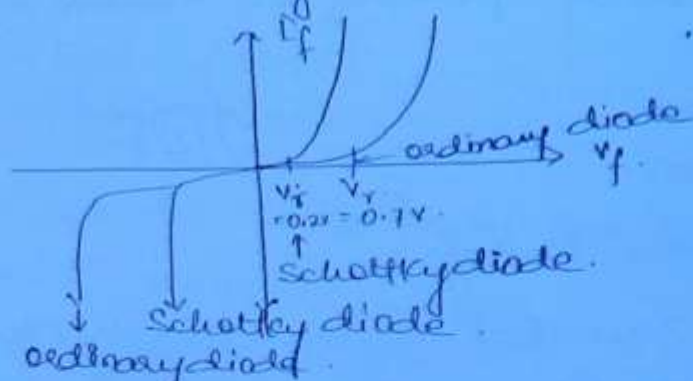

(11)

NOTE -

When Schottky diode is operated in FWD bias the e^- from N type will penetrate towards the metal side such ~~case~~ are called as hot carriers. That is the reason we called it as hot carrier diode.

Simple representation ->



Application ->

- 1) mainly used to rectify the signals above 300 MHz.
- 2) In digital comp., we already use this diode.
- 3) Digital clocks. (~~Special TTL diodes~~)
- 4) TTL high speed logic family)


BJT ->

(Bipolar j² transistor)

Introduction ->

Before 1957, Vacuum tubes are the devices which solve the per purpose of amplification.

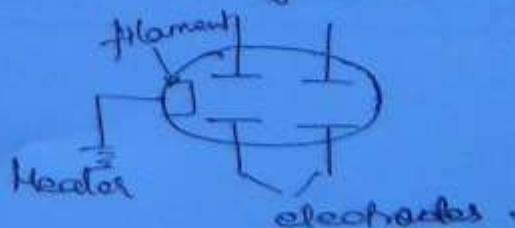The main disadvantage of vacuum tubes are



It is having an internal filament or heater which requires more power.

b) It takes more space.


c) Its life span is less.

d) Its power dissipation is high.

(1/2)

After 1957 BJT was invented which can also serve the purpose of amplification.

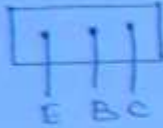The main advantage of BJT compare to vacuum tubes are



1) It is not having any internal filament or heater which requires more power.


2) It takes very less space.

3) Its life span is more.


4) Its power dissipation is very less in the order of ~~100~~ mW (milli watt).

Types of BJT: →

↳ PNP

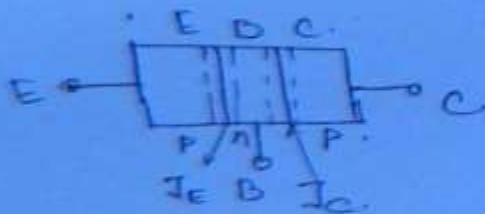

NPN

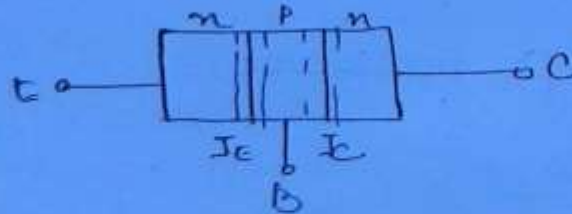

For proper working of BJT: →

conditions →

1) Doping level

$$E > C > B.$$

2) $w_B < l_p$ or l_n .

i) width of the base should be narrower.

✓ Transistor + Resistor = Transistor.

$Z_i \rightarrow$ low
 $Z_o \rightarrow$ high


(1/3)

Transfer of I from one place to another impd. is called transistor.

Types of operating region \rightarrow

Region	I_E	I_C
Active Region	FB	RB
Saturation region	FB	FB
Cutoff region	RB	RB
Reverse Active region	RB	FB

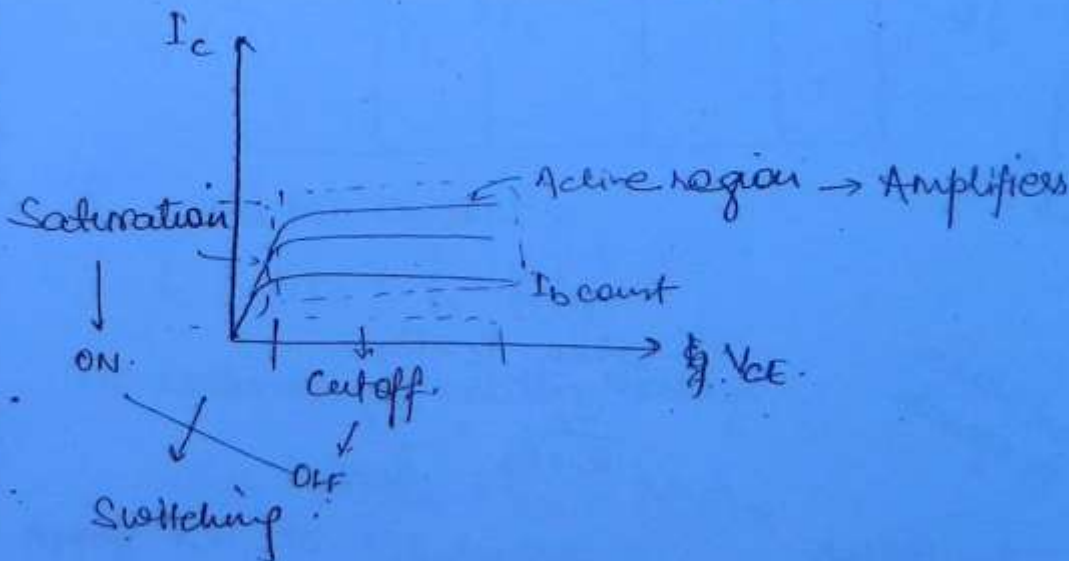\rightarrow BJT is current controlled device




Dc load line and operating pt

DC biasing and operating pt:-

CE amplifier →



(1/4)

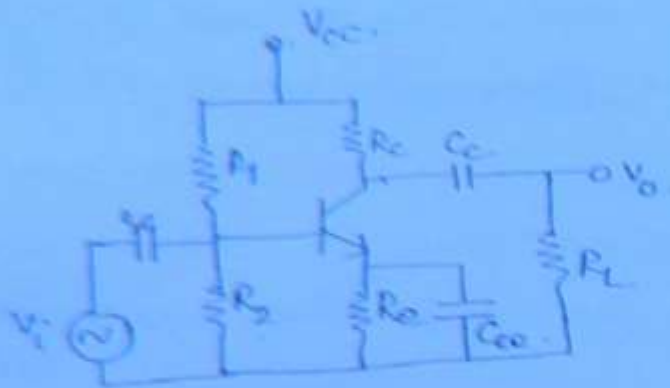

DC analysis →

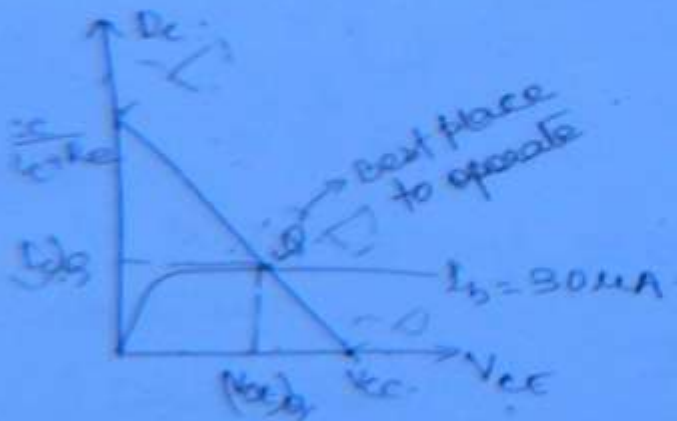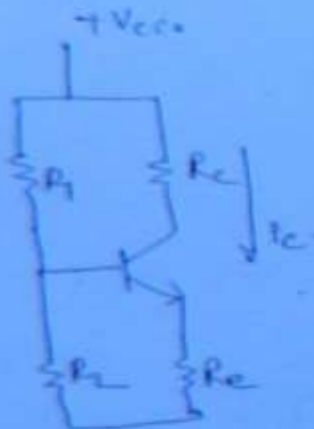1) ac should be grounded.

$$2) X_C \ll \frac{1}{f} \rightarrow 0 = \infty$$



When $I_C = 0$,

$$\frac{V_{CC}}{R_C + R_E} = \frac{V_{CE}}{R_C + R_E}$$

$$\Rightarrow V_{CE} = V_{CC}$$

O/P loop → $V_{CC} = I_C (R_C + R_E) + V_{CE}$

$$I_C = \frac{V_{CC}}{R_C + R_E} - \frac{V_{CE}}{R_C + R_E}$$

Conclusion :-

- For any analysis of BJT, we always prefer O/P char of BJT. [It is a current controlled device] (115)

- DC load line \rightarrow The locus of all the Q pts are conc. on a line is called as DC load line.

- Operating pt :-

(Quiescent pt)


\downarrow
Q active

It is the intersection pt b/w sample graph of I_c w.r.t dc load line

AC Analysis \rightarrow

DC should be grounded.
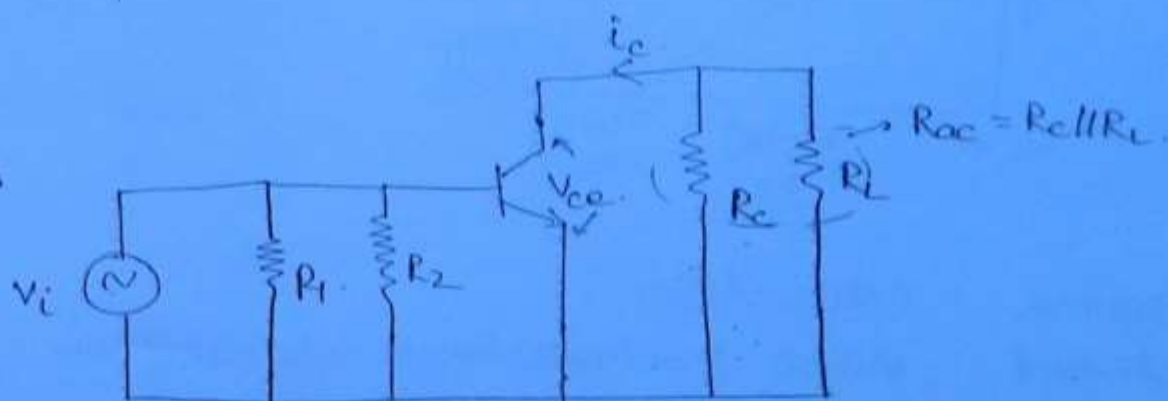
$$X_c \propto \frac{1}{f} \rightarrow 0$$



AC collector current =

$$i_c = \Delta I_c = i_c^0 - (I_c)_Q$$


ac collector to emitter voltage

$$v_{ce} = \Delta V_{ce} = V_{ce} - (V_{ce})_Q$$


Apply KVL to O/P loop

$$V_{ce} + i_c(R_{ac}) = 0$$
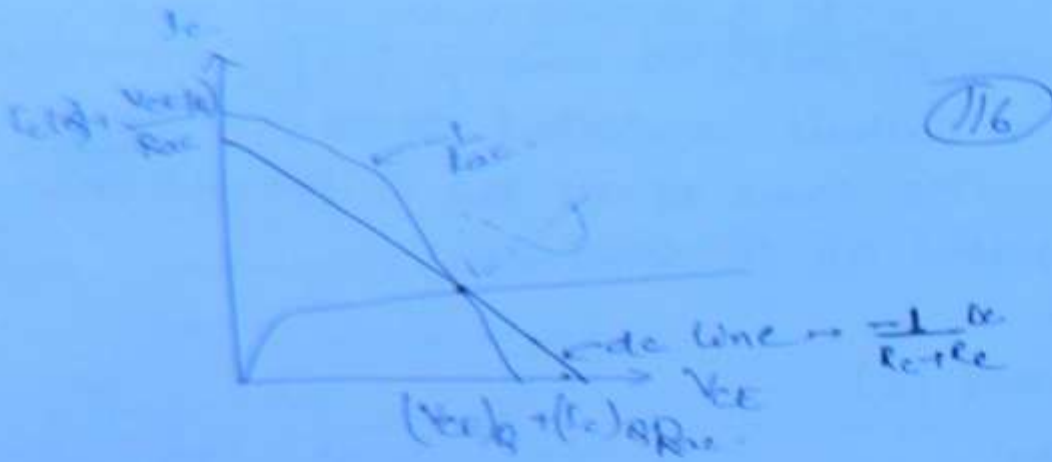
$$V_{ce} - (V_{ce})_Q + (i_c^0 - (I_c)_Q) R_{ac} = 0$$



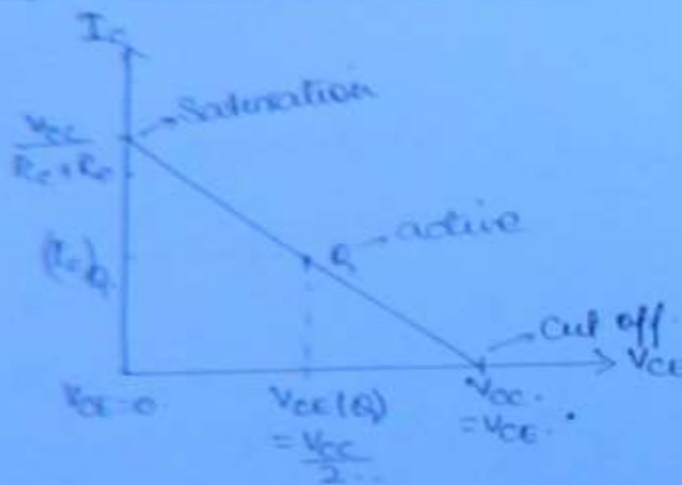
Conditions for V_{CE} in Saturation, active and cut off :-



Active Source
Power delivered
eg → Volt. Source
or
Current Source



Active device
which produces some internal gain.
eg → BJT, FET, MOSFET, OPAMP.

Simple representation of BJT :-

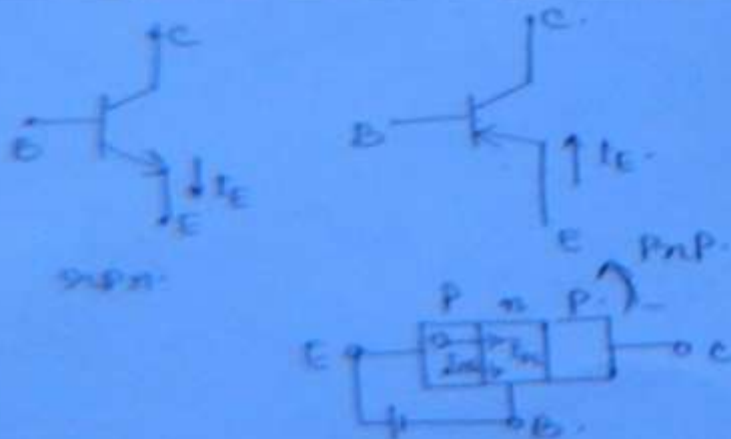


Ex. Band diagram concept in a p-n junction

(117)

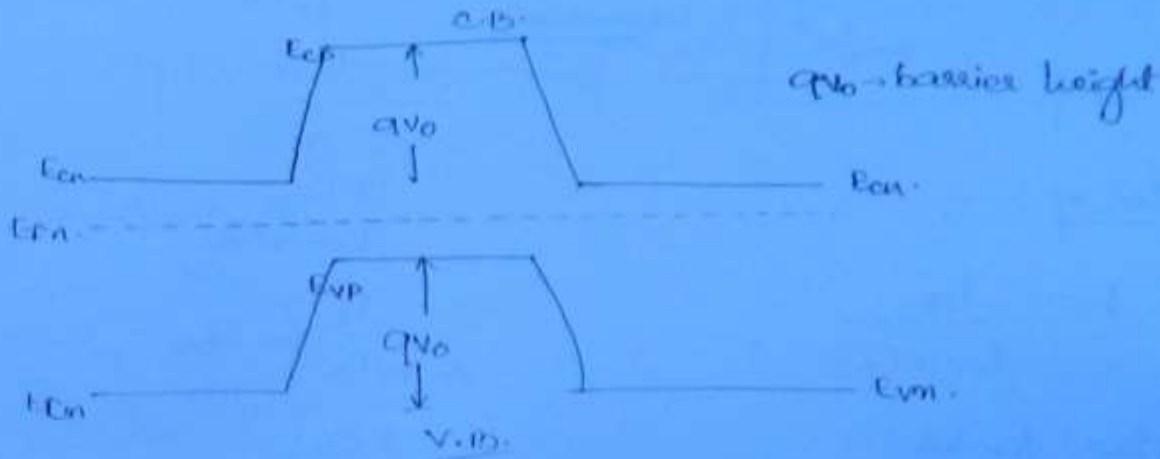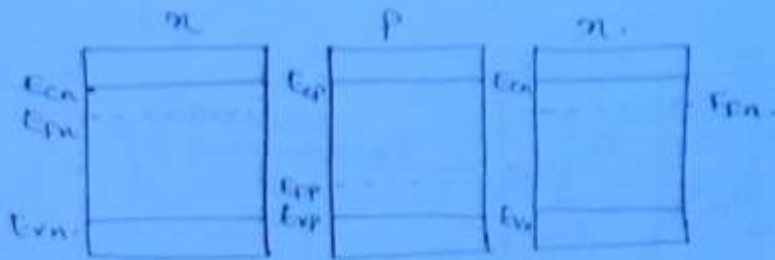


Conclusion →

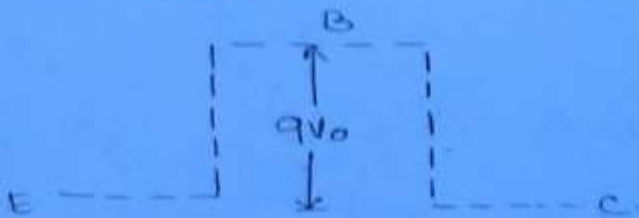


Note → Any no. of materials are joined, Fermi levels will be in aligned position.

Biased condition →

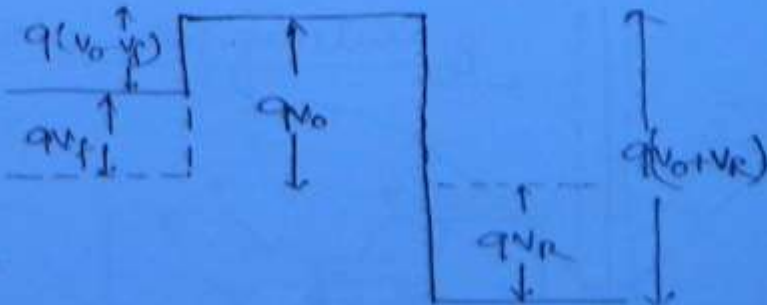

Transistor current components →

1/8

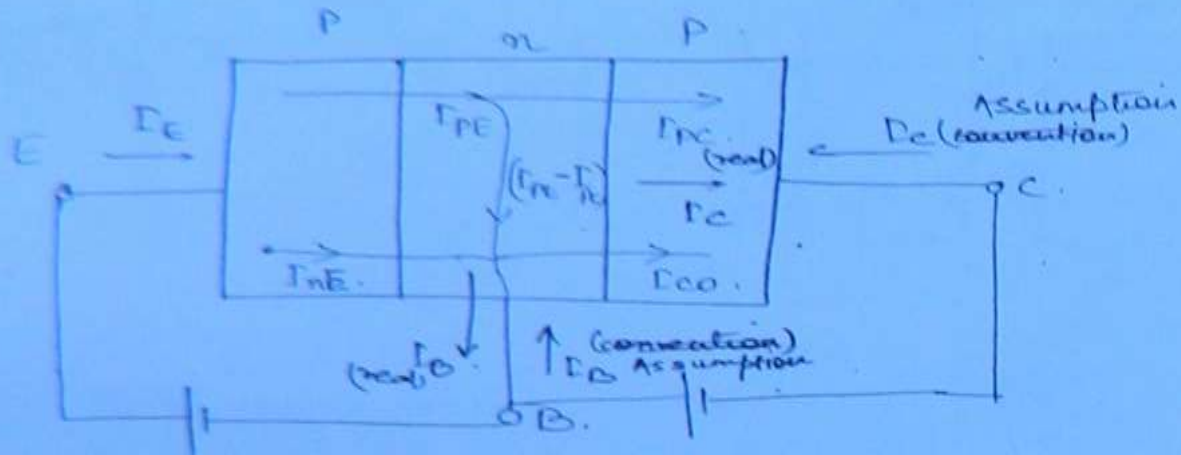

1) emitter η :-

$$\eta = \frac{I_{pE}}{I_{pE} + I_{nE}}$$

PnP.

I_E +ive

I_B }
 I_C } -ive.

2) Transport factor :-

$$\beta^* = \frac{I_{pC}}{I_{pE}}$$

nPN.


I_E -ive

I_B }
 I_C } +ive

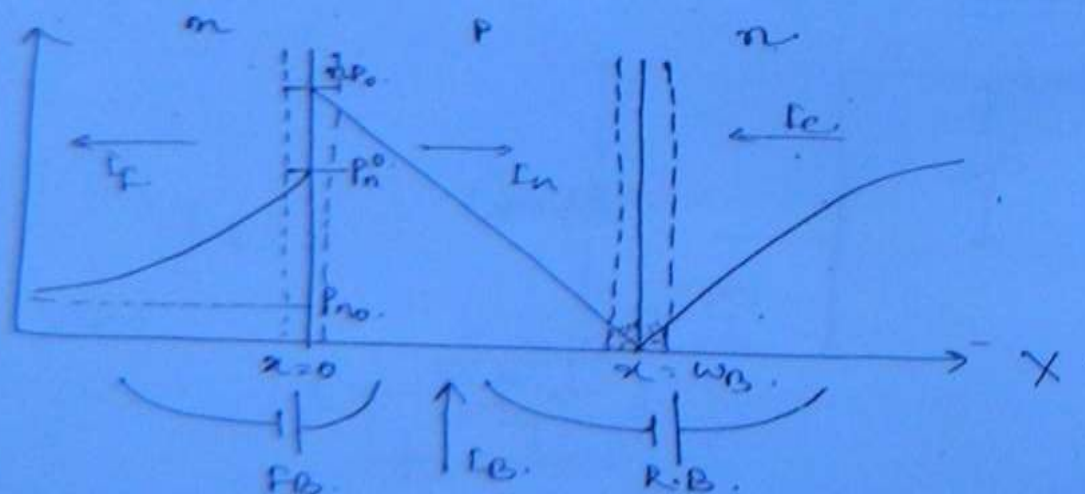3) large signal current gain α = $-\frac{(I_C - I_{CO})}{I_E - 0}$


$$\boxed{\alpha = \beta^* \eta}$$

Carrier Concentration V/s distance in BJT :-



npn →

(1/9)

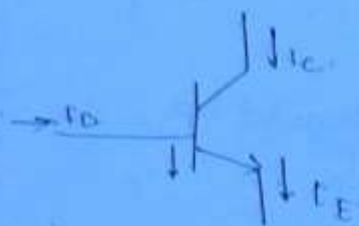

$$I_n = AqD_B \frac{dn(x)}{dx}$$

$$= AqD_B \frac{n_p(0) - 0}{0 - w_B}$$

$$= - \frac{AqD_B n_{p0}}{w_B}$$

$$I_C = -I_n = \left\{ \frac{AqD_B n_{p0}}{w_B} \right\} e^{\frac{V_{BE}}{V_T}}$$

↓
 I_S

$$n_{p(0)} = n_{p0} e^{\frac{V_{BE}}{V_T}}$$


↳ Law of I_n

$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

Where $I_S = \frac{AqD_B n_{p0}}{w_B}$

Transistor Configuration →


CB

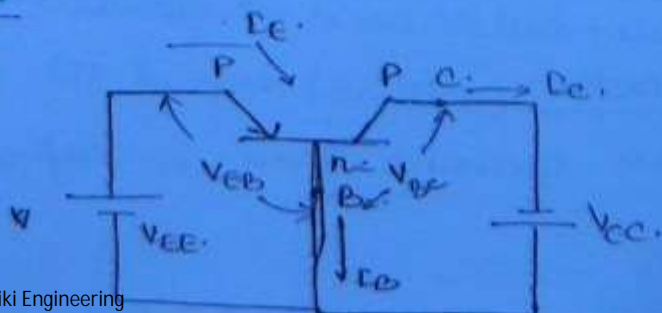

$$\text{Current gain} = \frac{I_C}{I_E} = \alpha$$

(120)


CE

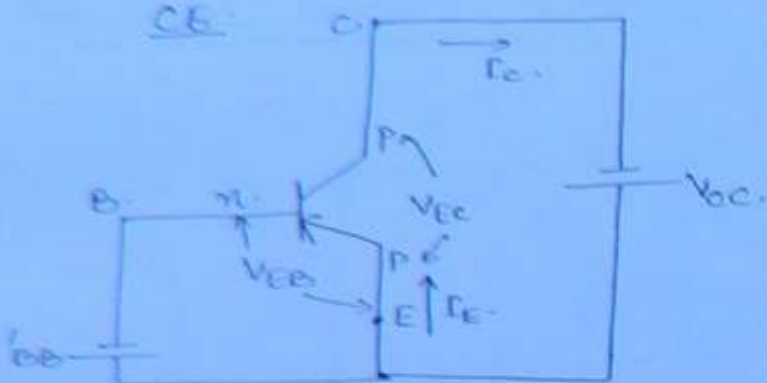

Collector should be always R.C.


$$\text{current gain} = \frac{I_C}{I_B} = \beta$$

CC

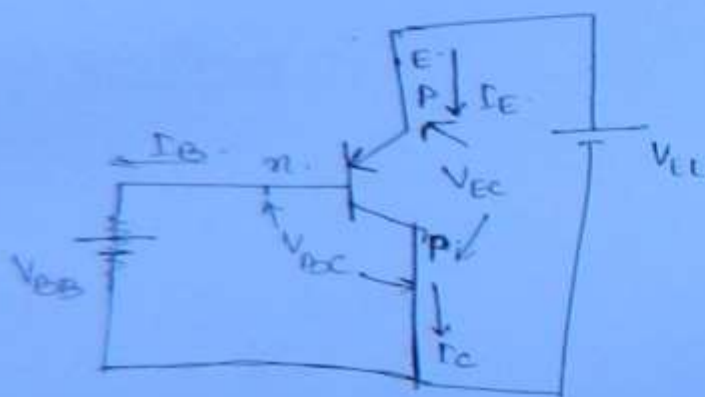


$$\frac{I_E}{I_B} = \gamma$$

n P n

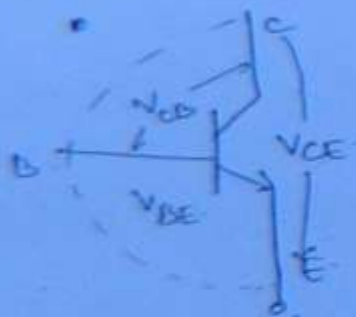

P n P

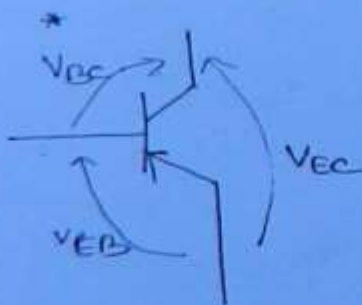

α, β, γ Relations \rightarrow

current amplification factor:—

1) In CE configuration the current gain is represented by α .

$$\alpha = \frac{I_C}{I_E}$$

Practically it lies b/w 0.9 to 0.99

2) In CE configuration, the current gain is represented by β

$$\beta = \frac{I_C}{I_B} \Rightarrow 20 \text{ to } 500.$$


(12)

3) In CC configuration, the current gain is represented by γ .

$$\gamma = \frac{I_E}{I_B} \Rightarrow 20 \text{ to } 500.$$

Total O/P current in CB:-

→ magnitude

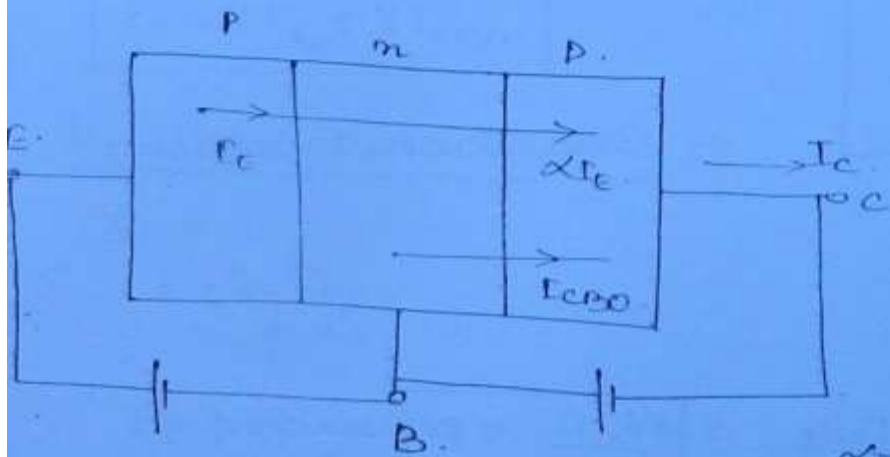

$$\alpha = \frac{I_C}{I_E}$$

$$I_C = \alpha I_E + I_{CEO}$$

$$I_E = I_B + I_C$$

$$I_C = \alpha (I_B + I_C) + I_{CEO}$$

$$\Rightarrow I_C (1 - \alpha) = \alpha I_B + I_{CEO}$$


$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{I_{CEO}}{1 - \alpha}$$

I_{CEO} → collector to base value reverse saturation current when I_B is open (emitter)

Total O/P current in CE \rightarrow

(122)

$$\beta = \frac{I_c}{I_b}$$

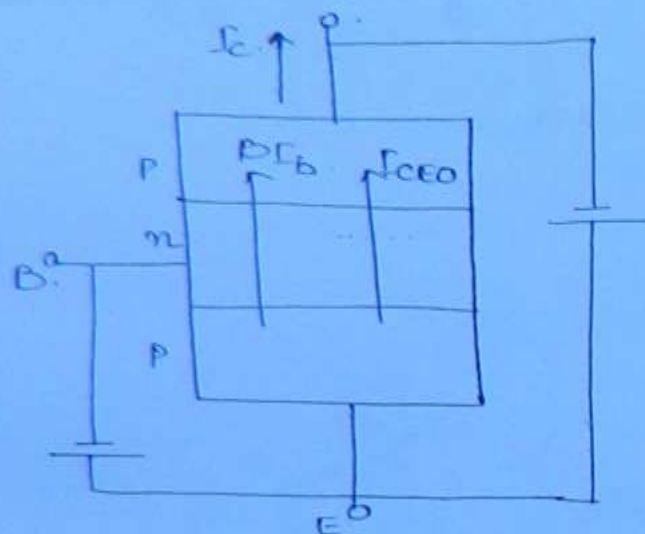

$$I_c = \beta I_b + I_{CEO}$$

$$I_{CEO} > I_{CBO}$$

$$\beta = \frac{I_c}{I_b} = \frac{I_c}{I_E - I_c} = \frac{I_c/I_E}{1 - I_c/I_E} = \boxed{\frac{\alpha}{1 - \alpha} = \beta}$$

$$\boxed{\frac{1}{1 - \alpha} = 1 + \beta}$$

$$I_c = \frac{\alpha}{1 - \alpha} I_b + \frac{1}{1 - \alpha} I_{CBO}$$

$$I_{CEO} = \frac{1}{1 - \alpha} I_{CBO}$$

$$\Rightarrow I_c = \beta I_b + (1 + \beta) I_{CBO}$$

$$\boxed{I_{CEO} = (1 + \beta) I_{CBO}}$$

Total O/P current in CE \rightarrow

$$I_E = I_B + I_c$$

$$I_c = \alpha I_E + I_{CEO}$$

$$I_E(1-\alpha) = I_B + I_{CBO}$$

$$I_E = \frac{I_B}{1-\alpha} + \frac{I_{CBO}}{1-\alpha}$$

(123)

$$I_E = (1+\beta) I_B + (1+\beta) I_{CBO}$$


$$\gamma = \frac{I_E}{I_B} = \frac{I_E}{I_E - I_C} = \frac{1}{1 - I_C/I_E} = \frac{1}{1-\alpha} = 1+\beta$$

$$\gamma = \frac{1}{1-\alpha} = 1+\beta$$

$$I_E = \gamma I_B + \gamma I_{CBO}$$


Transistor characteristics →

CB →

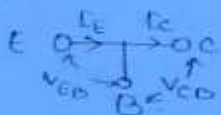

I/P parameters = I_E, V_{EB}

O/P parameters = V_{CB}, I_C

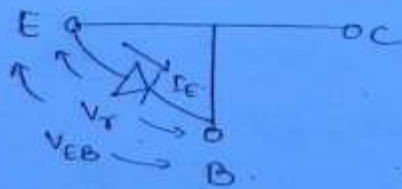


$V_{EB} \rightarrow 0.5 \text{ to } 0.7 \text{ V}$

$I_E \rightarrow 0 \text{ mA to } 140 \text{ mA}$

conclusion →

- 1) This is To get the I/P char., O/P voltage should be const
[O/P current I_C never change the I/P current I_E]
- 2) To get the O/P char., I/P current should be constant.
[I/P voltage will have less dynamic range]
- 3) BJT is current controlled device. That means the O/P char are controlled by I/P current but not voltage.

I/P char. in CB: →


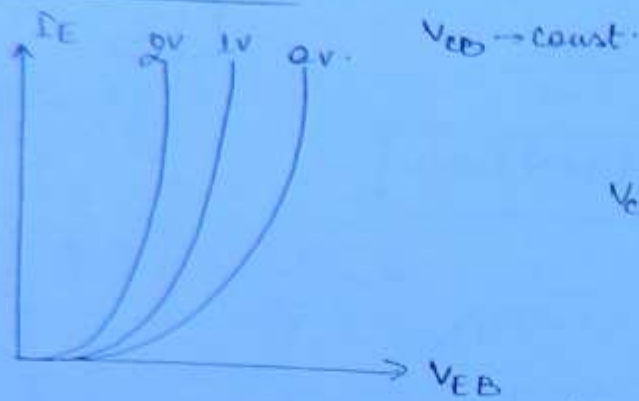


(124)

$V_{EB} \uparrow, W_B \downarrow, I_B \downarrow, I_{PFB} \uparrow, I_E \uparrow$

Early

Early effect or Base width modulation: —

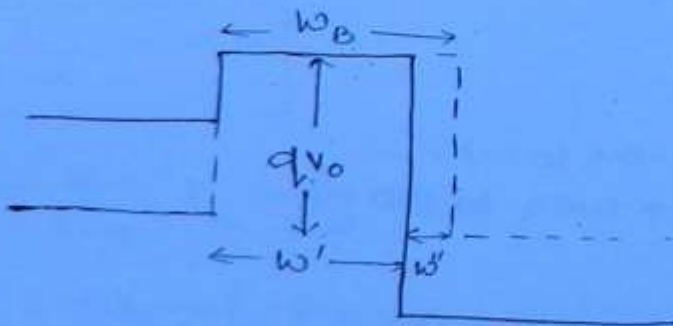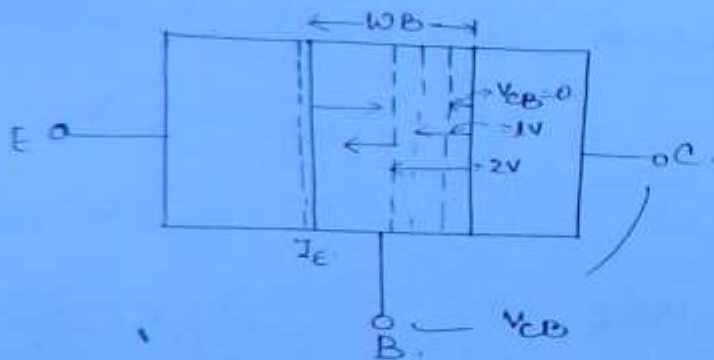


$$W_B = W' + W''$$

Physical width of base \uparrow effective base width \leftarrow penetration width.

$W_B = W''$
 $W' = 0$ } punch through or reach through.

C.B. O/P characteristics :-

(125)

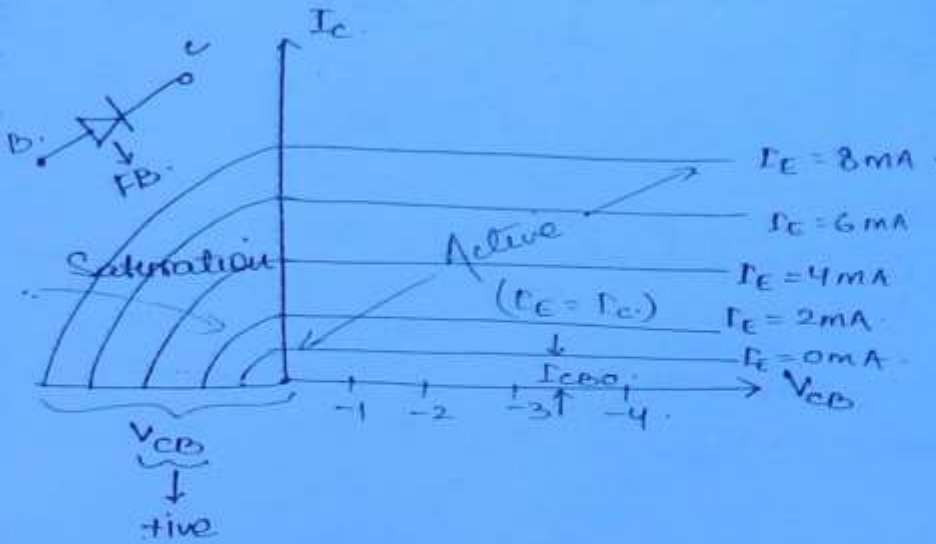


$$I_E = I_B + I_C$$

\downarrow \downarrow \downarrow
 mA mA mA

$$I_E \approx I_C$$

C.E. I/P characteristics :-

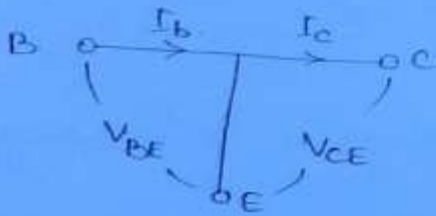


I/P parameters →

V_{BE}, I_B

O/P parameters →

V_{CE}, I_C

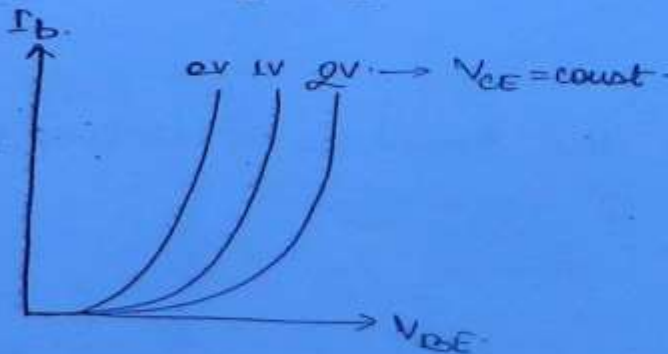


$V_{CE} \uparrow, I_C \downarrow, I_B \downarrow$

Early effect is possible in CE because collector terminal is R.B.

CE - O/P characteristics

(126)

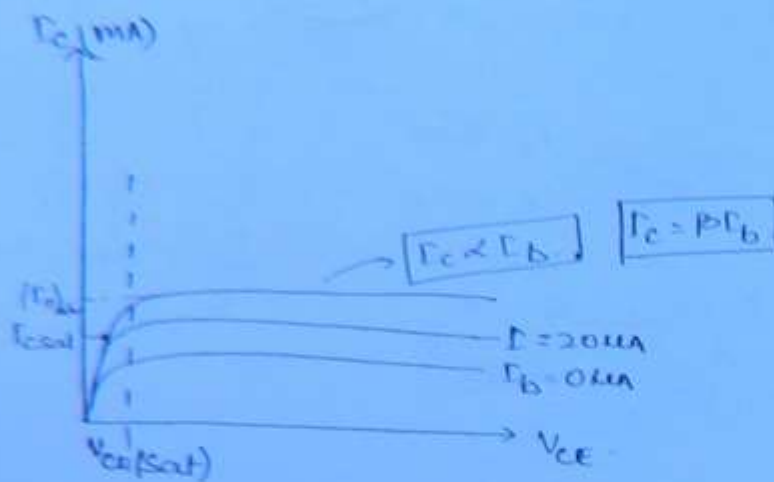

Q. In an npn si transistor if $V_{CE} = 0.3V$ then the transistor is acting in Active region.

Q. If $I_C = \beta I_B$ then the transistor is acting in Active region.


Q. If $I_B > \frac{I_C}{\beta}$, then the transistor is acting in Saturation region.

Q. If $(I_C)_{active} > I_C(sat)$, then the transistor is acting in Saturation region.

Q. If $(I_C)_{active} < I_C(sat)$ then the transistor is acting in Active region.

npn	$V_{CE(sat)}$	$V_{BE(sat)}$	$V_{BE(active)}$	$V_{BE(cutoff)}$	$V_{BE(cutoff)}$
si	0.2 V	0.8 V	0.7 V	0.5 V	0.0 V
Ge	0.1 V	0.3 V	0.2 V	0.1 V	-0.1 V



Pg-22
Ans 5

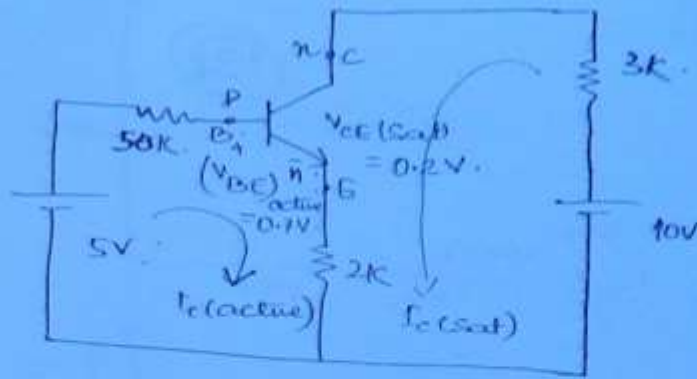

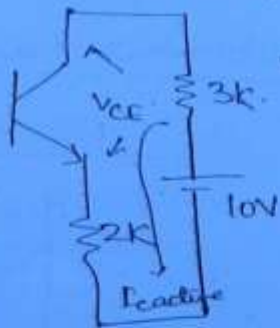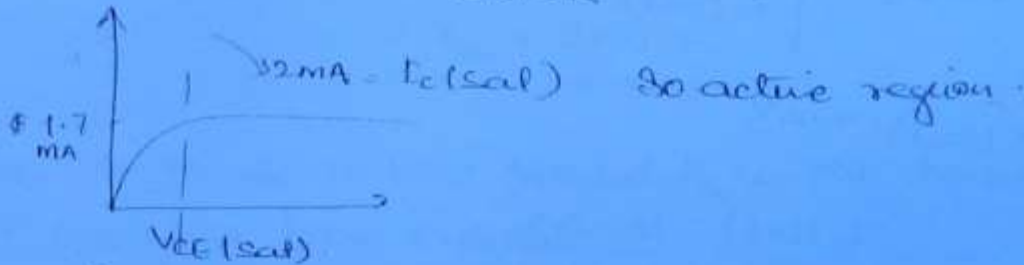(27)

$$I_C(\text{active}) = \frac{5 - 0.7}{2K} = 1.7 \text{ mA}$$


$$I_C(\text{sat}) = \frac{10 - 0.2}{2K + 3K} = \frac{10}{5K} = 2 \text{ mA}$$



$$V_{CE} = 10 - 5K \times I_C(\text{active}) \approx 1.5V$$

I/P	O/P
DB	R.B
Sat	L.B. L.B

Pg-21
Ch-4
B.L.

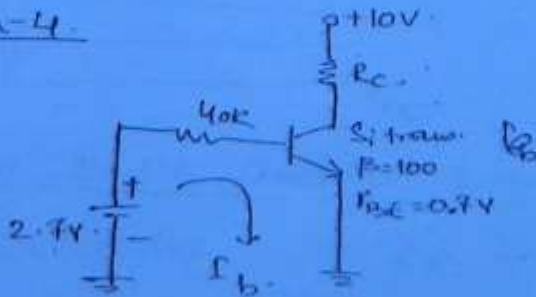

in active region only

$$I_B = \frac{2.7 - 0.7}{40K} = \frac{2}{40K} = \frac{1}{20} \text{ mA}$$

$$I_C = \beta I_B = 100 \times \frac{1}{20} \text{ mA} = 5 \text{ mA}$$



$$V_{CE} = 10 - 2.5 \times 5 \text{ mA} = -2.5V$$

$$V_{EB} + V_{BE} \approx V_{CE}$$

$$V_{EB} = -2.5 - 0.7$$

$$= -3.2V$$


(128)

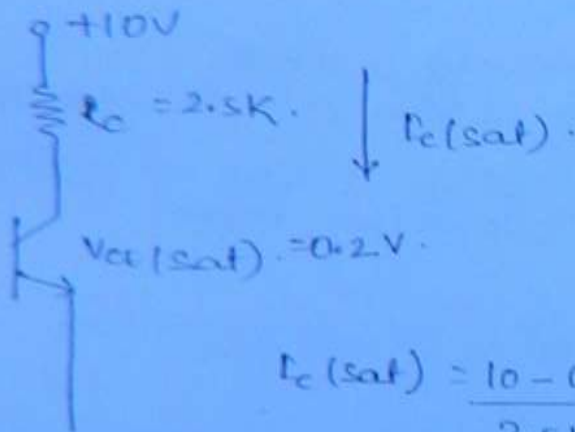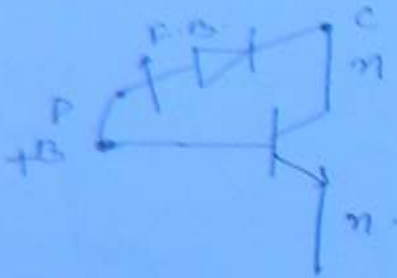

$$I_C(sat) = \frac{10 - 0.2}{2.5K}$$

$$= 3.9mA$$

Common Collector characteristics →

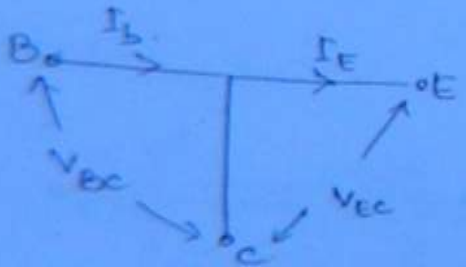



I/P parameters -

V_{EE}, I_B

O/P parameters -

V_{EE}, I_E

(124)

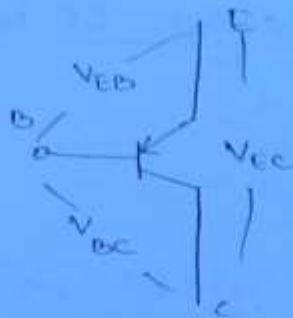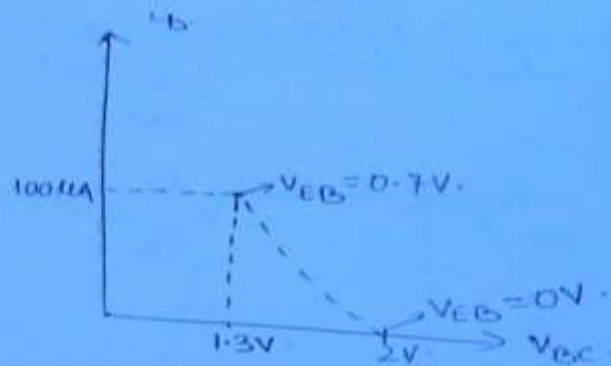

$$V_{EC} = V_{EB} + V_{EC}$$

$$V_{EC} = V_{EC} - V_{EB}$$


$$\text{Assume } V_{EC} = 2V$$

$$V_{EC} = 2 - 0.7 = 1.3V$$

V_{EB} can create a base current I_B in the transistor. V_E can also create a base current.

Common collector O/P characteristics \rightarrow


C.C. O/P

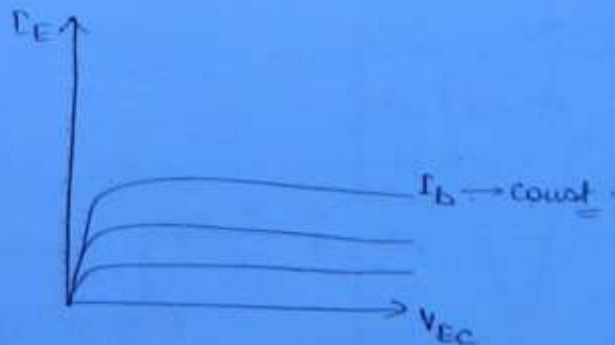

Diff b/w CB, CE, and C.C. characteristics \rightarrow

characteristics

1) Z_i

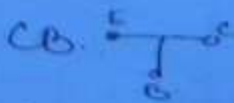

$$\frac{V_{BE}}{I_E} = \frac{0.7}{100 \mu A} = 7 \Omega$$

moderate

$$\frac{V_{EC}}{I_B} = \frac{10V}{1 \mu A} = 10^7 \Omega$$

2) Z_o

$$\frac{V_{BE}}{I_C} = \frac{10V}{10 \mu A} = 1k \Omega$$

moderate

$$\frac{V_{EC}}{I_E} = \frac{10V}{1 \mu A} = 10^7 \Omega$$

3) A_v

$$\frac{V_{CE}}{V_{EB}} \gg 1$$

$$A_v \gg 1$$

(130)

$$\frac{V_{CE}}{V_{EB}} \approx 1$$

4) A_I

$$\frac{I_C}{I_E} \approx 1$$

$$A_I \gg 1$$

$$\frac{I_C}{I_B} > 1$$


Conclusions →

- 1) In most of the practical application, we choose CE because power gain will be high. $A_v \gg 1, A_I \gg 1$
- 2) In CC, voltage gain = unity
- 3) In CB, current gain will be unity.

3/1/12

BJT Applications →

▷ Transistor as an amplifier →

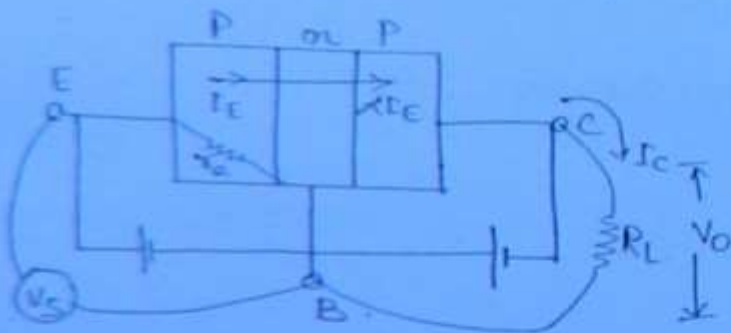

$$A_v = \frac{V_o}{V_i} = \frac{I_C R_C}{I_E R_E}$$

$$= \frac{\alpha I_E R_C}{I_E R_E}$$


$$= \frac{\alpha R_C}{R_E}$$

Assume $\alpha = 1$, $R_C = 3K\Omega$, $R_E = 30\Omega$

$$A_v = \frac{\alpha R_C}{R_E} = \frac{1 \times 3000}{30} = 100$$

2) Transistor switching times →

(131)

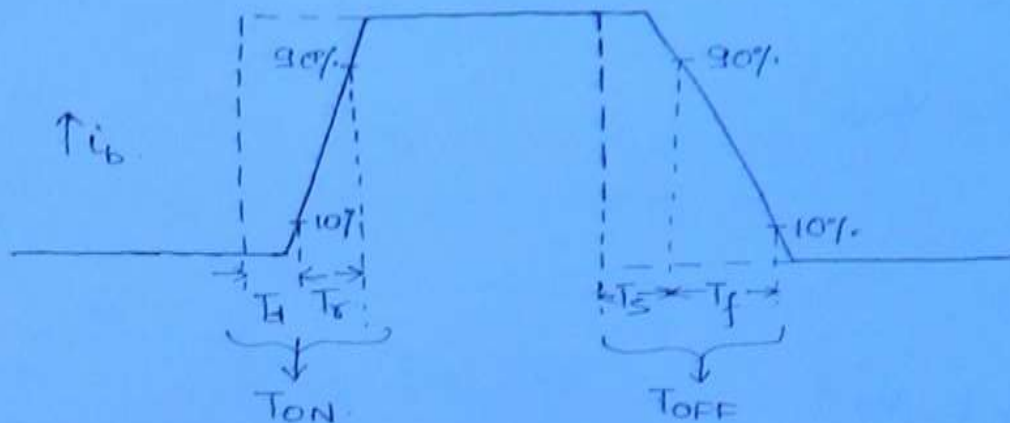


$$T_{ON} = T_d + T_r$$

\uparrow \uparrow
 delay rise
 time time


$$T_{OFF} = T_s + T_f$$

\downarrow \rightarrow
 storage fall
 time time

CE as 180° phase Shift :- →

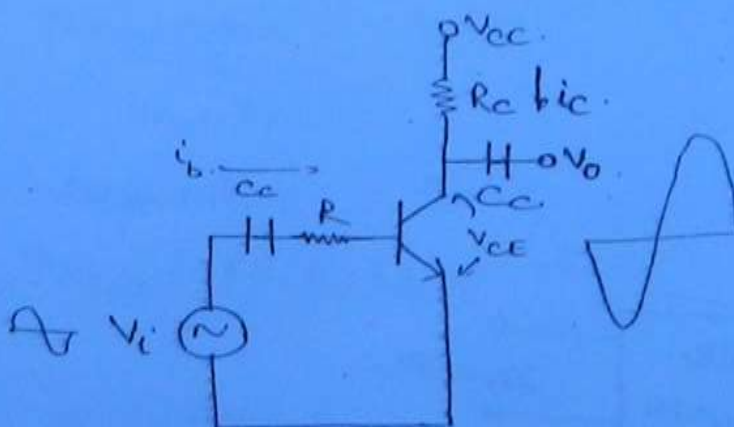

Ac Analysis

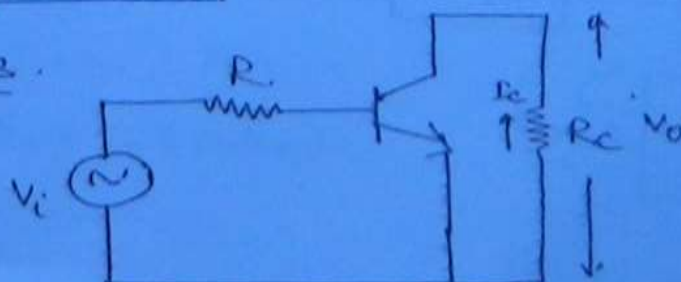

$$V_o = -I_c R_c$$

(132)

the half cycle →

$$i_b \uparrow, i_c \uparrow, i_c R_c \uparrow, V_o \downarrow$$

$$i_c = \beta i_b$$


-the half cycle →

$$i_b \downarrow, i_c \downarrow, i_c R_c \downarrow, V_o \uparrow$$


CC in impedance matching →

CC as emitter follower.

$$A_v = 1$$

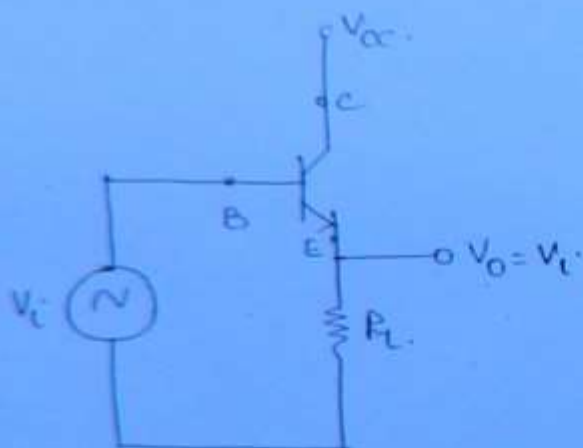



Impedance matching:

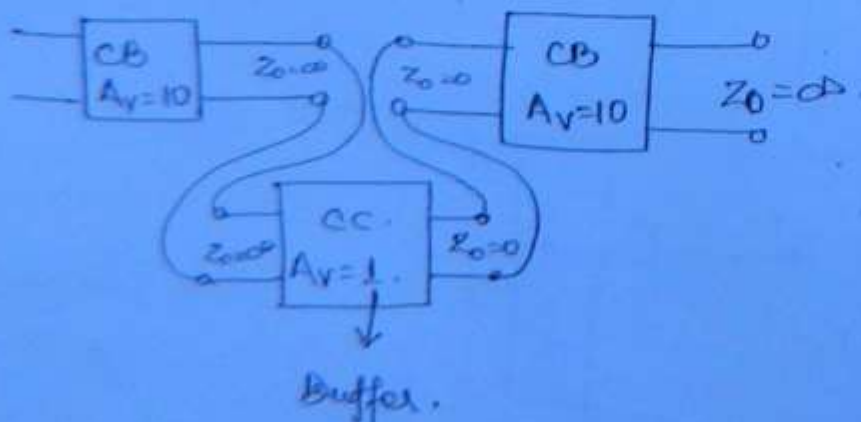

CB in high freq. application \rightarrow -

CE:

(133)

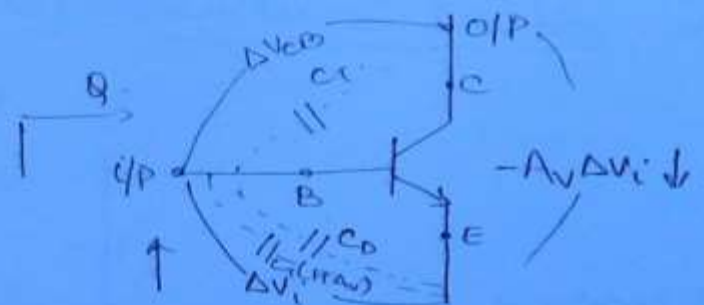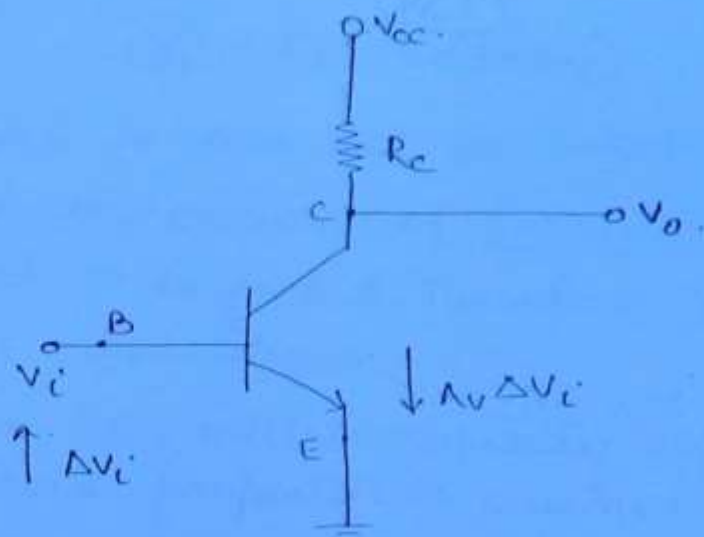

$$\Delta V_{CB} + \Delta V_i = -A_v \Delta V_i$$

$$V_B > V_C$$

$$-\Delta V_{CB} + \Delta V_i = -A_v \Delta V_i$$


$$\Delta V_{CB} = (1 + A_v) \Delta V_i$$

$$Q = C_T \Delta V_{CB}$$


$$= C_T (1 + A_v) \Delta V_i$$

$$C_{in}' = C_D + C_T (1 + A_v)$$


impedance network

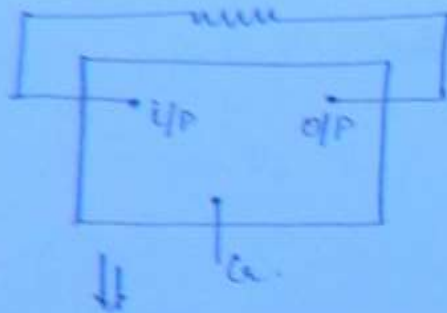

(134)

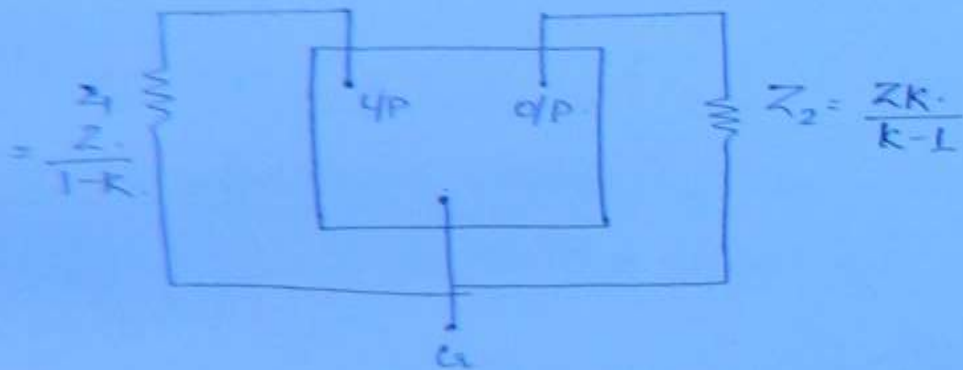

Proof →

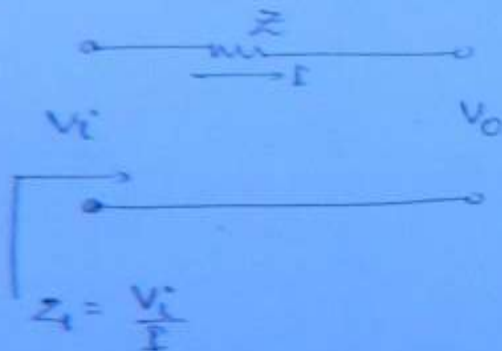

$$I = \frac{V_i - V_o}{Z}$$

$$= \frac{V_i \left[1 - \frac{V_o}{V_i} \right]}{Z}$$

$$Z_1 = \frac{V_i}{I} = \frac{Z}{1 - V_o/V_i}$$

$$\boxed{\frac{V_o}{V_i} = K}$$

Conclusion →

1) In CE, because of 180° phase shift property, miller's capacitive effect is existing at the CIP as

$$C_{in}' = C_D + C_T(1 + A_V)$$


(135)

Hence It can not be used for high freq. applications.

2) In CB, Because of inphase property, miller's capacity effect is neglected. Therefore it can be used for high freq. applications.

3) In CE, miller's capacity effect is neglected because of in phase property. It can not be used for high freq. because voltage gain is unity.

I_C dependence on V_{CE} →

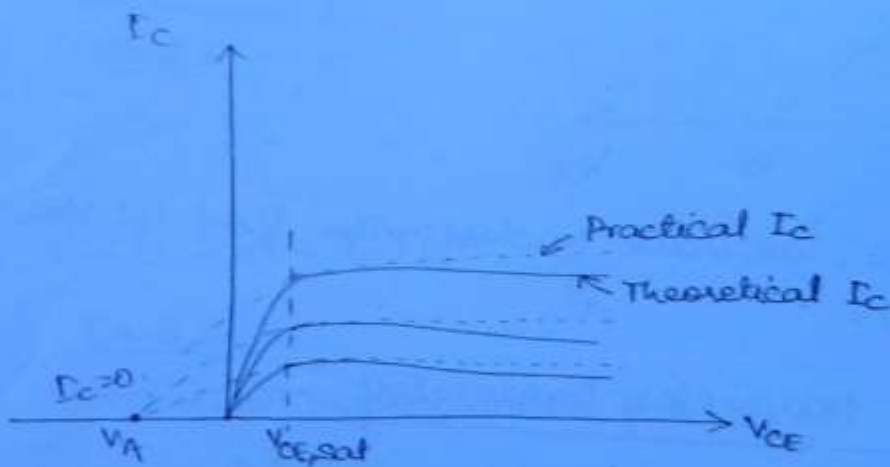

$$\boxed{I_C = I_S e^{V_{BE}/V_T}}$$

where $A_q \uparrow I_S = \frac{A_q D_0 P_{n0}}{W_B}$

early effect →

$V_{CE} \uparrow, W_B \downarrow$

$$I_C' = I_S e^{V_{BE}/V_T} \left[1 + \frac{V_{CE}}{V_A} \right]$$


if $V_A = \infty$
 $\boxed{I_c' = I_c}$

if $V_A = 0$,
 $\boxed{I_c' = \infty}$

(136)


BJT biasing →

Location of Q point on dc load line.

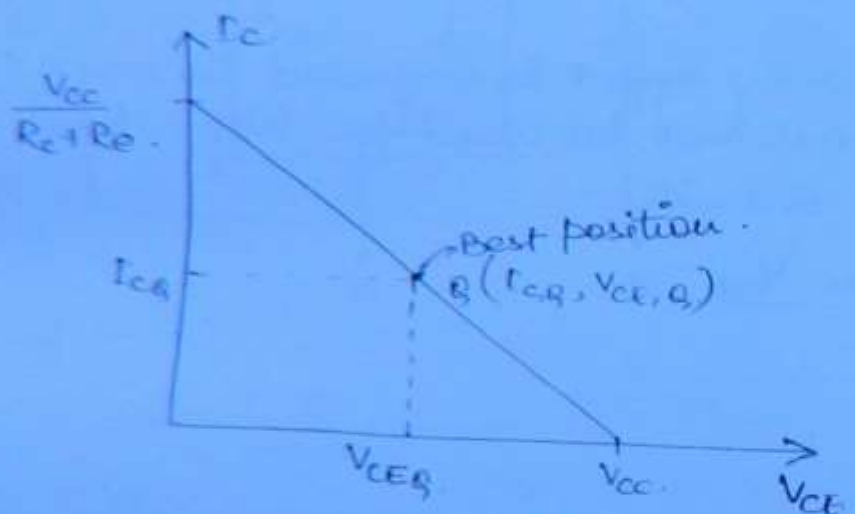

For amplifier analysis, we have to design the Q pt at the centre of dc load line.

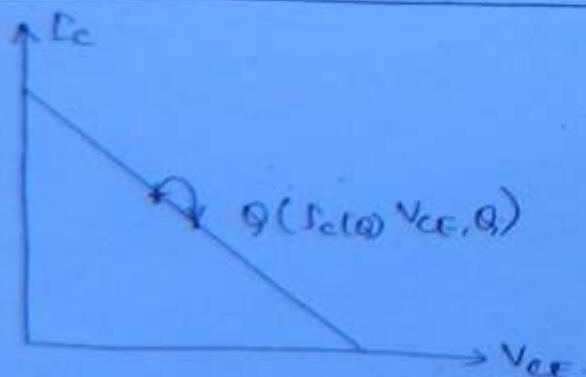Temp dependence on transistor parameters :-



$I_{CQ} \rightarrow \underbrace{I_{CQ}, V_{BE}, \beta}_{\text{Temp. dependence}}$

if $V_A = \infty$

$\boxed{I_{C'} = I_C}$


if $V_A = 0$,

$\boxed{I_{C'} = \infty}$

(136)


BJT biasing →

Location of Q point on DC load line.

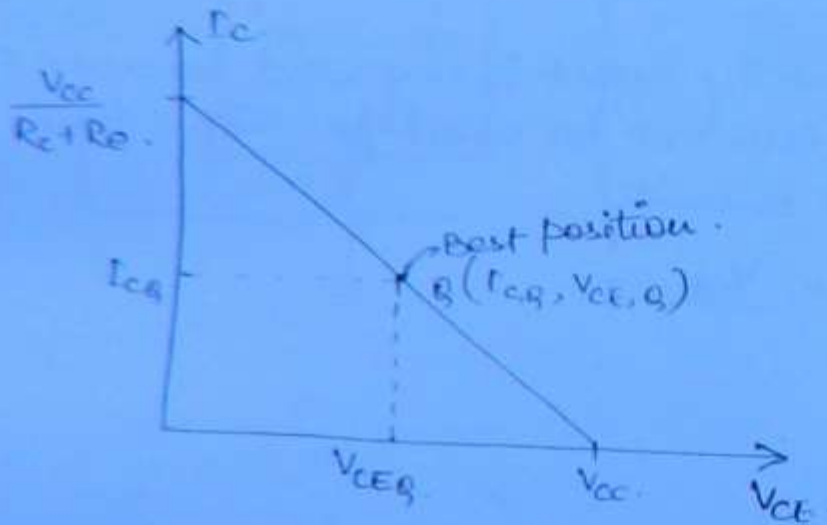

For amplifier analysis, we have to design the Q pt at the centre of dc load line.

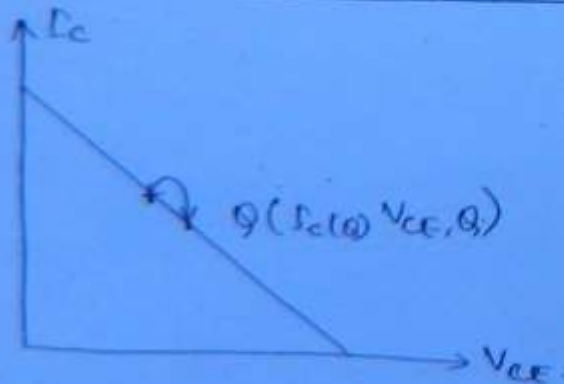Temp dependence on transistor parameters :-



$I_{CQ} \rightarrow \underbrace{I_{CQ}, V_{BE}, \beta}_{\text{Temp. dependence}}$

I_{CO} v/s temp -

I_{CO} increases by 7% for every $^{\circ}C$ rise in temp or doubles for every $10^{\circ}C$ rise in temp.

$T \uparrow, I_{CO} \uparrow$

(137)

As temp inc, I_{CO} will increase.

V_{BE} v/s temp -

$$\frac{dV_{BE}}{dT} = -2.5 \text{ mV}/^{\circ}C$$

$T \uparrow, V_{BE} \downarrow$

β v/s temp \rightarrow


Case 1. \rightarrow

$$\beta = \frac{I_C}{I_B}$$

$T \uparrow, I_{CO} \uparrow, I_C \uparrow, \uparrow \beta = \frac{I_C}{I_B}$


Case 2 \rightarrow

Transistor replacement problem.

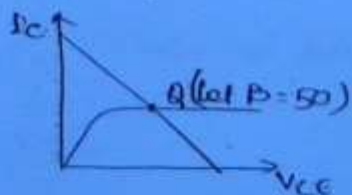

Stability factor \rightarrow
"S"

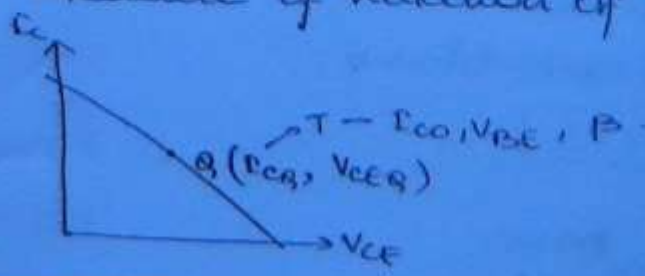It is a measure of variation of operating pt w.r.t. temp.



$$S_I = \frac{\partial I_C}{\partial I_{CO}} \quad \text{keeping } \beta, V_{BE} \rightarrow \text{const}$$

$$S_{II} = \frac{\partial I_C}{\partial V_{BE}} \quad \beta, I_{CO} \rightarrow \text{const}$$

(138)

$$S_{II'} = \frac{\partial I_C}{\partial \beta} \quad I_{CO}, V_{BE} \rightarrow \text{const}$$

Stability factor must be less.

NOTE:-

The most dominant parameter w.r.t temp is I_{CO} .

Ideally the Stability factor should be 0.

Practically the Stability factor should be min in Value

Expression for stability factor:-

$$I_C = \beta I_B + (1 + \beta) I_{CO}$$

diff w.r.t I_C ,

$$1 = \beta \frac{\partial I_B}{\partial I_C} + (1 + \beta) \left(\frac{\partial I_{CO}}{\partial I_C} \right)$$

$$S = \frac{1 + \beta}{1 - \beta \frac{\partial I_B}{\partial I_C}}$$

Biasing techniques →

Biasing →

1) Stabilization techniques

→ Fixed bias

→ collector to base bias

→ Voltage divider bias

or
Self bias

or
emitter base


or
Universal bias

2/ Compensation Techniques →

- Through diode
- Through Thermistor
- Through Sensistor.

(139)

Fixed Bias : —

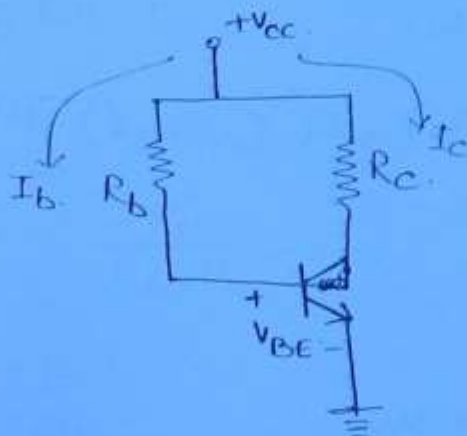

I/P loop →

$$V_{CC} = I_b R_b + V_{BE}$$

$$I_b = \frac{V_{CC} - V_{BE}}{R_b}$$

$$V_{CC} \gg V_{BE}$$

$$I_b \approx \frac{V_{CC}}{R_b}$$

$$I_c = \beta I_b \rightarrow \text{depend on } T \text{ \& } \beta \text{ replacement}$$

\downarrow \downarrow
fixed fixed

$$S = \frac{1 + \beta}{1 - \beta \frac{\partial I_b}{\partial I_c}}$$

$$S = 1 + \beta$$

Assume $\beta = 100$


$$I_b \approx \frac{V_{CC}}{R_b}$$

diff. w.r.t I_c

$$\frac{\partial I_b}{\partial I_c} = 0$$

$S = 101$ → so high so not preferred fixed biasing

Collector to base bias :-

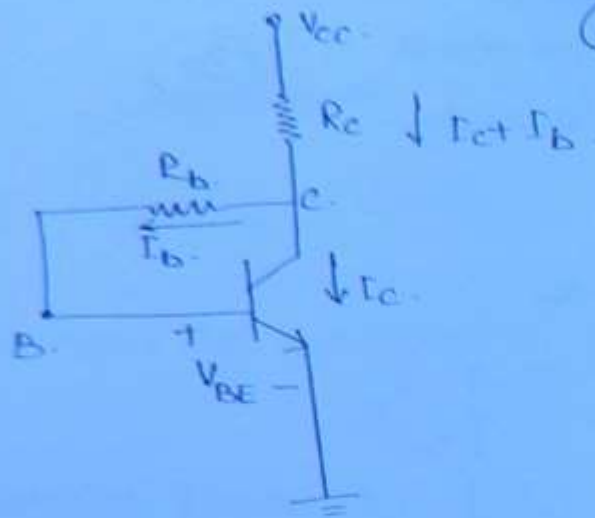

I/P loop \rightarrow

$$V_{CC} = (I_C + I_B) R_C + I_B R_B + V_{BE}$$

$$V_{CC} = I_B (R_B + R_C) + I_C R_C + V_{BE}$$

$$I_B = \frac{V_{CC} - I_C R_C - V_{BE}}{R_B + R_C}$$

O/P loop \rightarrow

$$V_{CC} = (I_C + I_B) R_C + V_{CE}$$

$$V_{CC} - I_C R_C = I_B R_C + V_{CE}$$

$$\therefore I_B = \frac{V_{CE} + I_C R_C - V_{BE}}{R_B + R_C}$$

Analysis \rightarrow

$$\text{If } T \uparrow, I_{CO} \uparrow, I_C \uparrow$$

$$(I_C + I_B) R_C \uparrow, V_{CE} \downarrow, I_B \downarrow, I_C \downarrow$$

$$\boxed{\downarrow I_C = \beta \downarrow I_B}$$

Stability factor in common emitter circuit

$$S = \frac{1+\beta}{1-\beta \frac{\partial I_b}{\partial I_c}}$$

(41)

$$V_{cc} = I_b(R_b + R_c) + I_c R_c + V_{BE}$$

diff. w.r.t. I_c .

$$0 = \frac{\partial I_b}{\partial I_c} (R_b + R_c) + R_c + 0$$

$$\frac{\partial I_b}{\partial I_c} = \frac{-R_c}{R_b + R_c}$$

$$S = \frac{1+\beta}{1+\beta \frac{R_c}{R_b + R_c}}$$

$$\Rightarrow S = \frac{1+\beta}{1+\beta \frac{R_b + 1}{R_c}}$$

When $\frac{R_b}{R_c} \ll 1$. $\boxed{R_c \gg R_b}$

$$S = \frac{1+\beta}{1+\beta}$$

$$\boxed{S = 1}$$

Conclusions -


- 1) If $\frac{R_b}{R_c} \ll 1$, The stability factor approaches to unity.
- 2) If R_b is less, base current drawn from the battery will be more that too means it reduces the battery life time.
- 3) If R_c is more, power dissipation losses increases and it may disturb the Q pt also.

Voltage divider bias :-

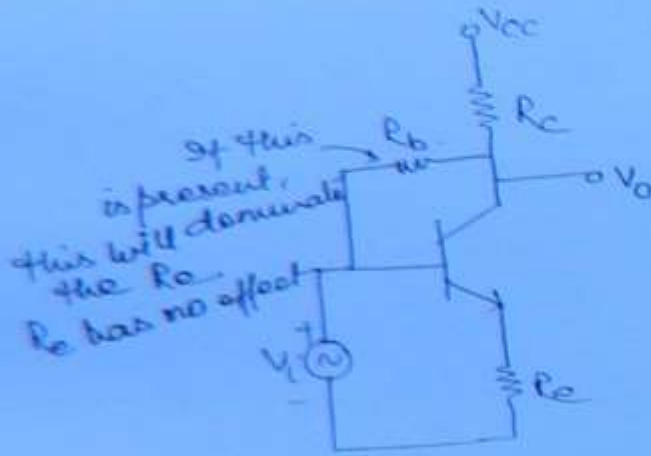(142)


Feedback

- +ve feedback $A_v \uparrow$, $S \downarrow$ → oscillators
- -ve feedback $A_v \downarrow$, $S \uparrow$ → Amplifier



* If we have two feedbacks in the ckt, we take the feedback which is nearest to the V_{cc} .

Voltage divider bias ckt :-

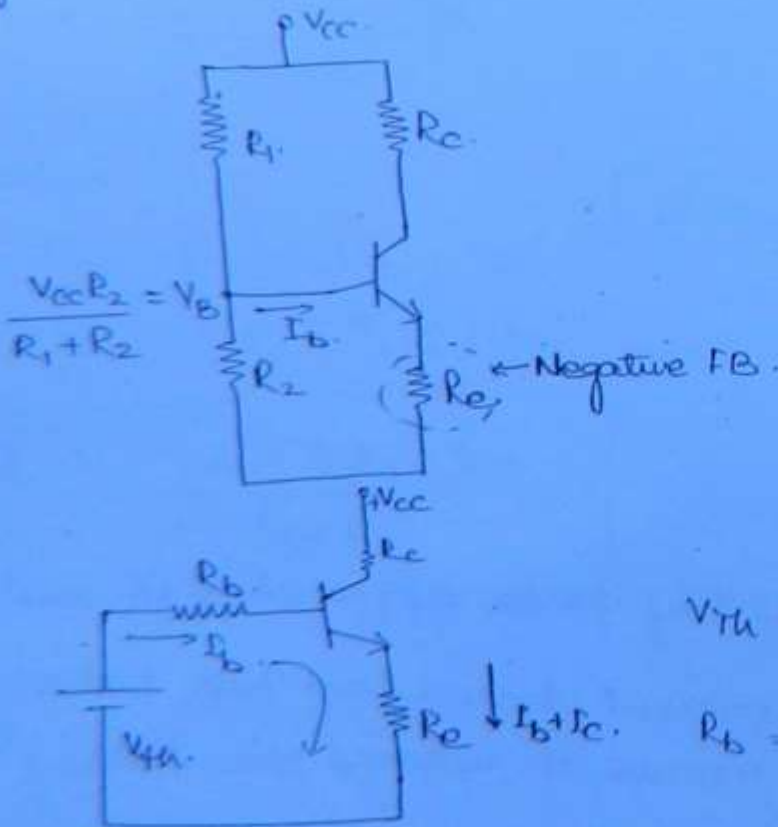

I/P loop :-

$$V_{th} = I_b R_b + V_{BE} + \frac{1}{\beta} I_c (I_b + I_c) R_e. \quad (143)$$

$$V_{th} = I_b (R_b + R_e) + V_{BE} + I_c R_e.$$

diff w.r.t. I_c .

$$0 = \frac{\partial I_b}{\partial I_c} (R_b + R_e) + R_e.$$

$$\Rightarrow \frac{\partial I_b}{\partial I_c} = \frac{-R_e}{R_b + R_e}$$

$$S = \frac{1 + \beta}{1 + \beta \frac{R_e}{R_b + R_e}}$$

$$= \frac{1 + \beta}{1 + \beta \frac{1}{R_b/R_e + 1}}$$

$$\text{if } \frac{R_b}{R_e} \ll 1$$

$$S = \frac{1 + \beta}{1 + \beta}$$


$$\boxed{S = 1}$$

Conclusions →

1) If $\frac{R_b}{R_e} \ll 1$, stability factor reaches to unity

2) R_b value should be less that means R_1 and R_2 resistors should be less. If R_1 is less, it reduces the battery life time. So, take $R_1 > R_2$ in the design.

3)

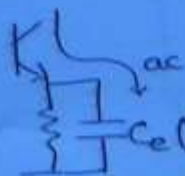


to make the gain stable


If R_E is more, it is increasing the V_{BE} across R_E of the ckt that means the gain be affected. This problem can be solved by keeping a shunt capacitor C_E to resistor R_E . (byp)

(144)

(by pass capacitor)

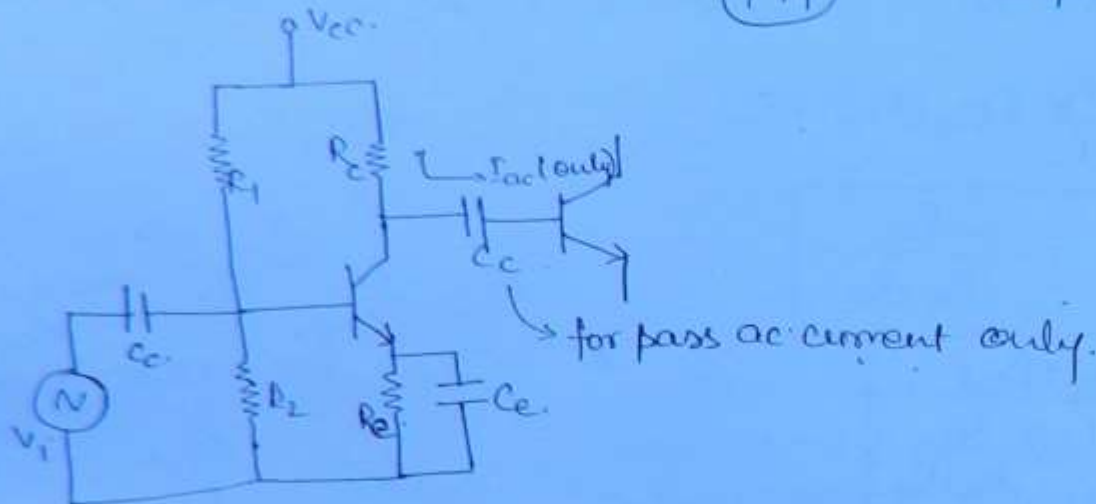

Analysis →

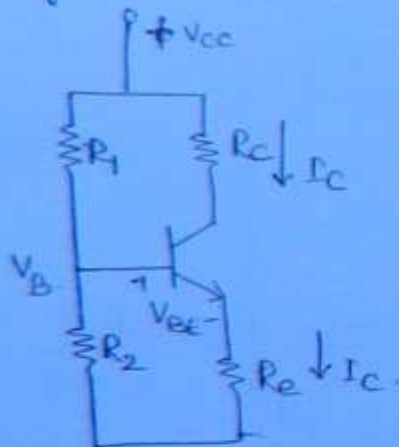

$$T \uparrow, I_{CO} \uparrow, I_C \uparrow$$


$$I_C R_E \uparrow, V_{BE} \downarrow, I_B \downarrow$$

$$I_C \downarrow$$

$$V_O = \downarrow V_{BE} + I_C R_E \uparrow$$

Compensation techniques →

Compensation through diode →


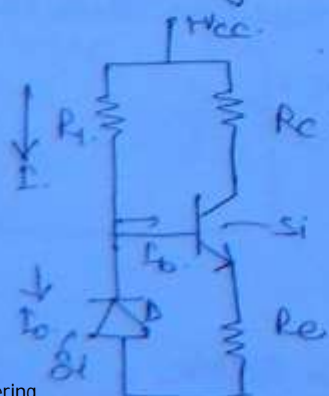


$$T \uparrow, I_{CO} \uparrow, I_C \uparrow, I_O \uparrow, I_B \downarrow, I_E \downarrow$$

Compensation through thermistor


Thermistor \rightarrow

(145)

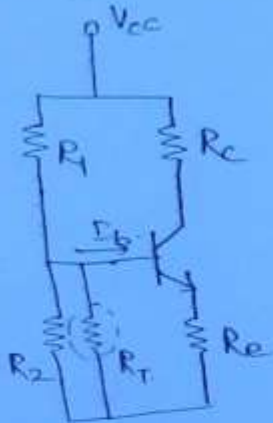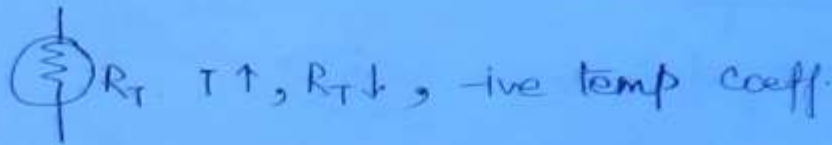

$T \uparrow, I_{CO} \uparrow, I_C \uparrow, R_T \downarrow, R_2 \parallel R_T \downarrow$

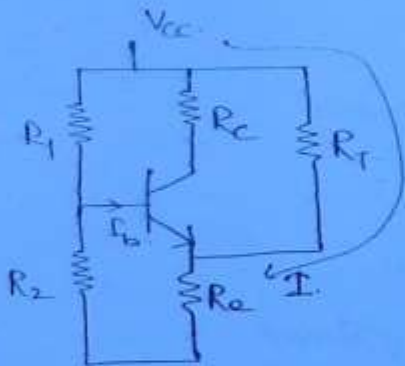$V_{BE} \downarrow, I_B \downarrow, I_C \downarrow$




$T \uparrow, I_{CO} \uparrow, I_C \uparrow, R_T \downarrow, I_C \uparrow, I_C R_E \uparrow,$

$V_{BE} \downarrow, I_B \downarrow, I_C \downarrow$

Compensation through Sensistor \rightarrow



$T \uparrow, R_s \uparrow$

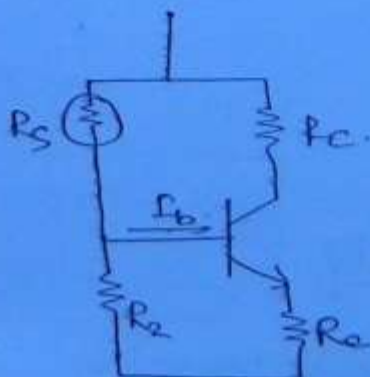

$T \uparrow, I_{CO} \uparrow, I_C \uparrow,$

$R_s \uparrow, R \downarrow, I_B \downarrow, I_C \downarrow$

10/1/12

Thermal runaway :-

$$T \uparrow, I_{co} \uparrow, I_c \uparrow, P_D = I_c^2 R_c,$$

(146)



Thermal Resistance (θ)

$$T_J - T_A \propto P_D$$


$$= \theta P_D \quad \theta \rightarrow \text{Thermal resistance}$$

$$T_J \rightarrow \text{Junction temp}$$

$$T_A \rightarrow \text{Ambient temp}$$

$$P_D \rightarrow \text{power dissipation}$$

eg

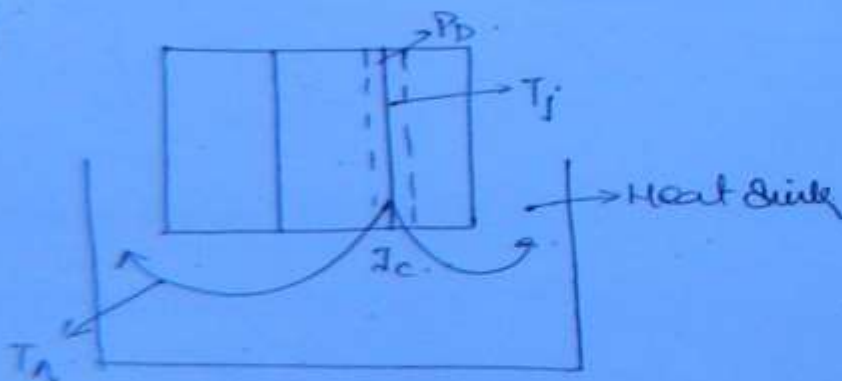


$$\theta = \frac{T_J - T_A}{P_D} \quad ^\circ\text{C/MW}$$

condition for Thermal stability

$$\frac{\partial P_c}{\partial T_J} < \frac{\partial P_D}{\partial T_J} \rightarrow \text{Safe operation}$$

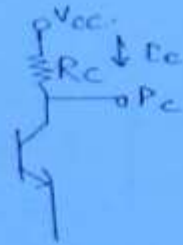The rate of heat generated at the collector j° should not exceed the heat dissipated at the collector j° .



(147)

P_c = Power dissipated generated at C- j° .

$$T_j - T_A = \theta P_D$$

diff w.r.t T_j

$$1 = \theta \frac{\partial P_D}{\partial T_j}$$

$$\frac{\partial P_D}{\partial T_j} = \frac{1}{\theta}$$

$$\left(\frac{\partial P_c}{\partial T_j} < \frac{1}{\theta} \right)$$

$$P_c =$$

$$\frac{\partial P_c}{\partial T_j} = \frac{\partial P_c}{\partial I_c} \frac{\partial I_c}{\partial T_j}$$

$$P_c = V_{cc} I_c - I_c^2 R_c$$

diff. w.r.t I_c ,

$$\frac{\partial P_c}{\partial I_c} = V_{cc} - 2 I_c R_c$$

$$\frac{\partial I_c}{\partial T_j} = \frac{\partial I_c}{\partial I_{co}} \frac{\partial I_{co}}{\partial T_j}$$

$$= S \times 0.07 I_{co}$$


$$\left((V_{cc} - 2 I_c R_c) S \times 0.07 I_{co} < \frac{1}{\theta} \right)$$

Small Signal Analysis :-

BJT :-

- low freq. Analysis


(48)

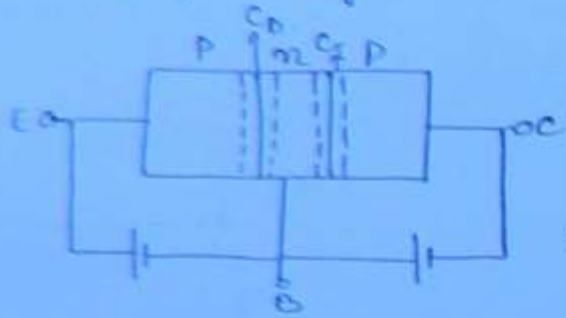

$$X_C \propto \frac{1}{f} \rightarrow 0$$

Internal Capacitance should be open in low freq.

- High freq. Analysis.

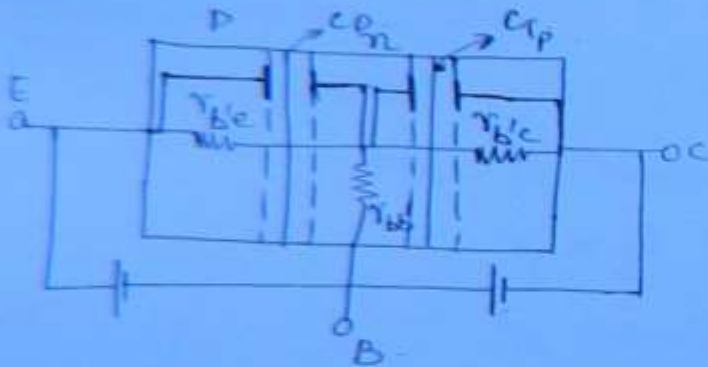




$$X_C \propto \frac{1}{f} \rightarrow \infty$$

∴ Internal capacitance are taken into account

We can not short ckt the capacitance as if it happens all resistance will be gone and no action as BJT.

Q. what is the diff. b/w small signal and large signal in amplifiers?


Ans.

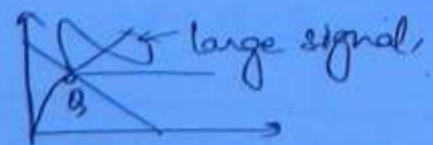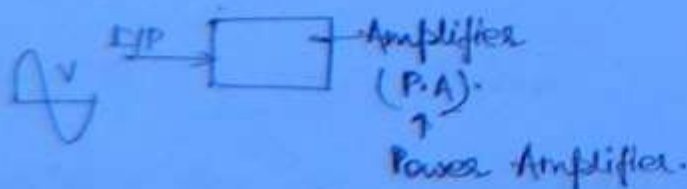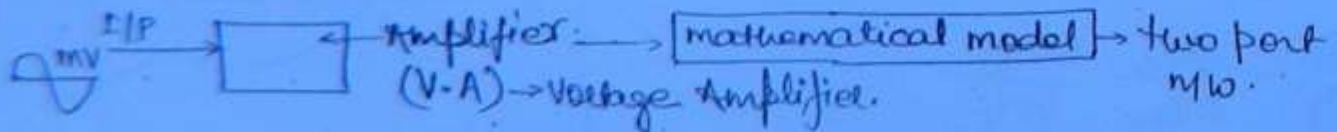

Low freq. Analysis →

Two port n/w →

(149)

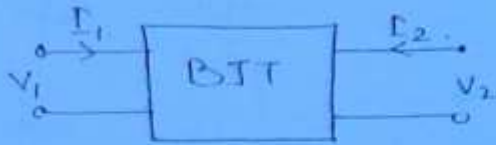

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

Case 1 →

$$V_2 = 0$$

$$h_{11} = \frac{V_1}{I_1} \rightarrow \text{I/P Impedance}$$

$$h_{21} = \frac{I_2}{I_1} \rightarrow \text{forward current gain}$$

Case 2 →

$$I_1 = 0$$

$$h_{12} = \frac{V_1}{V_2} \rightarrow \text{Reverse Voltage gain}$$

$$h_{22} = \frac{I_2}{V_2} \rightarrow \text{O/P admittance}$$

$$\begin{aligned} V_1 &= h_i I_1 + h_r V_2 \\ I_2 &= h_f I_1 + h_o V_2 \end{aligned}$$

For amplifier analysis, we require general char. like

1) Input Impedance Z_i

2) O/P Impedance Z_o


3) Voltage gain A_v

4) Current gain A_i

All these char. are efficiently explained by h-parameter model.

h-parameter model →
low freq. analysis.

(150)

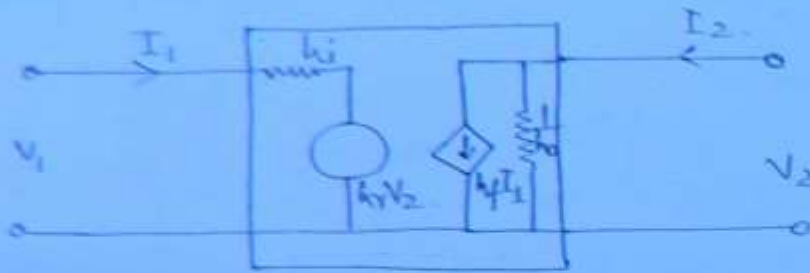

CE	CB	CC
h_{ie}	h_{ib}	h_{ie}
h_{fe}	h_{fb}	h_{fe}
h_{re}	h_{rb}	h_{re}
h_{oe}	h_{ob}	h_{oe}

Typical Values of h-parameters : →

Parameter	CE	CC	CB
h_i	1100Ω	1100Ω	22Ω
h_{fe}	50	$-51 \frac{I_E}{I_B}$	$-0.98 \frac{I_E}{I_E}$
h_r	2.4×10^{-4}	≈ 1	2.9×10^{-4}
h_o	$24 \times 10^{-6} A/V$	$25 \times 10^{-6} A/V$	$0.48 \times 10^{-6} A/V$

Conversion Techniques →

CE to CB

$$h_{ib} = \frac{h_{ie}}{1 + h_{fe}}$$

$$h_{fb} = \frac{-h_{fe}}{1 + h_{fe}}$$

$$h_{rb} = \frac{h_{ie} h_{oe}}{1 + h_{fe}} - h_{re}$$

$$h_{ob} = \frac{h_{oe}}{1 + h_{fe}}$$

CB TO CE →

$$h_{ie} = \frac{h_{ib}}{1 + h_{fb}}$$

$$h_{fe} = \frac{-h_{fb}}{1 + h_{fb}}$$

$$h_{re} = \frac{h_{ib}h_{ob}}{1 + h_{fb}} - h_{rb}$$

$$h_{oe} = \frac{h_{ob}}{1 + h_{fb}}$$

(157)

CE to CC →



$$h_{ic} = h_{re}$$

$$h_{fc} = -(1 + h_{fe})$$

$$h_{rc} = 1$$

$$h_{oc} = h_{oe}$$

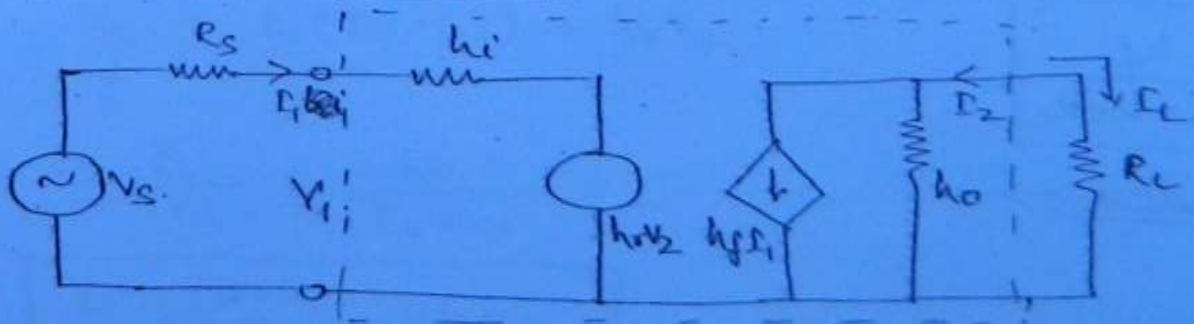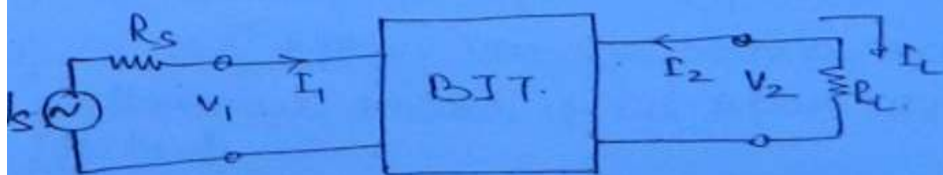Transistor Amplifier Analysis : →
[using exact model]



characteristics of amplifier →

- 1) current gain A_I
- 2) I/P Impedance Z_i
- 3) Voltage gain A_V
- 4) O/P Impedance Z_o
- 5) Voltage amplification A_{Vs}
- 6) Current Amplification A_{Is}
- 7) effective I/P impedance Z_i'
- 8) effective O/P impedance Z_o'

(152)

Current gain →

$$V_1 = h_i I_1 + h_r V_2$$

$$I_2 = h_f I_1 + h_o V_2$$

$$A_I = \frac{I_2}{I_1} = -\frac{I_2}{I_1}$$

$$I_2 = h_f I_1 + h_o V_2$$

$$V_2 = I_2 R_L$$

$$I_2 = h_f I_1 + h_o (-I_2 R_L) = -I_2 R_L$$

$$\Rightarrow I_2 (1 + h_o R_L) = h_f I_1$$

$$\Rightarrow \frac{I_2}{I_1} = \frac{h_f}{1 + h_o R_L}$$

$$A_I = -\frac{I_2}{I_1} = -\frac{h_f}{1 + h_o R_L}$$

Input Impedance →

$$Z_i = \frac{V_1}{I_1}$$

$$V_1 = h_i I_1 + h_r V_2$$

$$\frac{V_1}{I_1} = h_i + h_r \frac{V_2}{I_1} = h_i + h_r \left(\frac{-I_2 R_L}{I_1} \right) = h_i + A_I h_r R_L$$

$$Z_i = h_i + h_r A_I R_L$$

Voltage gain : — (153)

$$A_v = \frac{V_2}{V_1}$$

$$= \frac{-\beta_2 R_L}{\frac{I_1}{V_1 / \beta_1}}$$

$$A_v = \frac{A_I R_L}{Z_i}$$

Output Impedance →

$$Z_o = \frac{V_2}{I_2}$$

$$Y_o = \frac{I_2}{V_2}$$

$$= h_f \left(\frac{I_1}{V_2} \right) + h_o \left(\frac{V_2}{V_2} \right)$$

$$= h_f \left(\frac{I_1}{V_2} \right) + h_o$$

To cal. the o/p impedance, two conditions should be follow

- 1) R_L should be open. ($R_L = \infty$)
- 2) If the I/P is voltage source, make it as short ckt otherwise make it as open ckt if it is a current source

I/P loop →

$$V_2 = I_1 (R_s + h_i) + h_r V_2$$

$$\downarrow$$

$$0$$

$$\Rightarrow \frac{I_1}{V_2} = \frac{-h_r}{R_s + h_i}$$

$$Y_o = \frac{-h_f h_r}{R_s + h_i} + h_o$$

$$Z_o = \frac{1}{Y_o}$$

Voltage Amplification →

$$A_{vs} = \frac{V_2}{V_s}$$


$$= \frac{V_2}{V_1} \times \frac{V_1}{V_s}$$

$$= A_v \left(\frac{V_1}{V_s} \right)$$

$$A_{vs} = A_v \cdot \frac{R_i}{R_i + R_s}$$

When $R_s = 0$ [Ideality]

$$A_{vs} = A_v$$

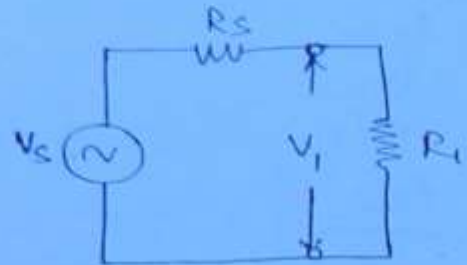

$$V_1 = \frac{R_i}{R_i + R_s} V_s$$

$$\frac{V_1}{V_s} = \frac{R_i}{R_i + R_s}$$

Current Amplification →


$$A_{is} = \frac{I_L}{I_s} = \frac{I_L}{I_1} \times \frac{I_1}{I_s}$$

$$= A_I \frac{I_1}{I_s}$$

$$= A_I \frac{R_s}{R_i + R_s}$$

When $R_i = 0$,


$$A_{is} = A_I$$

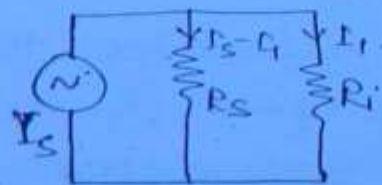

$$(I_s - I_1) R_s = I_1 R_i$$

$$\frac{I_1}{I_s} = \frac{R_s}{R_i + R_s}$$

Effective I/P and O/P Imp : →

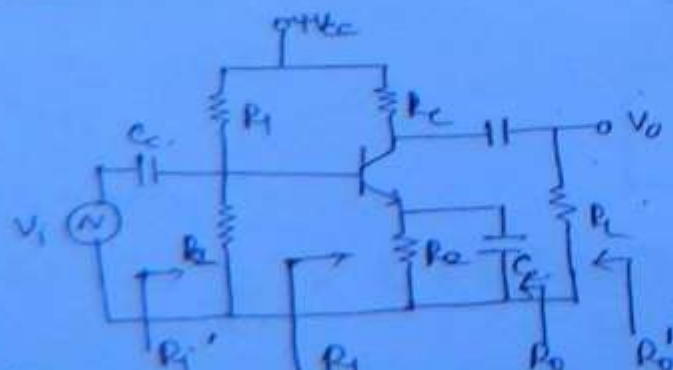

$$R_i = h_{ie}$$

$$R_i' = R_1 \parallel R_2 \parallel h_{ie}$$

$$R_o = \frac{1}{h_{oe}}$$

(55)

$$R_o' = \frac{1}{h_{oe}} \parallel R_c \parallel R_L$$

Conclusion →

Exact analysis is valid for all the 3 types of configurations like common emitter, CB, CC.

For eg →

$$(A_v)_{CB} = \frac{-h_{fb}}{1 + h_{ob} R_L}$$

$$(A_v)_{CC} = \frac{-h_{fc}}{1 + h_{oc} R_L}$$


Approximate model Analysis : →

1) $h_{oe} R_L \leq 0.1$

$$\begin{aligned} \text{eg. } A_v &= \frac{-h_{fe}}{1 + h_{oe} R_L} \\ &= \frac{-h_{fe}}{1 + 0.1} \\ &= -91 h_{fe} \end{aligned}$$



2) h_{re} and h_{oe} should be neglected

3) This is valid in CE mode only.

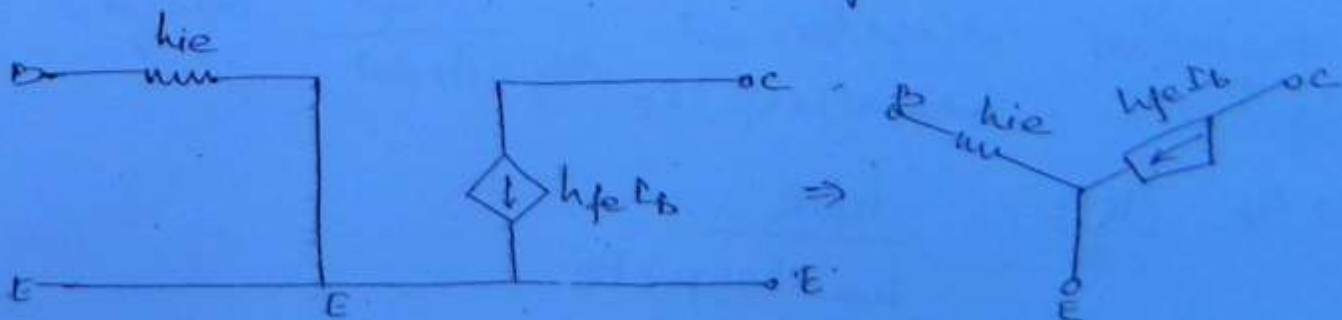

CE Unbypass Amplifier

156

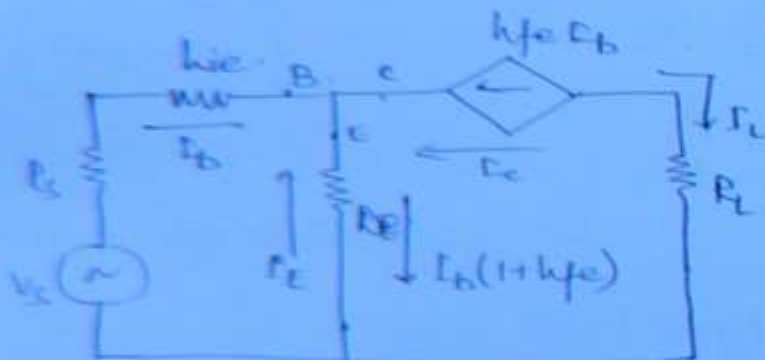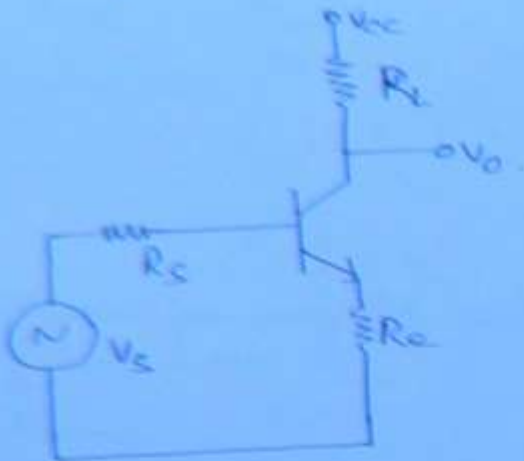

$$1) A_E = \frac{v_O}{I_b} = -\frac{h_{fe} I_b}{I_b} = -h_{fe}$$


$$\text{or } \frac{-h_{fe}}{1+h_{fe} R_E} \quad h_{oe} \rightarrow \text{neglected} = -h_{fe}$$

$$2) R_i = \frac{V_1}{I_b} = \frac{h_{ie} I_b + (1+h_{fe}) I_b R_E}{I_b} = h_{ie} + (1+h_{fe}) R_E$$

$$3) A_v = \frac{A_E R_L}{R_i} = \frac{-h_{fe} R_L}{h_{ie} + (1+h_{fe}) R_E}$$

$$4) R_o = \frac{V_2}{I} \rightarrow \infty$$

CE Bypass →

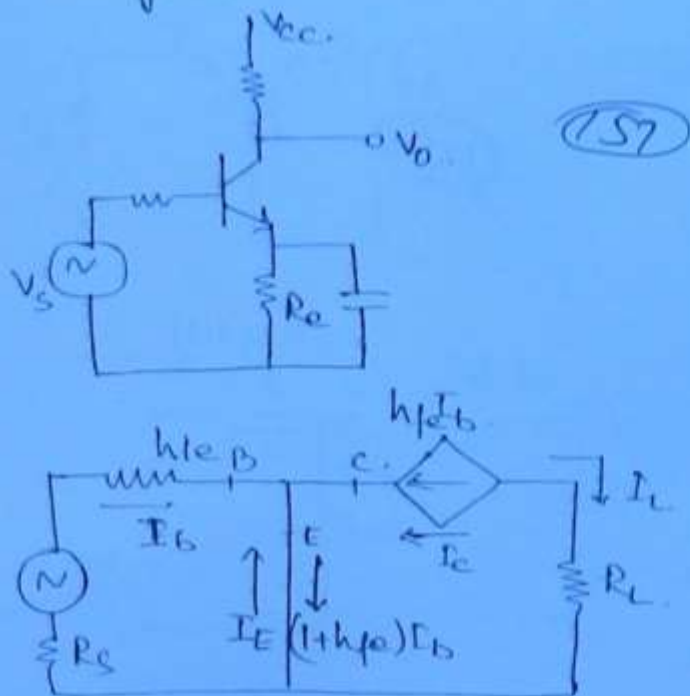

$$A_f = \frac{I_L}{I_b} = -h_{fe}$$

$$R_i = h_{ie}$$


$$A_v = \frac{-h_{fe} R_L}{h_{ie}}$$

$$R_o = \frac{V_2}{I_{c \rightarrow 0}} \Rightarrow \infty$$


Table →

	A_v	R_i	Feedback
CE Bypass	$-h_{fe} R_L$	h_{ie}	No
CE Unbypass	$\frac{-h_{fe} R_L}{h_{ie} + (1+h_{fe}) R_e}$	$h_{ie} + (1+h_{fe}) R_e$	Yes (Negative)

CC \rightarrow

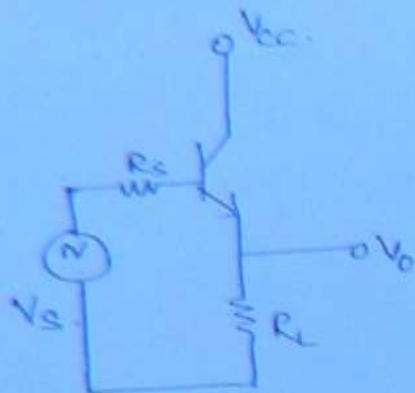

(158)

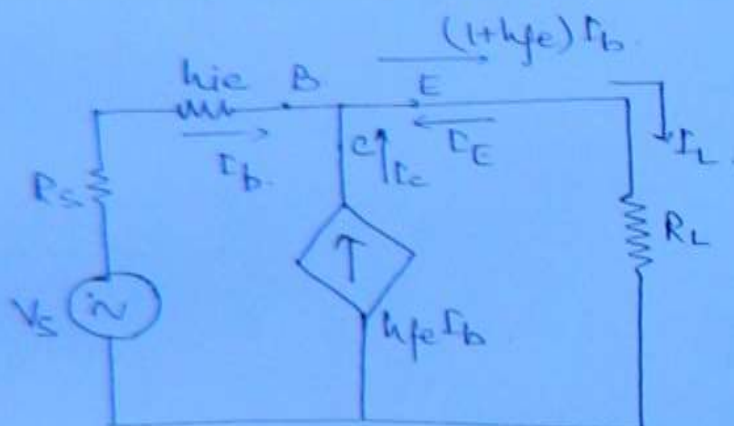

$$A_I = \frac{I_L}{I_b} = \frac{(1+h_{fe}) I_b}{I_b} = 1+h_{fe}$$

$$R_i = \frac{V_i}{I_b} = \frac{h_{ie} I_b + (1+h_{fe}) I_b R_L}{I_b}$$


$$= h_{ie} + (1+h_{fe}) R_L$$

$$A_v = \frac{(1+h_{fe}) R_L}{h_{ie} + (1+h_{fe}) R_L}$$


$$R_o = \frac{1}{\frac{h_{oc}}{h_{fe}} - \frac{h_{rc} h_{fe}}{h_{ic} + R_s}} \Rightarrow ?$$

$$= \frac{h_{ie} + R_s}{1+h_{fe}}$$

CB →

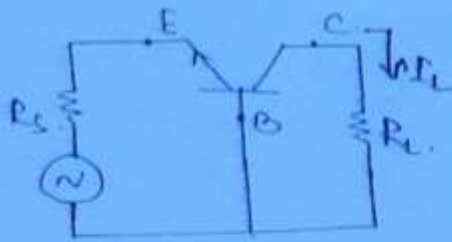

(159)

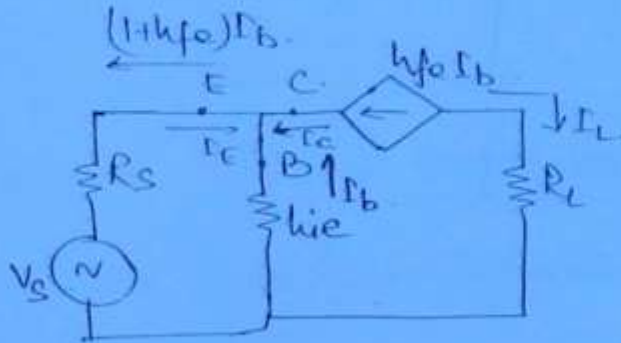

$$A_I = \frac{I_L}{I_E} = \frac{-h_{fe} I_B}{(1+h_{fe}) I_B}$$

$$= \frac{h_{fe}}{1+h_{fe}}$$

$$R_i = \frac{V_1}{I_E} = \frac{-h_{ie} I_B}{-(1+h_{fe}) I_B}$$


$$= \frac{h_{ie}}{1+h_{fe}}$$

$$A_v = \frac{h_{fe} R_L}{h_{ie}} \quad [\text{no minus sign because of same phase signal}]$$


$$R_o = \frac{V_2}{I_C} \Rightarrow \infty$$

High freq. analysis of BJT :-

(160)

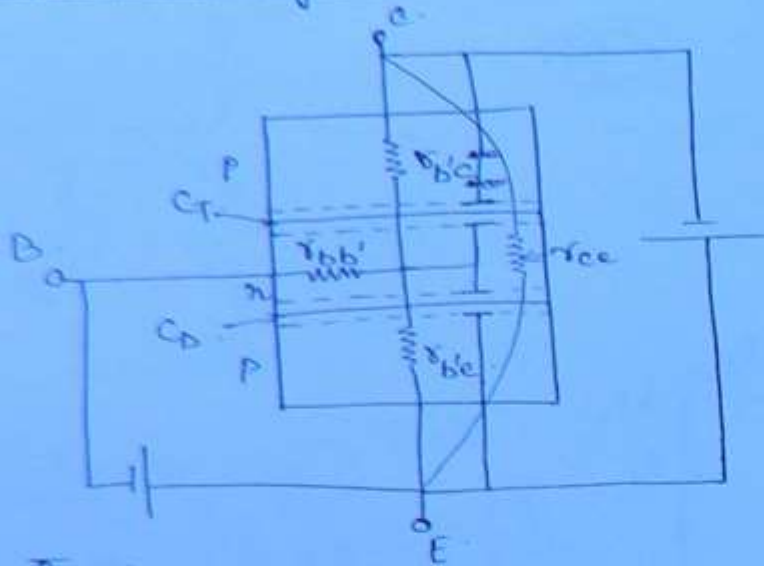


Hybrid $\pi \rightarrow$

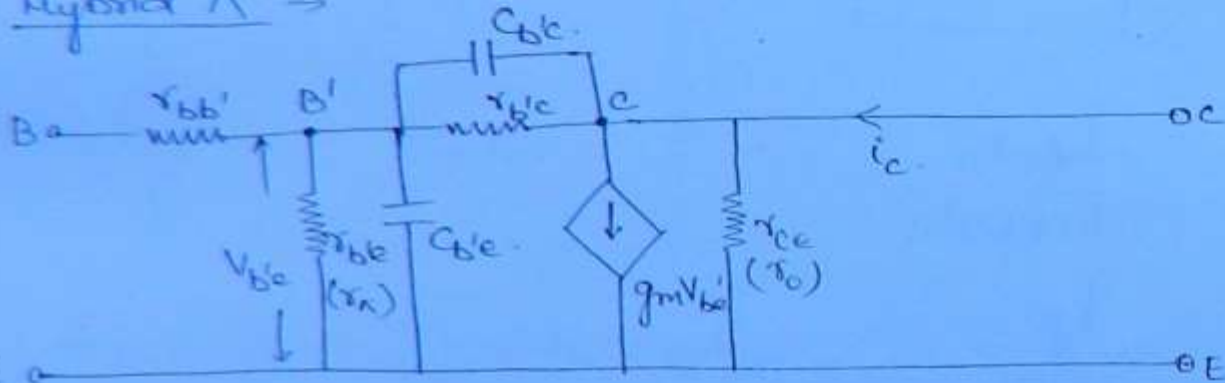

$$g_m V_{be} = \frac{i_c}{V_{be}} \times V_{be}$$

$$= i_c$$

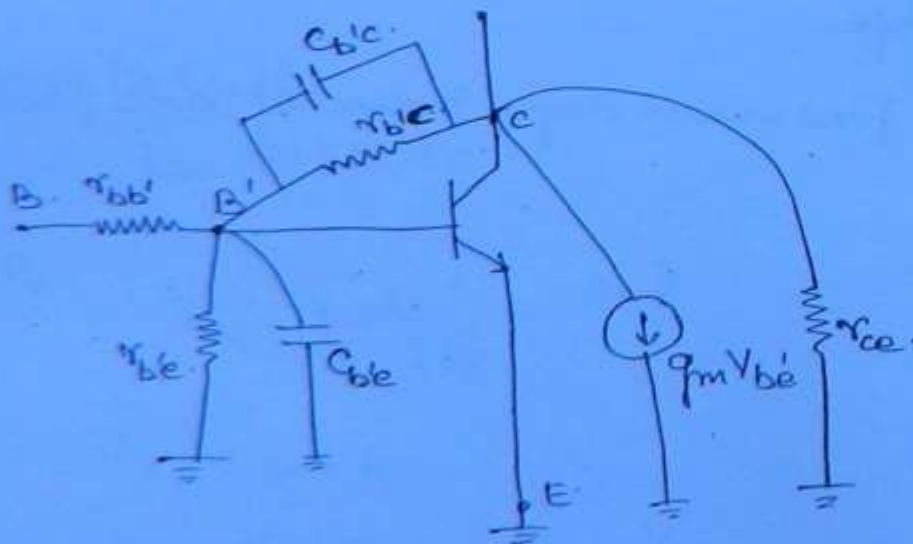

$g_m \rightarrow$ Transconductance = 50 mA/V

$r_{b'e} \rightarrow$ Input resistance = $1 \text{ k}\Omega$

(161)

$r_{b'c} \rightarrow$ feedback resistance = $4 \text{ M}\Omega$

$r_{bb'} \rightarrow$ base spread resistance = 100Ω

$r_{ce} \rightarrow$ O/P resistance = $80 \text{ k}\Omega$

$C_{b'e} \rightarrow$ Diffusion Capacitance = 100 pF

$C_{b'c} \rightarrow$ Transition Capacitance = 3 pF

Conclusion: \rightarrow


Hybrid π parameters are depending on 3 parameters

1) Collector current I_C

2) temp. T

3) Collector to Emitter Voltage V_{CE} .

Transconductance g_m : \rightarrow

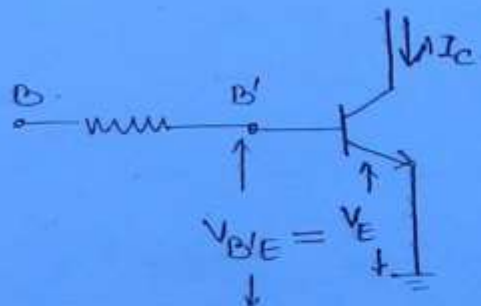

$$g_m = \frac{\partial I_C}{\partial V_{B'E}}$$

$$I_C = \alpha I_E$$

$$\partial I_C = \alpha \partial I_E$$

$$g_m = \alpha \frac{\partial I_E}{\partial V_{B'E}}$$

$$V_{B'E} = V_E$$

$$g = \frac{I + I_0}{\eta V_T}$$

A.B.

$$g = \frac{I}{\eta V_T}$$

$$g = \frac{\partial I_C}{\partial V_E} = \frac{I_E}{\eta V_T}$$

$$= \frac{\alpha I_E}{\eta V_T}$$

$$= \left| \frac{I_C}{V_T} \right| \quad \eta = 1 \quad I_C \rightarrow \text{dc current}$$

$$I_C \uparrow, g_m \uparrow$$

$$T \uparrow, g_m \downarrow$$

$$V_{CE} \uparrow, g_m \text{ const}$$

Common emitter

1) As collector current I_c increases, transconductance g_m also increases.

2) As temp increases, transconductance $g_m \downarrow$. $\boxed{g_m = \frac{I_c}{T} \times 11600}$


3)

$r_{b'e} \rightarrow$

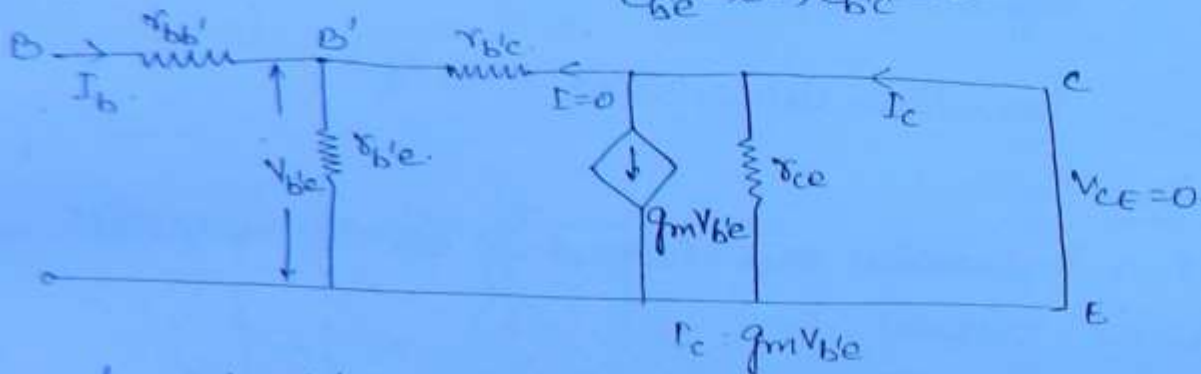
(162)

High freq. model to low freq.

$C_{b'e} \rightarrow \infty, C_{b'c} \rightarrow \infty$



low freq. model :-

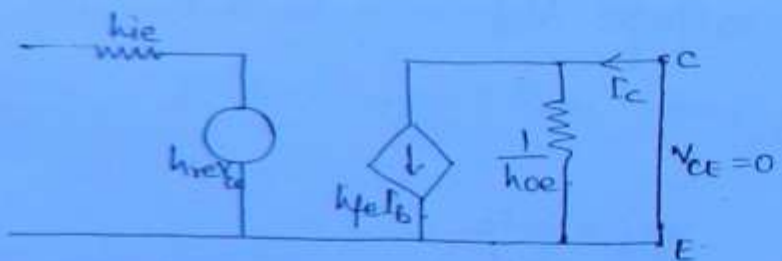

$$I_c = h_{fe} I_b$$

$$\boxed{\frac{I_c}{I_b} = h_{fe}}$$

High to low

$$I_c = g_m V_{b'e}$$

$$I_c = g_m I_b r_{b'e}$$

$$\frac{I_c}{I_b} = g_m r_{b'e}$$

$$h_{fe} = g_m r_{b'e}$$

$$\boxed{r_{b'e} = \frac{h_{fe}}{g_m}}$$

$$\boxed{V_{b'e} = I_b r_{b'e}}$$

Conclusion

- As I_C increases, $r_{b'e}$ value decreases
- As temp increases, $r_{b'e}$ value increases.

$r_{b'e}$ →

O/P parameter

$$I_B = 0$$


low freq model →

$$V_i = h_{ie} I_B + h_{re} V_{ce}$$

$$I_B = 0,$$

$$V_i = h_{re} V_{ce}$$

high freq model

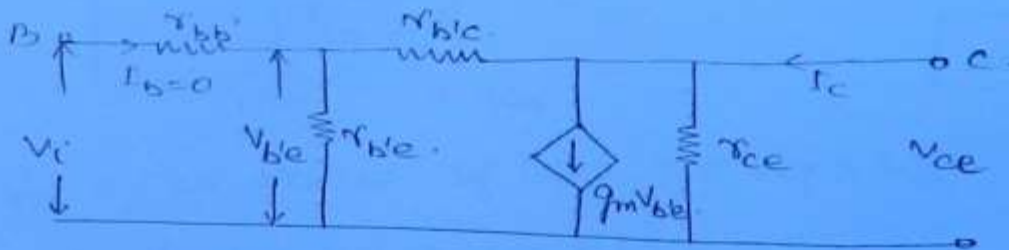

$$V_{b'e} = \frac{V_{ce} \times r_{b'e}}{r_{b'e} + r_{b'c}}$$

$$V_{b'e} = V_i = h_{re} V_{ce}$$

$$h_{re} V_{ce} = V_{ce} \frac{r_{b'e}}{r_{b'e} + r_{b'c}}$$

As $r_{b'e}$ is very small.

$$\Rightarrow h_{re} = \frac{r_{b'e}}{r_{b'c}}$$

$$\Rightarrow r_{b'c} = \frac{r_{b'e}}{h_{re}}$$


conclusions : —

- 1) As I_C current ↑, $r_{b'e}$ decrease.
- 2) As temp increases, $r_{b'e}$ increases.

'bb'

I/P parameter

$$V_{CE} = 0$$

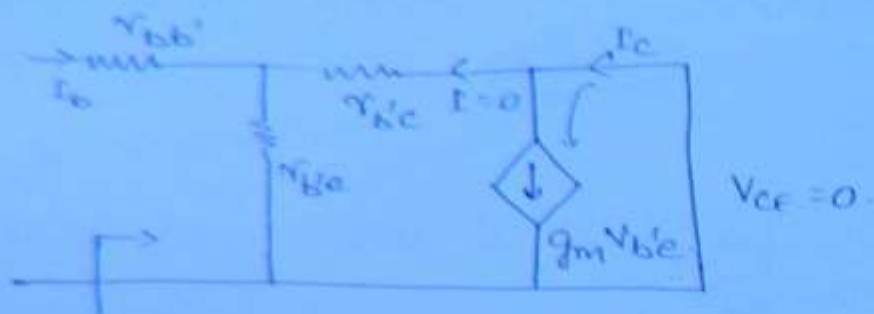

(164)

$$Z_i = r_{bb'} + r_{be}$$

low freq. model \rightarrow

$$Z_i = h_{ie}$$


$$h_{ie} = r_{bb'} + r_{be}$$

$$\Rightarrow \boxed{r_{bb'} = h_{ie} - r_{be}}$$

r_{ce} \rightarrow

O/P parameter

$$I_b = 0$$

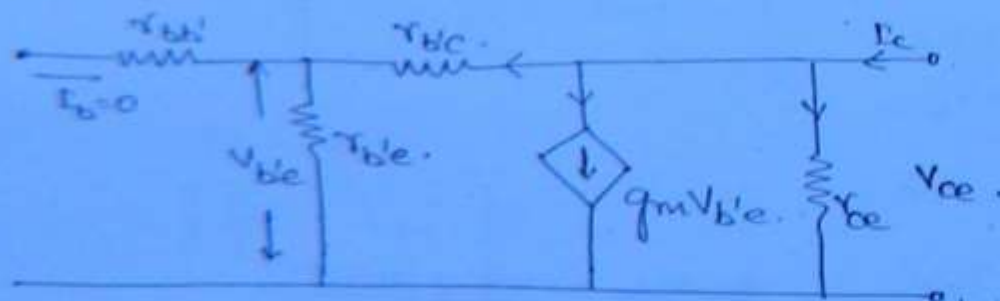

low freq \rightarrow

$$h_{oe} = \frac{I_c}{V_{ce}}$$

$$I_c = \frac{V_{ce}}{r_{ce}} + g_m V_{be} + \frac{V_{ce}}{r_{b'e} + r_{b'e}}$$

$$\approx \frac{V_{ce}}{r_{ce}} + g_m V_{ce} \frac{r_{b'e}}{r_{b'e} + r_{b'e}} + \frac{V_{ce}}{r_{b'e} + r_{b'e}}$$

$$h_{oe} = \frac{I_c}{V_{ce}} = \frac{1}{r_{ce}} + \frac{h_{fe} + 1}{r_{b'e} + r_{b'c}}$$


$$h_{oe} = g_{ce} + h_{fe} g_{b'c}$$

(165)

$$\therefore \boxed{g_{ce} = h_{oe} - h_{fe} g_{b'c}}$$

$$\boxed{r_{ce} = \frac{1}{g_{ce}}}$$

$C_{b'e} \rightarrow$

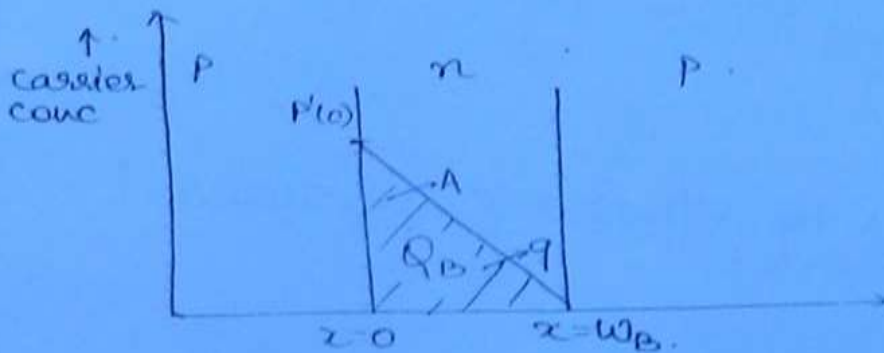

$$\begin{aligned} Q_B &= \text{av. value of conc.} \times A \times q \times w_B \\ &= \frac{1}{2} P'(0) \times A \times q \times w_B \end{aligned}$$

$$\begin{aligned} I &= -AqD_B \frac{dP(x)}{dx} \\ &= \frac{-AqD_B \{P'(0) - 0\}}{0 - w_B} \end{aligned}$$

$$I = AqD_B \frac{P'(0)}{w_B}$$

$$Q_B = \frac{1}{2D_B} I w_B^2$$

$$C_{b'e} = \frac{dQ_B}{dV} = \frac{1}{2D_B} w_B^2 \left(\frac{dI}{dV} \right) \leftarrow g_m$$

$$\boxed{C_{b'e} = \frac{1}{2D_B} w_B^2 g_m} \quad \boxed{C_{b'e} = \frac{1}{2D_B} w_B^2 \frac{1}{r_e}}$$

$$\boxed{r_e = \frac{1}{g_m} = \frac{V_T}{I_E}}$$

C_{bc} \rightarrow

transition capacitance.

$$C_T \propto \frac{1}{\sqrt{V_R}} \rightarrow \text{Alloy type.}$$

$$C_T \propto \frac{1}{\sqrt[3]{V_R}} \rightarrow \text{Grown jz.}$$

$$V_R \rightarrow V_{CE}$$

$$C_{bc} \propto \frac{1}{(V_{CE})^n}$$

$$n = \frac{1}{2} \rightarrow \text{Alloy}$$

$$= \frac{1}{3} \rightarrow \text{grown jz.}$$

(166)

Q1. As $V_{CE} \uparrow$, what happens to diffusion capacitance?

Ans. early effect


$$V_{CE} \uparrow; W_B \downarrow; C_{bc} \downarrow$$

$$C_{bc} = \frac{1}{2D_B} W_B^2 q n$$

am all the hybrid π parameter which parameter is dependent of V_C and temp?

C_{bc} .

Short ckt current gain \rightarrow

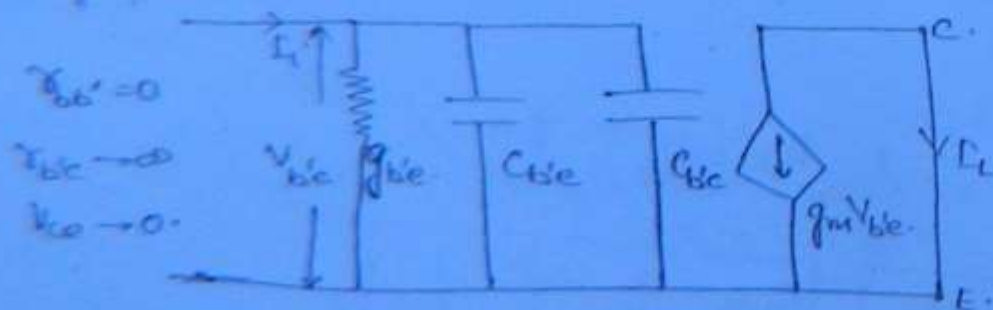

$$\begin{aligned}
 A_v &= \frac{+L}{r_i} \\
 &= \frac{-g_m V_{b'e}}{V_{b'e} (g_{b'e} + j\omega(C_{b'e} + C_{b'c}))} \\
 &= \frac{-g_m}{\frac{g_m}{h_{fe}} + j2\pi f} \\
 &= \frac{-g_m}{\frac{g_m}{h_{fe}} + j2\pi f \frac{g_m}{2\pi f_T}} \\
 &= \frac{-g_m}{\frac{g_m}{h_{fe}} \left[1 + j \frac{f}{f_T/h_{fe}} \right]}
 \end{aligned}$$


(167)

$$\begin{aligned}
 f_T &= \frac{1}{2\pi RC} \quad \frac{1}{R} = g_m \\
 &= \frac{g_m}{2\pi C_{be}}
 \end{aligned}$$

$$f_T = \frac{f_T}{h_{fe}}$$

$$A_v = \frac{-h_{fe}}{1 + j(f/f_T)}$$

freq. Response : →

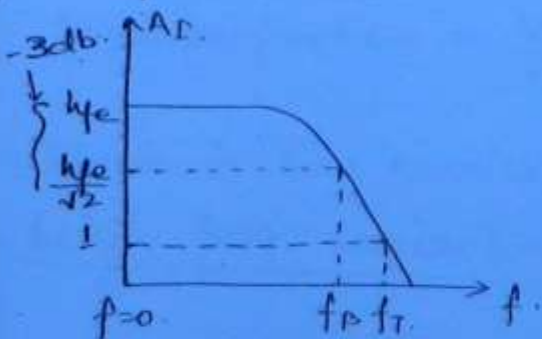

$$A_v = \frac{-h_{fe}}{1 + j(f/f_T)}$$

$$|A_v| = \frac{h_{fe}}{\sqrt{1 + (f/f_T)^2}}$$

Beta cut off freq : —
 $f_\beta \rightarrow$

It is the freq. at which C.E. short ckt current gain reduces by 3dB of its value

Unity gain band width freq (f_T) : —

It is the freq. at which CE short ckt current gain reduces to unity

f_x

$$f_T = h_{fe} f_\beta$$

(168)

α cut off freq: \rightarrow

It is the freq. at which CB short CKT 's gain reduces by 3dB of its value.

$$f_x = (1 + \beta) f_\beta$$



$$= \frac{1}{1 - \alpha} f_\beta$$

CB is used for high freq. than CE.
as bandwidth is higher.

Frequency response of an amplifier: \rightarrow

BJT

CE amplifier \rightarrow

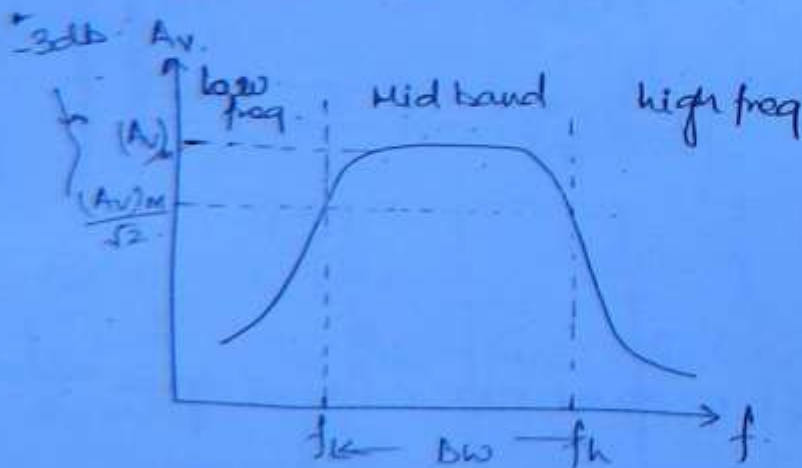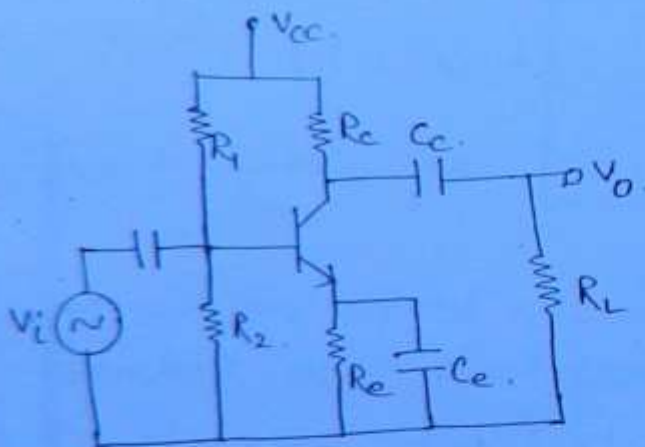

Capacitance \rightarrow

Internal Capacitance

- $\rightarrow C_D$ (Diffusion Capacitance)
- $\rightarrow C_T$ (Transition Capacitance)


(769)

external Capacitance

- $\rightarrow C_c$ (coupling)
- $\rightarrow C_e$ (by pass)

Low freq region \rightarrow

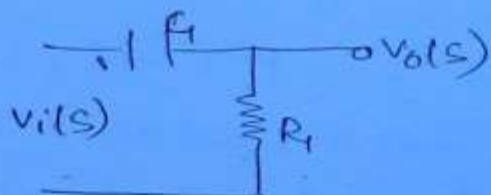
- At low freq. Analysis, internal capacitors are neglected which are parallel to the $j\omega$ of transistors [open]
- If ext. capacitors are open, the signal will not pass into the transistors that means C_c and C_e are affecting sys. response.
- The System response is considered as high pass response.



$$\text{transfer function} = \frac{V_o(s)}{V_i(s)} = \frac{s}{s + \frac{1}{R_1 C_1}}$$

There is one zero and one pole is considered.


High freq. region: \rightarrow

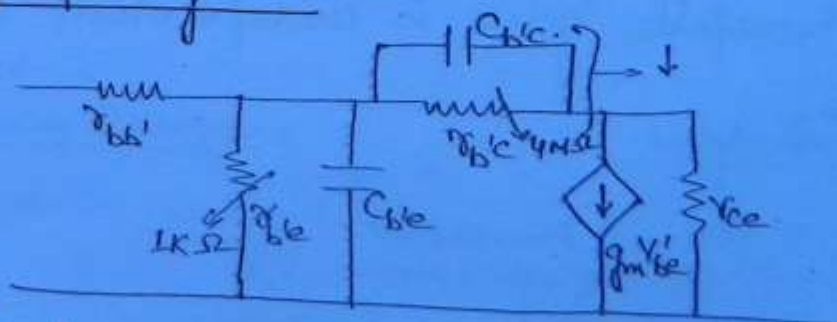

- At high freq. range, ext. capacitors are not affecting the system response because they are short ckt.
- When the int. capacitors are short ckt, it will affect

The $\frac{1}{s}$ unit $\frac{1}{s}$ is $\frac{1}{s}$ means. That means int. Capacitors are affecting the sys. response.

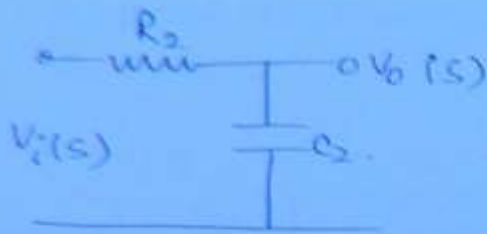
If The system response is considered as low pass response



(170)

$$T.F. = \frac{V_o(s)}{V_i(s)} = \frac{1}{s + \frac{1}{R_2 C_2}}$$

Mid band Range : \rightarrow

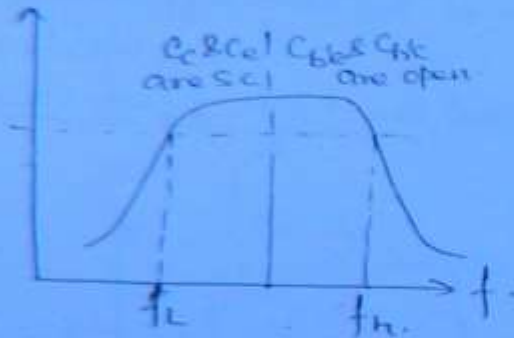


At low frequencies, mid band Range freq. is considered as high freq, therefore ext. capacitors are neglected. At high freq. range mid band range freq. are considered as low freq. Therefore int. capacitors are neglected. At the mid band range, all the internal and ext. capacitors are neglected. Therefore gain is independent of freq.

-3dB concept : \rightarrow

Bode plot \rightarrow
magnitude plot.




Phase Plot

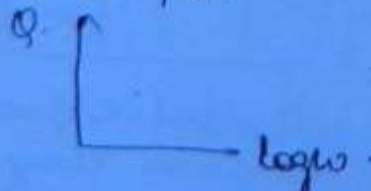

$$T.F. = \frac{Ks}{1+sT}$$


$$G(s) = K$$

$$|G(j\omega)|_{db} = 20 \log K$$

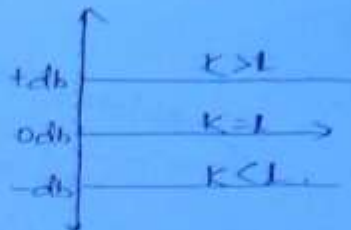

$$\Rightarrow G(s) = s$$

$$|G(j\omega)|_{db} = 20 \log \omega$$

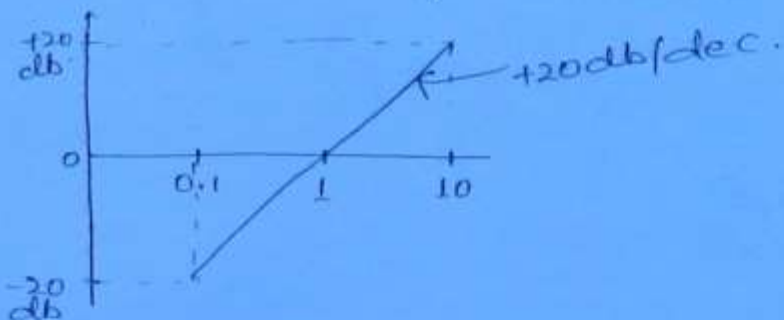

$$\Rightarrow G(s) = \frac{1}{1+sT}$$


$$|G(j\omega)|_{db} = -20 \log \sqrt{1+\omega^2 T^2}$$

$\omega T \ll 1$, low freq.

$$|G(j\omega)| = -20 \log 1 = 0db$$

$\omega T \gg 1$, high freq.

$$|G(j\omega)| = -20 \log \omega T$$

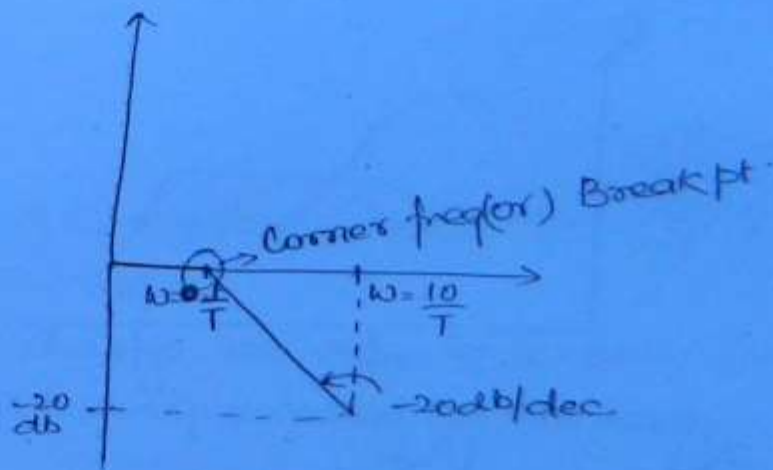

Bode plot →

Low freq Range →

$$T.F. = \frac{s}{s + \frac{1}{R_1 C_1}} \rightarrow \text{one } 0$$


one pole

one pole

High freq. Range! —

$$T.F. = \frac{1}{s + \frac{1}{R_2 C_2}} \rightarrow \text{one pole}$$

one pole

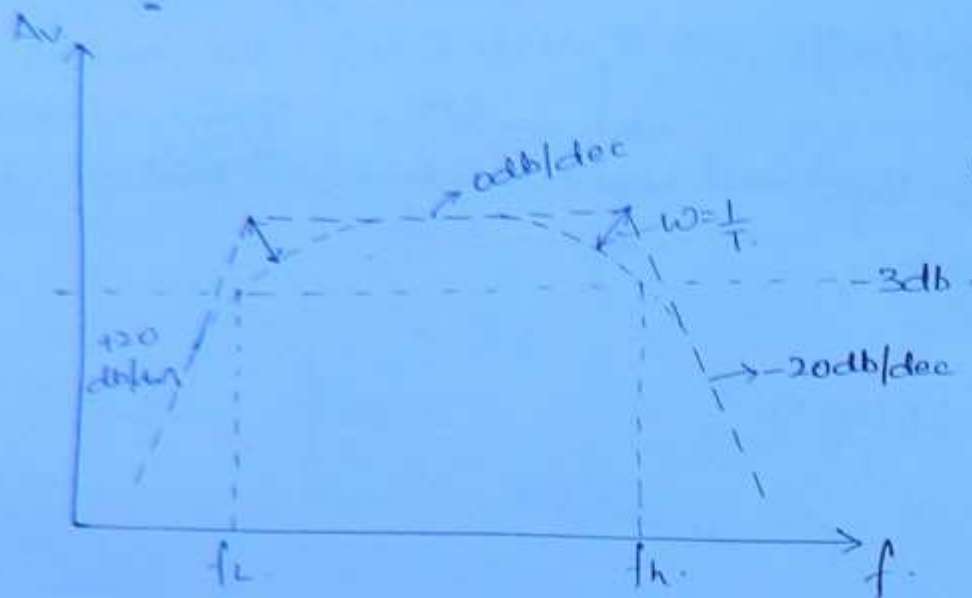


$$|A(j\omega)|_{dB} = -20 \log \sqrt{1 + \omega^2 T^2}$$

$$\omega = \frac{1}{T}$$

$$= -20 \log \sqrt{1+1}$$

$$= -20 \log \sqrt{2}$$

$$= -3 \text{ dB}$$

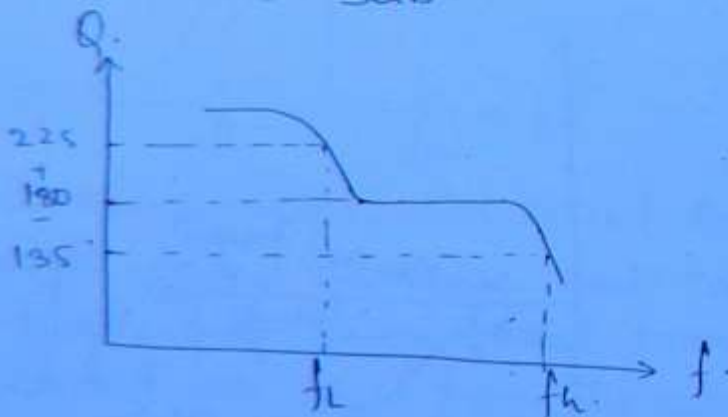

$$(A_v)_L = \frac{(A_v)_m}{1 - j \left(\frac{f_L}{f} \right)}$$


$$(A_v)_H = \frac{(A_v)_m}{1 + j \left(\frac{f}{f_H} \right)}$$

$$\theta_L = \tan^{-1} \left(\frac{f_L}{f} \right)$$

$$\theta_H = \tan^{-1} \left(\frac{f}{f_H} \right)$$


conclusion →

Concept of amplifier frequency.

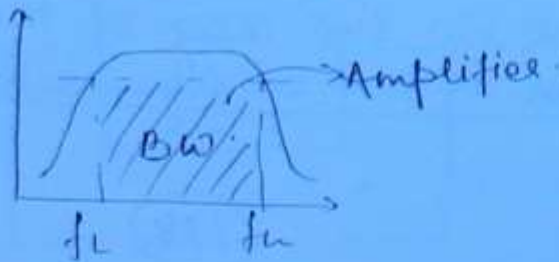

123

Amplifier \rightarrow

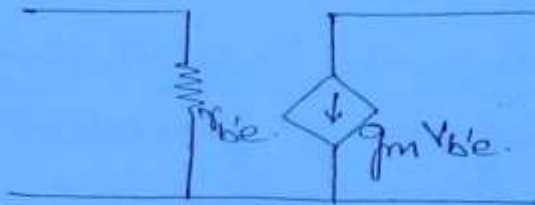

$$C_{b'e} \rightarrow \infty$$

$$C_{b'c} \rightarrow \infty$$

$$r_{bb'} \rightarrow 0$$

$$r_{b'c} \rightarrow \infty$$

$$r_{ce} \rightarrow \infty$$

Ch-2.

Ch-2

Ques. Q-4. 160 (d).

Ag-34.

Q10. b.

12/1/12.

Feedback Amplifier:—

- \rightarrow Amplifier The basic char. of an amplifier are input imp., O/P imp., voltage gain, BW. etc.
- \rightarrow Suppose if we want to change the char. of a basic amplifier, we have to use a technique called as feedback.

Feedback \rightarrow

"When a part or a fraction of the O/P feedback to I/P, feedback is said to be exist."


It classified into two ways:—

- 1) +ve feedback
- 2) -ve feedback.

Positive feedback : \rightarrow

If the net effect of the feedback inc. the mag. of the I/P signal, it is called as positive or direct or regenerative feedback.


eg.

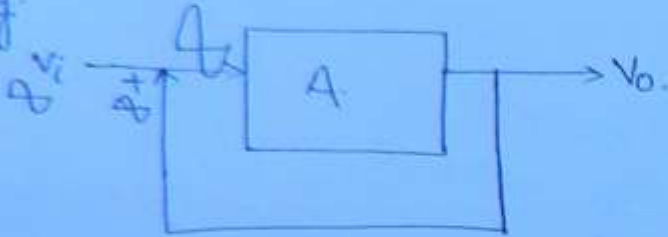

negative feedback : \rightarrow

If the net effect of the feedback decreases the mag. of the I/P signal, it is called as negative or inverse or degenerative feedback.


eg.

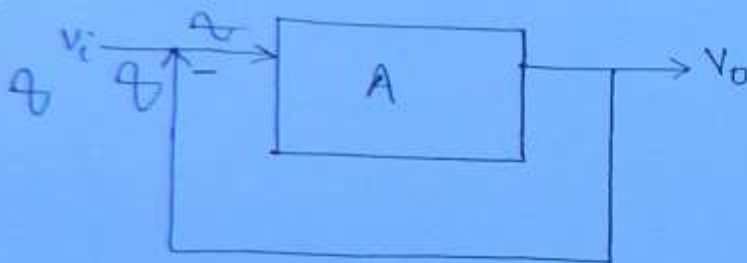

Feedback can also be classified as


- 1) voltage feedback.
- 2) current feedback.

Voltage feedback : $-$

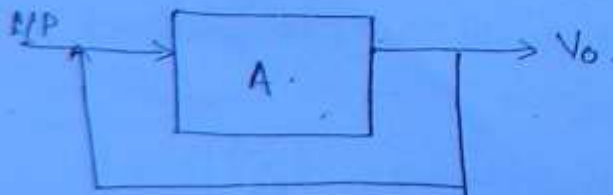

feedback signal $\propto V_o$.

current feedback \rightarrow

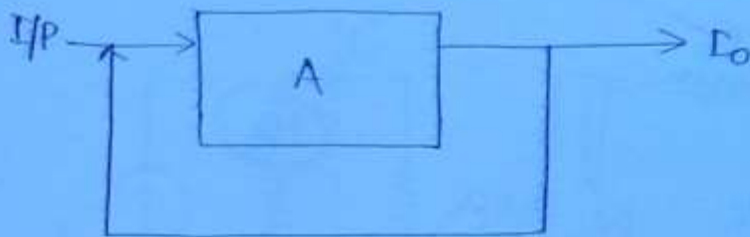

(25)

feedback signal $\propto I_O$.

Limitations of basic amplifiers \rightarrow


- 1) Instability of ac gain.
 - Due to power supply variation
 - Due to change in μ parameter
 - age of the device.
- 2) I/P impedance is low.
- 3) Output impedance is high.
- 4) Noise level is high.
- 5) Distortion is more
- 6) BW is not sufficiently large.

Types of basic amplifiers \rightarrow


based on Z_i and Z_o \rightarrow

- 1) Voltage amplifiers
- 2) Current amplifier.
- 3) Transconductance amplifiers.
- 4) Transresistance amplifiers.


Voltage amplifiers \rightarrow

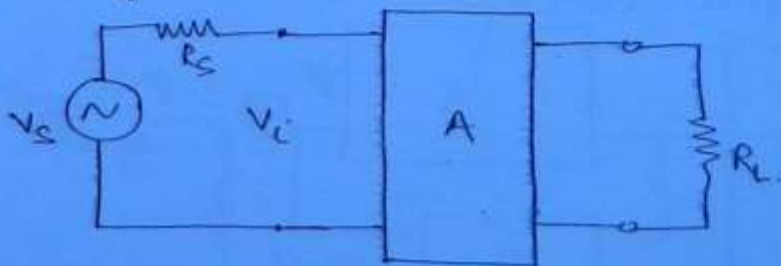

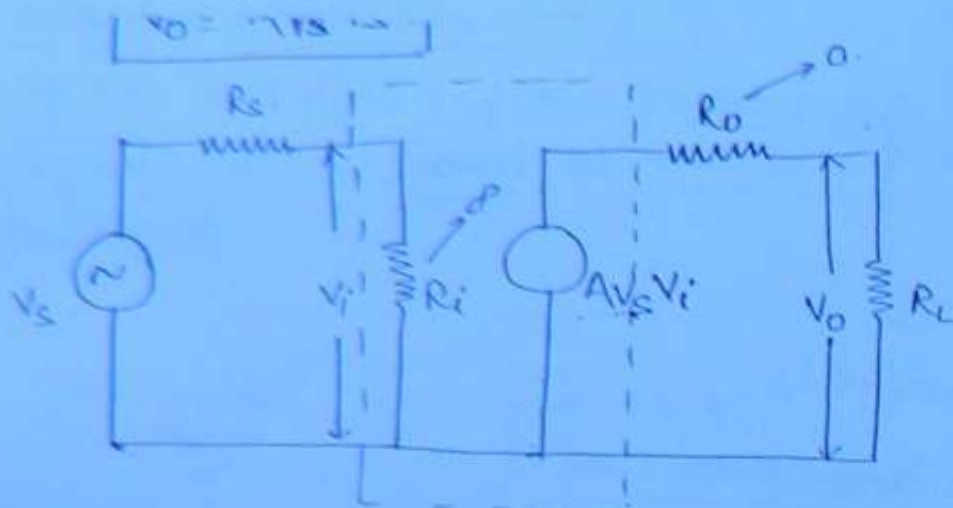Voltage gain $A_v = \frac{V_o}{V_i}$. Voltage Amplification $A_{vs} = \frac{V_o}{V_s}$




Current Amplifier →

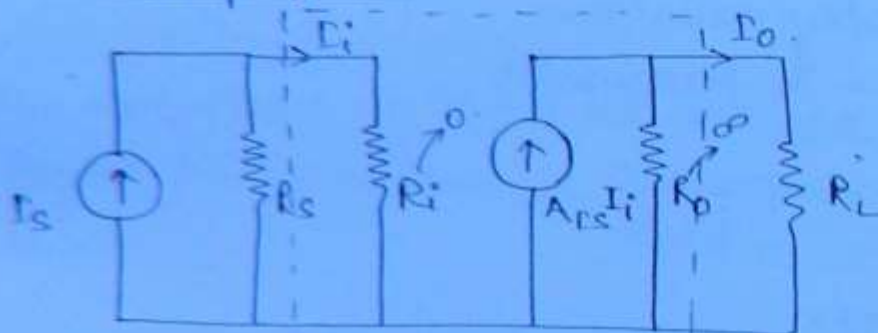

$$I_o = A_{IS} I_s$$


Transconductance Amplifier →

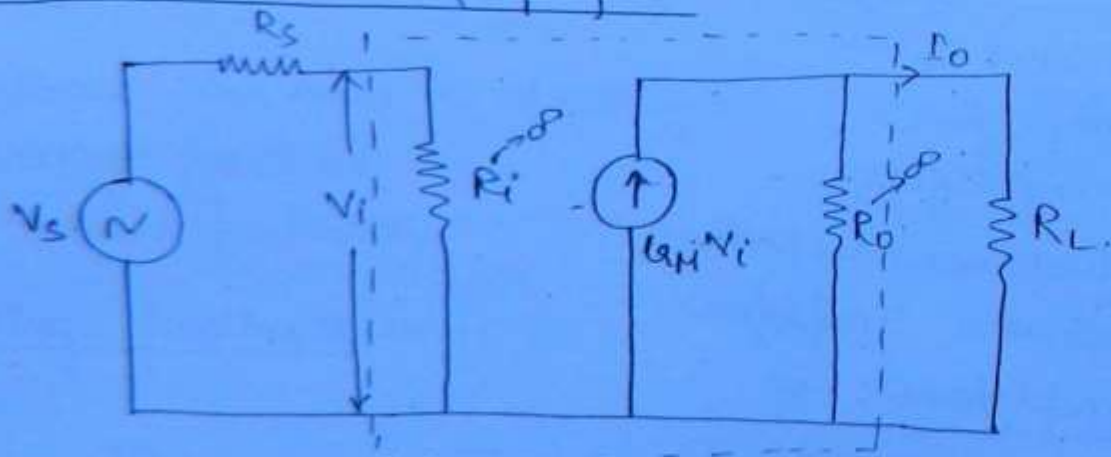

$$G_m = \frac{I_o}{V_s}$$

$$I_o = G_m V_s$$

Transresistance amplifier: —

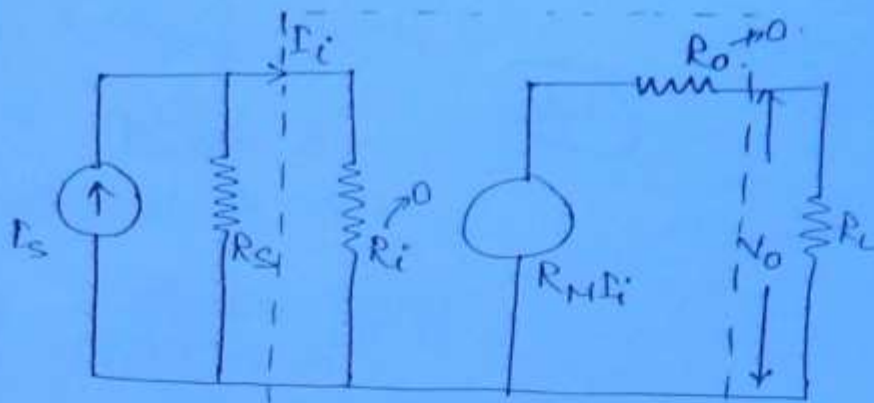


(177)

$$R_M = \frac{V_o}{I_s}$$

$$V_o = R_M I_s$$

#Q. In most of the practical applications why we choose Voltage Amplifiers Only?


Aus.

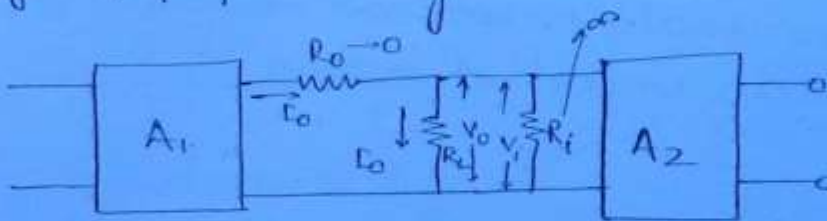

For any ideal amplifier, I/P impedance should be ∞ and O/P impedance should be 0.

Therefore voltage amplifier specification are matching with ideal amplifier specification. That is the reason, most of the practical applications, voltage amplifiers are used.

General theory of feedback: →

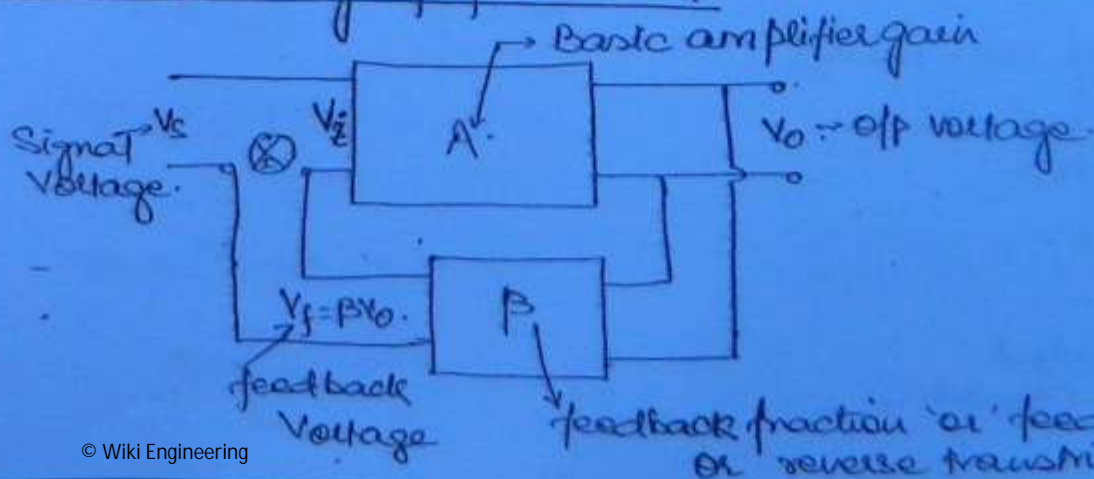

Positive FB

$$V_o = AV_i$$

$$V_i = V_s + V_f$$

$$V_o = A(V_s + \beta V_o)$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{A}{1 - A\beta}$$

Negative FB

$$V_o = AV_i$$

$$V_i = V_s - V_f$$

$$V_o = A(V_s - \beta V_o)$$

$$\frac{V_o}{V_s} = \frac{A}{1 + A\beta}$$

(178)

Conclusions →

$$> A_{pf} > A > A_{nf}$$

$$> A_{nf} = \frac{V_o}{V_s} = \frac{A}{1 + A\beta}$$

$$A_{nf} \downarrow, S \uparrow$$

Always for amplifier analysis we use negative feedback because stability is an important criteria.

$$s) A_{pf} = \frac{V_o}{V_s} = \frac{A}{1 - A\beta}$$

$$|A\beta| = 1.$$

$$A_{pf} \rightarrow \infty, S \rightarrow 0.$$

Five feedback is always be applied for unstable sys' like oscillators.

Negative FB amplifiers →

Adv →

1) Stability of ac gain.

$$A_f = \frac{A}{1 + A\beta}$$

$$A\beta \gg 1.$$

$$A_f = \frac{1}{\beta} \rightarrow \text{fixed (Resistor)}$$

resistance of an amplifier then the fractional change of gain with feedback is .

$$A_f = \frac{A}{1+AB}$$

(179)

diff. w.r.t. A.

$$\frac{\partial A_f}{\partial A} = \frac{(1+AB) - A(B)}{(1+AB)^2}$$

$$= \frac{1}{(1+AB)^2}$$

$$\Rightarrow \frac{\partial A_f}{A_f} = \frac{1}{(1+AB)^2} \frac{\partial A}{A}$$


$$\boxed{\frac{\partial A_f}{A_f} < \frac{\partial A}{A}}$$

$\frac{\partial A}{A} \rightarrow$ w/o Feedback fractional change of gain.
 $\frac{\partial A_f}{A_f} \rightarrow$ with Feedback fractional change of gain

$$\Rightarrow \frac{1}{1+AB} \rightarrow \text{Sensitivity}$$

$$\Rightarrow 1+AB \rightarrow \text{Desensitivity}$$

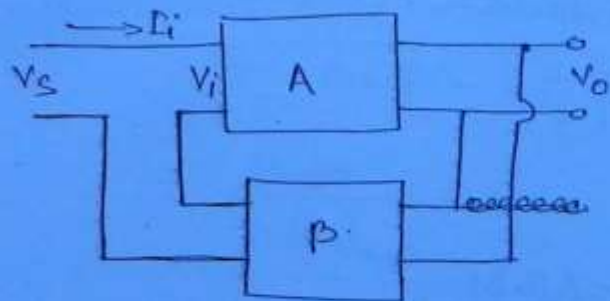Increase in I/P impedance \rightarrow
(Z_i)



$$Z_f = \frac{V_s}{I_i}$$

$$Z_i = \frac{V_i}{I_i}$$

$$V_i = V_s - BV_o$$


$$= V_s - BAV_i$$

$$(1+AB) \frac{V_i}{I_i} = \frac{V_s}{I_i}$$

$$\boxed{(1+AB)Z_i = Z_f}$$

3) Voltage in negative feedback:


(180)

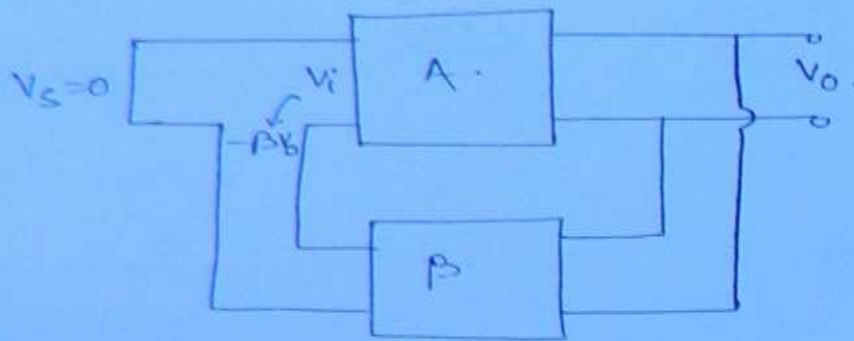

$V_s =$

$$V_i = V_s - \beta V_o, \quad V_s = 0$$

$$\boxed{V_i = -\beta V_o}$$

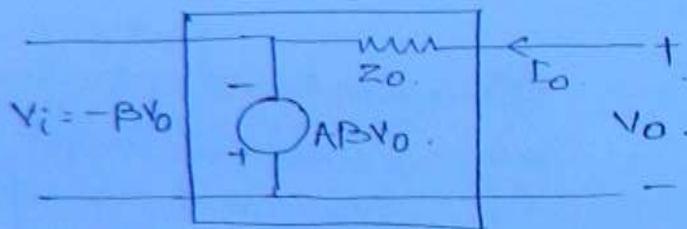



$$V_o + ABV_o = I_o Z_o$$

$$V_o (1 + AB) = I_o Z_o$$

$$\boxed{\frac{V_o}{I_o} = Z_{of} = \frac{Z_o}{1 + AB}}$$

Reduction in distortion and noise: \Rightarrow

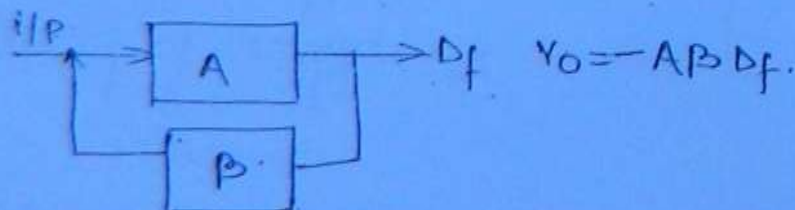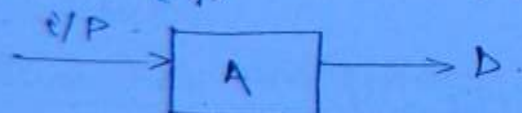Net distortion = Original distortion + distorted O/P.



$$D_f = D - AB D_f$$

$$D_f (1 + AB) = D$$


$$\boxed{D_f = \frac{D}{1 + AB}}$$

Similarly,

$$N_f = \frac{N}{1+AB}$$

(18)

Increase in Bandwidth: →

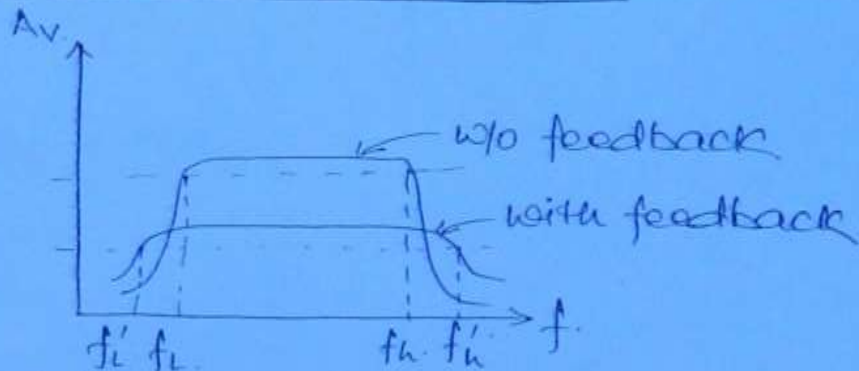

cut off lower freq →

$$(A_v)_e = \frac{(A_v)_m}{1 - j(f_L/f)}$$

$$= \frac{(A_v)_e}{1 + (A_v)_e \beta}$$

$$= \frac{(A_v)_m}{1 - j(f_L/f)} \cdot \frac{1}{1 + \frac{(A_v)_m \cdot \beta}{1 - j(f_L/f)}}$$

$$(A_v)_{kf} = \frac{A_{vm}}{1 + A_{vm} \beta - j\left(\frac{f_L}{f}\right)}$$

$$= \frac{(A_v)_m}{1 + (A_v)_m \beta}$$


$$= \frac{1 - j \frac{f_L}{f}}{f(1 + (A_v)_m \beta)}$$

$$= \frac{(A_v)_{nf}}{1 - j(f'_L/f)}$$

$$f'_L = \frac{f_L}{1 + (A_v)_m \beta} \quad \Rightarrow \quad f'_H = f_H(1 + (A_v)_m \beta)$$

Topology : →

(182)


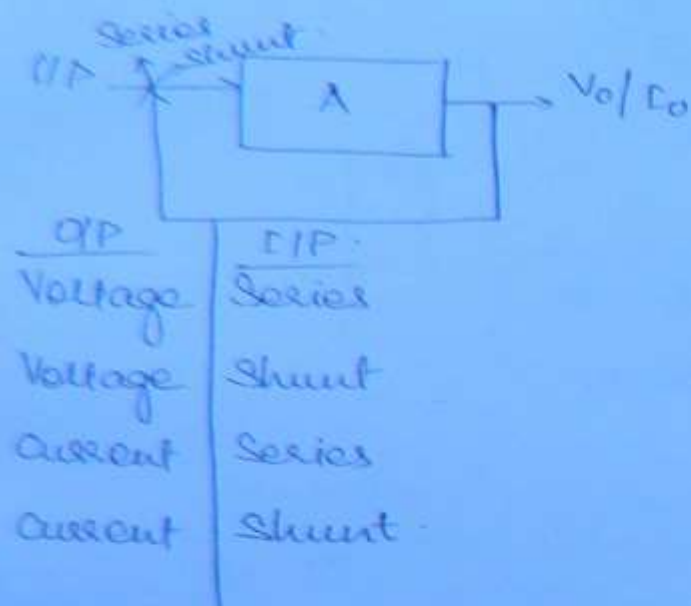


Topology →



- Block diagram Analysis.
- Practical ckt Analysis.

Block diagram Analysis : →


i/P.

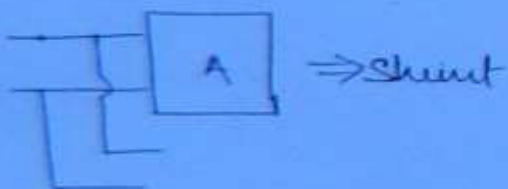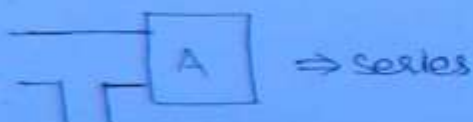

O/P Side.

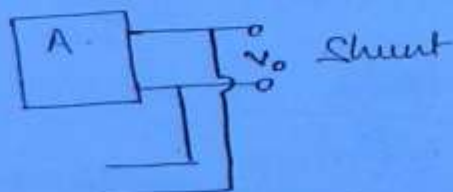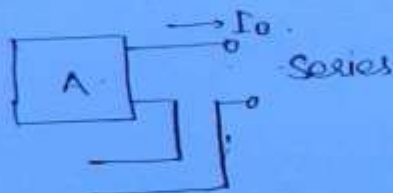


Voltage Series →

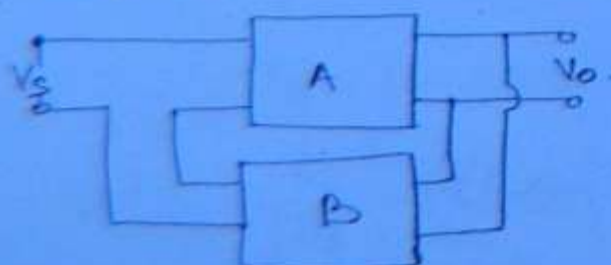


→ Voltage amplifier.

Voltage source


(183)

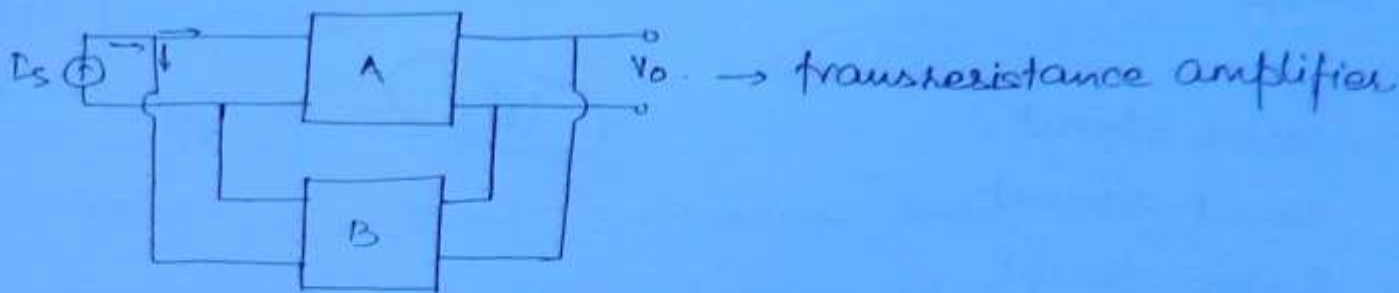

Current Series

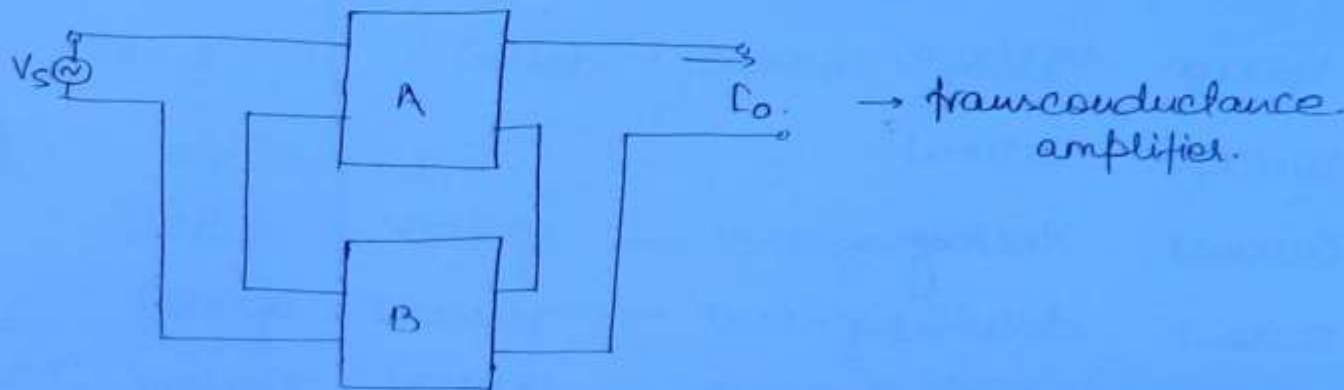

Current Shunt

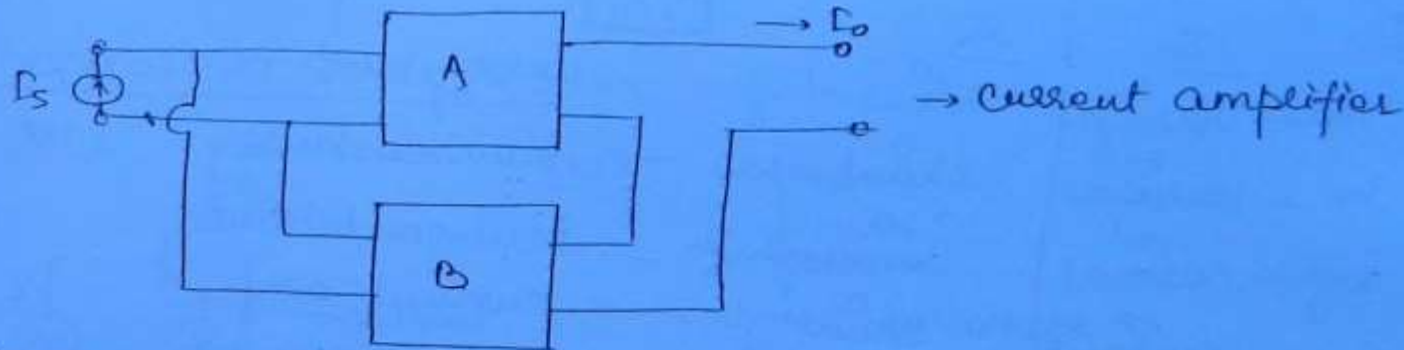

1) In Voltage Series _____ amplifier is used.

2) In Voltage Shunt _____ amplifier is used.

3) In Current Series _____ amplifier is used.

4) In Current Shunt _____ amplifier is used.


II 1) In S/P is series connection Voltage source is taken

2) In S/P is Shunt connection Current source is taken

III 1) $V_C V_S$
 $V_C I_S$

Topology : \rightarrow



(182)

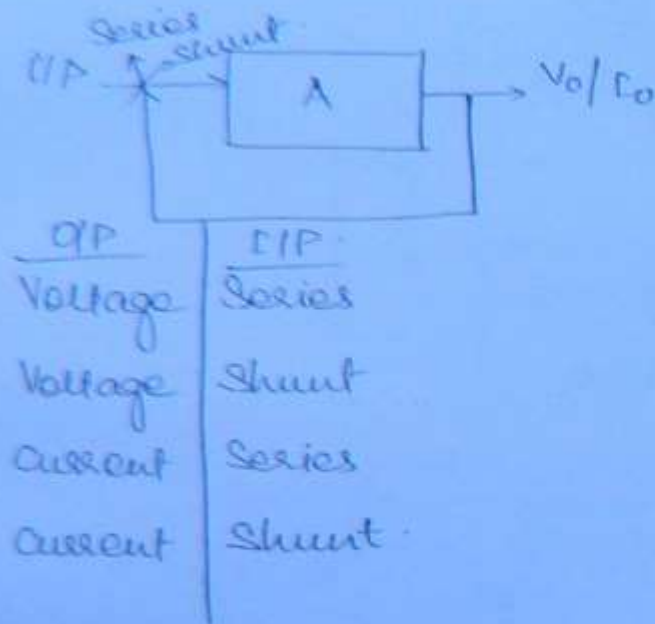


Topology \rightarrow

- \rightarrow Block diagram Analysis.
- \rightarrow Practical ckt Analysis.

Block diagram Analysis : \rightarrow

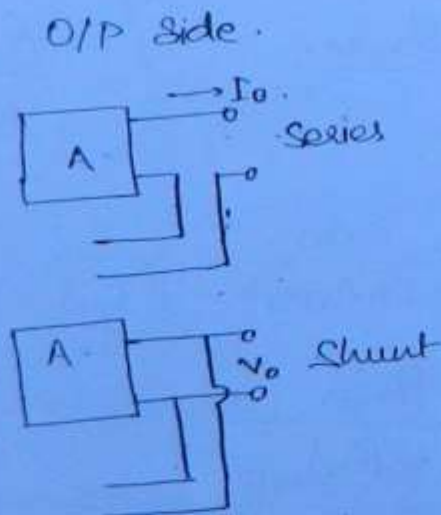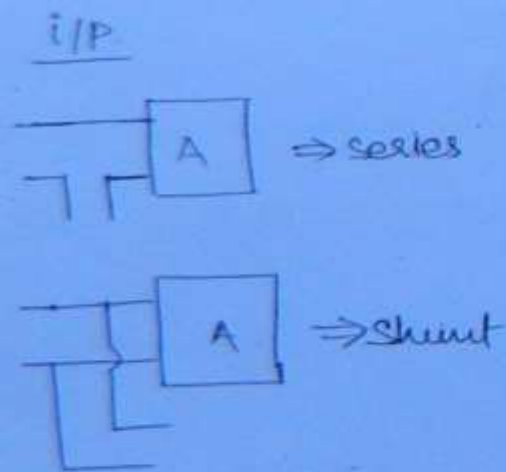


Voltage Series \rightarrow

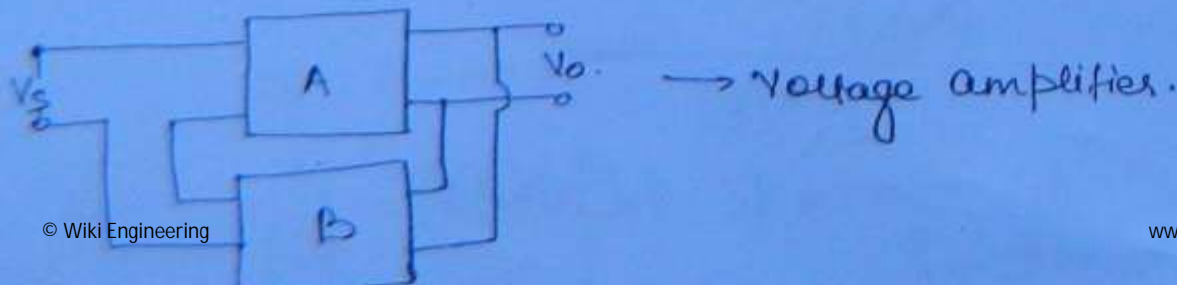


Voltage series


(183)

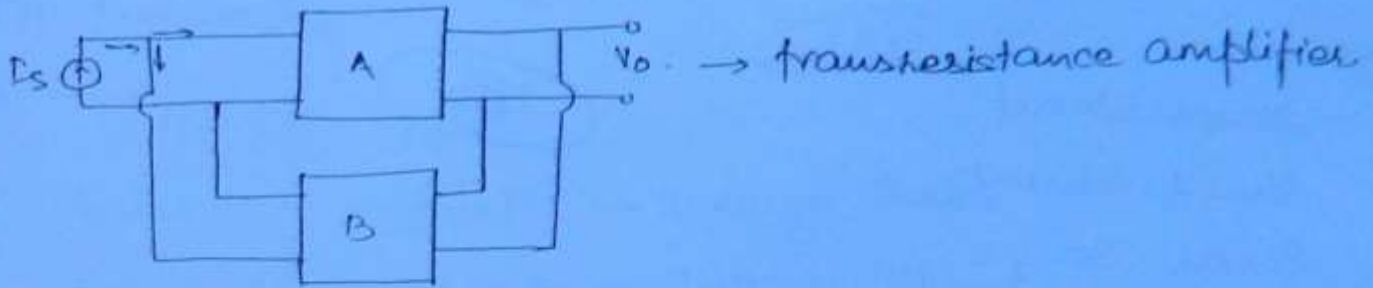

Current Series

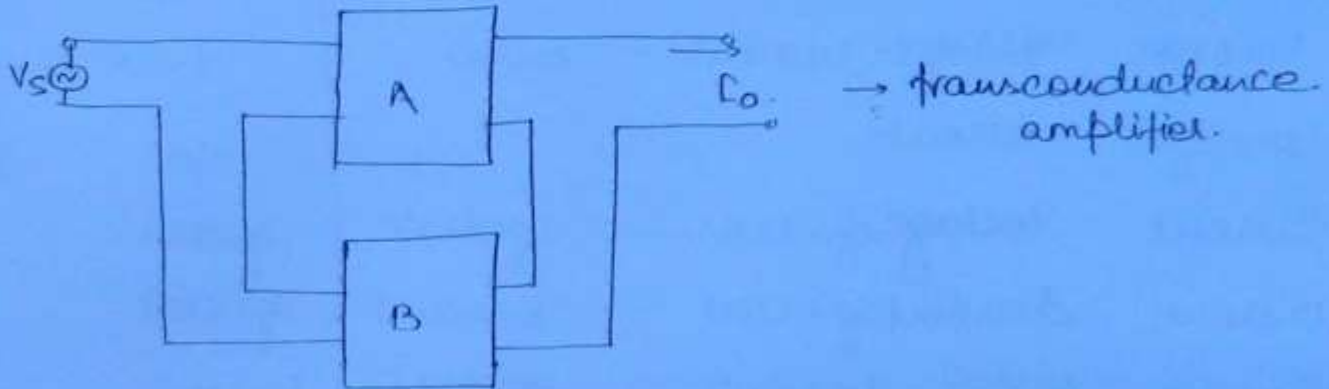

Current Shunt

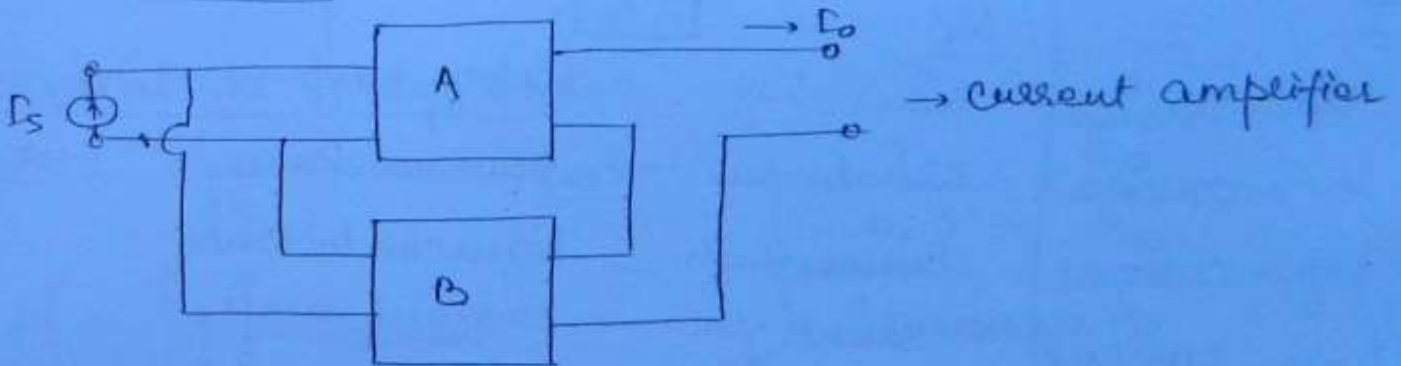

I) In Voltage Series _____ amplifier is used.

2) In Voltage Shunt _____ amplifier is used.

3) In Current Series _____ amplifier is used.

4) In Current Shunt _____ amplifier is used.

II) 1) In S/P is series connection Voltage source is taken

2) In S/P is Shunt connection Current source is taken

III) 1) $V_c V_s$
 $V_c I_s$
 $V_c V_s$

IV

Series Shunt
Shunt Shunt
Series Series
Shunt Series

184

V Voltage Voltage
Voltage current
Current Voltage
Current current.

Answers →

<u>I</u>	<u>Z_o</u>	<u>Z_i</u>	<u>$Z_i Z_o$</u>
low	Voltage	Series → high	→ voltage amp.
low	Voltage	Shunt → low	→ transresistance
high	Current	Series → high	→ transconductance
high	Current	Shunt → low	→ current amp.

opamp is a voltage control device → $V_{od} \propto V_{id}$

FET is a voltage control device → $I_d \propto V_{gs}$

BJT is a current control device → $I_c \propto I_b$

<u>III</u>	<u>IP</u>	<u>OP</u>
Series VC	VS	→ voltage series
Series VC	IS	→ current series.
Shunt IC	VS	→ voltage shunt
Shunt IC	IS	→ current shunt.

Any device containing current source is characterised by the I/P parameter.

(183)

IV


I/P	O/P
Series	Shunt \rightarrow Voltage Series
Shunt	Shunt \rightarrow Voltage Shunt
Series	Series \rightarrow Current Series
Shunt	Series \rightarrow Current Shunt

V


O/P	I/P
Voltage	Voltage \rightarrow Voltage Series
Voltage	Current \rightarrow Voltage Shunt
Current	Voltage \rightarrow Current Series
Current	Current \rightarrow Current Shunt

Practical CKT Analysis: \rightarrow


CKT 1.

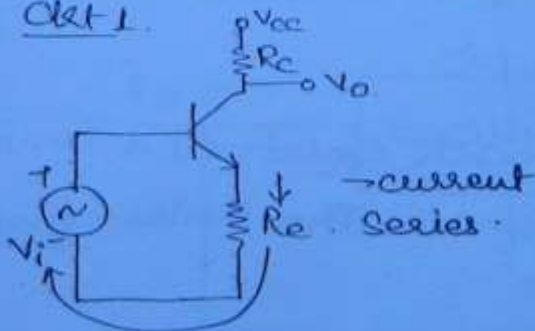


CKT 2.

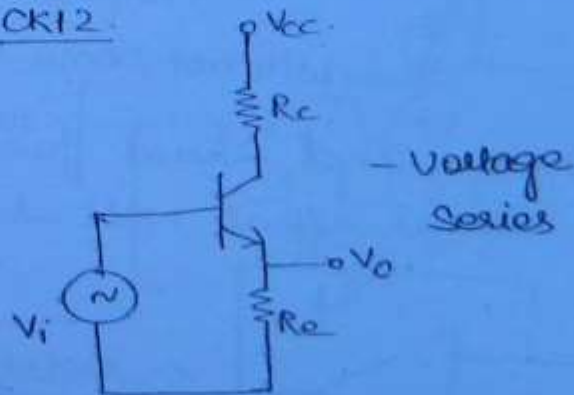


CKT 3.

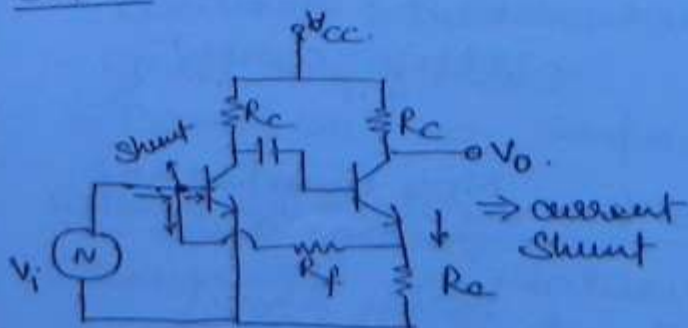


CKT 4.

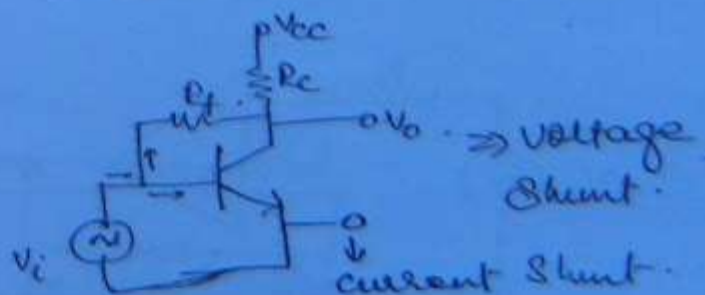


⇒

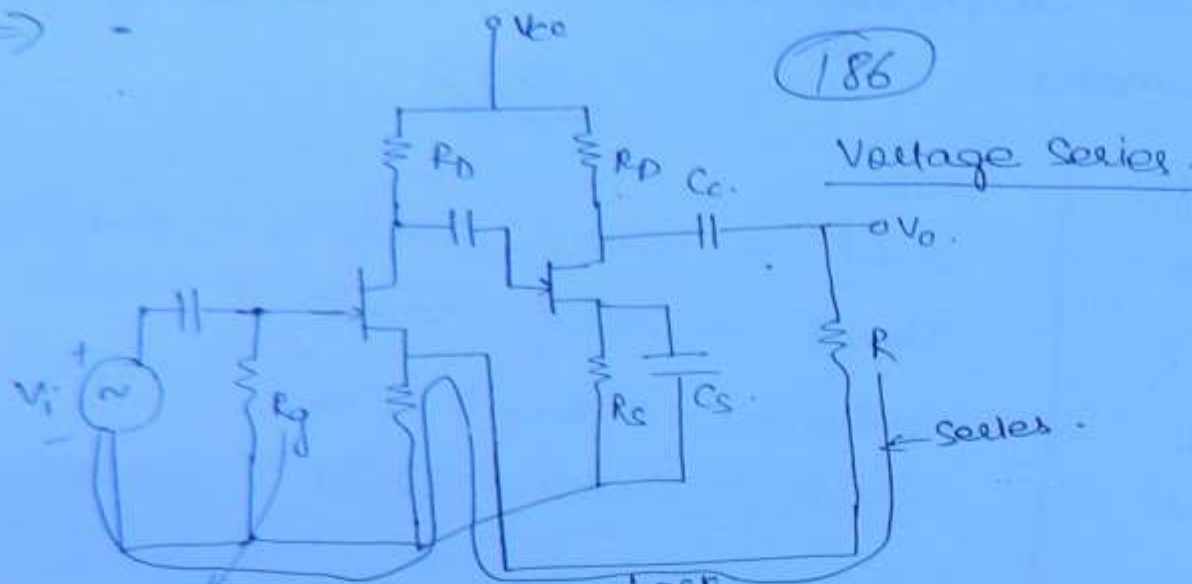

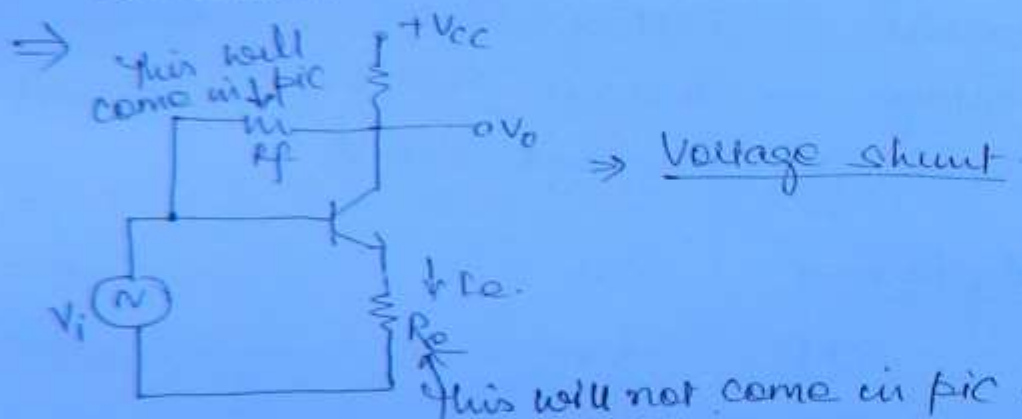
R_g → this is not feedback resistance. so, it is series connection.



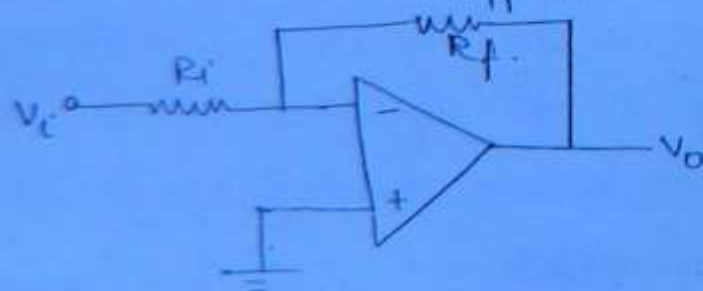Whenever Series and Shunt feedback exist at a time in the ckt, Shunt effect will dominate the Series effect.



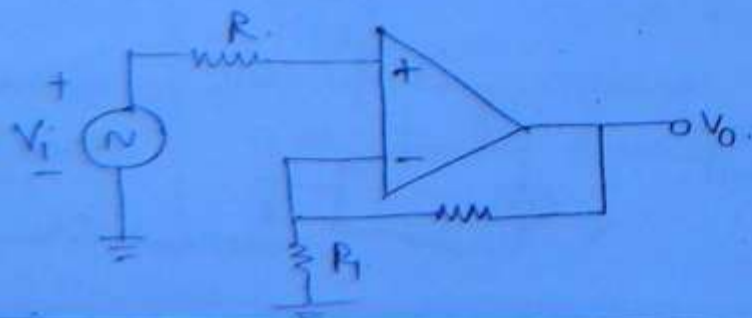inverting amplifier
Voltage shunt
Shunt Shunt
Voltage current



Non inverting amp.
Voltage series
Series shunt
Voltage Voltage

Calculation of Z_{if} impedance with Z_{in} Impedance of diff. topology \rightarrow


(187)

	$Z_o=0$ Voltage	$Z_i=\infty$ Series	$Z_o=0$ Voltage	$Z_i=0$ Shunt	$Z_o=\infty$ Current	$Z_i=\infty$ Series	$Z_o=\infty$ Current	$Z_i=0$ Shunt
Z_{if}	$Z_i(1+AB)$		$Z_i/1+AB$		$Z_i(1+AB)$		$Z_i/1+AB$	
Z_{of}	$Z_o/1+AB$		$Z_o/1+AB$		$Z_o(1+AB)$		$Z_o(1+AB)$	

OSCILLATORS \rightarrow

Definitions \rightarrow

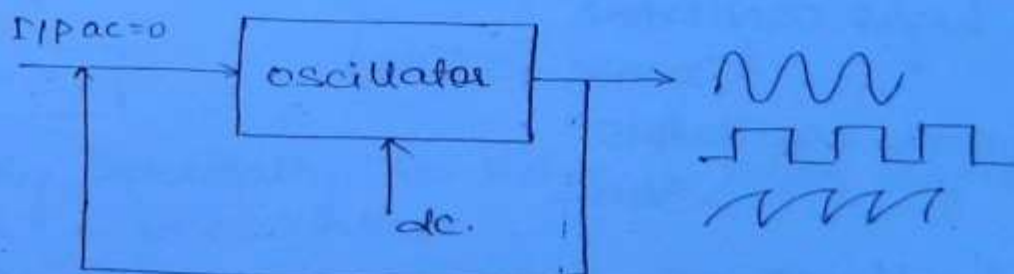- \rightarrow It is a ckt which converts dc en. into ac en. at any required freq.
- \rightarrow It is an electronic ckt of alternating current and voltage having sine, square, sawtooth waveform etc.
- \rightarrow It is a ckt which generates ac o/p signal w/o requiring any ac i/p signal.
- \rightarrow It is an unstable amplifier.



classification of oscillators \rightarrow

- Based on nature of wave generated
- Based on fundamental mechanism involved.
- Based on feedback
- Based on freq. response.

Based on nature of wave generated \rightarrow

- \rightarrow Sinusoidal oscillations
eg tunnel diode, RC, LC oscillation.

- non-inverting - inverting

188

eg - UJT, Astable multivibrator using opamp.

Based on fundamental mechanism involved:-

- Negative resistance region
x Tunnel diode, UJT.
- Feedback
RC oscillator
LC oscillator.

Based on freq. response:-

- Audio freq oscillators
(20Hz - 20kHz)
- Radio freq oscillators.
(30kHz to 30MHz)
- Very high freq. oscillators.
(30MHz - 300MHz)
- Ultra high oscillators
(300MHz - 3GHz)
- Microwave oscillators
> 3GHz

Based on feedback ->

- > RC oscillators
 - [RC Phase shift oscillators
 - Wien bridge oscillators.
- > LC Oscillators.
 - [Hartley
 - Colpitts
 - Clapp
- > Crystal oscillators

Effect of $|A\beta|$ on oscillations: \rightarrow

$$|A\beta| = 1.$$

(189)



$$|A\beta| < 1.$$



$$|A\beta| > 1$$



$$|A\beta| \geq 1$$

Q. Why practically $A\beta$ value is taken slightly greater than 1. in oscillators.

Ans. Because of the non linearities in the CKT, we take $A\beta$ slightly greater than 1.

Q. w/o giving any input how an oscillator can produce an O/P?

Ans:





any external noise will behave like a resistor because of the random moment of e^- in an electronic device a noise voltage will be produce. Such noise voltage will be feedback to the I/P which will be a regenerative action, that means there is no requirement of giving an ext. I/P.


3/11/2

Basic diff. b/w Amplifier and oscillator :-


(90)

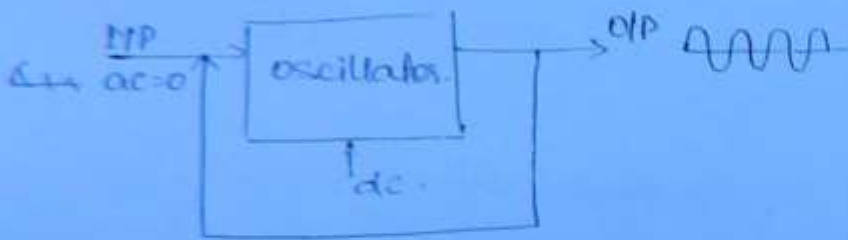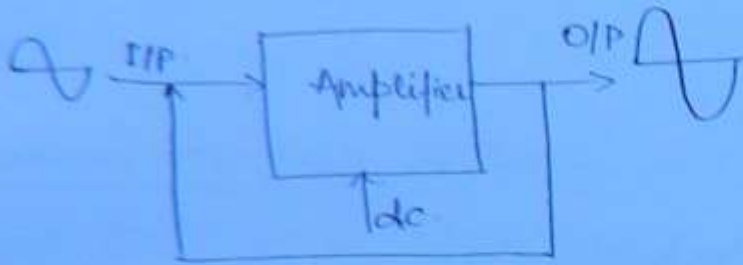

Feedback oscillators —

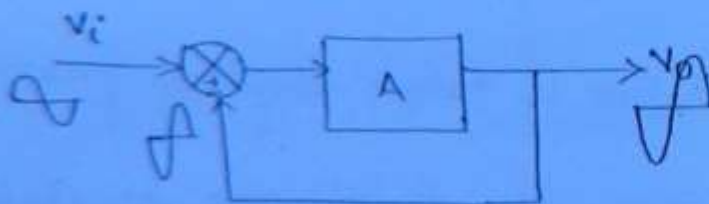

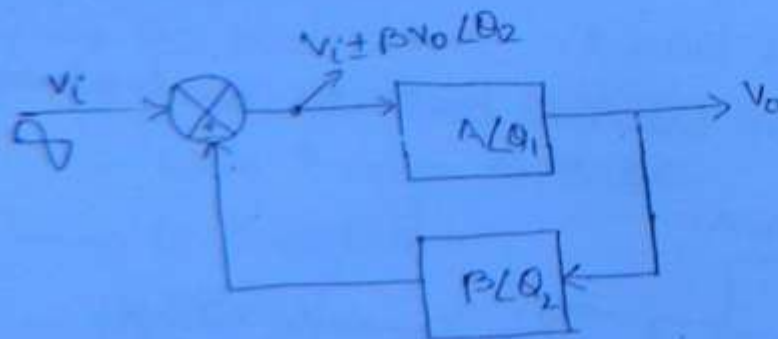→ CE give 180° phase shift
at O/P for I/P-A
So phase shift is taken
↓
at A and β



$$V_0 = A/LQ_1 \{ V_i \pm \beta V_0 / LQ_2 \}$$

for positive feedback.

$$V_o = A \angle \theta_1 \{ V_i + \beta V_o \angle \theta_2 \}$$

$$= A \angle \theta_1 V_i + A \beta V_o \angle (\theta_1 + \theta_2)$$

(191)

$$\Rightarrow V_o (1 - A \beta \angle (\theta_1 + \theta_2)) = A \angle \theta_1 V_i$$

$$\Rightarrow \frac{V_o}{V_i} = \frac{A \angle \theta_1}{1 - A \beta \angle (\theta_1 + \theta_2)}$$

For Oscillators,

for $V_i = 0$,

$$1 - A \beta \angle (\theta_1 + \theta_2) = 0.$$

magnitude
 $|A \beta| = 1$

Phase,


$$\theta_1 + \theta_2 = 0 \text{ or multiple of } 2\pi$$

θ_1

} Barkhausen criteria.

RC oscillators \rightarrow

Phase Shift:—

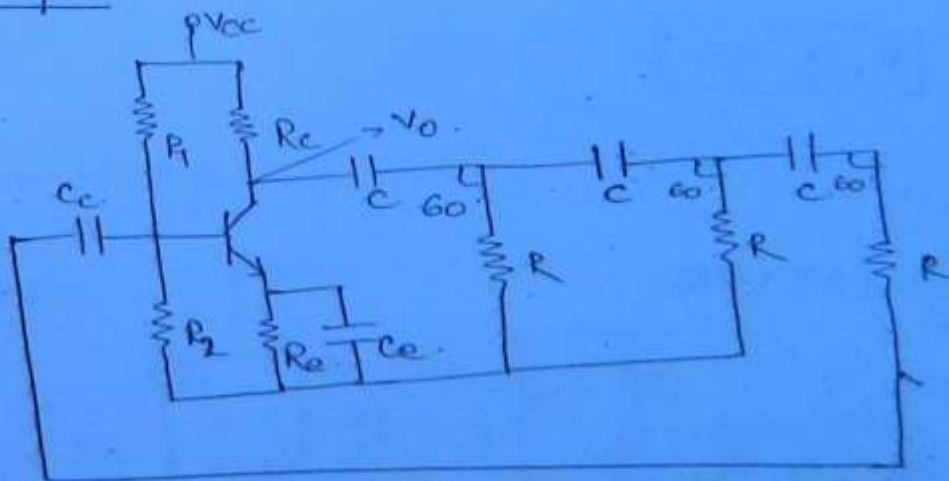

conclusion:—

$$1) \quad Q + \text{RC} \rightarrow 90^\circ \rightarrow \text{ideal.}$$

\downarrow
360°

$$3 \text{ sets of RC} = 360^\circ$$

(180°)

$$2) f = \frac{1}{2\pi RC \sqrt{4K+6}}$$

$$\text{where } K = \frac{R_c}{R}$$

for $K=1$,

(192)

$$f = \frac{1}{2\pi RC \sqrt{10}}$$

for $K \ll 1$,

$$f = \frac{1}{2\pi RC \sqrt{6}}$$

$$3) -h_{fe} \frac{R_c}{R} = -29 - 23K - 4K^2.$$

$$\downarrow$$

$$\boxed{A_v = -29} \quad K \ll 1.$$

$$B = \frac{+1}{A_v} \quad \text{as } |AB| = 1.$$

$$= \frac{1}{-29}$$

$$A_v < -29 \quad \boxed{A_v \geq -29}$$

4) $(h_{fe})_{\min}$

$$h_{fe} = \frac{29}{K} + 23 + 4K.$$

diff. w.r.t. K .

$$\frac{\partial h_{fe}}{\partial K} = -\frac{29}{K^2} + 4 = 0$$

$$K = 2.7.$$

$$\boxed{h_{fe \min} = 44.5}$$

DRAWBACKS of RC phase shift oscillator:

for 3 KHz - 20 KHz

(193)


$$f = \frac{1}{2\pi RC\sqrt{6+4K}}$$

We cannot make it for dynamic frequency as R and C can't be change as phase is affected.


- 1) RC phase shift oscillator is used for single freq. operation
- 2) Due to thermal variation Resistance tolerance value may change which will disturb the phase relations
- 3) This type of CKT can be used for low freq oscillation [audio range] [20 Hz - 20 KHz] because Q-factor of RC n/w is poor

Wien bridge oscillator: →

Block diagram: →

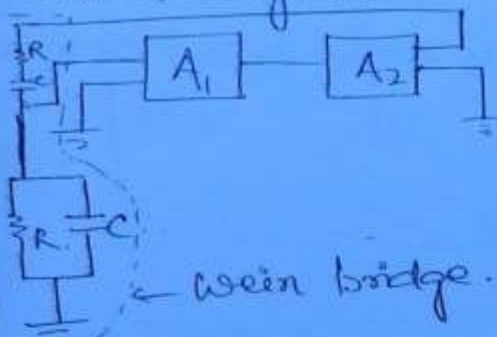

CKT diagram →

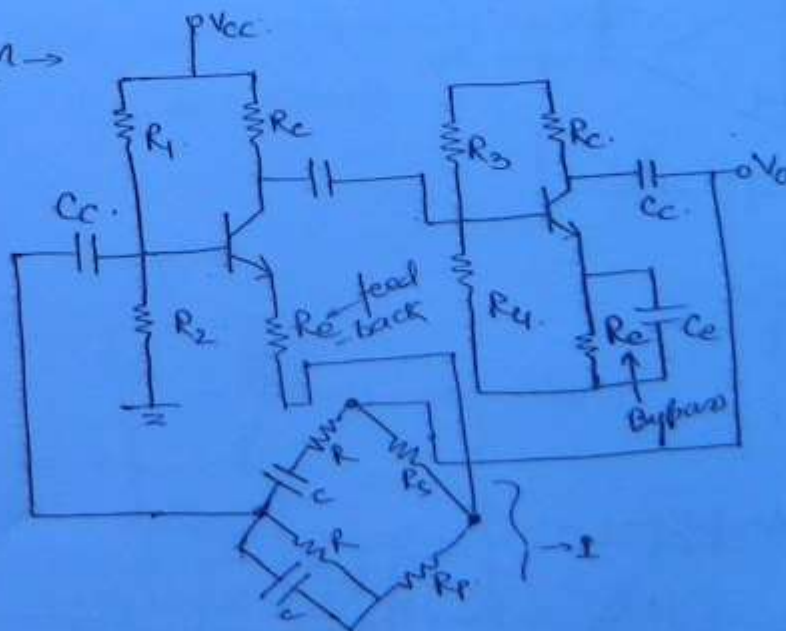

Wien bridge

1) $Q_1 + Q_2$ Wien bridge
 $\downarrow \quad \downarrow$
 $180^\circ \quad 180^\circ$
 $0^\circ \rightarrow 360^\circ$

(194)

2) $f = \frac{1}{2\pi\sqrt{C_1 C_2 R_1 R_2}} \rightarrow \text{3rd I.}$

$R_1 = R_2 = R, C_1 = C_2 = C.$

$f = \frac{1}{2\pi RC}.$

3) $A_V = -3.$


$\beta = -\frac{1}{3}.$

Gain Stabilization \rightarrow

In Wien bridge oscillator, the gain requirement is 3 but because of cascading of two transistors the gain is becoming very high.

To reduce the gain, a -ve feedback is implemented across the transistor Q_1 by R_E resistor.

Bridge balance condition :—

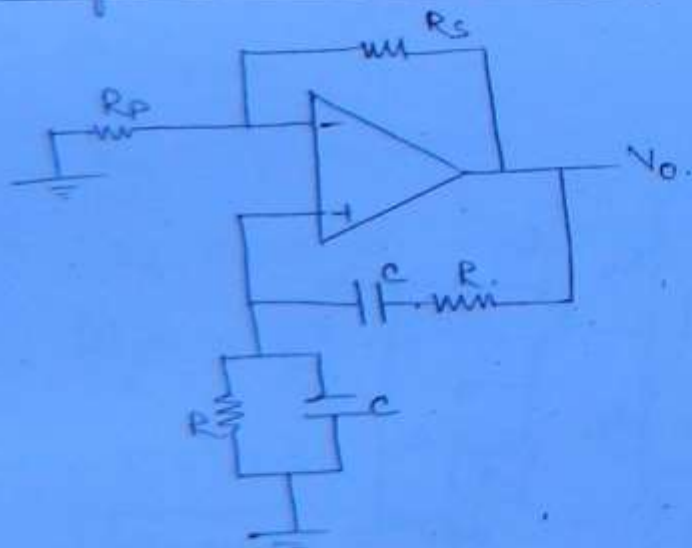

Non inverting Amplifier \rightarrow

$A_V = 1 + \frac{R_f}{R_i} = 1 + \frac{R_s}{R_p} = 3. \Rightarrow \boxed{\frac{R_s}{R_p} = 2}$

$$K_s = 2R_p$$

Importance of Wien bridge :—

(195)

- It has good freq. stability.
- It can be used for dynamic range of freq. because Wien bridge do not depend on phase.


$$f = \frac{1}{2\pi RC}$$

Drawbacks →

- ckt complexity is more.
- It can not be used for high freq. because Q-factor of RC m/w is poor.

LC Oscillators :→


Block diagram :—

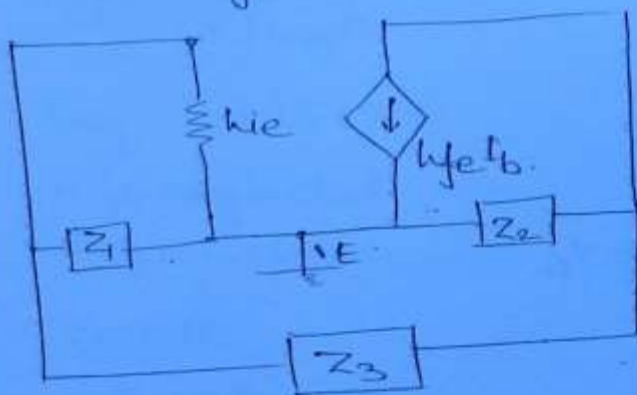


condition :—

- Z_1 and Z_2 are same reactive comp.
- Z_3 is opp. reactive comp.

Hartley →

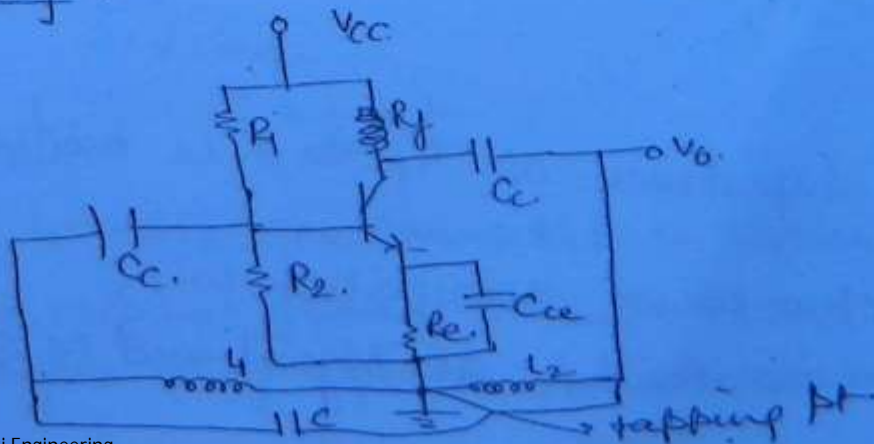


coupling

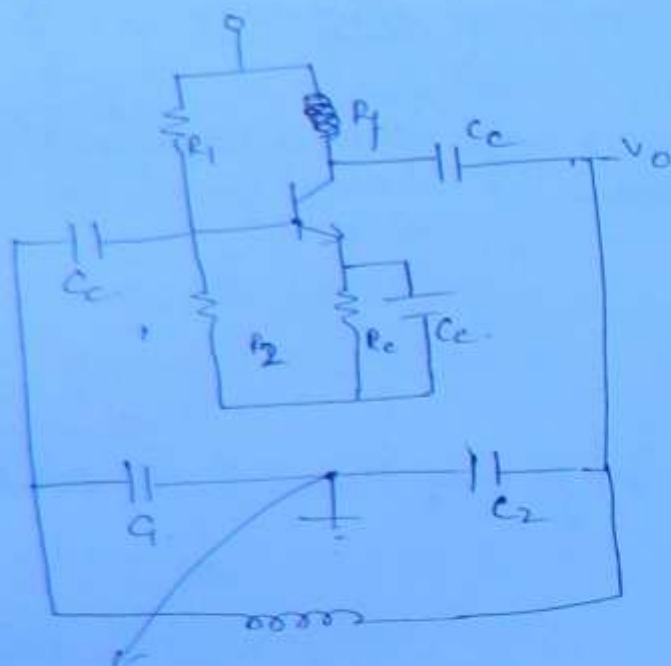

196

tapping pt

clapp →

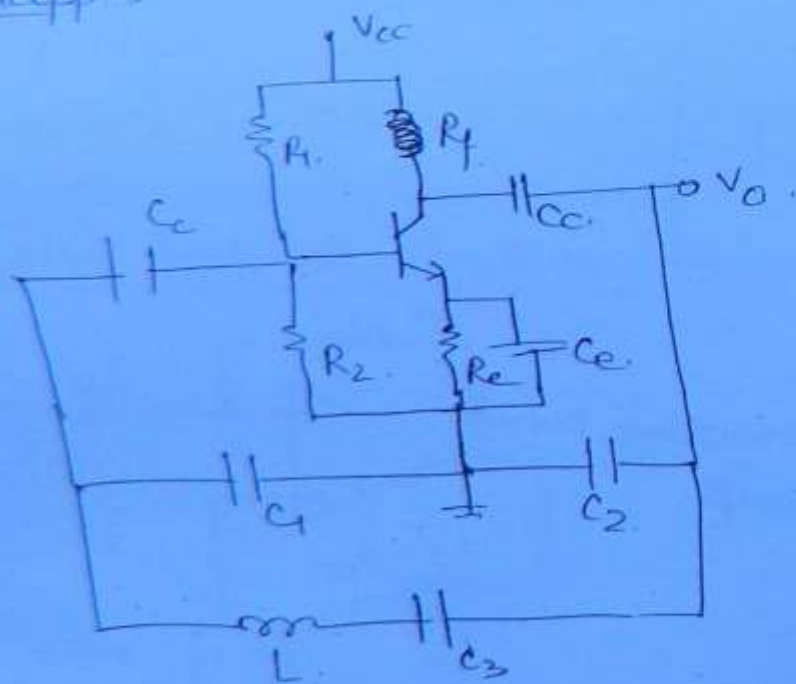


Analysis →

Q1 What is the importance of R_f in LC oscillatory circuit.

Ans 1) To reduce the power dissipation loss,

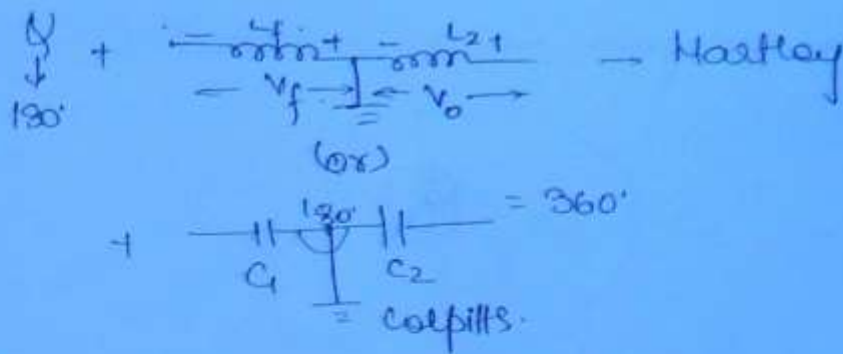2) ~~provides~~ ^{gives} an isolation b/w ac signal and DC supply.



(197)

Tapping pt is an adjustable moving pt which can control the time feedback nature in the ckt.

→ Explain the freq. of oscillation in the LC oscillators?

Ans. $f = \frac{1}{2\pi\sqrt{LC}}$

Hartley →

$$f = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

$$L_{eq} = L_1 + L_2 + 2M$$

M is neglected

$$L_{eq} = L_1 + L_2$$

Colpitts

$$f = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

$$= \frac{1}{2\pi\sqrt{L \frac{C_1 C_2}{C_1 + C_2}}}$$

Clapp

$$f = \frac{1}{2\pi\sqrt{LC_{eq}}}$$


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

Q. Why L_1 and L_2 are connected in series in LC oscillators?

Ans. The current flowing through L_1 and L_2 are same. Therefore they are connected in series.

example is convenient for you in LC oscillators.

Hartley

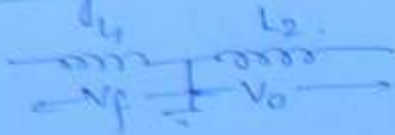


(98)

$$\beta = \frac{V_f}{V_o} = \frac{M_1}{M_2} = \frac{L_1}{L_2}$$

$$A = \frac{L_2}{L_1}$$

Colpits

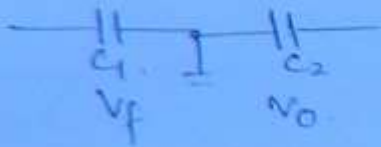

$$\beta = \frac{V_f}{V_o} = \frac{1 \times C_2}{1 \times C_1} = \frac{C_2}{C_1}$$

$$A = \frac{C_1}{C_2}$$

→ Why LC oscillators can not be designed for low freq. of operation.

$$\downarrow f = \frac{1}{2\pi\sqrt{LC}}$$

Size of equipment become large.


As the freq. of design reduces, the comp's L and C values will increase. Practically it is impossible to design for very low freq.

⇒ LC oscillators are used for high freq. design because the Q-factor is more.

→ What is the imp. of clapp oscillators?

computs → :

(149)

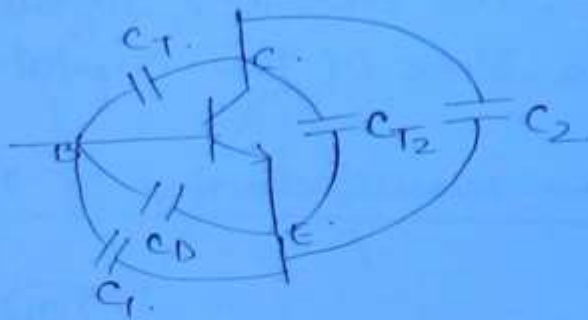

$$f = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$f = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$C_1 \gg C_3$$

$$C_2 \gg C_3$$


$$\boxed{\frac{1}{C_{eq}} = \frac{1}{C_3}}$$

$$f = \frac{1}{2\pi\sqrt{LC_3}} \rightarrow \text{independent of internal capacitors.}$$

Crystal oscillators →

when ever high freq. stability is required.

Piezoelectric effect :-

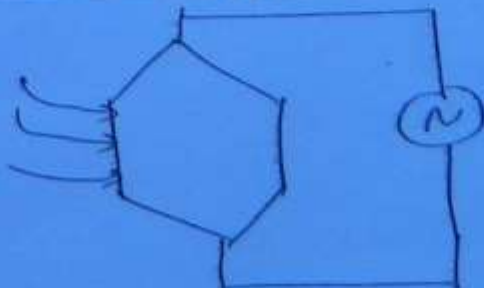

When a mechanical force is applied on one face of the crystal, an Electrical signal will be generated on the other side of the crystal and vice versa.

Substances used for the manufacturing of the crystal:-

- 1) Rochelle Salts
- 2) Quartz
- 3) Tourmaline.

(200)

Q. Which substance will have more piezoelectric effect?

Ans. Rochelle Salts > Quartz > Tourmaline.



Q. Which substance is mechanically strongest?

Ans. Tourmaline > Quartz > Rochelle Salt


Quartz is a compromise b/w Rochelle Salts and Tourmaline as easily available in nature.

Crystal equivalent model:-

non vibrating mode \rightarrow

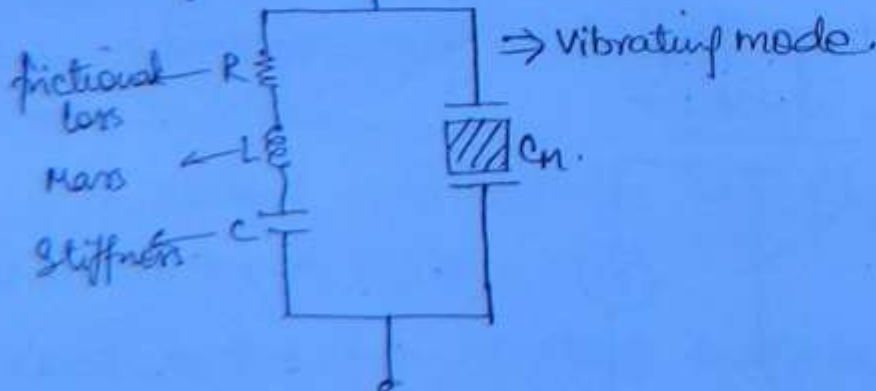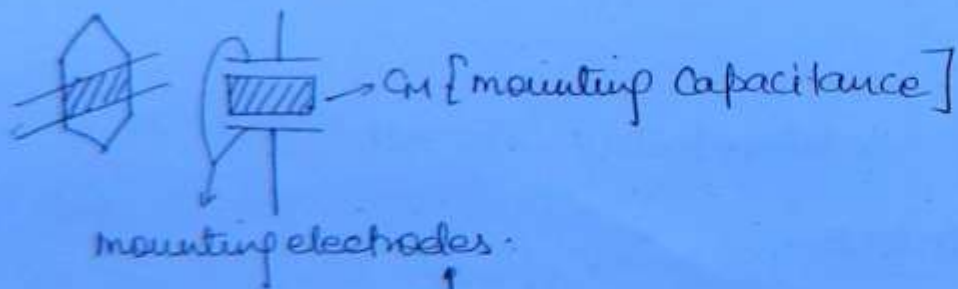

Crystal operating mode

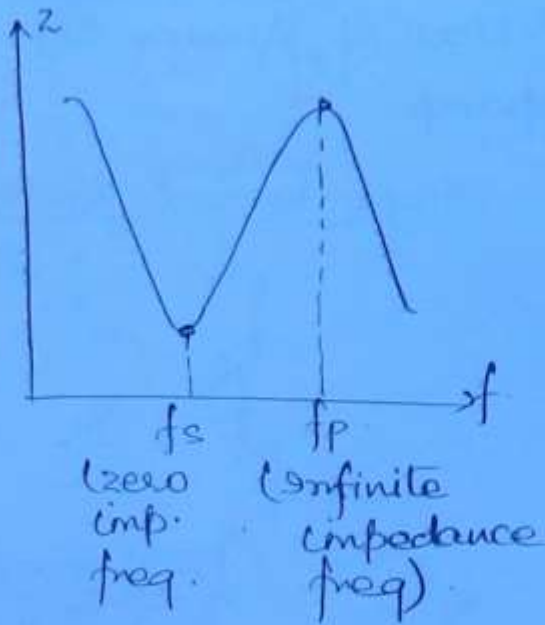

(201)


$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

$$f_p = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 + \frac{C}{C_M}}$$


$$* C_M \gg C$$

$$f_p \approx f_s$$

Ckt 1.

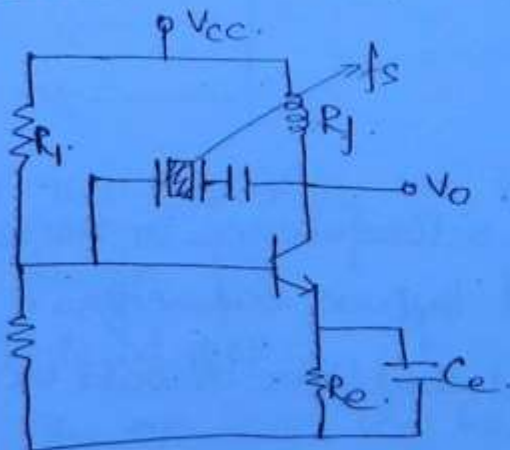

Ckt 2.

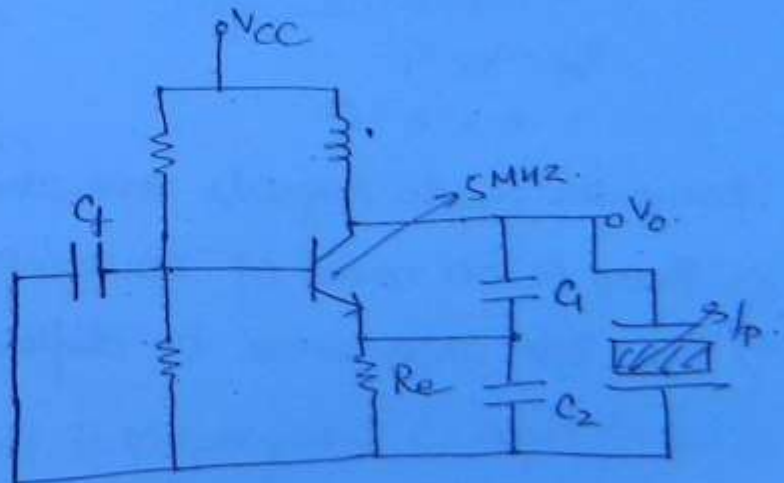


Differential Amplifiers →


(202)

It is the basic building block of Analog ckt.
It is the I/P stage of opamp.

Diff. Amp →

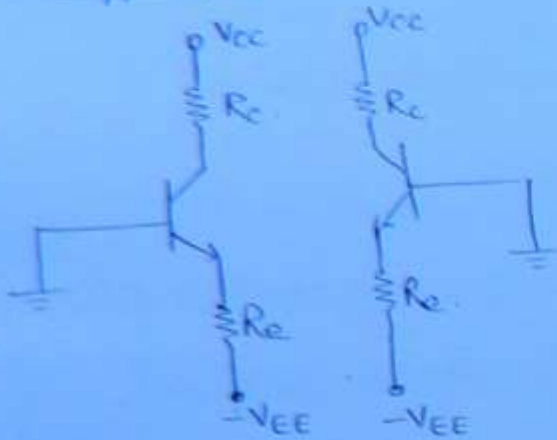

Single ended Amplifier

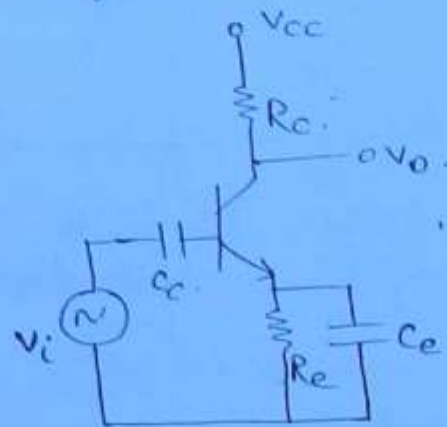

The comp. of differential amplifiers compare to single ended amplifiers are

1) It is having best noise rejection capability.

eg -





$$V_d = V_2 - V_1 \\ = 2 - 2 = 0$$

common mode signals are always interference or noise signals




2) There is no need of coupling and bypass capacitors.

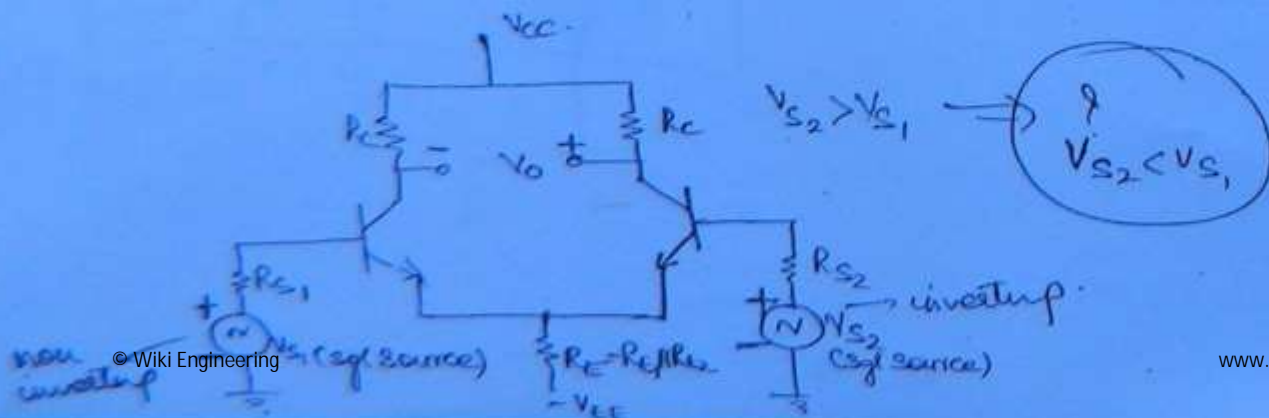3) The I/P impedance of differential amplifier should be high.



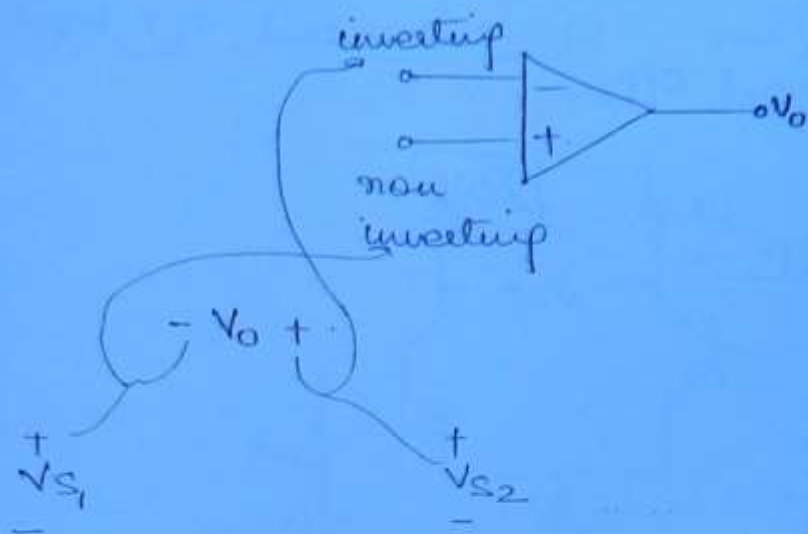

Ckt Configuration : \rightarrow

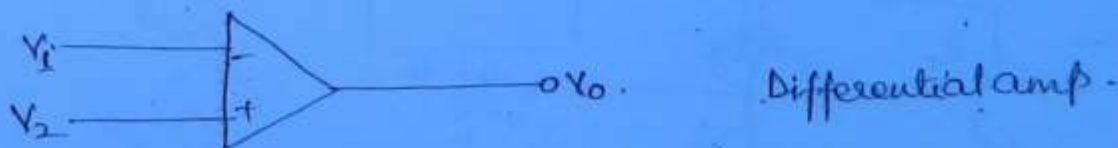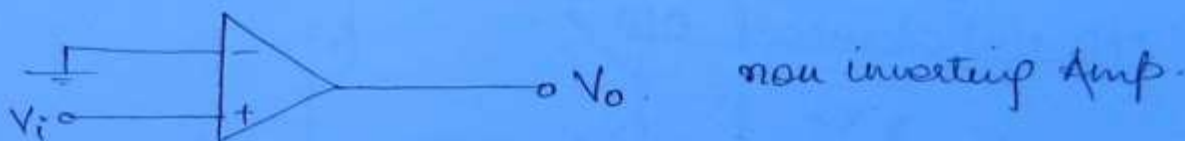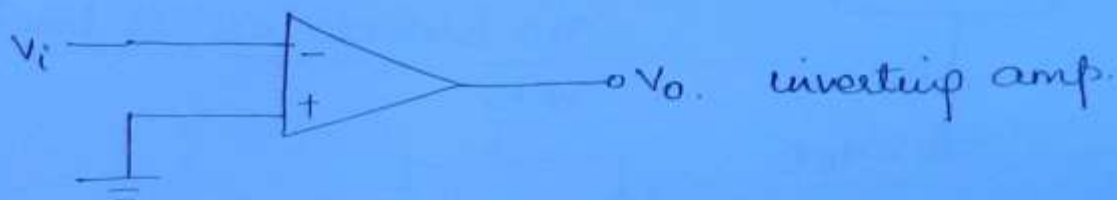

At the I/P Side, we have,

- 1) Single I/P.
- 2) dual I/P.

At the O/P Side, we have,

- 1) balanced output [Output is taken across C_1 and C_2]
- 2) Unbalanced output [Output is taken across C_1 to ground or C_2 to ground].

Acc. to this we have four types of configuration.


- 1) Single I/P balanced O/P.
- 2) Single I/P Unbalanced O/P.

- 3) Dual I/P balanced O/P
 4) Dual I/P Unbalanced O/P


Ckt diagrams →

(204)


Single I/P balanced O/P →

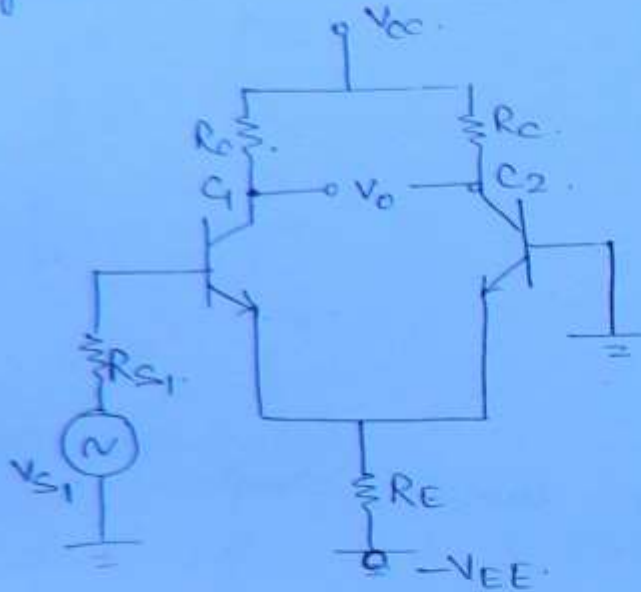


Single I/P Unbalanced O/P →

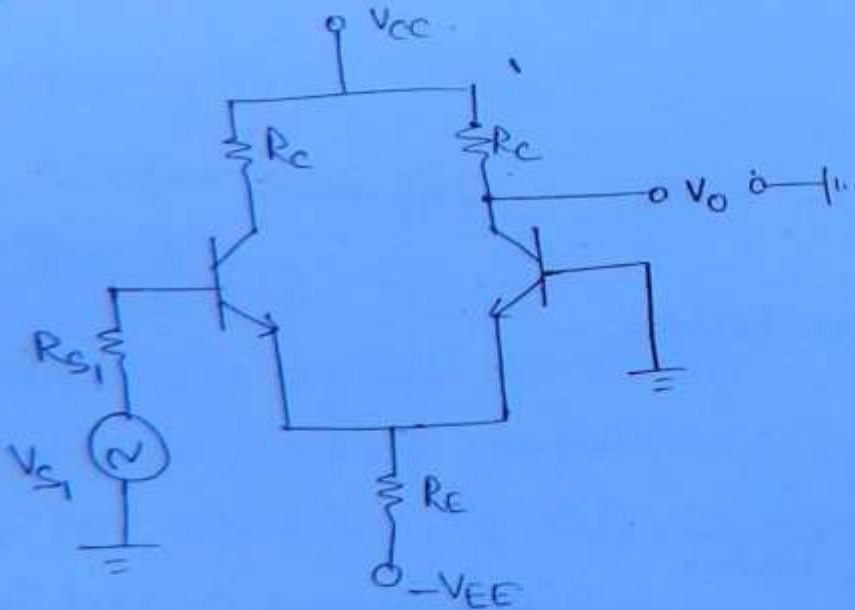

Dual I/P Balanced O/P.

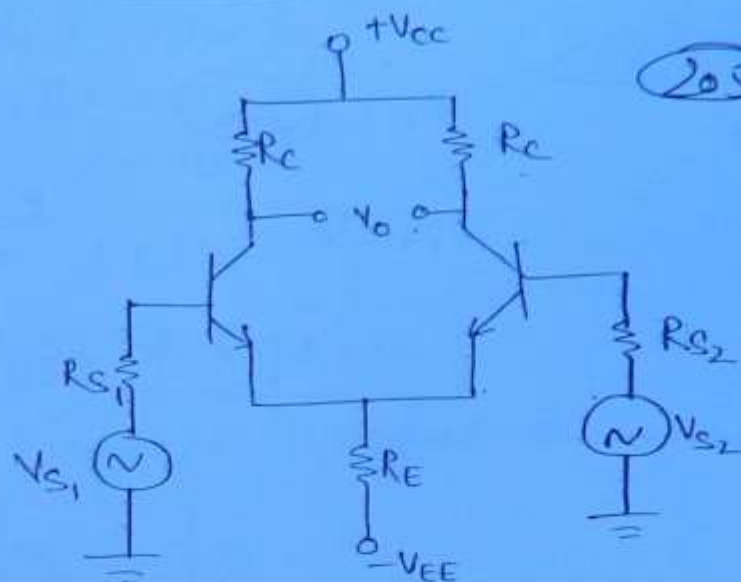

Dual I/P unbalanced o/p.

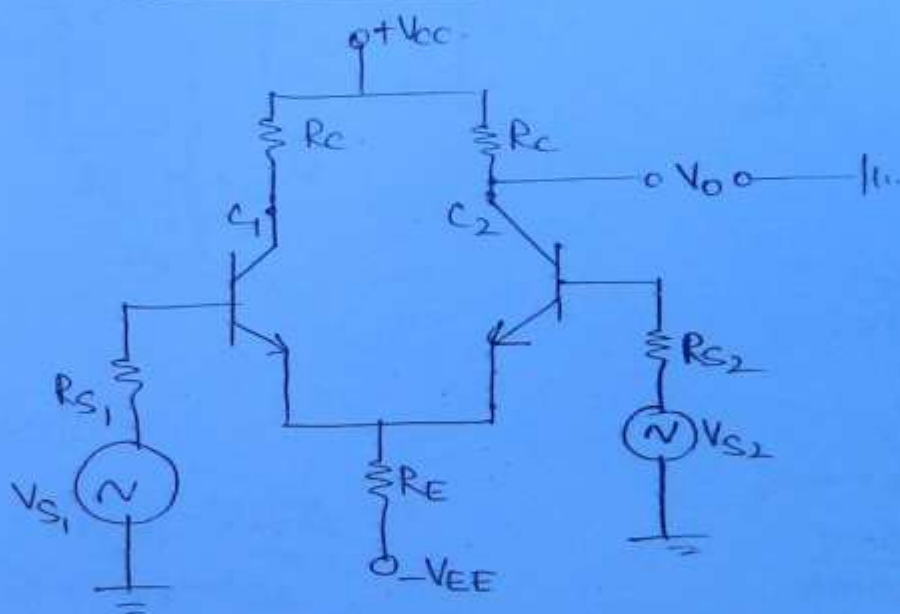

Problems →

- 1) Cal. Voltage gain of a single I/P balanced O/P. or dual I/P balanced O/P. differential amplifier ckt with $R_C = 1\text{K}\Omega$ and $I_E = 26\text{mA}$.
- 2) Cal. Voltage gain for a single I/P & unbalanced O/P or dual I/P unbalanced O/P differential amplifier ckt with $R_C = 1\text{K}\Omega$ and $I_E = 26\text{mA}$.
- 3) Cal. I/P impedance of a differential amplifier ckt with $\beta_{ac} = 50$, $I_E = 26\text{mA}$.

v. can v. impedance of \rightarrow \rightarrow computer ckt with R_c
 $R_c = 1K\Omega$

	A_v	R_i (206)	R_o
Single D/P balanced O/P	$\frac{R_c}{r_e}$	$2\beta_{ac} r_e$	R_c
Single D/P unbalanced O/P	$\frac{1}{2} \frac{R_c}{r_e}$	"	R_c
Dual D/P balanced O/P	$\frac{R_c}{r_e}$	"	"
Dual D/P unbalanced O/P	$\frac{R_c}{2r_e}$	"	"

Answers \rightarrow

$$1) A_v = \frac{R_c}{r_e}$$


$$r_e = \frac{V_T}{I_{E \rightarrow dc}}$$

$$= \frac{26mV}{26mA}$$

$$= 1\Omega$$

$$R_c = 1K\Omega$$
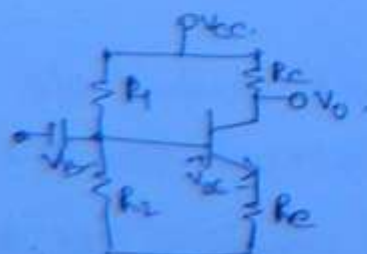
$$A_v = \frac{1K\Omega}{1\Omega} = 1000 \rightarrow \text{for both ckt}$$



$$\rightarrow A_v = \frac{R_c}{r_e} = \frac{R_c \cdot I_c}{V_T}$$

$$V_o = \frac{R_2}{R_1 + R_2} V_{cc} \quad \frac{V_o - V_{BE}}{R_2 + R_e} = I_c$$

$$2) V_V = 500\mu$$


$$3) R_i = 2\beta ac r_e \\ = 2 \times 100 \times 1 \\ = 100 \Omega$$

$$4) R_o = 1 K \Omega$$

207

Calculation of Q-pt: →

neglect Ac. concept

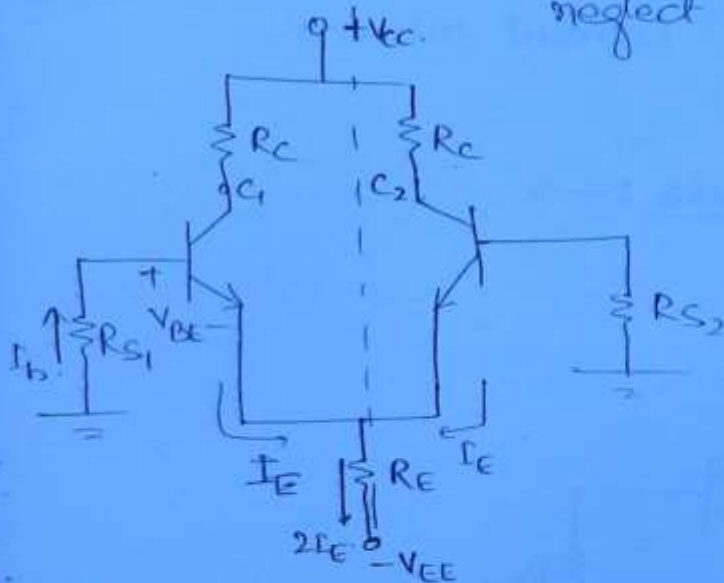

Q1

I/P loop →

$$V_{EE} - I_B R_{S1} - 2I_E R_E = 0$$

$$I_E = \frac{V_{EE} - V_{BE}}{2R_E + \frac{R_{S1}}{1+\beta}}$$

$$1+\beta \gg R_{S1}$$

$$I_E = \frac{V_{EE} - V_{BE}}{2R_E}$$

$$(I_C)_Q = I_E = \frac{V_{EE} - V_{BE}}{2R_E}$$

$$(V_{CE})_Q = V_C - V_E$$

$$V_C = V_{CC} - (I_C)_Q R_C \Rightarrow V_E = -V_{BE}$$

$$(V_{CE})_Q = V_{CC} - (I_C)_Q R_C + V_{BE}$$

Various problems in experimental amplifiers :-

1) $A_v = \frac{R_c}{r_e}$ — gain is not stable.

2) $R_i = 2\beta r_e R_c = 2 \times 80 \times 1$
 $= 160 \Omega$

208


Rectify & techniques
 Sampling
 resistor techniques

3) $R_c (V_{CE}) (V_{CE})$


$r_e = \frac{V_{CE} - V_{BE}}{2 R_c}$

Rectify techniques
 constant current source
 current mirrors.

Sampling resistor techniques :-

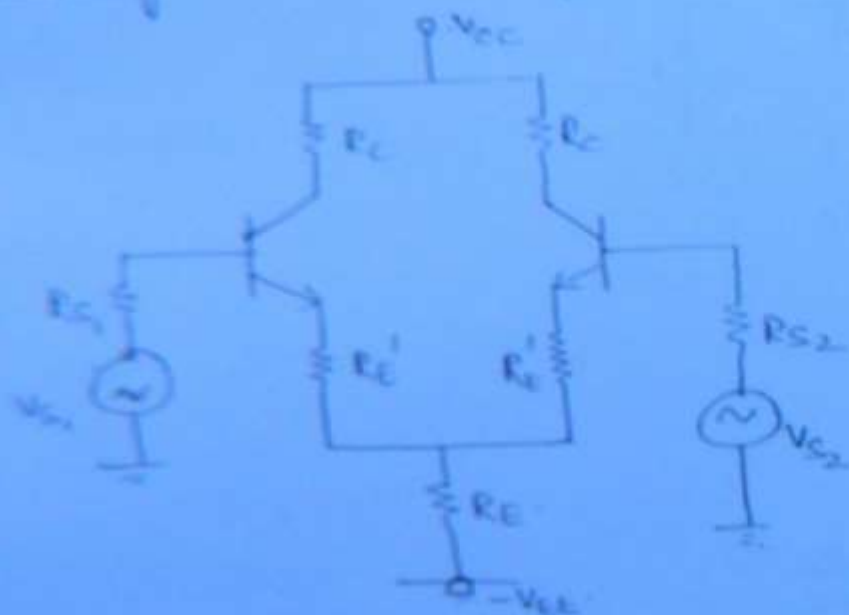

r_e model

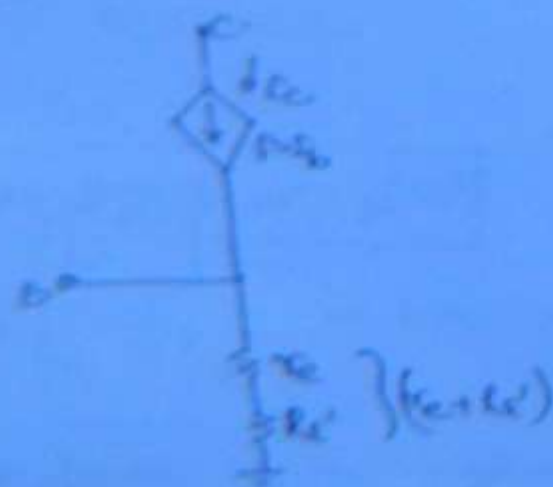

$A_v = \frac{R_C}{r_e}$
 ↓ sampling

$A_v = \frac{R_C}{r_e || R_C}$
 $= \frac{R_C}{R_C}$ $R_C \gg r_e$
 → gain is stable.

$$R_i = 2R_{ac} R_{cc}$$

↓ sampling

$$R_i = 2R_{ac} (R_c + R_{c'})$$

(209)

Assume $R_{c'} = 100K$.


$$R_i = 2 \times 50 \times 100K$$

$$= 10 M\Omega$$

6/1/12

CONST CURRENT SOURCE →

Ckt 2.

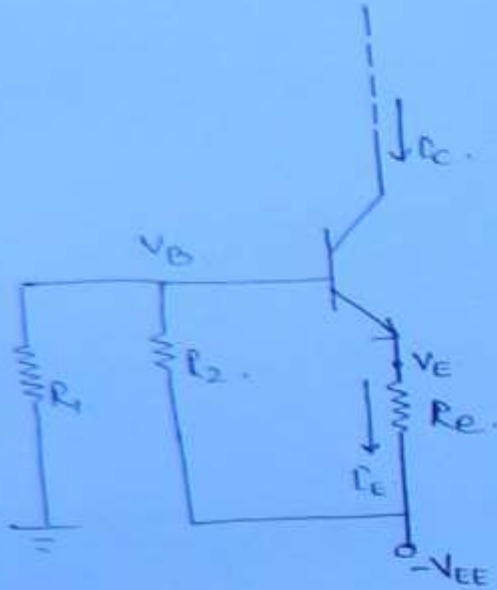

$$I_E = \frac{V_E - (-V_{EE})}{R_E}$$

$$V_E = V_B - V_{BE}$$


$$V_B = \frac{-V_{EE} \times R_1}{R_1 + R_2}$$

$$I_E = \frac{V_B - V_{BE} + V_{EE}}{R_E}$$

↓

The main drawback is I_E is depending on V_{EE} supply

Ckt 3

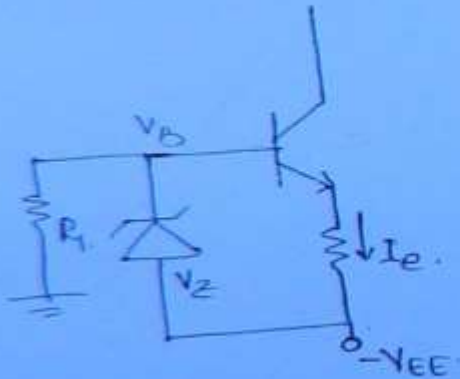

$$I_E = \frac{V_Z - V_{EE} - V_{BE} + V_{EE}}{R_E}$$


$$V_B = V_Z - V_{EE}$$

Current mirror →

Ckt 1.


$$\begin{aligned} I_{neg} &= I_{C1} + I \\ &= I_{C1} + I_{B1} + I_{B2} \\ &= I_{C2} + 2I_{B2} \\ &= I_{C2} + 2 \frac{I_{C2}}{\beta} \\ &= I_{C2} \left[1 + \frac{2}{\beta} \right] \end{aligned}$$
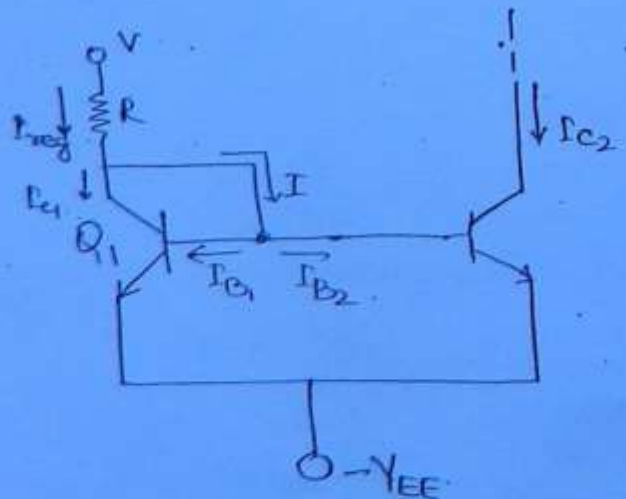
$$I_{C2} = \frac{I_{neg}}{1 + \frac{2}{\beta}}$$



n stage \rightarrow ckt2

(211)

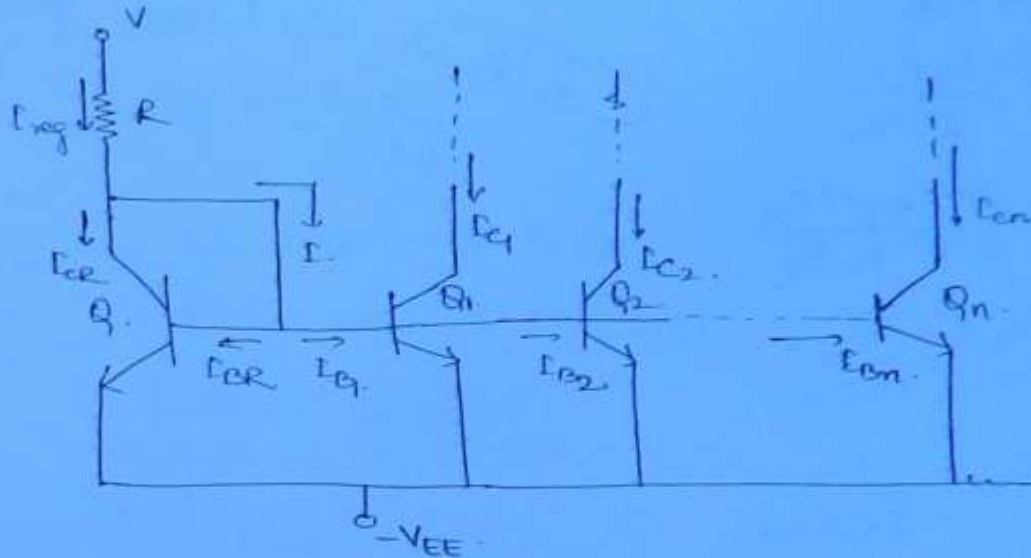

$$I_{C1} = I_{C2} = \dots = I_{Cn} = I_{CR} \\ = I_{Ci} \quad (i = 1, 2, 3, \dots, n)$$

$$I_{BR} = I_{B1} = I_{B2} = \dots = I_{Bn} = I_{Bi}$$

$$I_{reg} = I_{CR} + I$$

$$= I_{CR} (I_{BR} + I_{B1} + I_{B2} + \dots + I_{Bn})$$

$$= I_{CR} + I_{BR} (1 + N)$$


$$= I_{CR} + \frac{I_{CR}}{\beta} (1 + N)$$

$$= I_{CR} \left[1 + \frac{1 + N}{\beta} \right]$$

$$I_{CR} = \frac{I_{reg}}{1 + \frac{(1 + N)}{\beta}}$$

N should be less for less error.

Ckt 3 \rightarrow

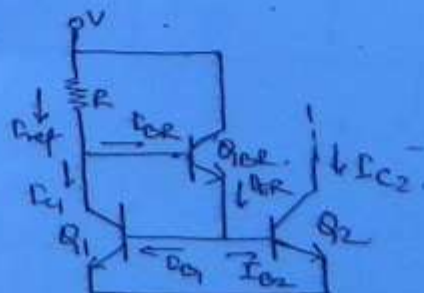

$$I_{ref} = I_{C1} + I_{B2}$$

$$= I_{C1} + \frac{I_{C2}}{1 + \beta_R}$$

2/2

$$= I_{C2} + \frac{I_{B1} + I_{B2}}{1 + \beta_R}$$

$$= I_{C2} + \frac{2 I_{B2}}{1 + \beta_R}$$


$$= I_{C2} + \frac{2 I_{C2}}{\beta(1 + \beta_R)}$$

$$I_{C2} = \frac{I_{ref}}{1 + \frac{2}{\beta(1 + \beta_R)}}$$

$$I_{C2} \approx I_{ref}$$

$$\text{as } \beta(1 + \beta_R) \gg 2$$

n stage \rightarrow (crt-4)

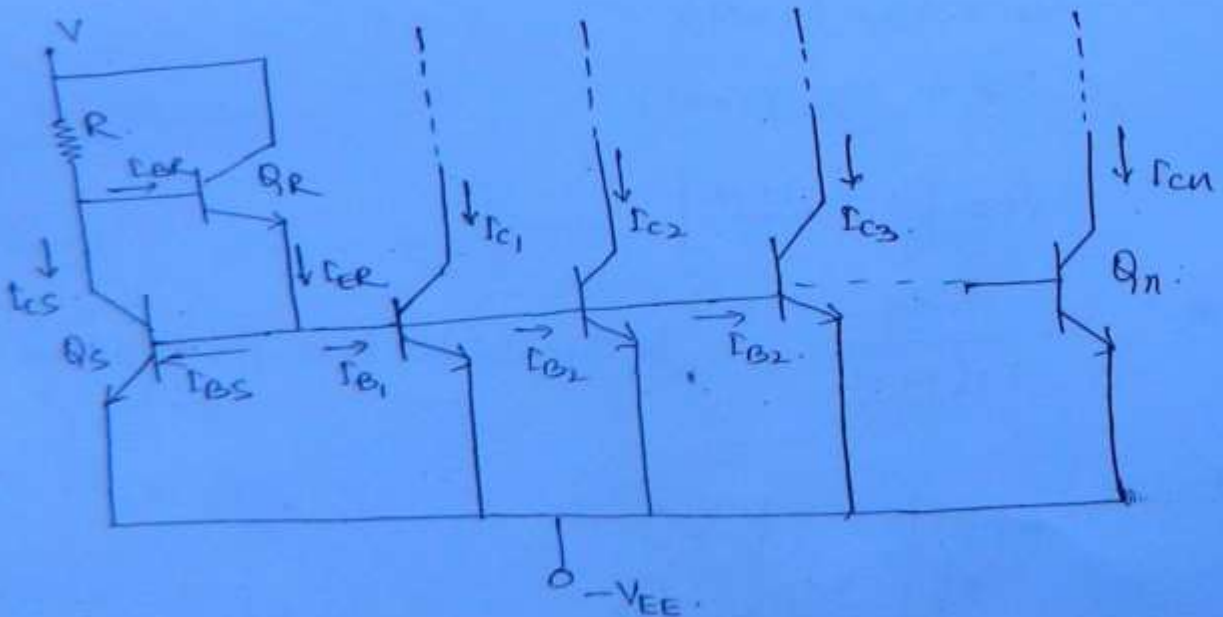

$$I_{C1} = I_{C2} = \dots = I_{Cn} = I_{CS}$$

$$= I_{C1}$$

$$I_{BS} = I_{B1} = I_{B2} = \dots = I_{Bn}$$

$$= I_{B1}$$

(213)

$$I_{ref} = I_{CS} + I_{BR}$$

$$= E_{CS} + \frac{E_{ER}}{1 + PR}$$

$$= I_{CS} + (I_{BS} + I_{B1} + I_{B2} + \dots + I_{Bn}) / (1 + \beta_R)$$

$$= F_{CS} + F_{BS}(1+N)/1+BR$$


$$= I_{CS} + \frac{I_{CS}(1+N)}{\beta(1+\beta R)}$$

$$= F_{C2} \left[1 + \frac{1+N}{P(1+P_R)} \right]$$

$$P_{C2} = \frac{I_{ref}}{1 + \frac{(1+N)}{P(1+P_R)}}$$

Active load in differential amplifiers \rightarrow
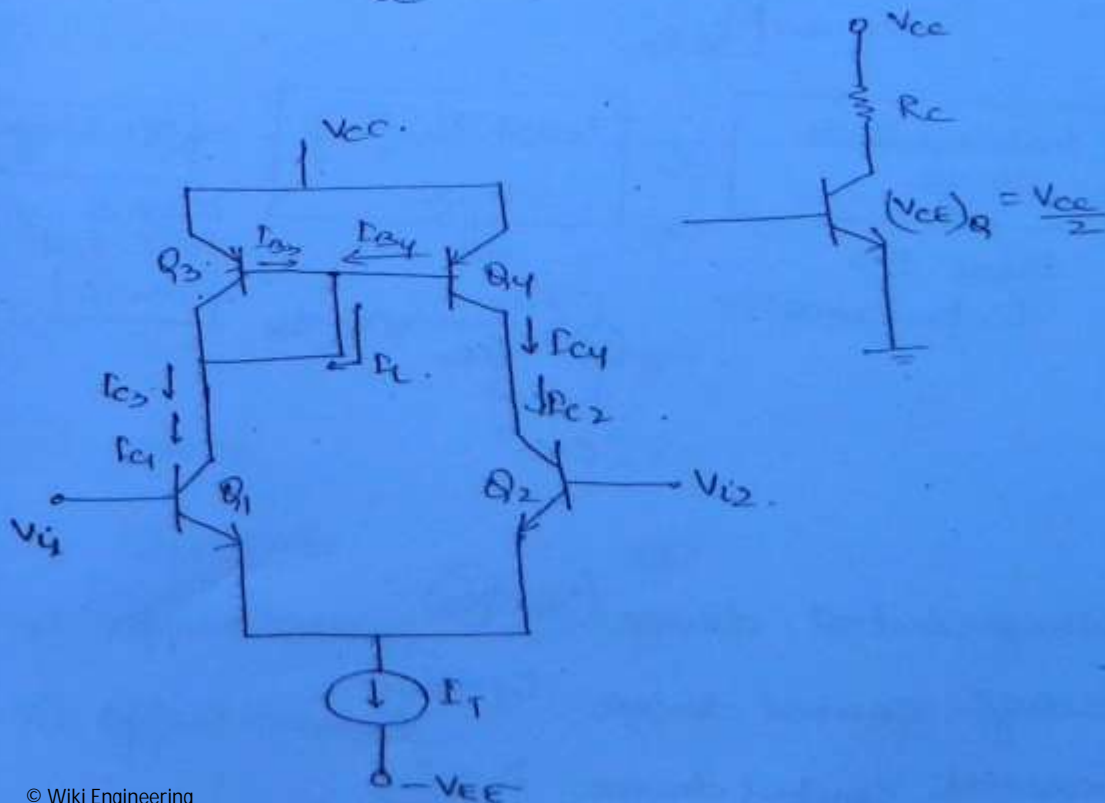
$$\uparrow A_d = \frac{R_c \uparrow}{r_o}$$



Assume N_1, N_2, N_3, N_4 are identical.

$$\begin{aligned} I_c &= I_{C3} + I_{C4} \\ &= \frac{1}{\beta} (I_{C3} + I_{C4}) \\ &= \frac{1}{\beta} (I_{C1} + I_{C2}) \\ &= \frac{1}{\beta} I_T \approx 0. \end{aligned}$$

(2/4)

Active Load = ∞


$$CMRR \uparrow = \frac{A_d \uparrow}{A_c}$$

Active loads are used in differential amplifiers to improve

- 1) Differential gain A_d .
 - 2) CMRR (common mode rejection ratio)
- $$= \frac{A_d}{A_c}$$

OPAMP \rightarrow

Block diagram \rightarrow

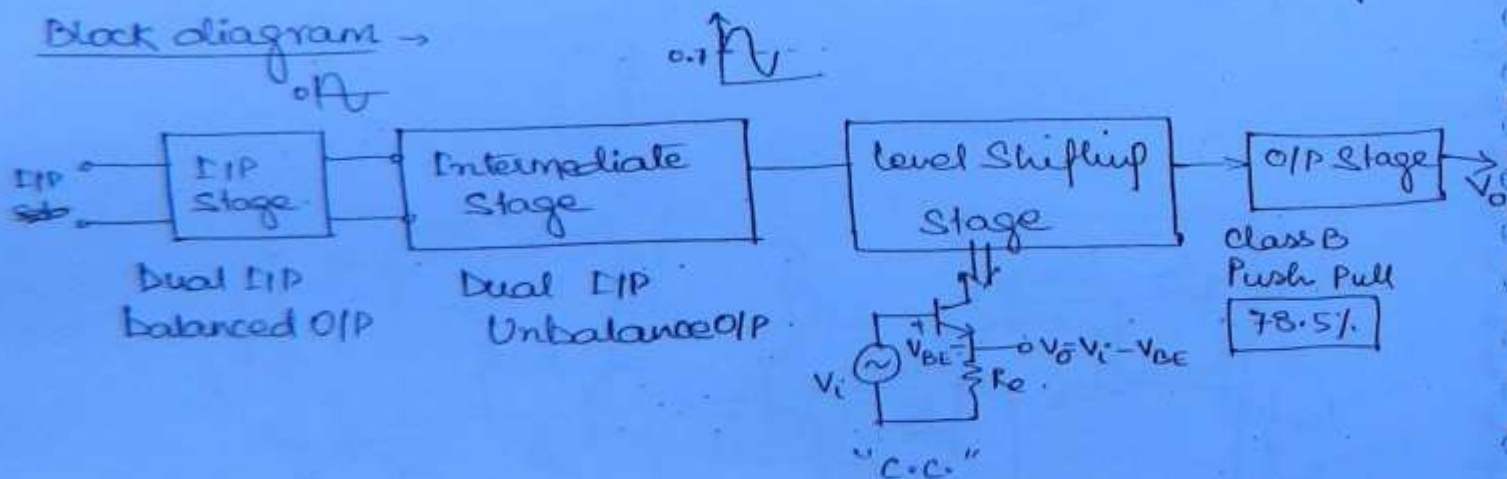

Imp. pts \rightarrow

- 1) Opamp is a Voltage control device ($V_O \propto V_{i1}$)
- 2) FET is a Voltage control device ($I_d \propto \sqrt{V_{gs}}$)
- 3) BJT is a Current control device ($I_{C1} \propto I_B$)

II Match 1

2) V_{ce} vs I_{ce}

3) V_{ce} vs I_{ce}

I_{ce} vs I_{ce}

1) I_{ce} vs I_{ce}

(215)

Match 2.

1) BJT

2) Opamp

3) FET.

III Increasing order of $Z_i \rightarrow$

BJT, Opamp, FET, MOSFET. \checkmark

Typical Values \rightarrow

BJT $\rightarrow 1K\Omega$

OPAMP $\rightarrow 10^6\Omega$

FET $\rightarrow 10^7$ to 10^{10}

MOSFET $\rightarrow 10^{11}$ to $10^{14}\Omega$

Characteristics of OP-AMP: \rightarrow

Characteristics	Ideal	Practical.
1) Z_i	∞	10^6
2) Z_o	0	100Ω
3) A_v	∞	10^6
4) BW	∞	10^6 Hz
5) CMRR	∞	10^6 or 120 dB
6) Slew rate	∞	80V/ μ s
7) Offset Voltage	0	min
8) Offset current	0	min

CMRR \rightarrow

$$\text{CMRR} = \frac{A_d}{A_c}$$

(216)

$$(\text{CMRR})_{\text{dB}} = 20 \log \left(\frac{A_d}{A_c} \right)$$



It is a linear IC. So, superposition theorem is applied.

$$V_0 < V_d$$

$$V_0 = A_1 V_1 + A_2 V_2 \quad \text{--- (1)}$$

$$V_d = V_2 - V_1$$

$$V_c = \frac{V_1 + V_2}{2}$$

$$2V_c = V_1 + V_2$$

$$V_1 = V_c + V_d/2$$

$$V_2 = V_c - V_d/2$$

Substitute in eq: (1)

$$V_0 = A_1 (V_c + V_d/2) + A_2 (V_c - V_d/2)$$

$$= (A_1 + A_2) V_c + \left(\frac{A_1 - A_2}{2} \right) V_d$$

$$\downarrow$$
$$A_c$$

$$\downarrow$$
$$A_d$$

$$V_0 = A_c V_c + A_d V_d$$

$$V_0 = A_d V_d \left[1 + \frac{A_c}{A_d} \frac{V_c}{V_d} \right]$$

$$\frac{A_c}{A_d} \rightarrow \frac{1}{\text{CMRR}}$$

Q. A differential Amplifier has I/P $V_1 = 1050 \text{ mV}$, $V_2 = 950 \text{ mV}$.

$$\text{CMRR} = 1000$$

$$\text{diff. error o/p} = ?$$

(2/7)

Ans.

$$\frac{1}{1000} \times \frac{V_c}{V_d}$$

$$V_1 = V_c + V_d/2$$

$$1050 = V_c + V_d/2$$

$$950 = V_c - V_d/2$$

$$2V_c = 2000$$

$$V_c = 1000$$

$$V_d = 50 \times 2$$

$$= 100$$

$$100 \times 100$$

$$\text{diff error o/p} = \frac{1}{1000} \times \frac{1000}{100} \times 100 = 1\%$$

SLEW RATE →

$$\text{SR} = \left. \frac{dV_o}{dt} \right|_{\mu\text{s}}$$

$$= \frac{\Delta V_o}{\Delta V_i} \frac{\Delta V_i}{\Delta t}$$

$$\boxed{\text{S.R.} = A_{cl} \frac{\Delta V_i}{\Delta t}}$$



$$\omega_{\text{map}} = \frac{\text{S.R.}}{K} = \frac{\text{S.R.}}{A_{cl} \Delta V_i}$$

$$f_{\text{map}} = \frac{\text{S.R.}}{2\pi A_{cl} \Delta V_i}$$

$$f_{\text{map}} = \frac{\text{S.R.}}{K}$$

$\omega_{\text{input}} < \omega_{\text{map}} \rightarrow$ o/p will be replica of I/P

$\omega_{\text{input}} > \omega_{\text{map}} \rightarrow$ o/p will be distorted.

It is a measure of maximum V_i \rightarrow \sim \sim \sim I/P in μ s.

OFF SET :-

(218)



$$V_{io} = V_B - V_A$$


\downarrow

I/P Offset Voltage.

used to make $V_o = 0$


W/o giving any I/P to the terminals of the opamp, output is not 0 [small magnitude] The reason is I/P stage is differential amplifier where the two transistors should be identical. Practically it is not possible. To make the O/P V_o to 0 we use offset condition at the I/P of the OPAMP.

Prob

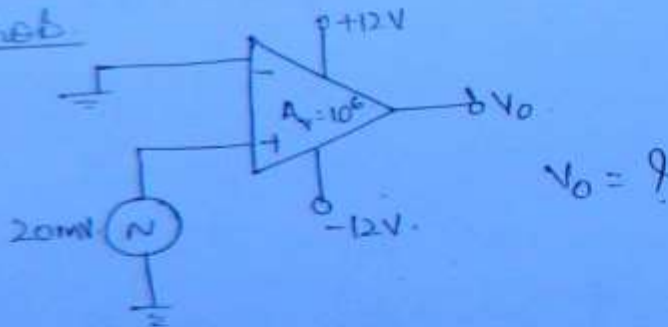


$V_o = 12V$ irrespective of supply because $+12V$ and $-12V$ is the sat value of this opamp.

transfer char :-

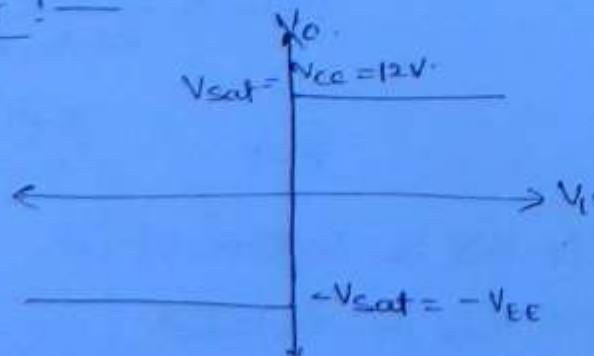

virtual ground -

(219)

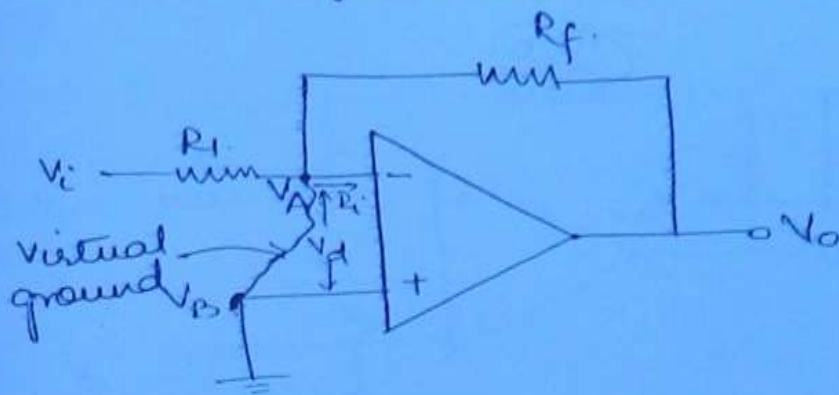

$$V_d = V_B - V_A$$

Ideal →

$$R_i \rightarrow \infty$$


$$I_i \rightarrow 0$$

$$V_d \rightarrow 0$$

$$0 = V_B - V_A$$

$$\Rightarrow \boxed{V_B = V_A}$$

Inverting Amplifier →

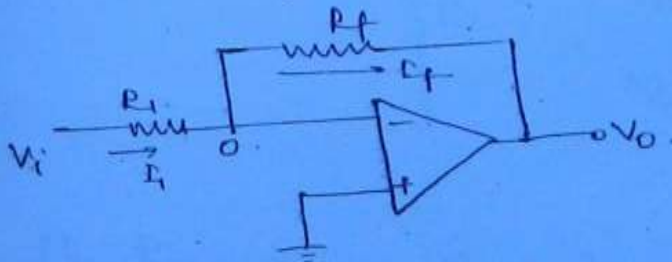


$$R_i = R_f$$

$$\frac{V_i - 0}{R_i} = \frac{0 - V_o}{R_f}$$

$$\frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

non inverting amplifier

(220)

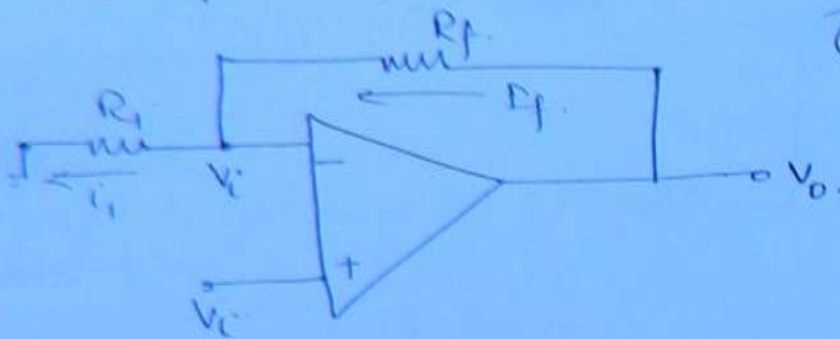


$$I_f = I_1$$

$$\frac{V_o - V_{o1}}{R_f} = \frac{V_o - 0}{R_i}$$


$$\Rightarrow \boxed{\frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}}$$

Phase Shifter →

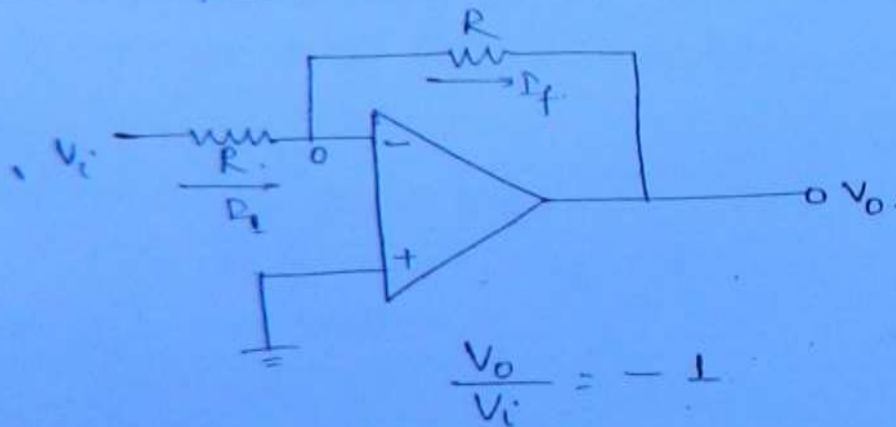

$$\frac{V_o}{V_i} = -1$$

Voltage follower →

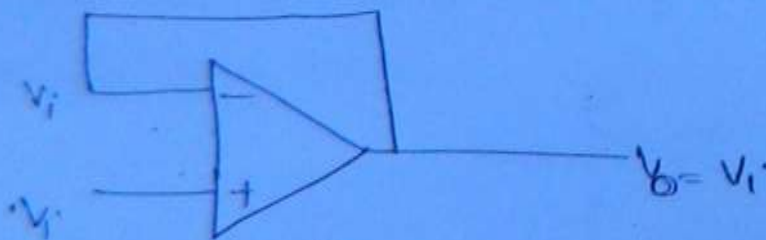


$$R_f = 0$$

$$R_i = \infty$$


Differential Amplifier →

(221)

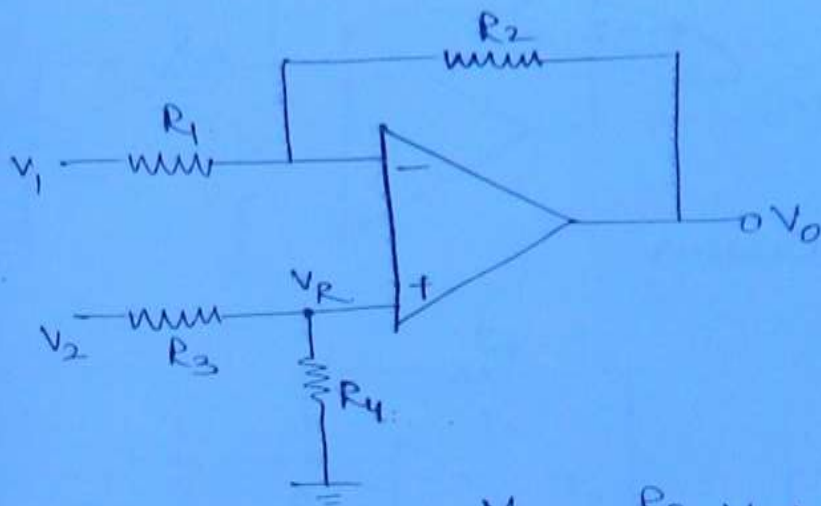

$$V_0 = -\frac{R_2}{R_1} V_1 + \left(1 + \frac{R_2}{R_1}\right) V_R$$

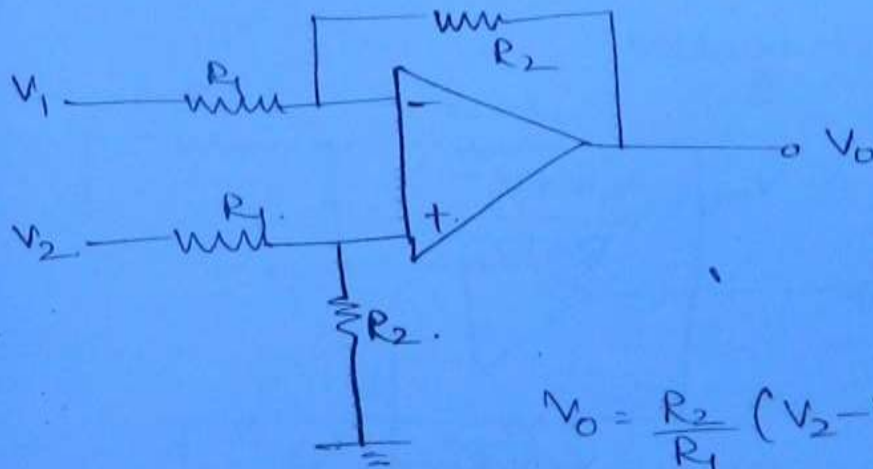
$$V_R = \frac{V_2 \times R_4}{R_3 + R_4}$$



$$V_0 = \frac{R_2}{R_1} (V_2 - V_1)$$

if $R_2 = R_1$, $V_0 = V_2 - V_1 \rightarrow$ Subtractor.

Inverting adder →

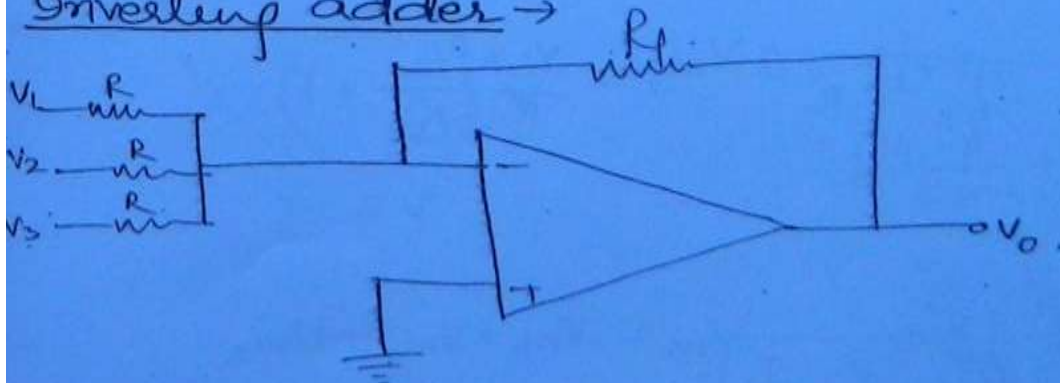

$$I = I_f = -$$

$$I_1 + I_2 + I_3 = I_f$$


$$\Rightarrow \frac{(V_1 + V_2 + V_3)}{R} = -\frac{V_0}{R_0}$$

$$\Rightarrow \boxed{V_0 = -(V_1 + V_2 + V_3)}$$

222

Non inverting adder \rightarrow


Case 1.

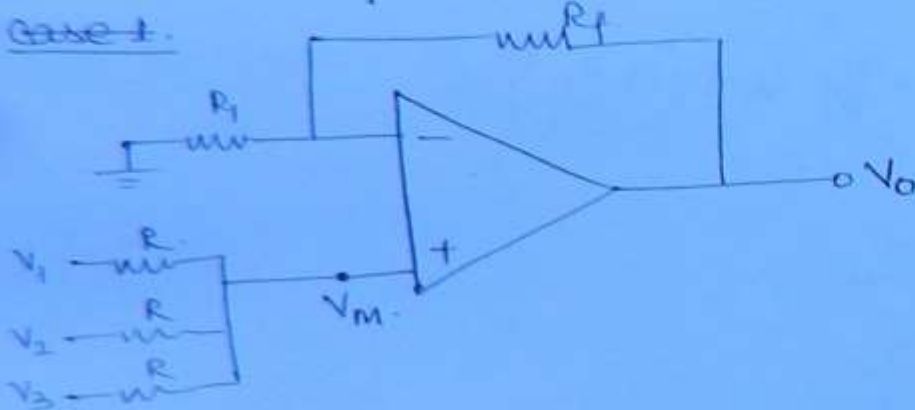


Case 1.



Case 2.

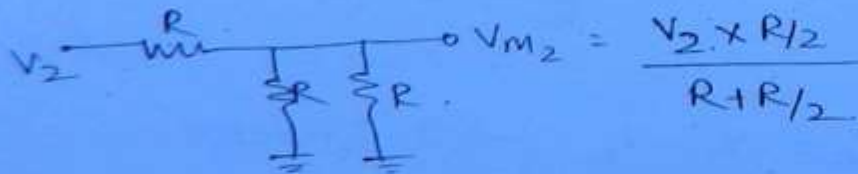


Case 3.

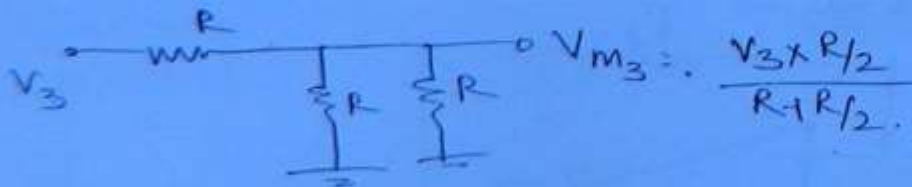


$$V_0 = \left(1 + \frac{R_f}{R_1}\right) V_m$$


$$V_m = V_{m1} + V_{m2} + V_{m3}$$

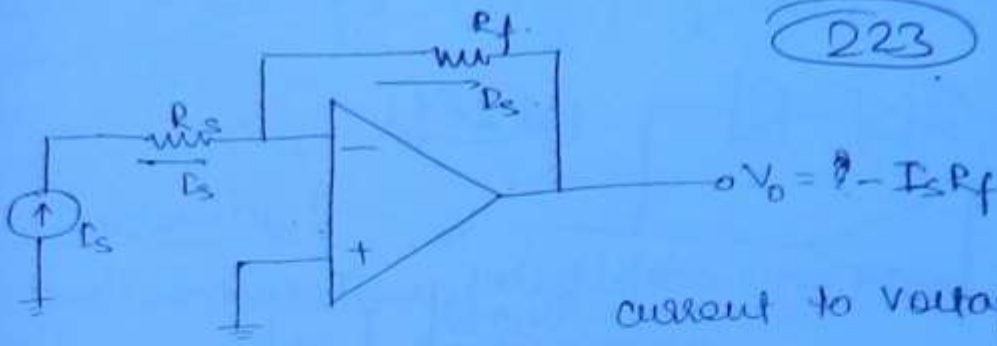

current to voltage converter

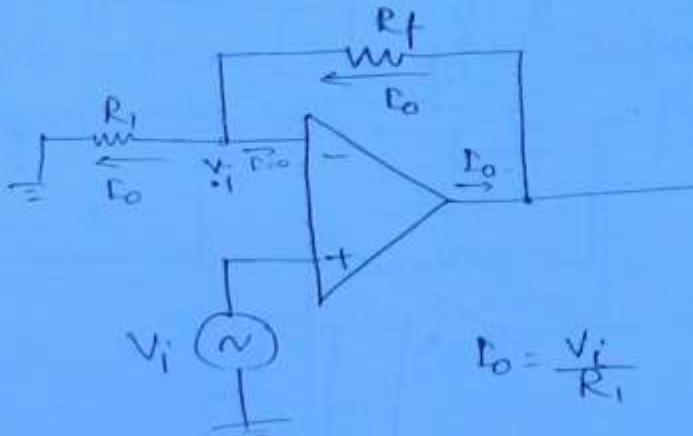

voltage to current converter

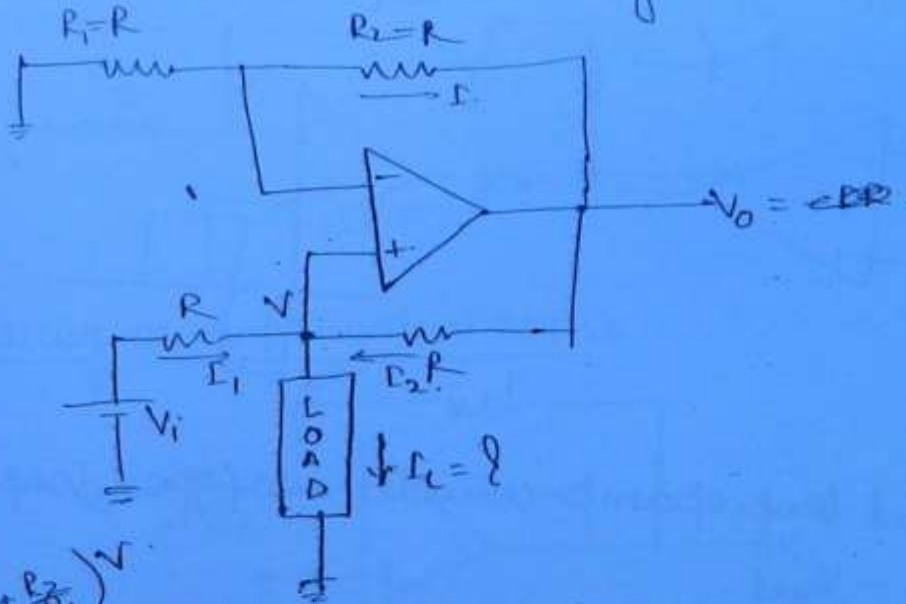

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V$$

$$V_o = \left(1 + \frac{R}{R}\right) V$$

$$= 2V$$

$$I_L = I_1 + I_2$$




$$= \frac{V_i - V}{R} + \frac{V_o - V}{R}$$

$$= \frac{V_i}{R} - \frac{V}{R} + \frac{2V - V}{R}$$

$$I_L = \frac{V_i}{R}$$


Voltage limiters

(224)

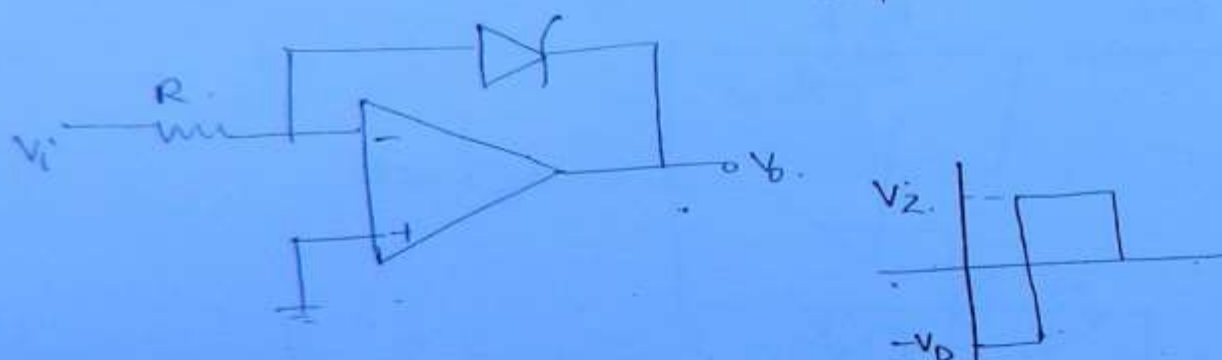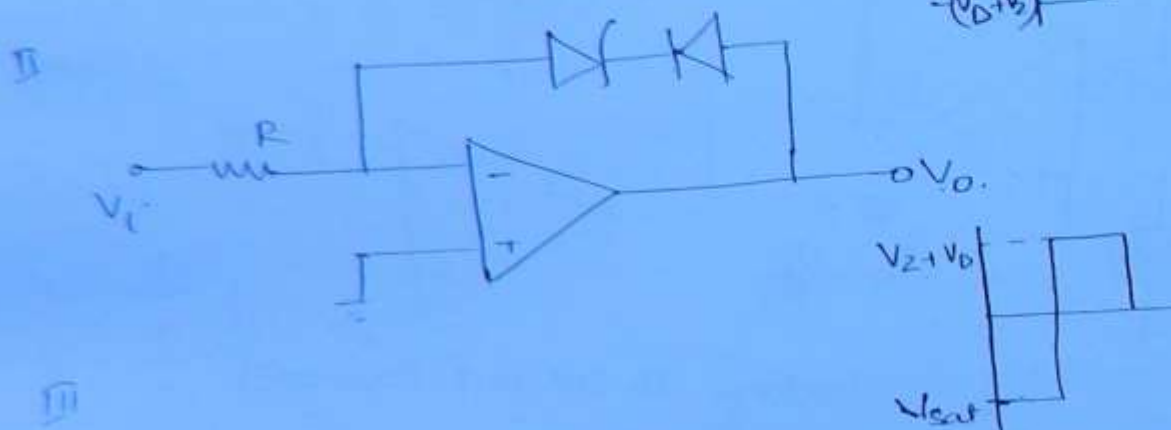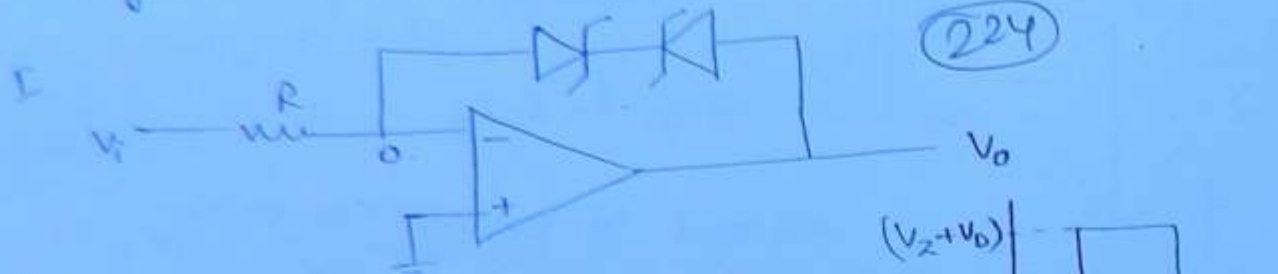

whenever a closed loop opamp converts into open loop
Op will be $+V_{sat}$ or $-V_{sat}$

Instrumentational amplifier →

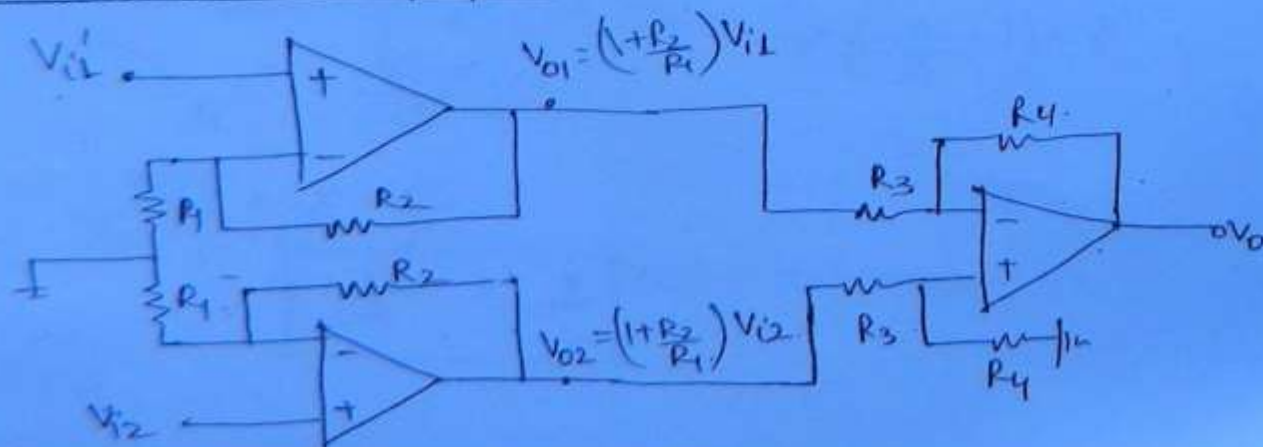

$$-V_o = \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) (V_{i2} - V_{i1})$$

$$V_{i2} - V_{i1} = V_d$$

(225)


Conclusion: —

Instrumentational amplifiers are used to improve

1) Differential voltage gain.

2) to improve the input impedance of differential amplifier

Logarithmic ckt →

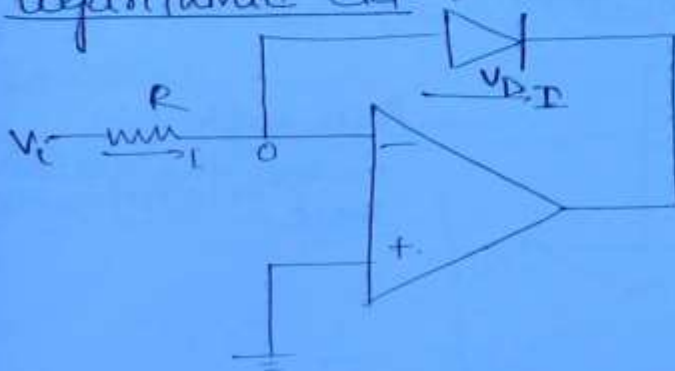

$$0 - V_o = -V_D$$

$$0 - V_o = V_D$$

$$V_o = -V_D$$


$$I = I_0 (e^{V_D / nV_T} - 1)$$

But FB,


$$V_D = nV_T \ln \left(\frac{I}{I_0} \right)$$

$$V_o = -nV_T \ln \left(\frac{I}{I_0} \right)$$

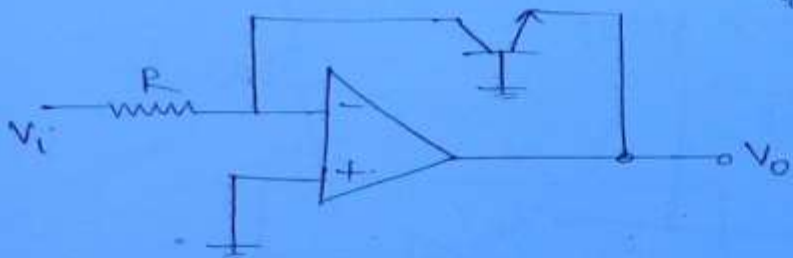
$$V_o = -nV_T \ln \left(\frac{I_0 R}{V_i} \right) \quad I_0 = \frac{V_i}{R}$$



Antilog or exponential ckt →

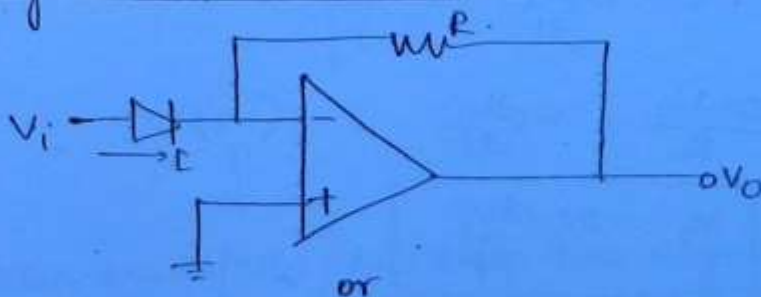


or

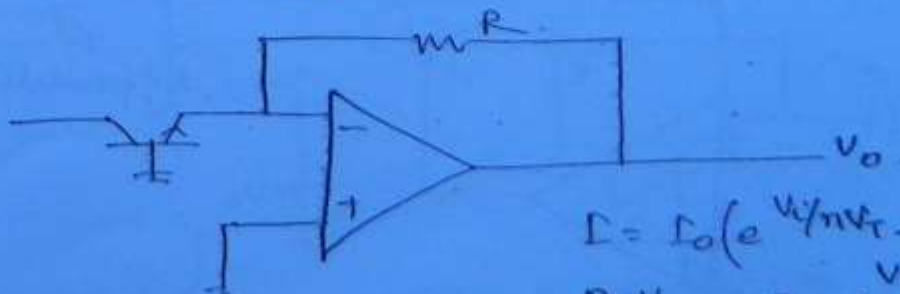

$$I = I_0 (e^{V_i / nV_T} - 1)$$

$$0 - V_o = I_0 R e^{V_i / nV_T}$$

$$V_o = -I_0 R e^{V_i / nV_T}$$

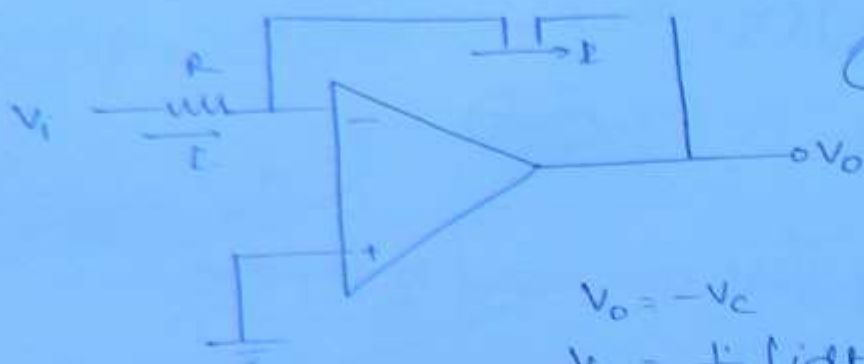


226 -
 \Rightarrow Integrator

$$V_o = -V_c$$


$$V_c = \frac{1}{C} \int i dt$$

$$V_o = -\frac{1}{RC} \int V_i dt$$

$RC \rightarrow$ time const.

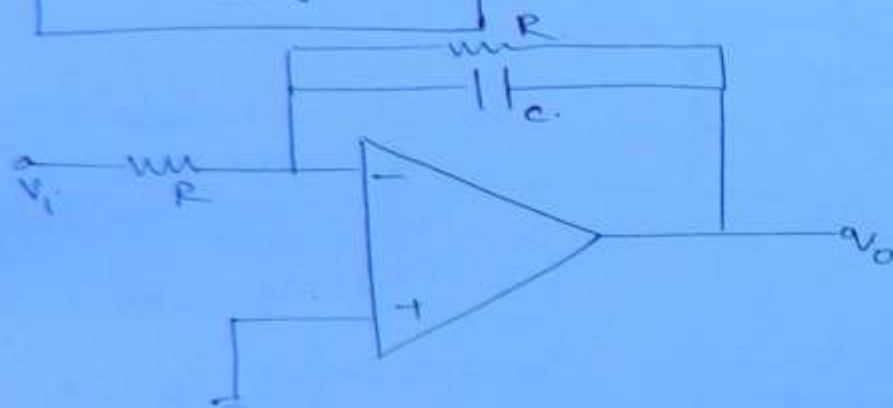


R is added to
 make the stability
 more.

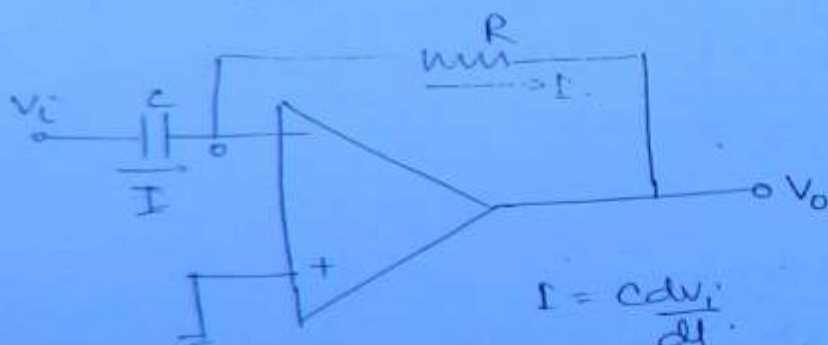

$$I = C \frac{dV_i}{dt}$$

$$\frac{0 - V_o}{R} = C \frac{dV_i}{dt}$$
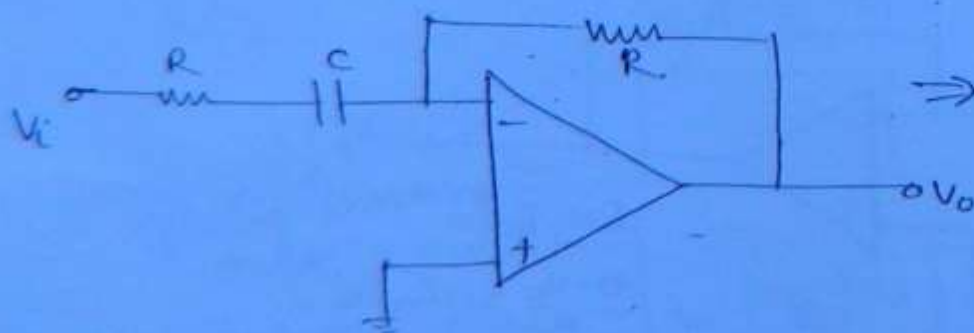
$$\Rightarrow V_o = -RC \frac{dV_i}{dt}$$



\Rightarrow differentiator.

Integrator →


For practical integrator, we take resistor shunt to the capacitor because at low freq, capacitor becomes O.C. which make the opamp to work in open loop system.

Differentiator:—

At the I/P resistor is in the series with the capacitor because at high freq capacitor acts as a S.C. High current flow through the device which creates a problem.


Precision rectifier →

when $V_i < 0.7$

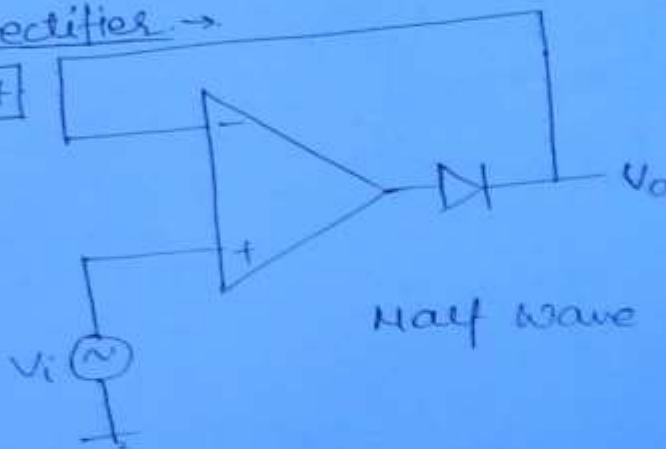


the half cycle,
D is F.B.

Half wave rectifier.

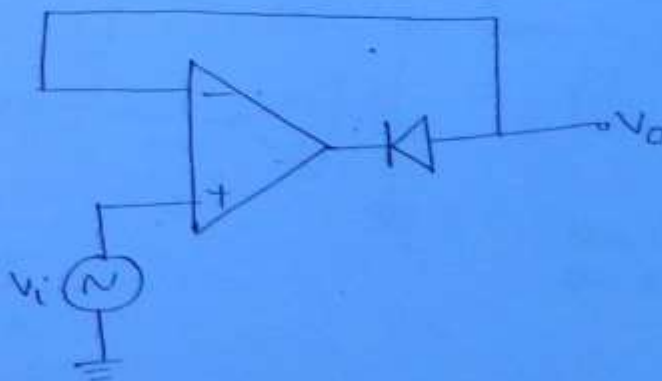


for -ive half cycle,
D is R.B.

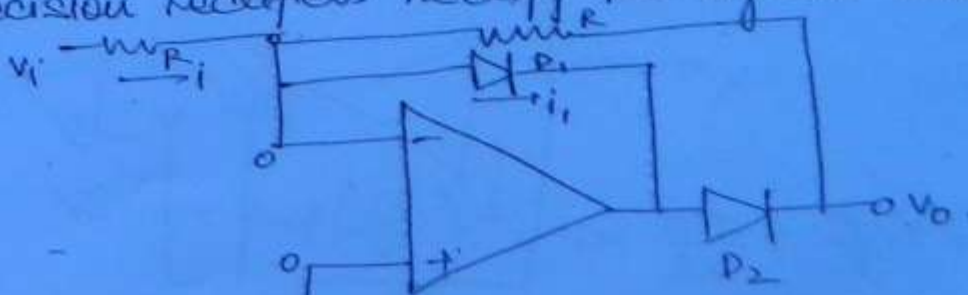Precision rectifiers rectify the signals below 0.7 Volts.




for +ive half,
for -ive half,

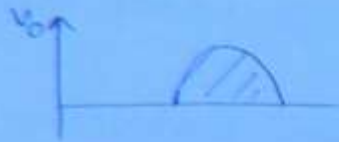$V_o = V_i$ for +ive half,
 $V_o = -V_i$ for -ive half




228

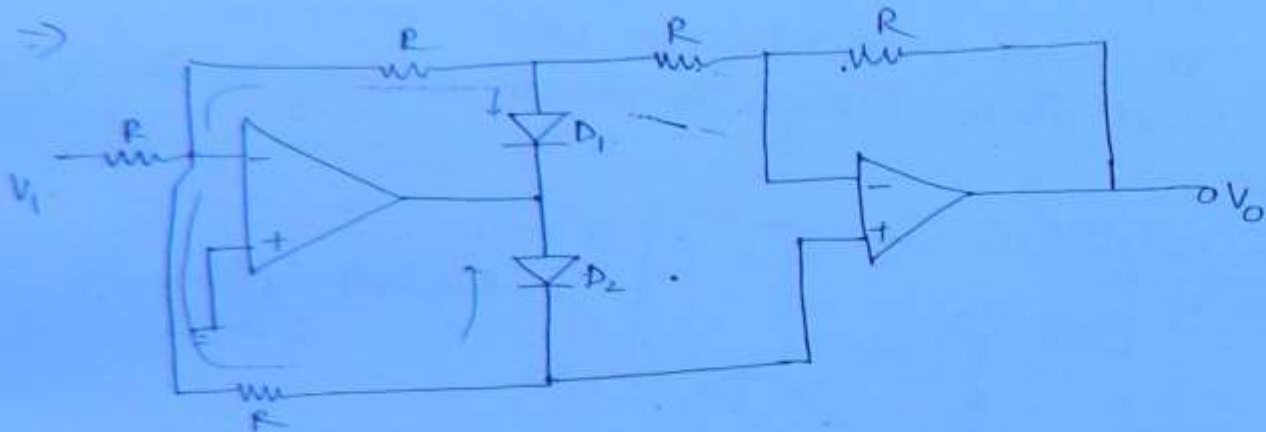

Positive half cycle →

$D_1 \rightarrow F.B.$

$D_2 \rightarrow R.B.$

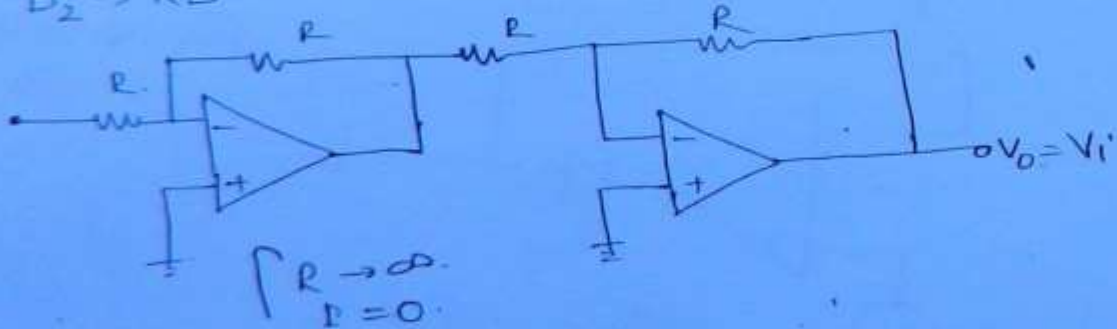


Negative half cycle →


$D_1 \rightarrow R.B.$

$D_2 \rightarrow F.B.$

$$\frac{V_i - 0}{R} + \frac{V - 0}{R} + \frac{V - 0}{2R} = 0$$

$$V = -\frac{2}{3} V_i$$

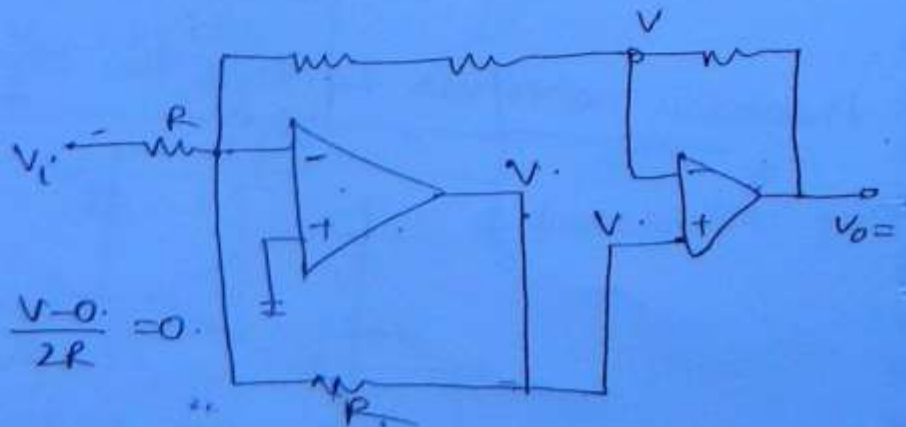

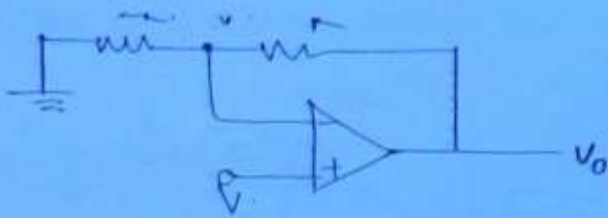



229

$$V_o = \left(1 + \frac{R}{2R}\right) V$$

$$= \frac{3}{2} V$$

$$= \frac{3}{2} \times \left(-\frac{2}{3}\right) V_i$$

$$= -V_i$$

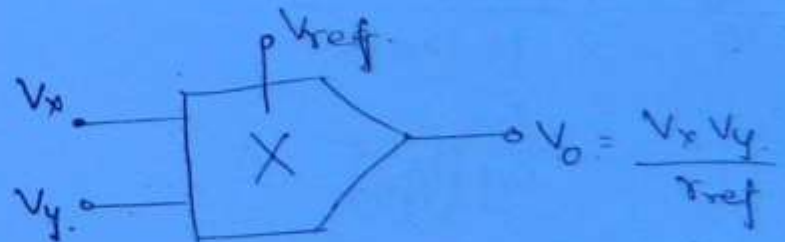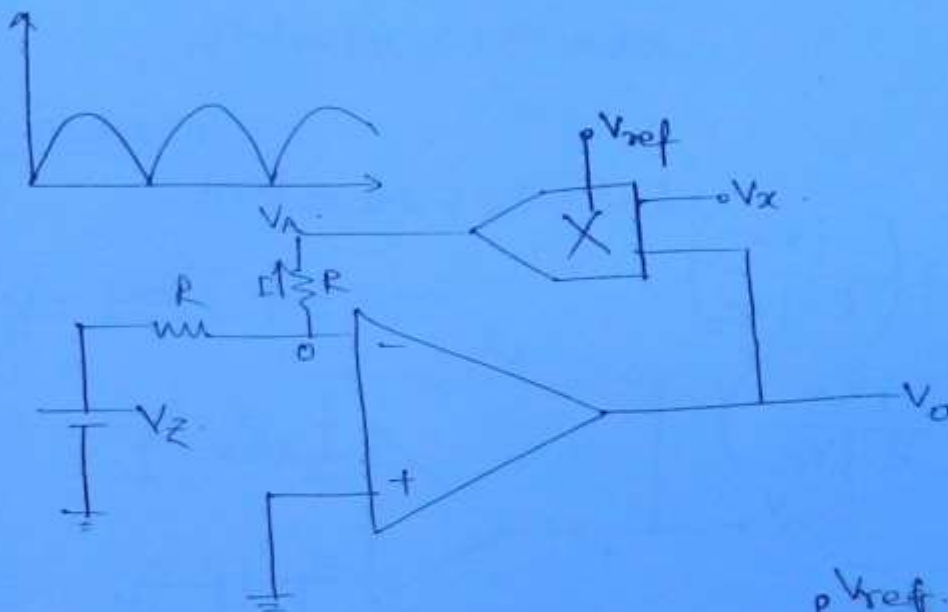


$$V_A = \frac{V_x V_o}{V_{ref}}$$

$$\Rightarrow -IR = \frac{V_x V_o}{V_{ref}}$$

$$\Rightarrow -V_Z = \frac{V_x V_o}{V_{ref}}$$

$$V_o = -V_{ref} \left(\frac{V_Z}{V_x} \right)$$

active circuits →
low pass filters →

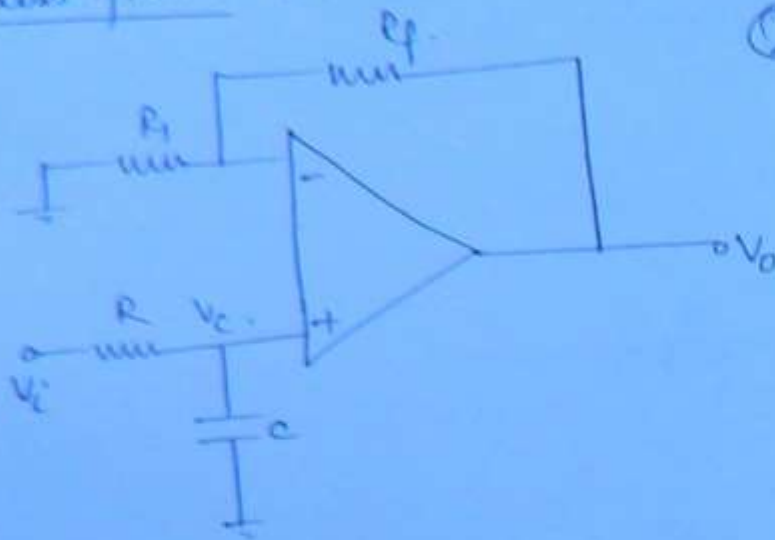

(230)

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_c$$



$$= \left(1 + \frac{R_f}{R_i}\right) V_i \times \left(\frac{-j\omega C}{R - j\omega C}\right)$$

$$\frac{V_o}{V_i} = \left(1 + \frac{R_f}{R_i}\right) \left(\frac{-j\omega C}{R - j\omega C}\right)$$


$$\frac{V_o}{V_i} = \frac{A_{cl}}{1 + j2\pi fRC}$$

$$= \frac{A_{cl}}{1 + j\left(\frac{f}{f_H}\right)}$$

$$f_H = \frac{1}{2\pi RC}$$

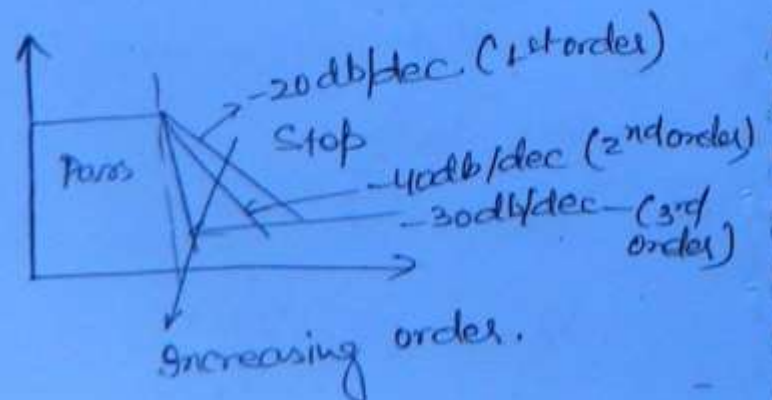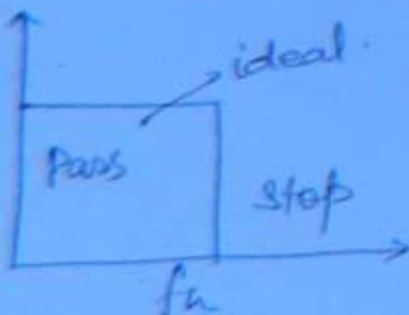

2nd order low pass filter →

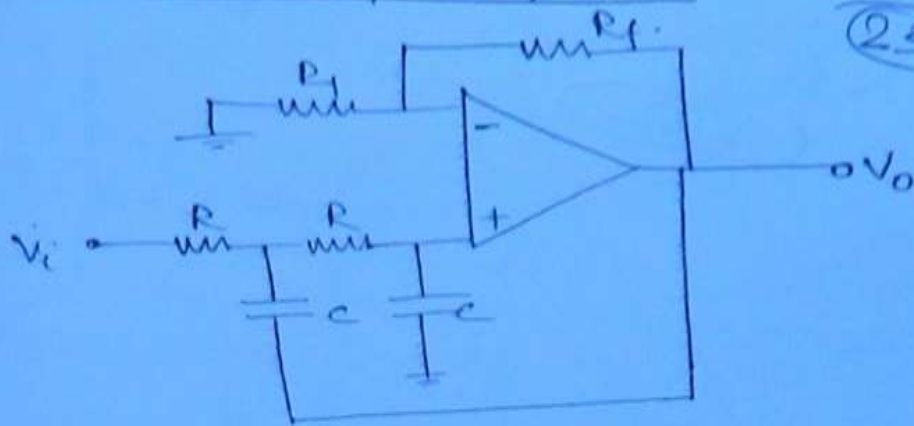

(231)


3rd order →

2nd order + 1st order

4th order →

2nd order + 2nd order

High pass filter →

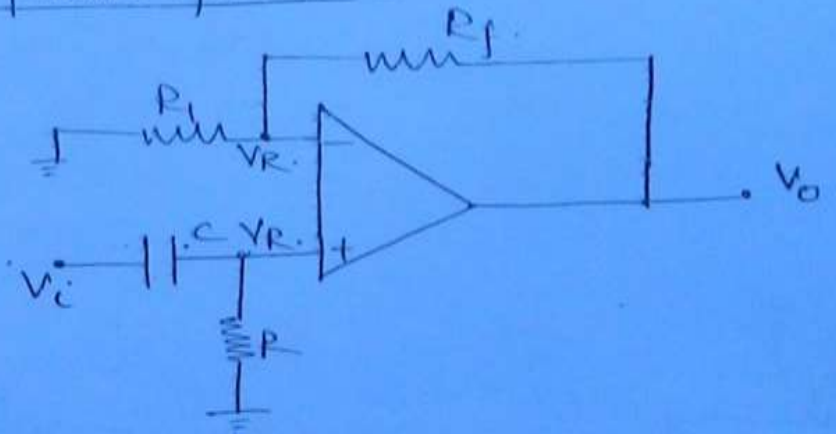


$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_R$$

$$= \left(1 + \frac{R_f}{R_1}\right) V_i \left(\frac{R}{R - jX_C}\right)$$


$$= \frac{A_{cl}}{1 - j(f/f_c)}$$

$$f_L = \frac{1}{2\pi RC}$$



232

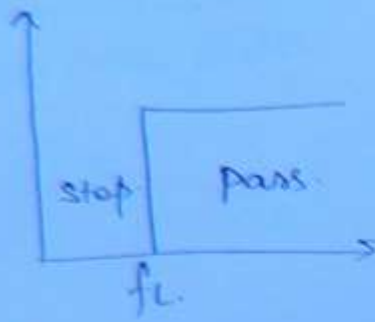

2nd order high pass →


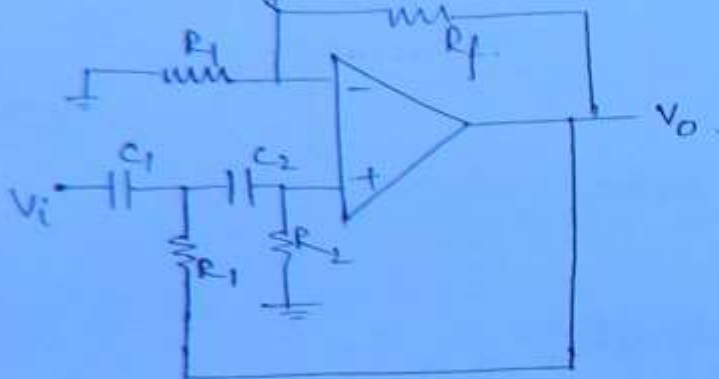


Band pass →

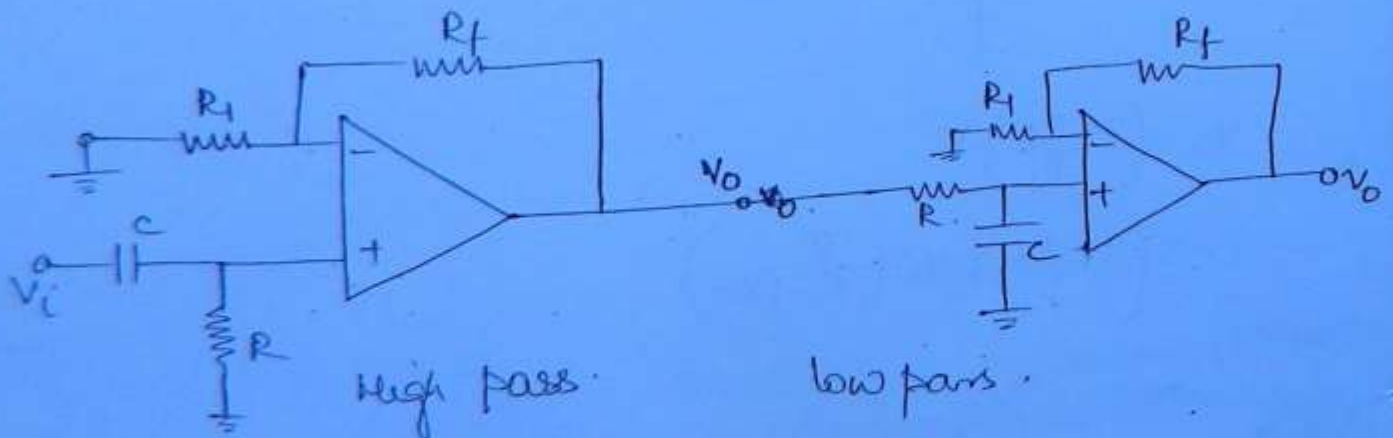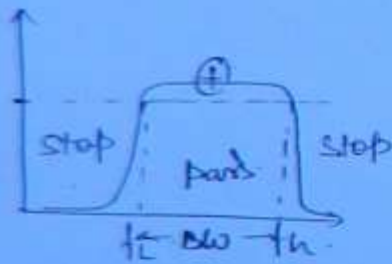


band reject \rightarrow


233

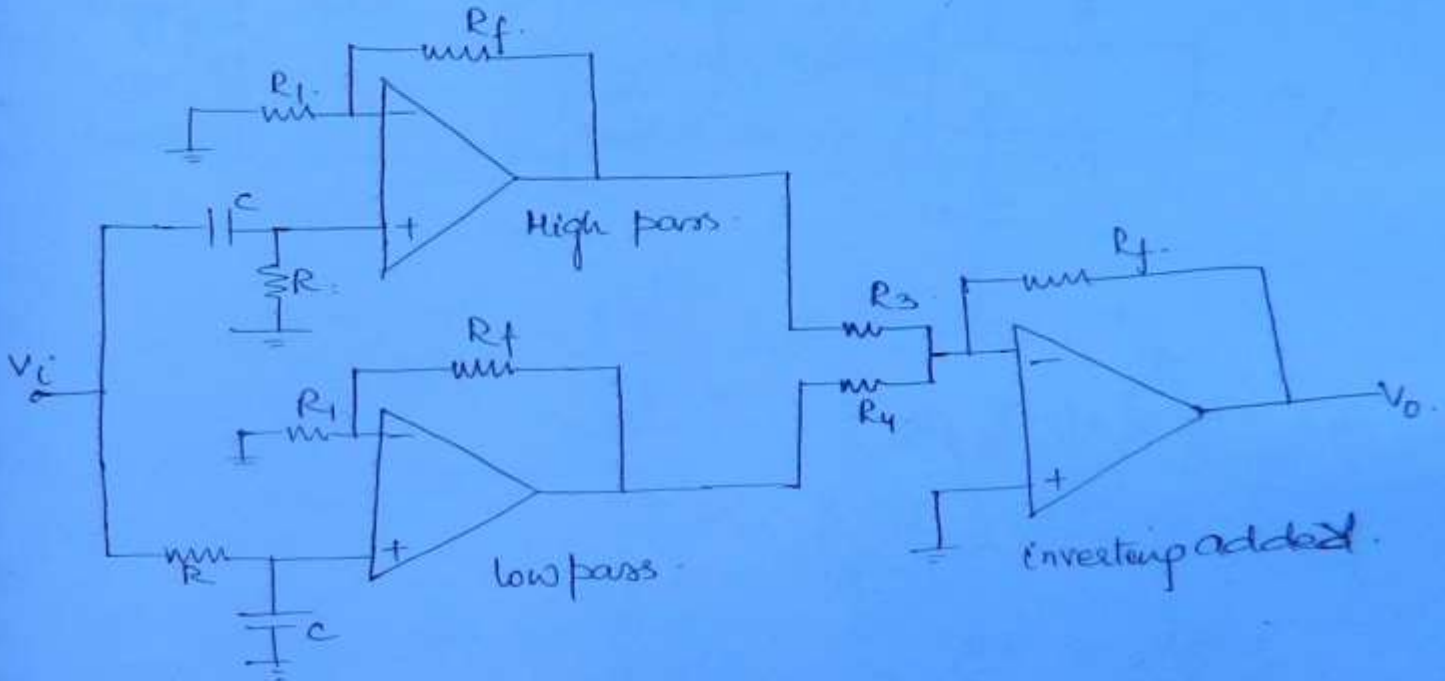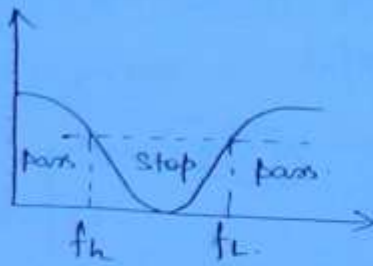

Notch filter \rightarrow

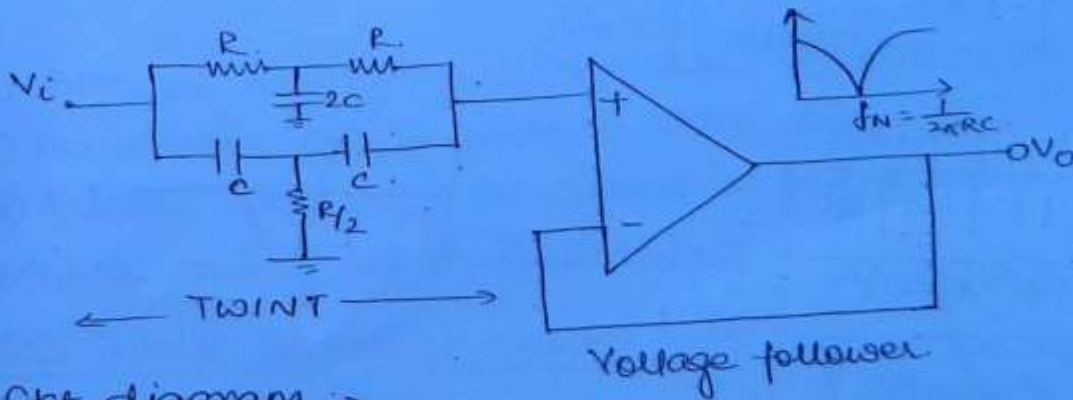


Ckt diagram \rightarrow

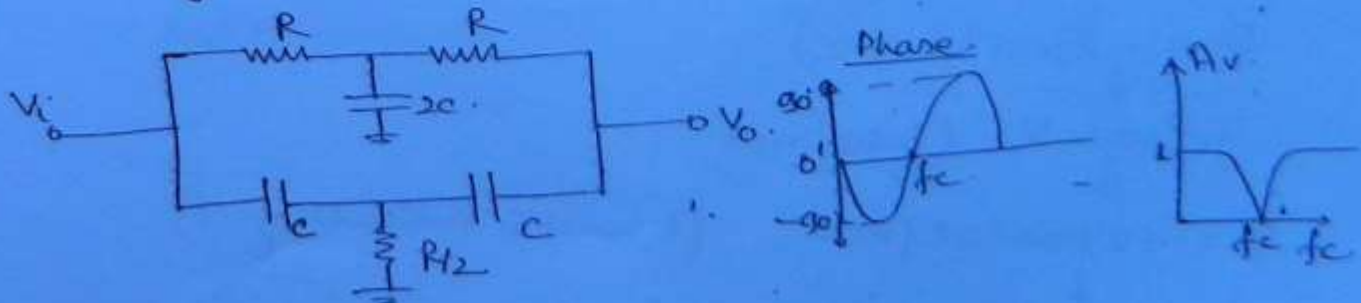

A voltage follower n/w is added to the twint n/w because to improve the quality factor of RC n/w.

All pass filter →


(234)

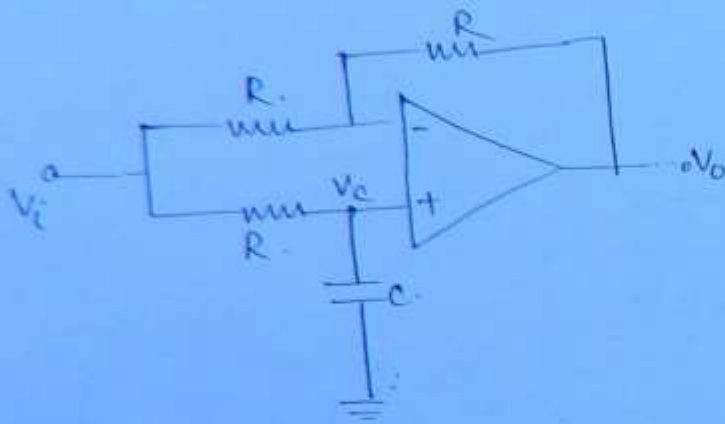

$$\begin{aligned}
 V_o &= -\frac{R}{R} V_i + \left(1 + \frac{R}{R}\right) V_c \\
 &= -V_i + 2V_i \left(\frac{-jX_c}{R - jX_c}\right) \\
 &= -V_i + \frac{2V_i}{1 + j2\pi fRC} \\
 &= V_i \left[-1 + \frac{2}{1 + j2\pi fRC}\right]
 \end{aligned}$$

$$\frac{V_o}{V_i} = \frac{1 - j2\pi fRC}{1 + j2\pi fRC}$$

$$\left|\frac{V_o}{V_i}\right| = \frac{\sqrt{1 + (2\pi fRC)^2}}{\sqrt{1 + (2\pi fRC)^2}} = 1$$

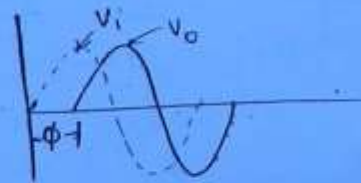

$$\phi = -2 \tan^{-1}(2\pi fRC)$$


↓
Vo lags Vi (low pass)

$$\phi = +2 \tan^{-1} 2\pi fRC \quad (\text{R and C is interchanged})$$

↓
Vo leads Vi (high pass)

Whenever time delay is required.


285

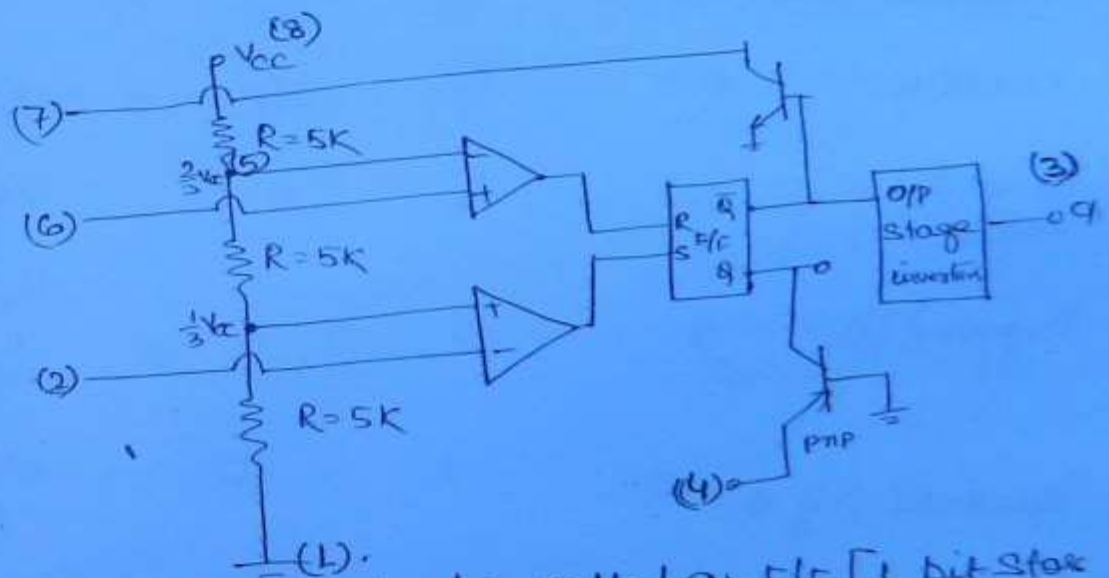

- ### 555 timer operating modes:—

- © Wiki Engineering



monostable

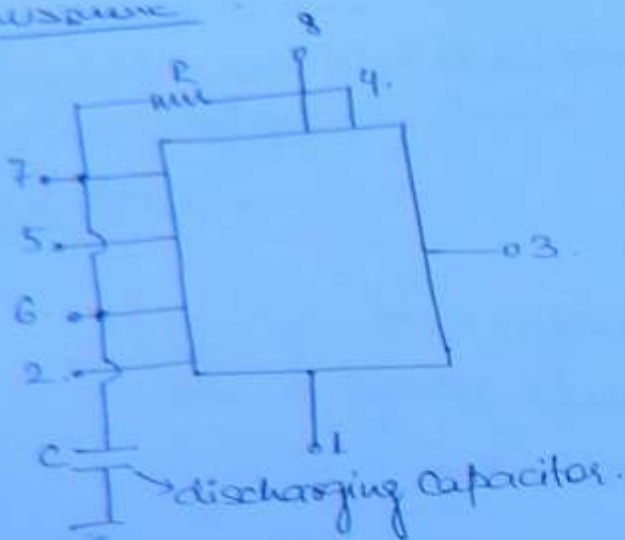

236

tabular form →

condition	Q	\bar{Q}	Q/P	capacitor position
stand by mode	0	1	0	discharging (stable)
Trigger $< \frac{1}{3} V_{cc}$	1	0	1	[because transition is in sat.] charging (quasi)
threshold $> \frac{2}{3} V_{cc}$	0	1	0	discharging (stable)

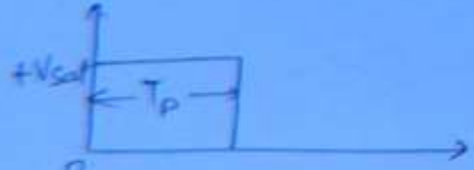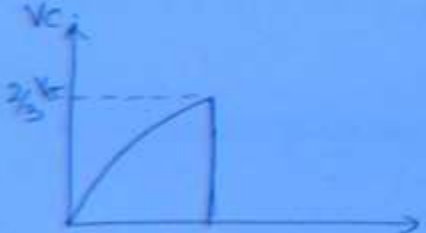

$$V_c = V(1 - e^{-t/RC})$$


$$\frac{2}{3} V_{cc} = V_{cc}(1 - e^{-t_p/RC})$$

$$t_p = 1.1RC$$

R will be fixed always = ?


Astable →

(237)

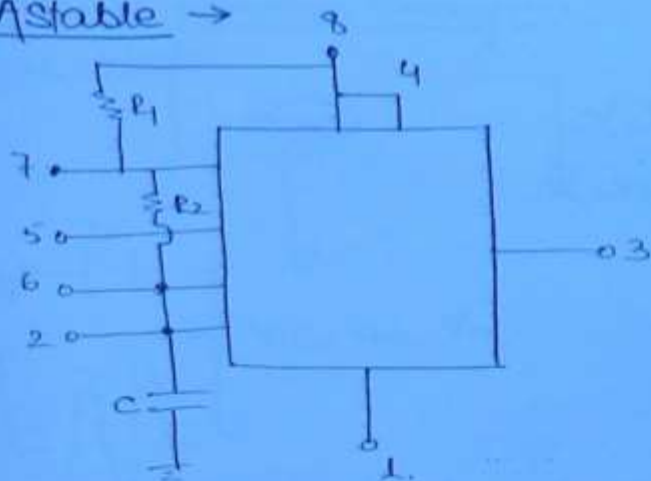

tabular form →

condition	Q	\bar{Q}	O/P	capacitor position
standby	0	1	0	discharging (stable)
trigger $< \frac{1}{3} V_{cc}$ (capacitor)	1	0	1	charging (Quasi)
threshold $> \frac{2}{3} V_{cc}$	0	1	0	discharging (Quasi)

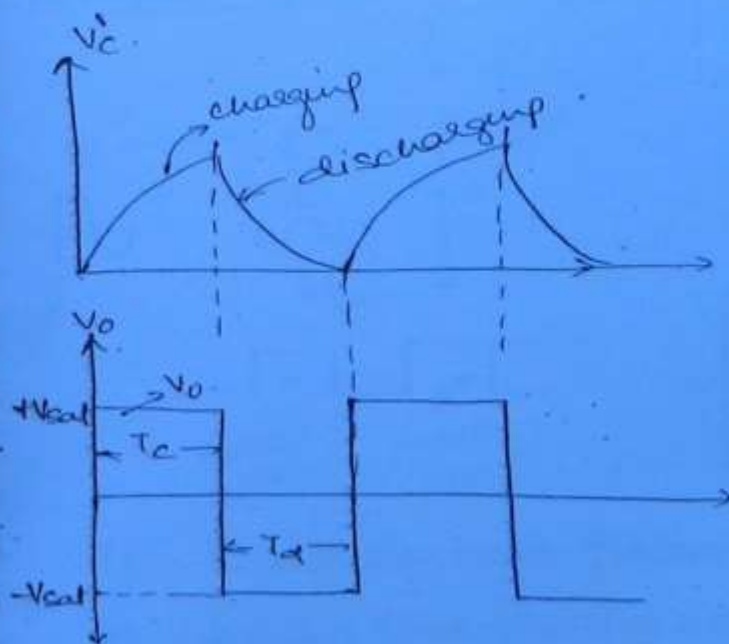

$$T_c = 0.69 (R_1 + R_2) C$$

$$T_d = 0.69 R_2 C$$

$$T = T_c + T_d = 0.69 (R_1 + 2R_2) C$$

Duty cycle =


$$\begin{aligned} & \frac{T_o + T_d}{0.69(R_1 + R_2)C} \\ & = \frac{0.69(R_1 + R_2)C}{0.69(R_1 + 2R_2)C} \\ & = \frac{R_1 + R_2}{R_1 + 2R_2} \end{aligned}$$

(238)

$$f = \frac{1}{T} = \frac{1}{0.69(R_1 + 2R_2)C}$$

Q Design a stable multivibrator to generate square wave oscillation.

for duty cycle = 50%.

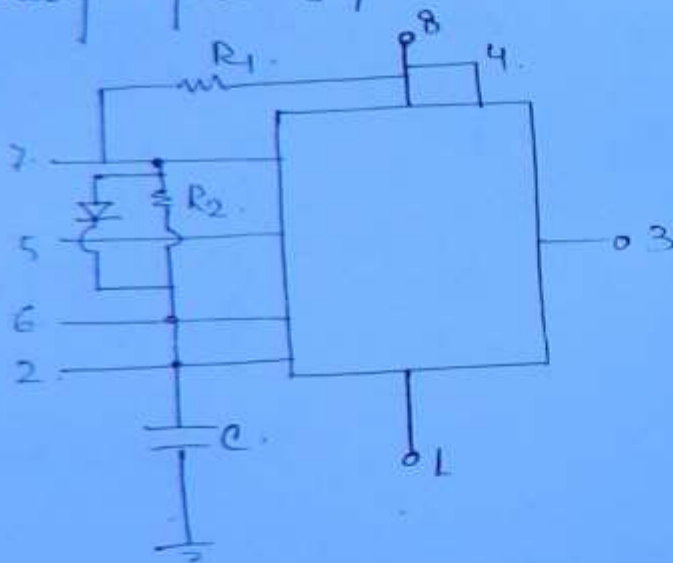

$$D.C. = \frac{R_1}{R_1 + R_2}$$



$$R_1 = R_2 = R$$

$$D.C. = 50\%$$




Special opamp design.

Peak detector

(239)

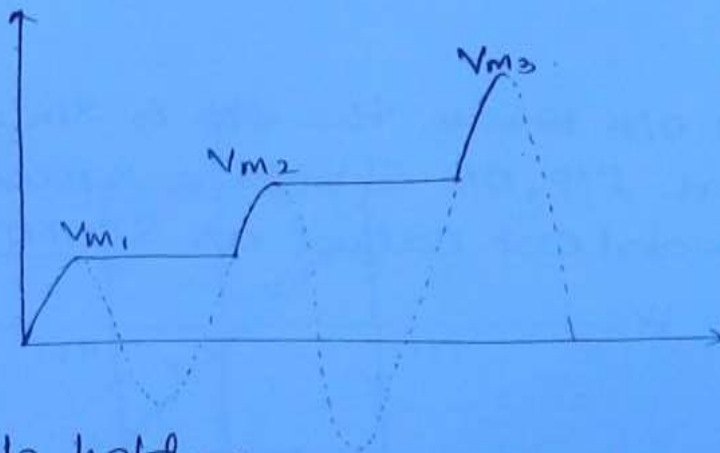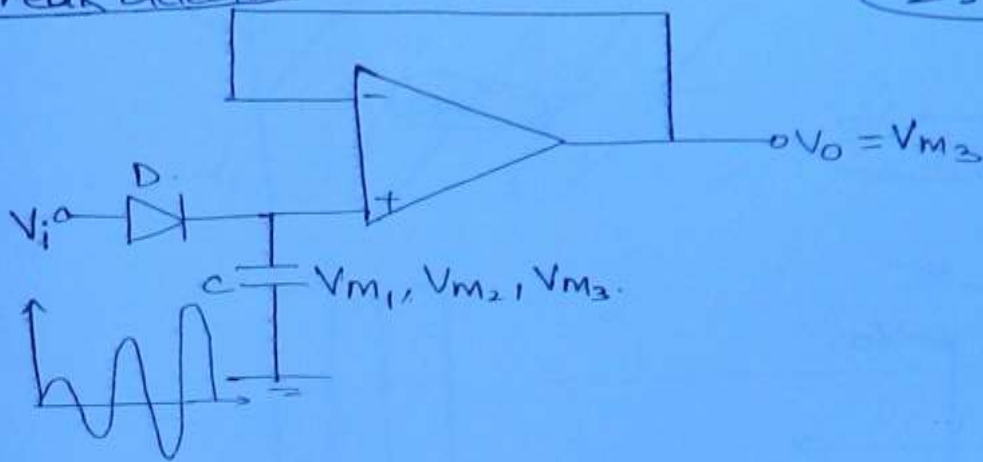


Sample hold →

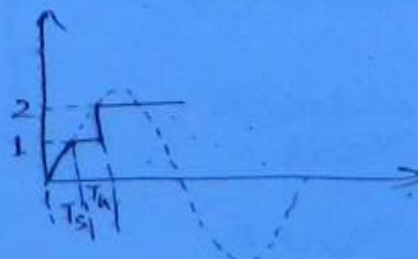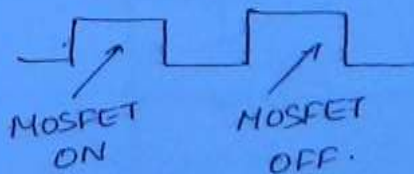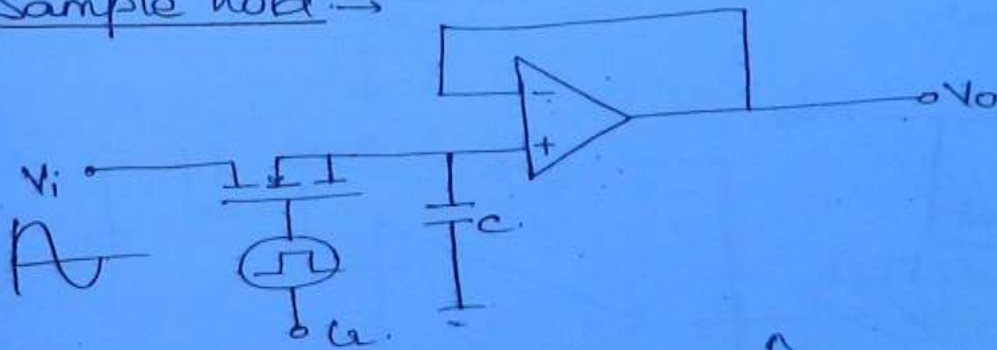


$T_s \rightarrow$ Sampling time [MOSFET ON]

$T_h \rightarrow$ holding time [MOSFET OFF].

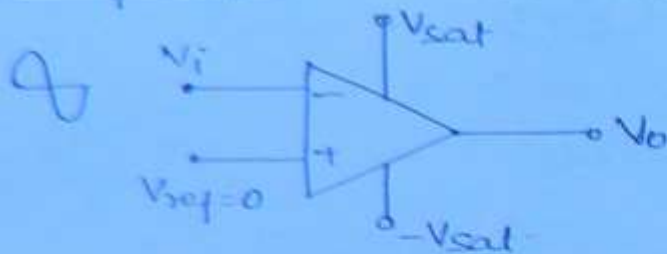comparator → ZCD → zero crossing detector




(240)

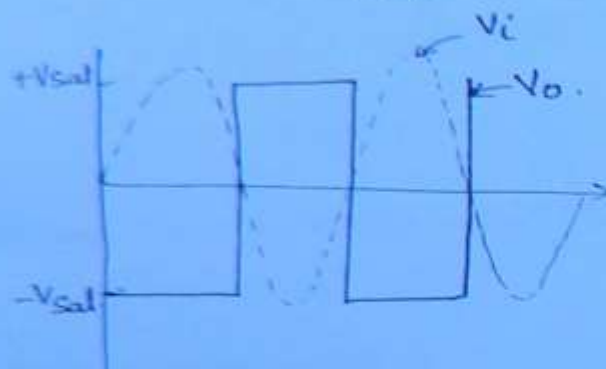

ZCD can give square wave O/P when the I/P is sinusoidal signal. But for any irregular I/P, O/P should be square wave. It is possible with a special CKT called as SCHMITT TRIGGER.

SCHMITT TRIGGER →



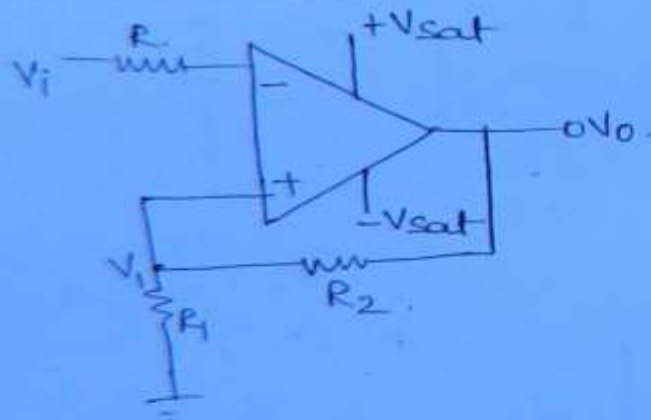


Assume $V_o = +V_{sat}$


[UTP] $V_1 = \frac{V_{sat} R_1}{R_1 + R_2}$
Upper trigger pt design


$V_o = -V_{sat}$

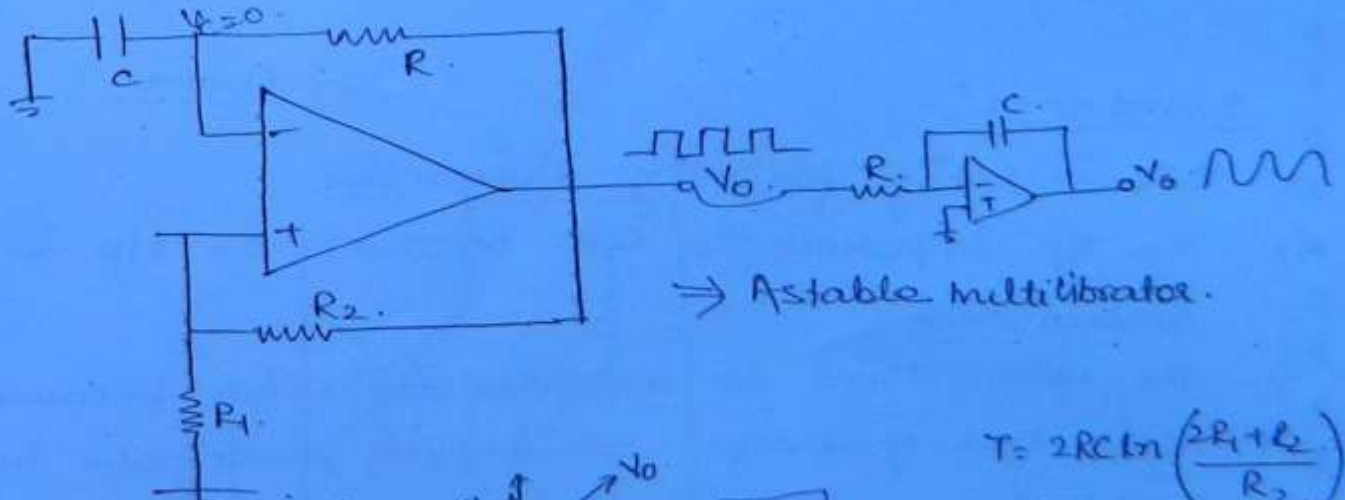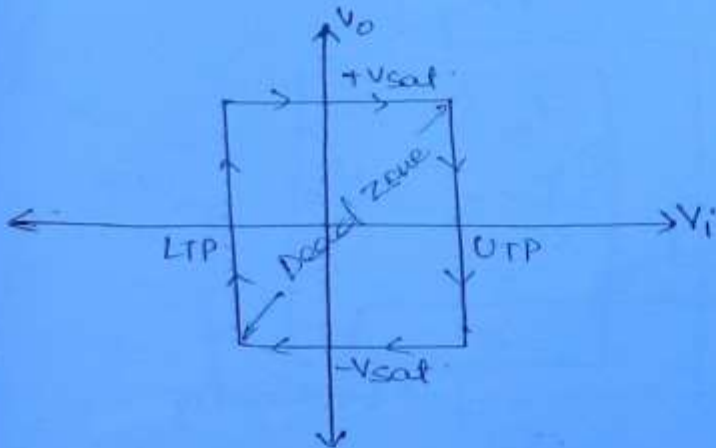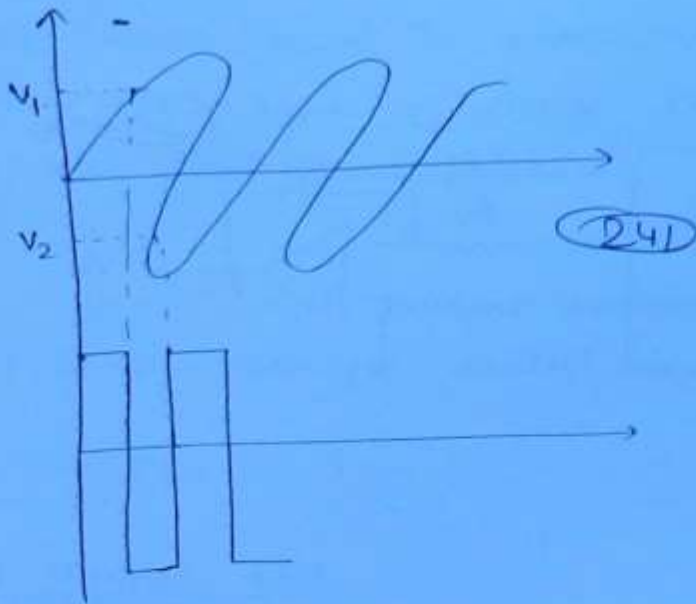$V_2 = \frac{-V_{sat} \times R_1}{R_1 + R_2}$
LTP




$V_C > UTP$, discharging.

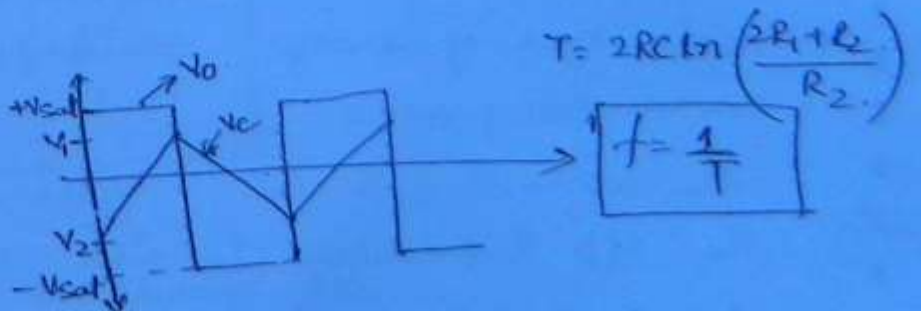

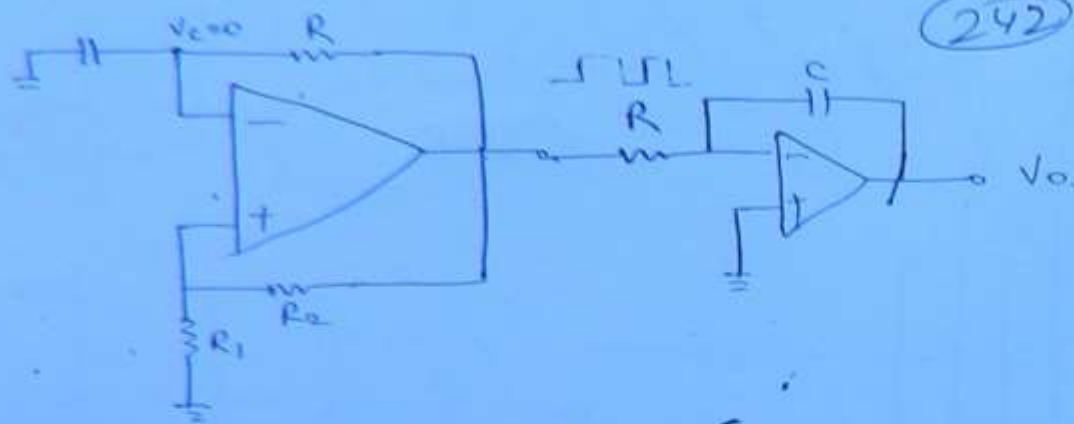

17/1/2012

FET :-

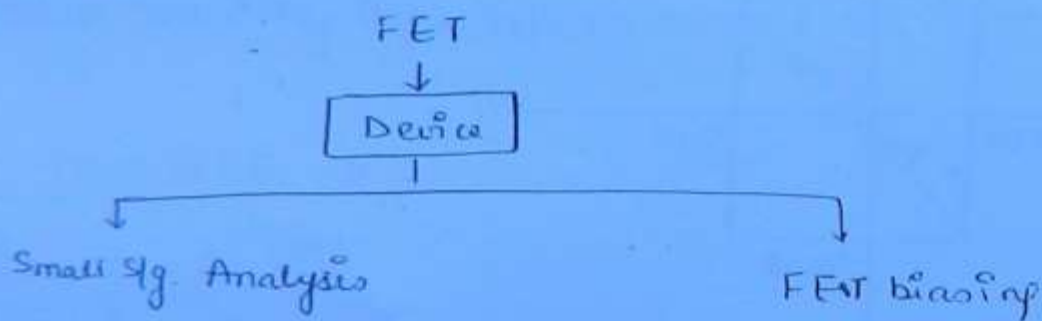

Introduction :-

- BJT is having following disadvantage.
- i) The I/p impedance is low because the I/p is forward bias.
 - ii) The noise level is comparatively high because both type of charge carriers will participate in the conduction process.

The advantage of FET compared to BJT is as follows.

- i) The I/p impedance is high because the I/p is always operated with reverse bias.

- i). The noise level is comparatively low because only one type of charge carrier will participate in the conduction process.



(243)

Note:-



BJT is a current control device whereas FET is a voltage control device.

Types of FET:-

1) n channel FET.

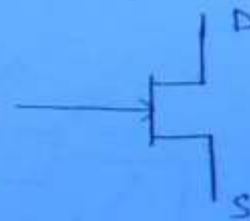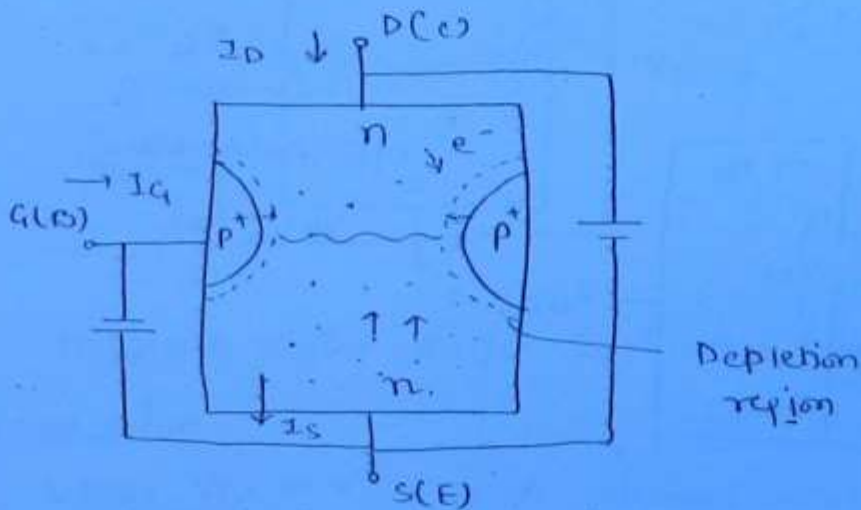

2) P channel FET:-

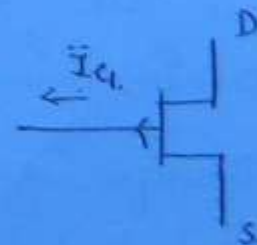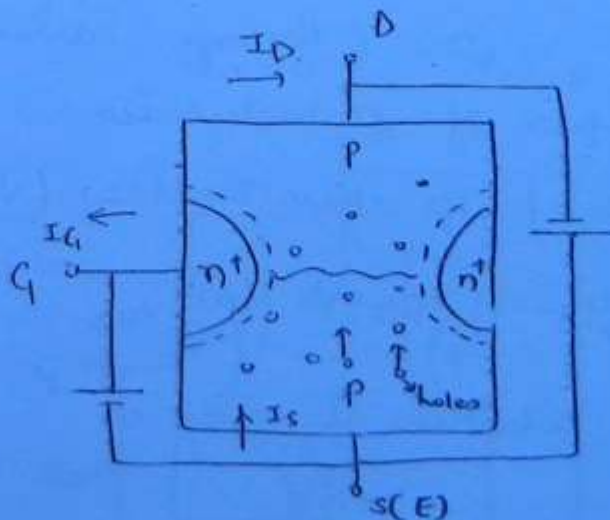


Note:-

Drain should be always RB.

Symbol and relations :-

1) N-Channel FET

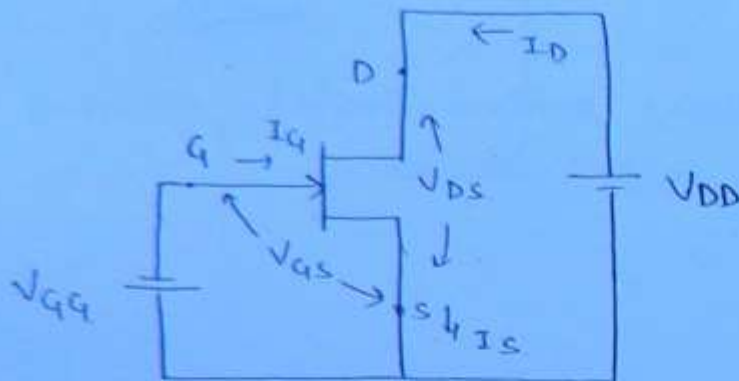

(244)

$$\left. \begin{array}{l} V_{GG} = -ve. \\ I_D \\ V_{DS} \end{array} \right\} = +ve.$$


I/p parameters -

$$V_{GS}, I_G = 0.$$

o/p parameter

$$V_{DS}, I_D.$$

2) P-Channel FET :-

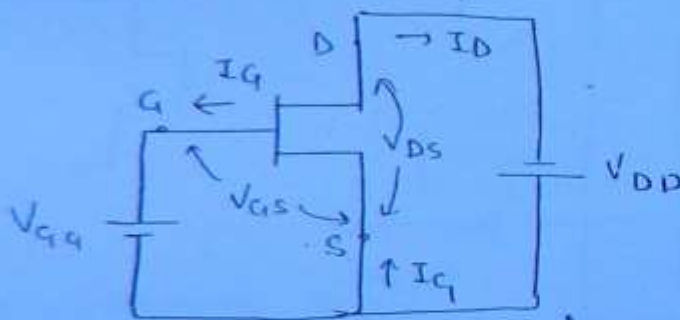

Conclusion :-

1) There will be no I/P characteristics in FET, because I_G is approximately $= 0$. (leakage current)

2) There are two types of characteristics.

i) Drain characteristics / o/p characteristics $(-V_{DS} \text{ vs } I_D) |_{V_{GS}}$

ii) Transfer characteristics $(V_{GS} \text{ vs } I_D) |_{V_{DS}}$

In N-channel, the polarities are given as.

$$V_{GS} = -ve$$

$$\left. \begin{array}{l} I_D \\ V_{DS} \end{array} \right\} = +ve.$$

In P-channel the polarities are given as -

$$V_{GS} = +ve$$


(245)

$$\left. \begin{matrix} I_D \\ V_{DS} \end{matrix} \right\} = -ve.$$

Working principle :- FET :-

Case-1 :-

$$V_{GS} = 0V, V_{DS} = 0V.$$

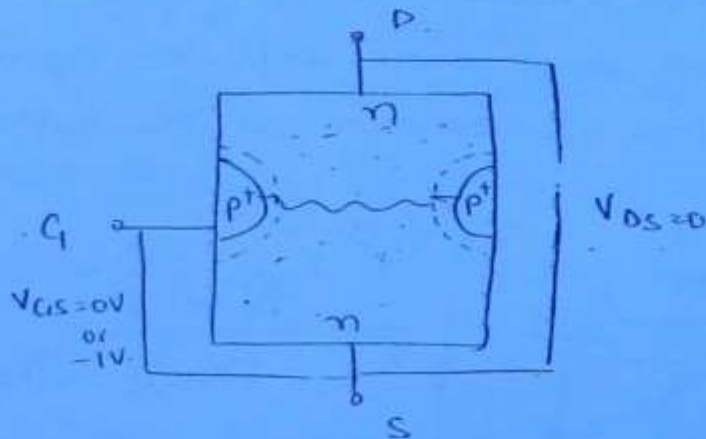


Depletion region layer is ↑. then region ↓

Conclusion :-


- 1) When $V_{GS} = 0V$ max. channel can be achieved.
- 2) When $V_{DS} = 0V$ Drain current I_D becomes 0.

Case-2 :-

$$V_{GS} = 0V, V_{DS} \neq 0V.$$

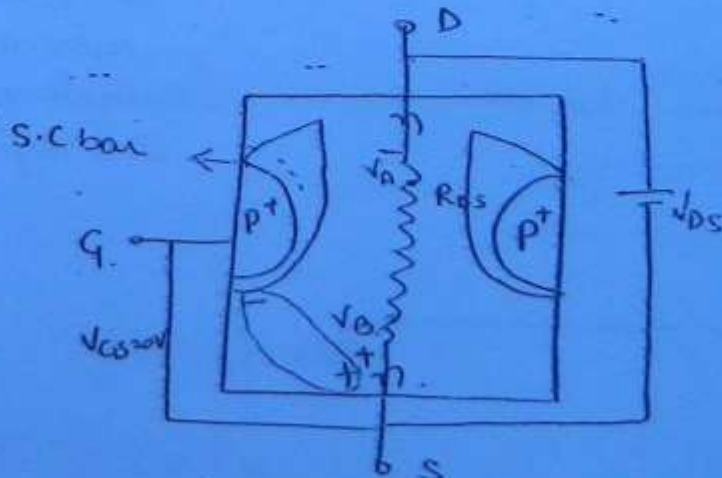

$$V_{DS} \propto I_D$$

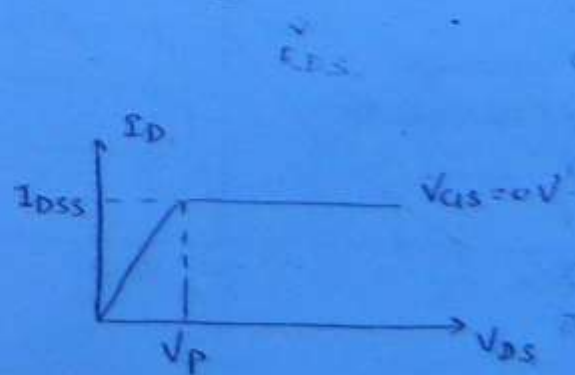

I_{DSS} = Short ckt Drain current


Conclusion of Q3:-

- 1) When $V_{GS} = 0V$ max. channel can be achieved.
- 2) When $V_{GS} \neq 0V$ the ^{S.C} bar will act like a resistor.
($V_{DS} \propto I_D$)
- 3) The basic mechanism of FET is top side of the drain is covered with R. Bias & bottom side of the source is covered with F. Bias.
- 4) Due to the internal Reverse bias of gate to source the depletion region penetration will be more at the top side & less penetration at the bottom side.

(246)


Case-3:-

$V_{GS} \neq 0$ $V_{DS} \neq 0$

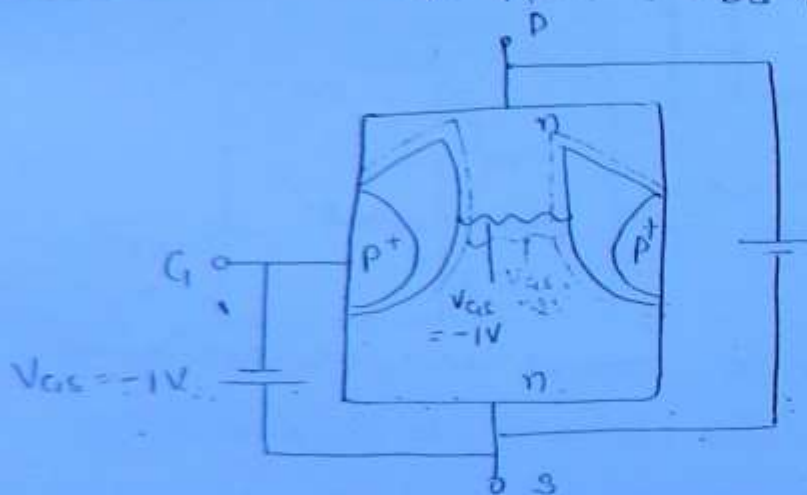

Q point-

$(V_{GS})_Q, (I_D)_Q$

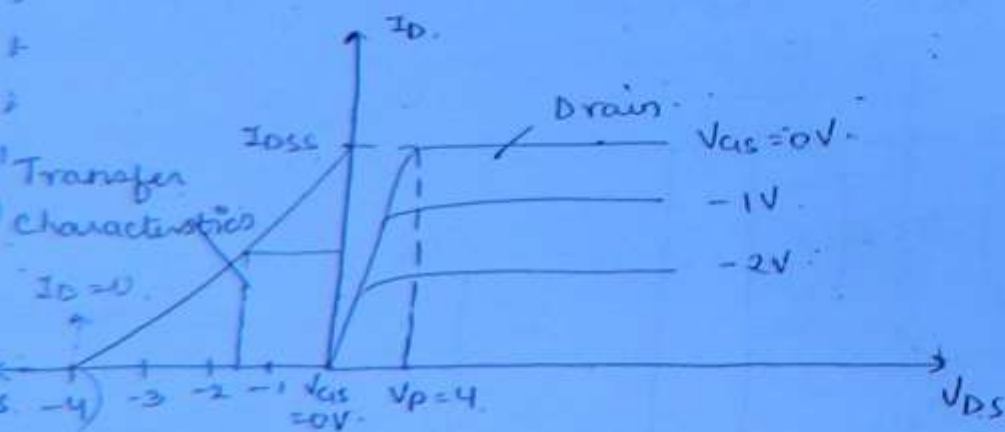

$(V_{GS}) = 0V$ means
no channel
current is 0.
Both penetration
will together

Transfer characteristics

$$I_D = I_{DS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$

(247)

$$|V_{GS}|_{\text{off}} = |V_P|$$

V_P = pinch off voltage & it depends on doping concentration

⇒ For FET device analysis we have to concentrate on transfer characteristics but not drain characteristic

⇒ In FET Biasing Q point is defined as $[V_{GS}Q, I_{DQ}]$

FET is always thermally stable that means I_D is independent of temperature.

FET Parameters :-

$\Delta V_{GS}, \Delta V_{DS}, \Delta I_D$

1). AC drain resistance

$$r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{V_{GS}}$$

2). Transconductance

$$g_m = \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_{V_{DS}}$$

3). Amplification factor

$$\mu = \left. \frac{\Delta V_{DS}}{\Delta V_{GS}} \right|_{I_D}$$

$$\mu = g_m r_d$$

$$r_d > R_D$$

Expressions for transconductance g_m

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

(248)

$$= \frac{\partial I_{DSS}}{\partial V_{GS}} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$

$$g_m = - \frac{\partial I_{DSS}}{\partial V_P} \left[1 - \frac{V_{GS}}{V_P} \right]$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_P} \right]$$

$$g_{m0} = - \frac{\partial I_{DSS}}{\partial V_P}$$

↓
max. transconductance.

Prove $g_m = \frac{2}{|V_P|} \sqrt{I_D - I_{DSS}}$

Sol:

$$g_m = - \frac{\partial I_{DSS}}{\partial V_P} \left[1 - \frac{V_{GS}}{V_P} \right]$$

$$\sqrt{\frac{I_D}{I_{DSS}}} = \left[1 - \frac{V_{GS}}{V_P} \right]$$

$$g_m = - \frac{\partial I_{DSS}}{\partial V_P} \sqrt{\frac{I_D}{I_{DSS}}}$$


$$g_m = \frac{2}{|V_P|} \sqrt{I_D - I_{DSS}}$$

Pinch off voltage:

$$V_P = \left| \frac{a^2 q N_A}{2e} \right| = \left| \frac{a^2 q N_D}{2e} \right|$$

↓
p channel

↓
n channel.

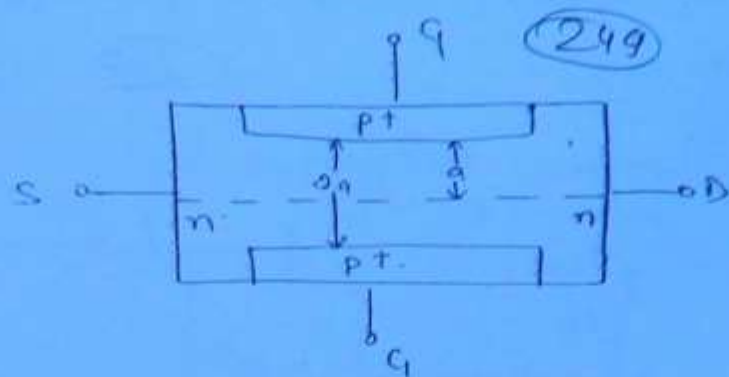

a = half channel height
 $2a$ = full channel height

Problems:-

Small S/g. Analysis of FET.

Low freq. Analysis



$$I_D = f(V_{GS}, V_{DS})$$

$$I_D = \frac{\partial I_D}{\partial V_{GS}} + \frac{\partial I_D}{\partial V_{DS}} \cdot V_{DS}$$


$$= g_m V_{GS} + \frac{V_{DS}}{r_d}$$

High freq. Analysis

Interelectrode Capacitance

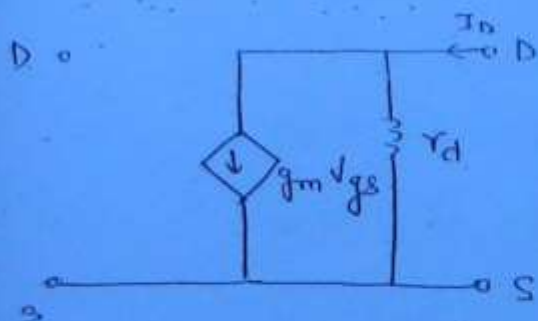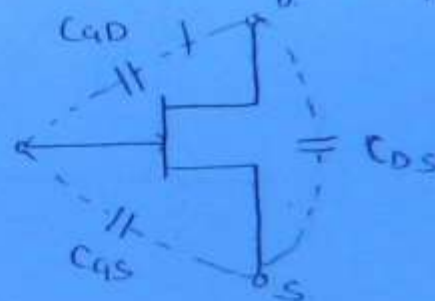

Low freq.

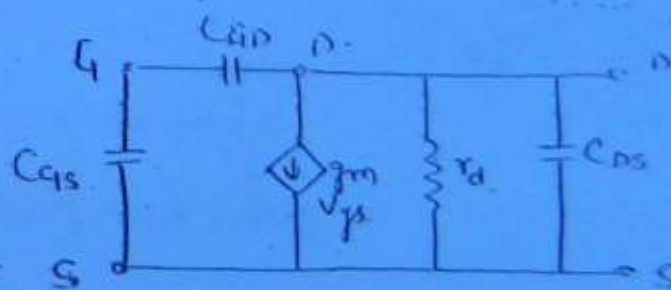



High freq.

Conclusion:-

- ⇒ Amp^r analysis should be done in mid band range therefore the high freq. model of FET when it is represented in the mid band range it converts


Like a low freq model. (All the Interelectrode Capacitances are open). (250)

Common Source Bypass Amplifier:

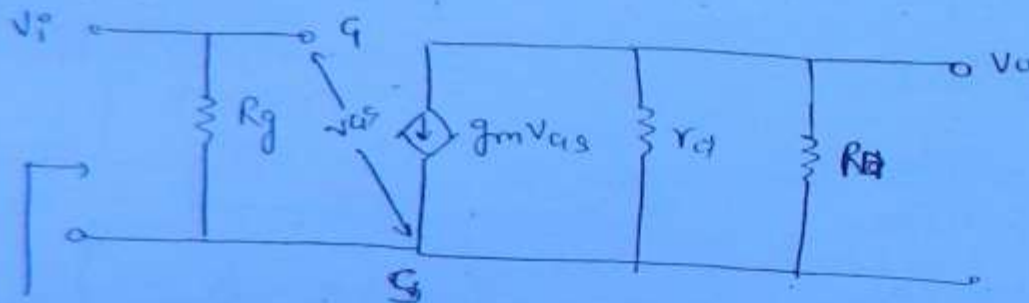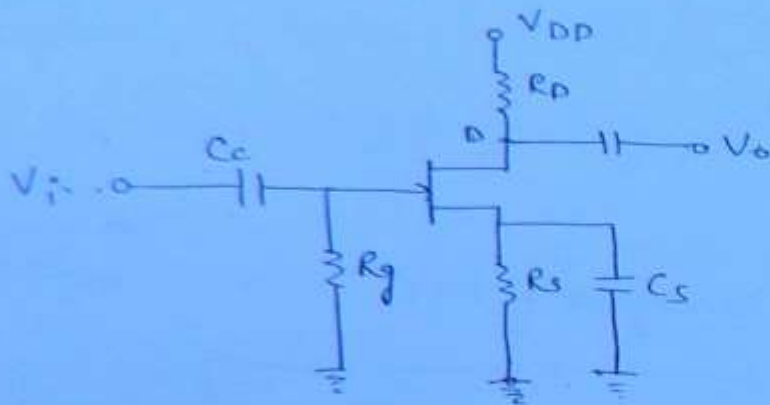

Z_o

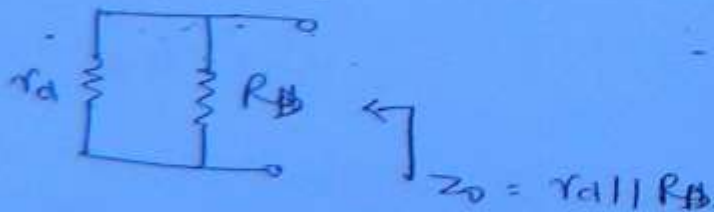$V_i = 0$
 $V_{gs} = 0$
 \downarrow
 $g_m V_{gs} = 0$ (open)





$$A_v = \frac{V_o}{V_i}$$

$$V_o = -g_m V_{gs} R_D \parallel R_L$$

$$\frac{V_o}{V_i} = -g_m R_D \parallel R_L$$

Common source amplifier circuit

(257)

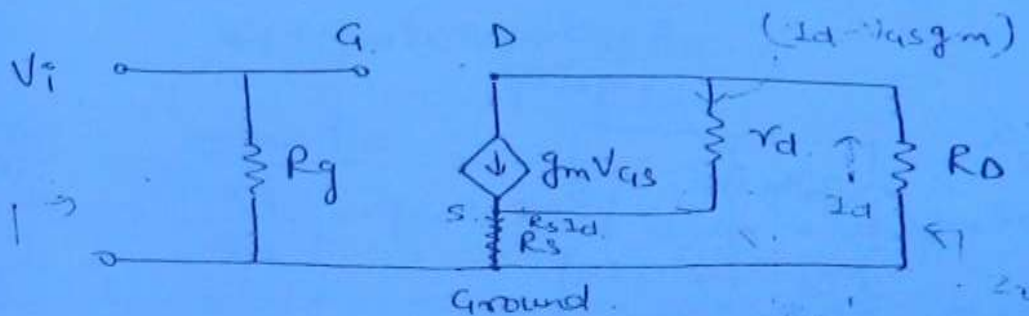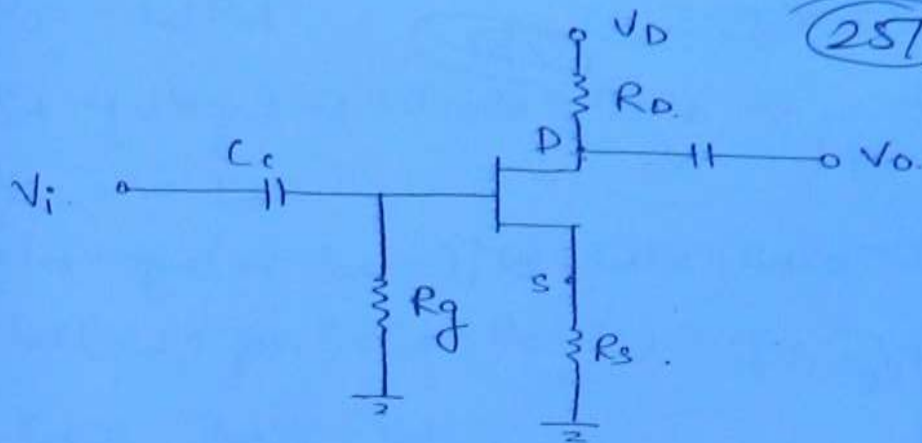

$$Z_i = R_g$$

$$Z_o =$$

$$V_i = V_{gs} + I_D R_s$$

$$V_i = 0$$

$$V_{gs} = -I_D R_s$$

$$V_o = (I_D - V_{gs} g_m) r_d + R_s I_D$$

$$V_o = \{ I_D - g_m (-I_D R_s) \} r_d + R_s I_D$$


$$= I_D (r_d + g_m R_s r_d + R_s)$$

$$Z_o' = \frac{V_o}{I_D} = r_d (1 + \mu) R_s$$


$$Z_o = Z_o' \parallel R_D$$

$$= \{ r_d (1 + \mu) R_s \} \parallel R_D$$

CS amplifier →

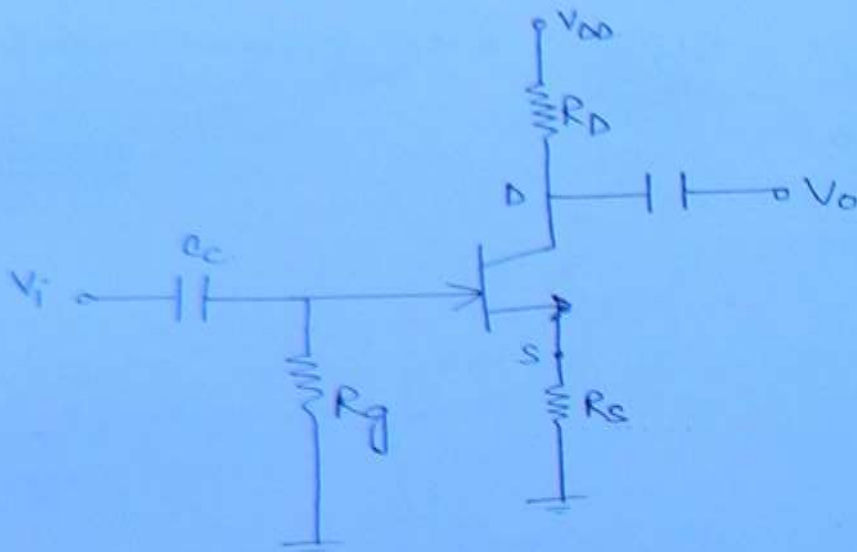

252

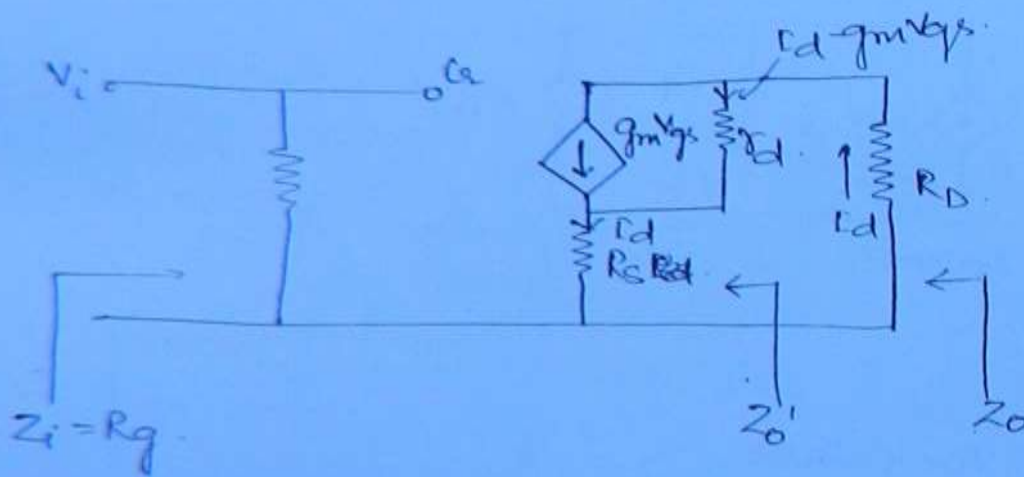

$Z_o \Rightarrow$

$$V_i = V_{gs} + I_D R_S$$

$$V_i = 0$$

$$V_{gs} = -I_D R_S$$

$$V_o = (I_D - g_m V_{gs}) r_d + I_D R_S$$

$$= \{ I_D - g_m (-I_D R_S) \} r_d + I_D R_S$$

$$= I_D \{ r_d + R_m R_S r_d \} + R_S$$

$$Z_o' = \frac{V_o}{I_D} = r_d + (1 + \mu) R_S$$

$$Z_o = Z_o' \parallel R_D$$

$$A_v =$$

$$V_o = -I_d R_d$$

(253)

$$(I_d - g_m V_{gs}) r_d + I_d R_s + I_d R_d = 0$$

$$V_{gs} = V_i - I_d R_s$$

$$\{I_d - g_m (V_i - I_d R_s)\} r_d + I_d R_s + I_d R_d = 0$$

$$\Rightarrow I_d (r_d + g_m R_s r_d + R_s + R_d) = g_m V_i r_d$$



$$\Rightarrow I_d = \frac{g_m V_i + V_d}{r_d + g_m R_s r_d + R_s + R_d}$$


$$\frac{V_o}{V_i} = \frac{-g_m R_d}{\frac{r_d}{r_d} + g_m R_s \frac{r_d}{r_d} + \frac{R_s + R_d}{r_d}} \leftarrow \text{neglected}$$

$$r_d \gg R_s + R_d$$

$$A_v = \frac{-g_m R_d}{1 + g_m R_s}$$

Common drain amplifiers :-

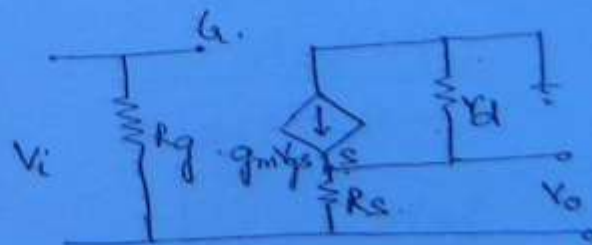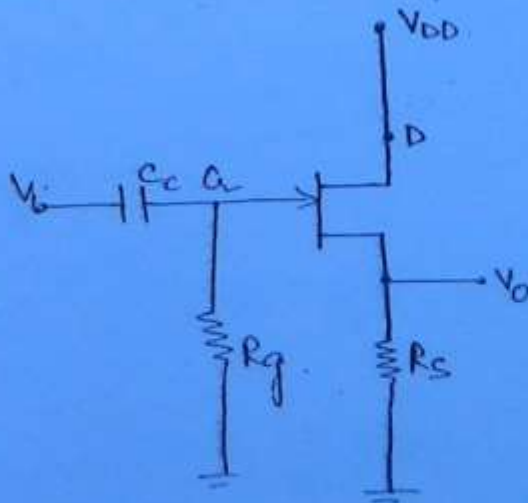

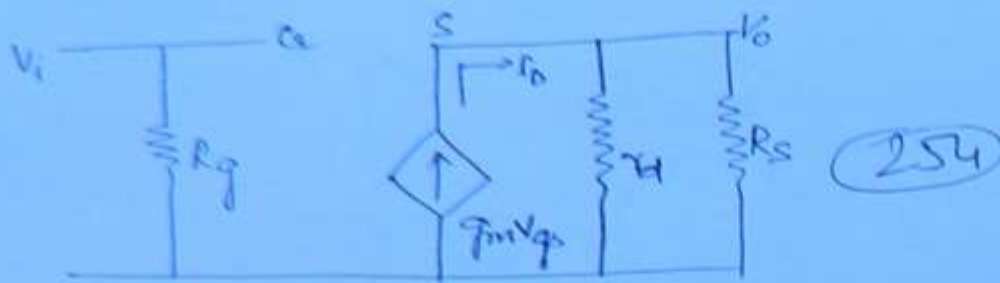

$$1) Z_i = R_g$$

$$2) Z_o :-$$

$$V_i = -V_{gs} + V_o$$

$$\Rightarrow V_i + V_{gs} = V_o$$

$$\text{If } V_i = 0$$

$$V_{gs} = V_o$$

source is at higher potential than gain.

$$I_d = g_m V_{gs} \xrightarrow{V_o}$$

$$Z_o' = \frac{V_o}{I_d} = \frac{1}{g_m}$$

$$Z_o = Z_o' \parallel R_s$$

$$= \frac{1}{g_m} \parallel R_s$$

$$A_v = \frac{V_o}{V_i}$$

$$V_o = -g_m V_{gs} R_D \parallel R_s$$


$$V_i = -V_{gs} + V_o$$

$$= -V_{gs} - g_m V_{gs} R_D \parallel R_s$$

$$\frac{V_o}{V_i} = \frac{-g_m V_{gs} R_s}{-V_{gs} (1 + g_m R_s)}$$

$$A_v = \frac{g_m R_s}{1 + g_m R_s}$$

Common gate amplifier

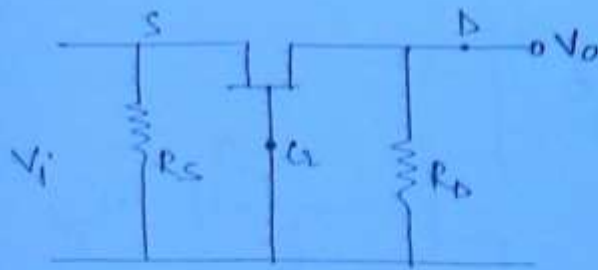


(255)

$$R_i = \frac{1}{g_m} \parallel R_s$$

$$R_o = R_d \parallel r_d$$

~~R_o~~

$$A_v = g_m R_d$$

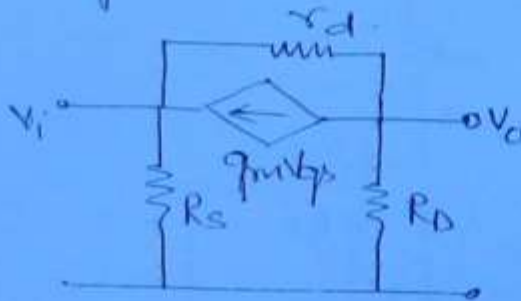

Conclusion →

	R_i	R_o	A_v
CS by pass	R_g	$r_d \parallel R_d$	$-g_m R_d$
CS Unbypass	R_g	$r_d + (1 + \mu) R_d \parallel R_d$	$\frac{-g_m R_d}{1 + g_m R_g}$
CD	R_g	$\frac{1}{g_m} \parallel R_s$	$\frac{g_m R_s}{1 + g_m R_s}$
CC	$\frac{1}{g_m} \parallel R_s$	$r_d \parallel R_d$	$g_m R_d$

FET Biasing →

Condition


1) $I_{G} = 0$

2) $I_D = I_S$

3) $I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$

256

Fixed Bias

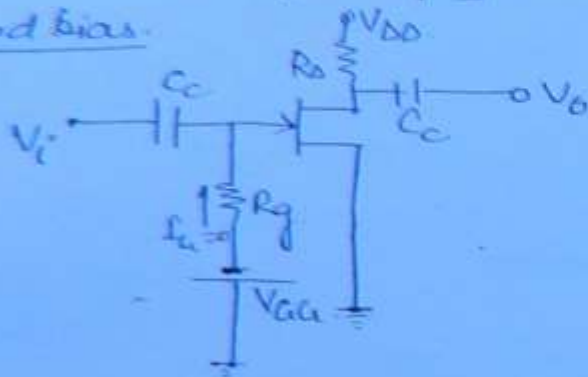

Calculate

$$(V_{GS})_Q = -V_{GS}$$



$$(I_D)_Q = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$

$$V_{DS} = V_{DD} - I_D R_D$$


$$V_D = V_{DS}$$

$$V_S = 0$$


$$V_G = -V_{GS}$$

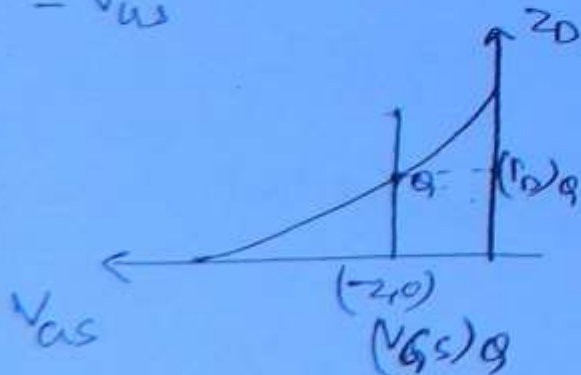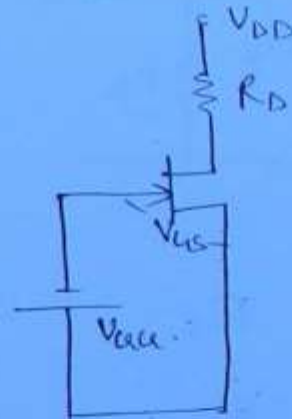

Self bias -

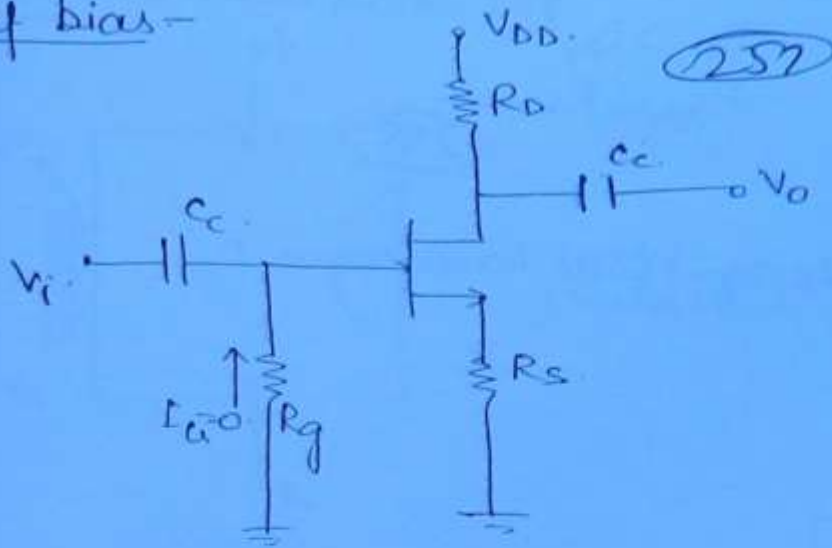


$$V_{GS} = -I_D R_S$$

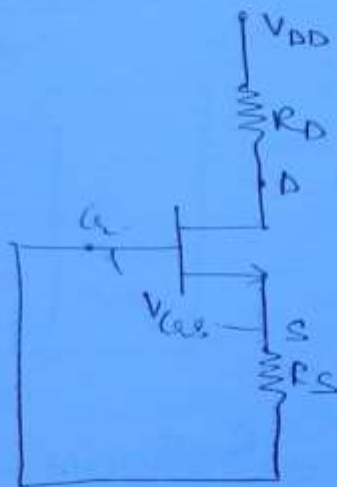

$$\left. \begin{array}{l} V_{GS} = -1V \\ R_S = 1K\Omega \end{array} \right\} I_D = 1mA$$
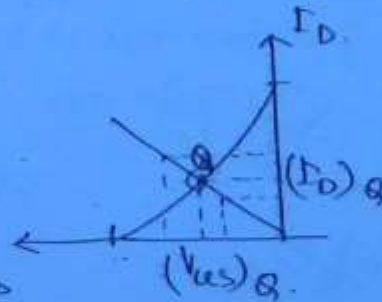
$$\left. \begin{array}{l} V_{GS} = -2V \\ R_S = 1K\Omega \end{array} \right\} I_D = 2mA$$




$$(I_D)_Q = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right] \quad V_{GS} = -I_D R_S$$

$$(V_{GS})_Q = (I_D)_Q R_S$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$
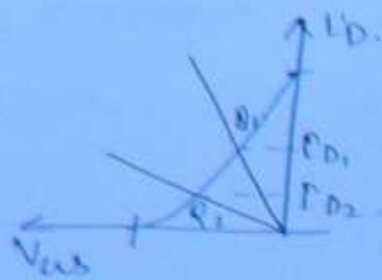
$$V_D = V_{DD} - I_D R_D, \quad V_S = I_D R_S$$



$$I_{D1} > I_{D2}$$


$$R_{S1} < R_{S2}$$

(258)

Q. which transistor design will have more R_S .

Ans. $R_{S2} \rightarrow Q_2$

Voltage divider

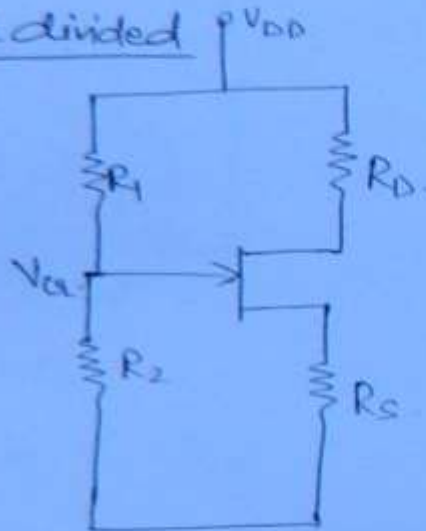

$$V_{GS} = V_{DD} + I_D R_S$$

$$V_{GS} = V_{GS} - I_D R_S$$

$$V_{GS} = 0, \quad I_D = 0$$

$$I_D = \frac{V_{GS}}{R_S}$$

$$I_D = 0$$

$$V_{GS} = V_{GS}$$


$$(I_D)_Q = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$

$$(V_{GS})_Q = V_{GS} - (I_D)_Q R_S$$


$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$V_D = V_{DD} - I_D R_D$$


$$V_S = I_D R_S$$

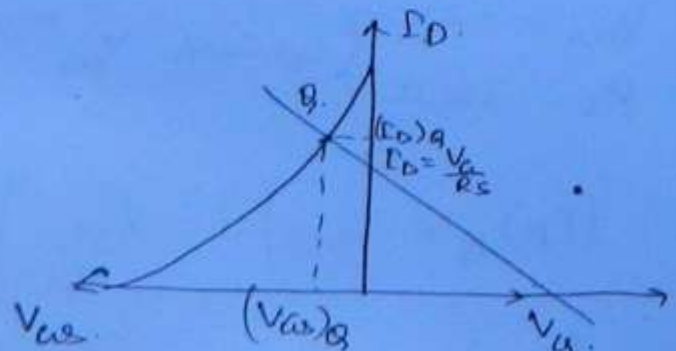


MOSFET \rightarrow Metal oxide FET.

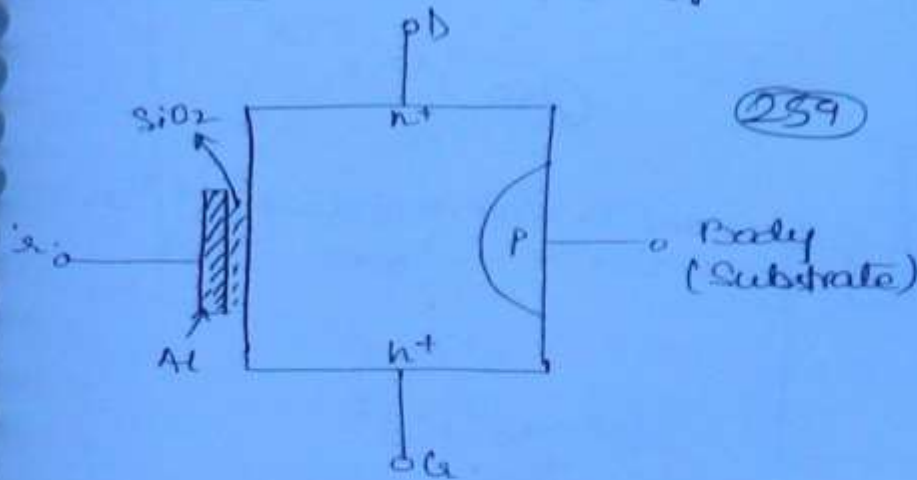

Depletion MOSFET \rightarrow

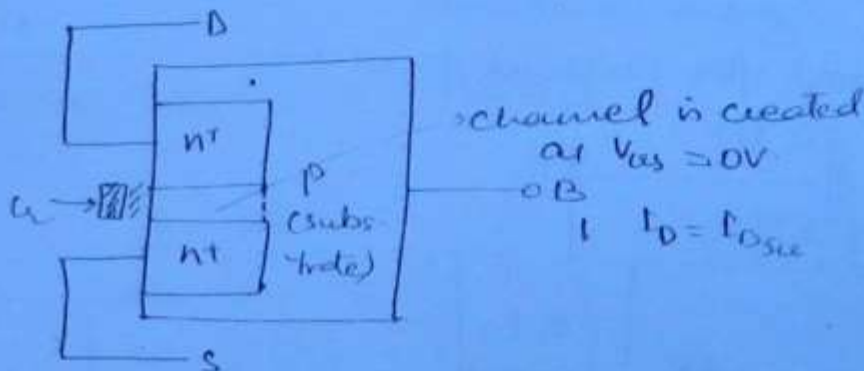

Enhancement MOSFET \rightarrow

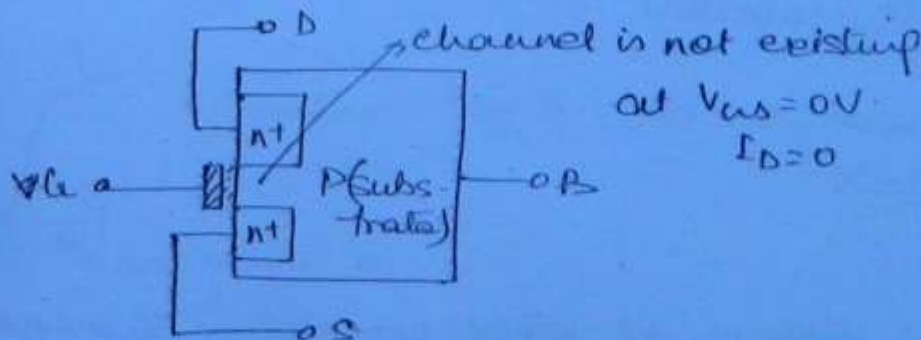

1) Depletion MOSFET analysis is same as FET analysis because channel is max. at $V_{gs} = 0V$.

2) In enhancement MOSFET channel is not existing at $V_{gs} = 0V$, $I_D = 0$.


3) To analyse the MOSFET we always consider enhancement mode (ON state)

N channel enhancement MOSFET analysis

Case 1 →


When $V_{GS} = 0V$.

(260)

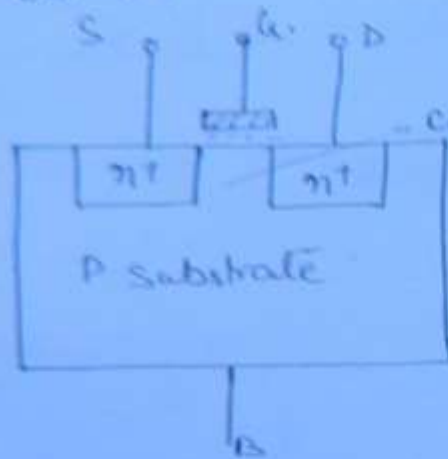

Case 2

Creating a channel for current flow:—

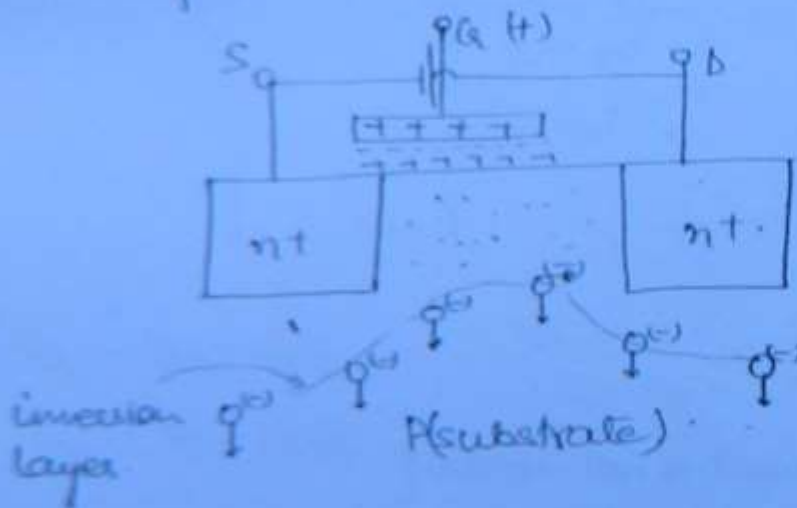

V_T → threshold voltage = 0.5
= Gate Voltage.


Threshold Voltage →

- It is the min V_{GS} Voltage at which conducting channel will be formed.
- Practically it lies b/w 0.5 to 1 V.

Case 3

Small V_{GS} (mV)

$V_{DS} < V_D$

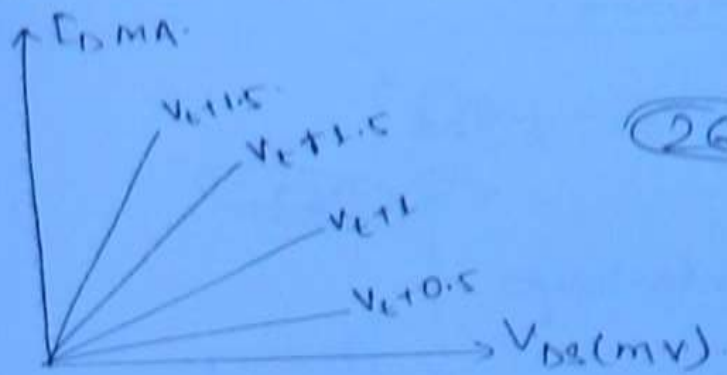

(261)



$$V_{DS} \propto I_D$$

$$I_D \propto (V_{GS} - V_T)$$

effective voltage
or
overdrive voltage.

Case 4.

large V_{DS} (V) is applied.

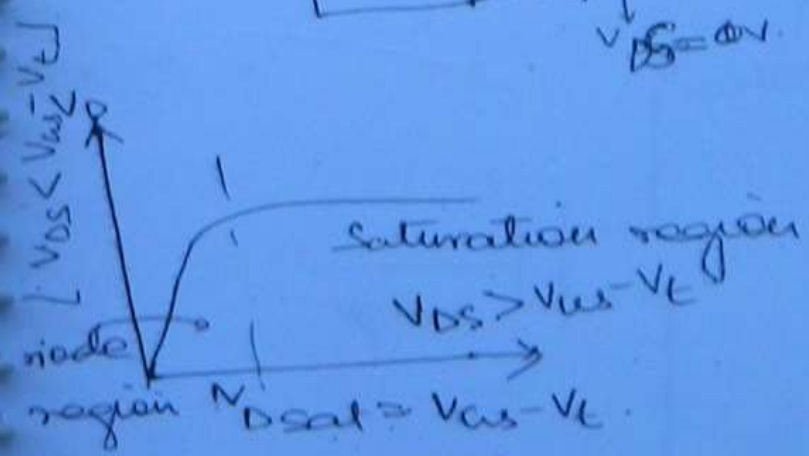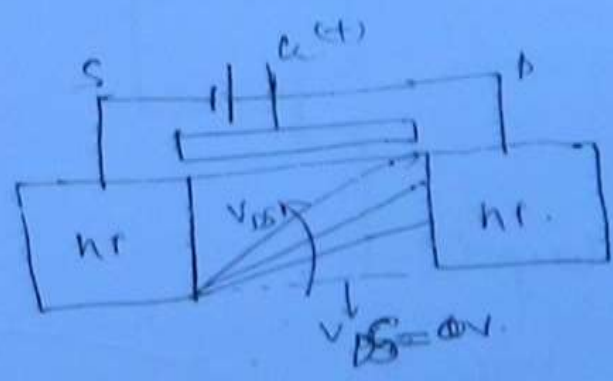

$$V_{DS} < V_{GS} - V_T$$


VI characteristics eq- of MOSFET.

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left\{ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right\}$$

$\mu_n \rightarrow$ mobility of e^-

$C_{ox} \rightarrow$ capacitance of oxide layer.

262

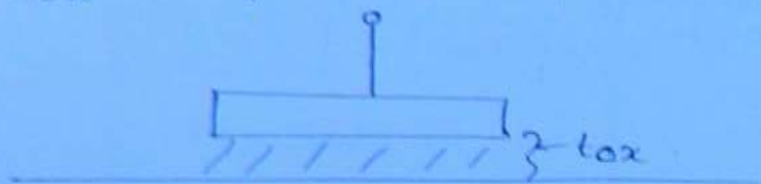

$$C_{ox} = \frac{C_{ox}}{t_{ox}}$$

$C_{ox} \rightarrow$ permittivity of oxide layer.

$$\epsilon_{ox} \rightarrow 3.9 \epsilon_0$$

$$\epsilon_0 \rightarrow 8.85 \times 10^{-12} \text{ F/m}$$

$$\begin{aligned} \epsilon_{ox} &\rightarrow 3.9 \times 8.85 \times 10^{-12} \\ &= 3.45 \times 10^{-11} \text{ F/m} \end{aligned}$$

$t_{ox} \rightarrow$ thickness of oxide layer.

$\frac{W}{L} \rightarrow$ aspect ratio

$V_{GS} - V_t \rightarrow$ effective voltage
'or'
overdrive voltage.

Triode region \rightarrow

$$V_{GS} \geq V_t$$

$$V_{DS} < V_{GS} - V_t$$

$$I_D = \underbrace{\mu_n C_{ox} \left(\frac{W}{L} \right)}_{k_n'} \{ (V_{GS} - V_t) V_{DS} \}$$


Saturation region \rightarrow

$$V_{GS} \geq V_t$$


$$V_{DS} \geq V_{GS} - V_t$$

$$\begin{aligned} V_{Dsat} &= V_{GS} - V_t \quad \uparrow k_n' \\ I_D &= \frac{1}{2} \mu_n \epsilon_0 C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2 \end{aligned}$$


CKT-1. →

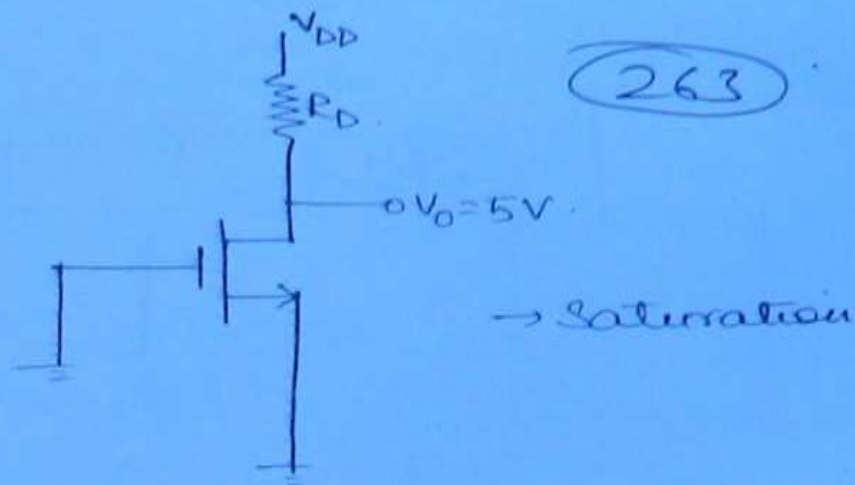


CKT2 →

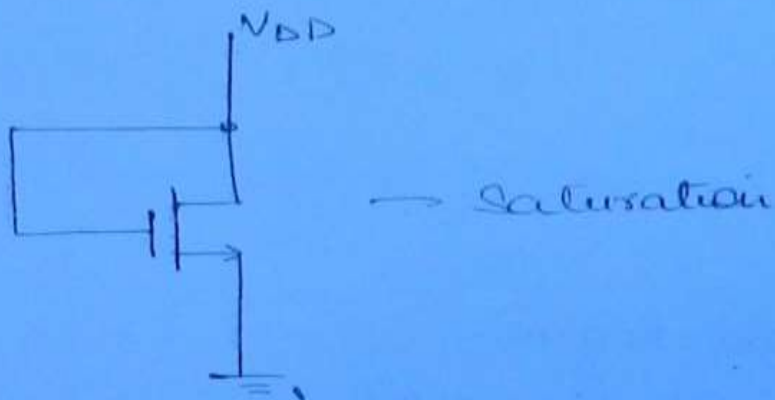

CKT3 →

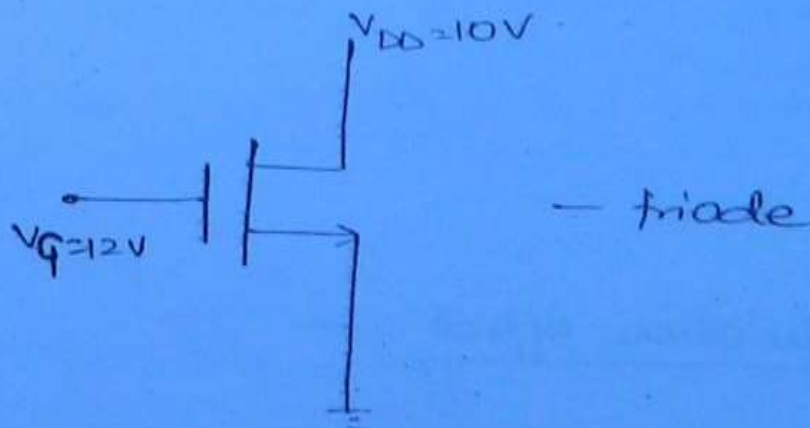

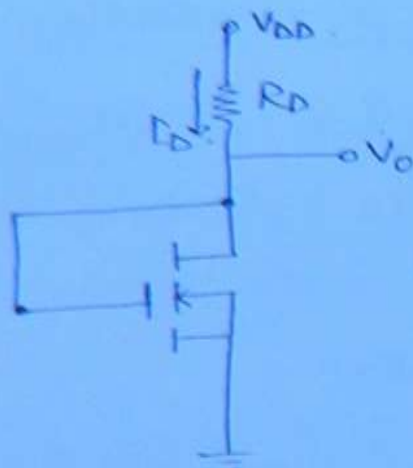$V_D > V_{ce}$
 $V_D > V_{ce}$ } → Saturation
 $V_D < V_{ce}$ } → triode



264

Given data →

$$I_{D1}$$

Cal. V_o and R_d

$$\left(\frac{W}{L}\right)$$

$$\mu_n$$

$$C_{ox}$$

$$\lambda = 0$$


This is in Saturation Region.

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_t)^2$$


$$V_{GS} = V_o$$

$$R_D = \frac{V_{DD} - V_o}{I_D}$$

Channel length modulation effect : —

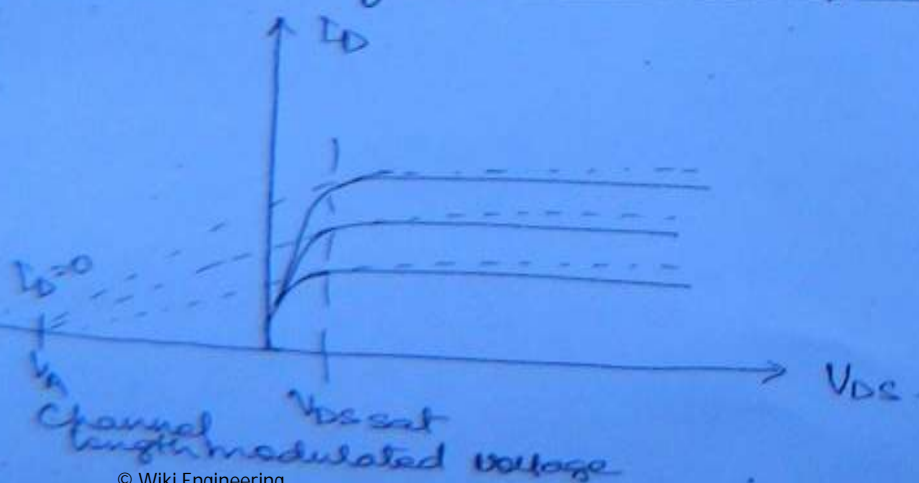
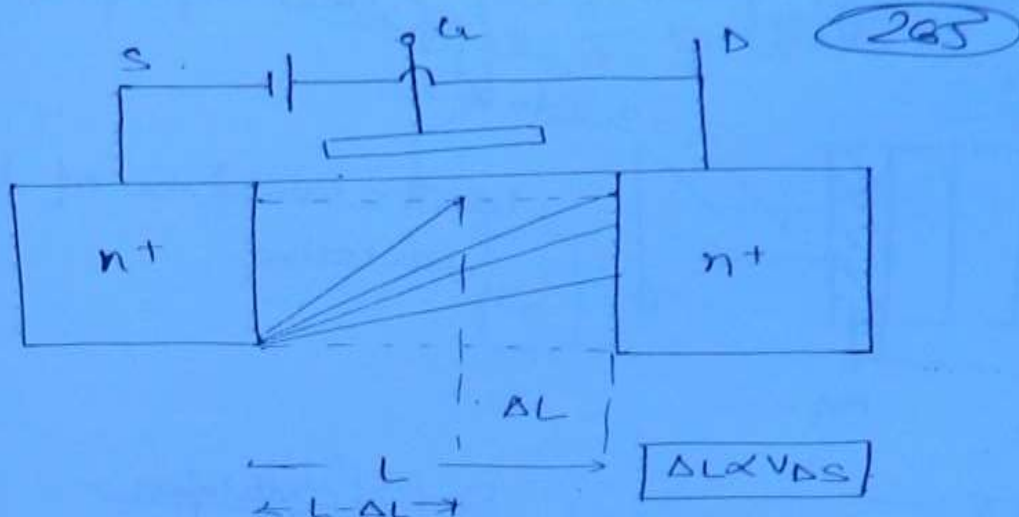
$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$



$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L - \Delta L} \right) (V_{GS} - V_t)^2$$

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[1 + \frac{\Delta L}{L} \right] (V_{GS} - V_t)^2$$

$$\Delta L \propto V_{DS}$$

$$\downarrow \lambda'$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \left[1 + \left(\frac{\lambda'}{L} \right) V_{DS} \right] (V_{GS} - V_t)^2$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

for $I_D = 0$

$$1 + \lambda V_{DS} = 0$$

$$V_{DS} = -\frac{1}{\lambda} = V_A$$

$$|V_A| = \frac{1}{\lambda}$$


$$\lambda = 0, V_A = \infty$$

$$I_D = k_n (V_{GS} - V_t)^2 \left(1 + \frac{V_{DS}}{V_A} \right)$$

Power amplifier :-


PAS → Public addressing System.

(266)

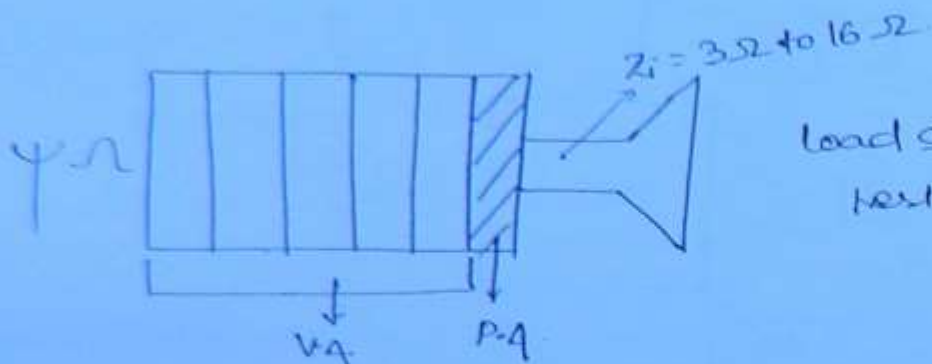


load should be of less resistance.

Voltage amplifier :-

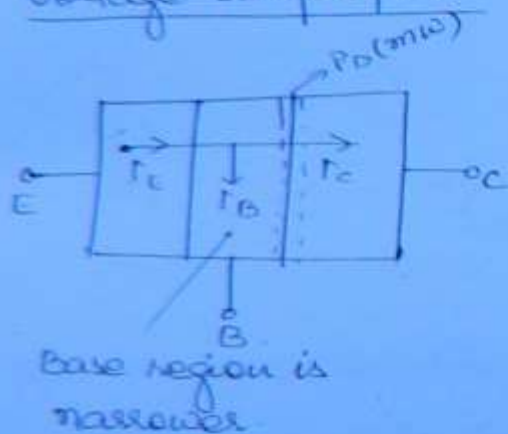

$$\beta = \frac{I_C}{I_B}$$

Power amplifier :-

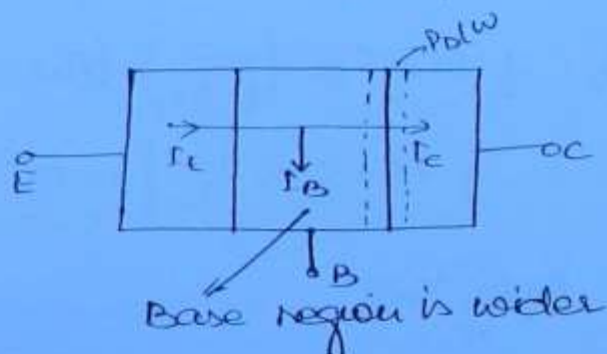

$$\beta = \frac{I_C}{I_B}$$



Diff. b/w power ampifier amplifier and Voltage amplifier :-

Parameter	V. A.	P. A.
1) β	more	less
2) R_c	more	less
3) V_{in}	Small	large
4) P_o	less	more
5) I_C	less	more
6) coupling		

Resistive coupling
is used.



Inductive or
X-over coupling
is used.

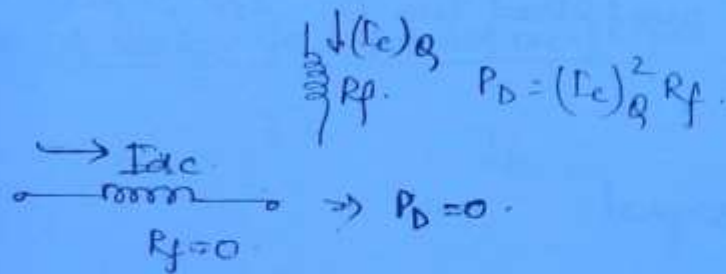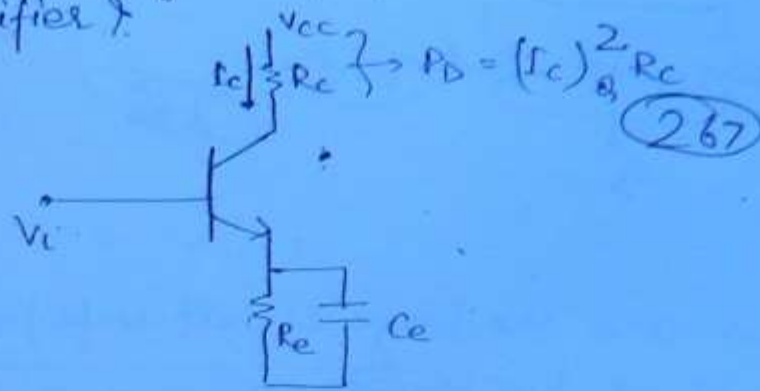Q. Why a Voltage amplifier can not be used as a power amplifier?




For power amplifier, power dissipation should be negligible. So, in case of resistive load inductive load is preferred.

Power diagram analysis —

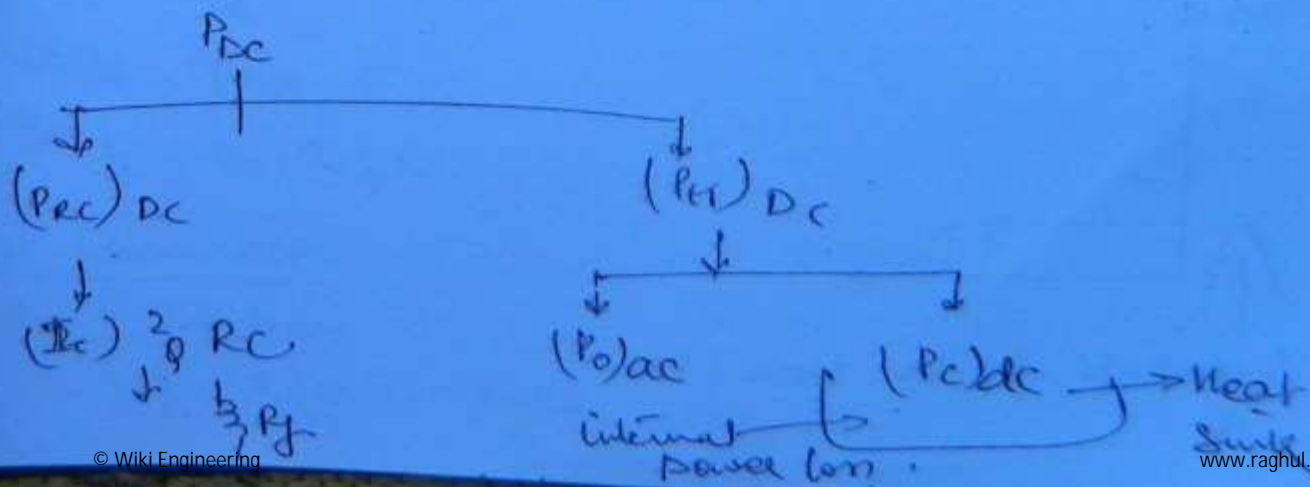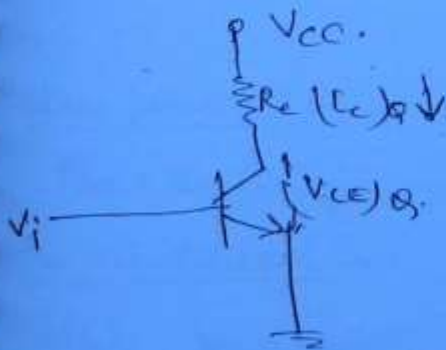

$$P_{DC} = P_{AC} + P_{Losses}$$

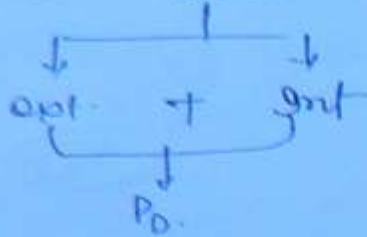

268


Definitions:—

- Power amplifiers are the large signal amplifiers which rises the power level of the signals.
- It is a device which converts dc power into ac power and whose action is controlled by ac I/P signal.


Classes →

Class A →

I_C conducts for 360° of I/P signal.

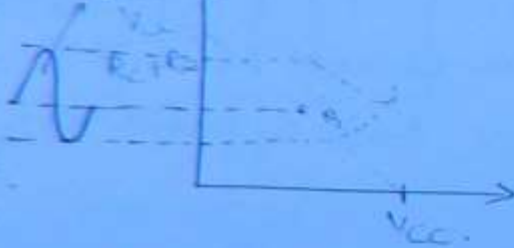

Class B →

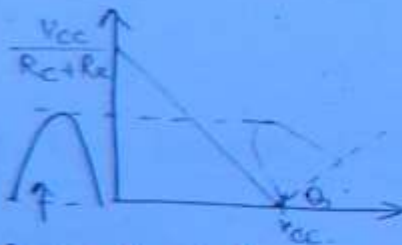


I_C conducts for 180° of I/P.

Class C



I_C conducts for less than 180°

Class AB

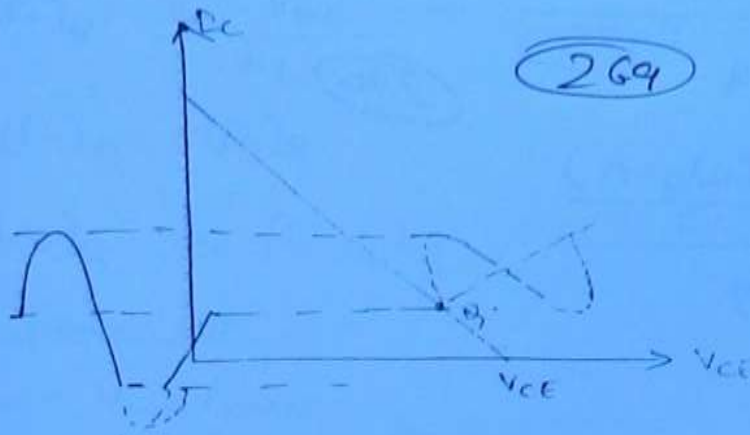

Class A series fed power amplifier:—



DC power I/P \rightarrow

$$P_{DC} = V_{CC}(I_C)_Q$$

DC conditions \rightarrow

$$(I_B)_Q = \frac{V_{CC} - V_{BE}}{R_b}$$

$$(I_C)_Q = \beta(I_B)_Q$$

$$(V_{CE})_Q = V_{CC} - (I_C)_Q R_c$$

ac power o/p.


$$P_{ac} = V_{rms} I_{rms}$$

$$= \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}} = \frac{V_m I_m}{2}$$


$$\frac{P_{ac}}{P_{dc}} = \frac{\frac{1}{2} \left(\frac{V_{max} - V_{min}}{2} \right) \left(\frac{I_{max} - I_{min}}{2} \right)}{V_{cc}(I_c)_Q} \quad (270)$$

$$= \frac{\frac{1}{2} \left(\frac{V_{cc} - 0}{2} \right) \left(\frac{2(I_c)_Q - 0}{2} \right)}{V_{cc}(I_c)_Q}$$

$$= \frac{1}{4} = 25\%$$

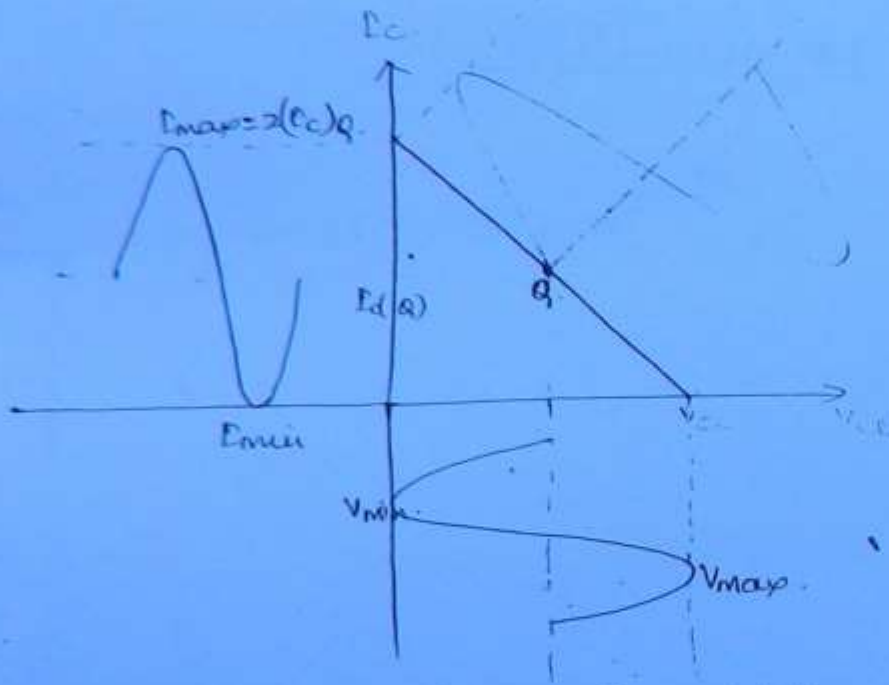

class A x-mec coupled power amplifier :-

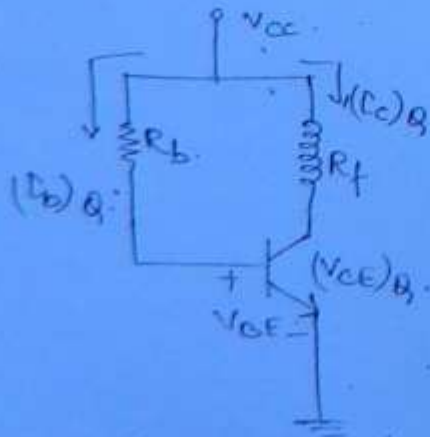

$$\begin{aligned} &\rightarrow E_{dc} \\ &\text{---} \\ &R_L = 0 \end{aligned}$$

Dc power I/P →

$$P_{dc} = (V_{cc})(I_c)_Q$$

Dc condition →

$$(I_B)_Q = \frac{V_{CC} - V_{BE}}{R_B}$$

(271)

$$(I_C)_Q = \beta (I_B)_Q$$

$$(V_{CE})_Q = V_{CC} - (I_C)_Q R_f$$

ac power O/P →


$$P_{ac} = V_{rms} I_{rms}$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

$$= \frac{V_m I_m}{2}$$

$$\frac{P_{ac}}{P_{dc}} = \frac{\frac{1}{2} (V_{max} - V_{min}) (I_{max} - I_{min})}{V_{CC} (I_C)_Q}$$

$$= \frac{1}{2} = 50\%$$

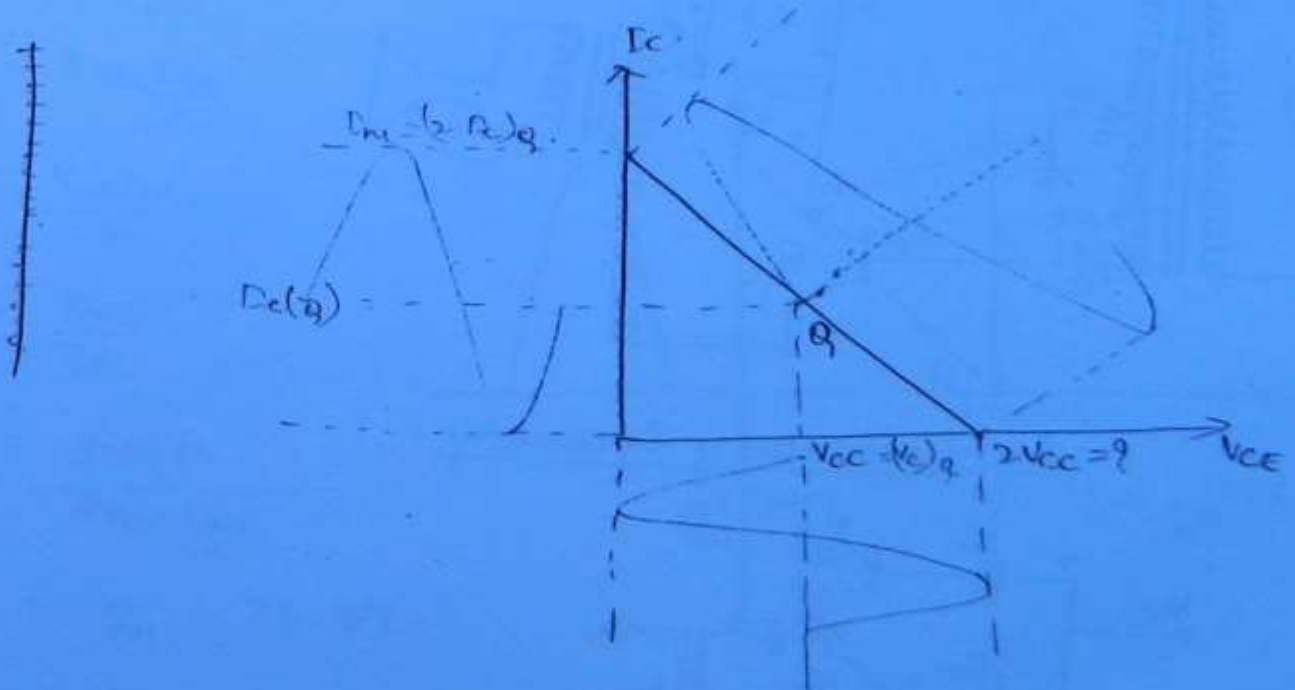

$$P_{DC} = P_{AC} + P_D$$

$$P_D = P_{DC} - P_{AC}$$

$$= V_{CC}(I_C) - \frac{V_m I_m}{2}$$

(272)

At zero signal conditions :-

$$V_m = 0, I_m = 0$$

$$P_D = P_{DC}$$

When signal is applied,


$$P_D = V_{CC}(I_C) - \frac{V_m I_m}{2}$$




P_D decreases.

Class B Power amplifier :-


- pushpull amplifier.

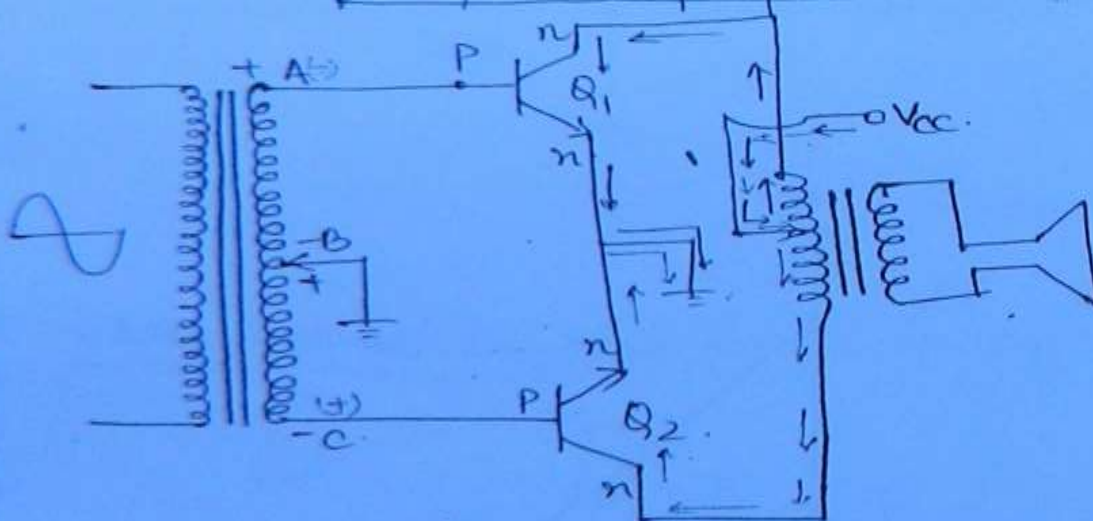

- Complementary Symmetry →

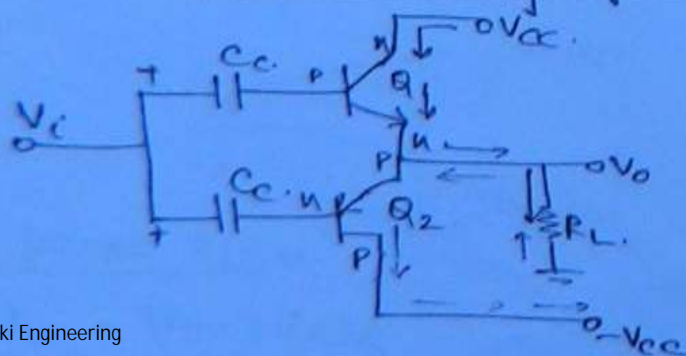


Block diagram →

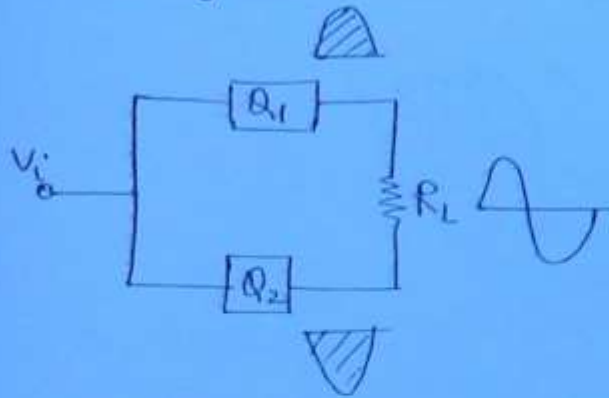

(223)

Efficiency cal. in a class B :-

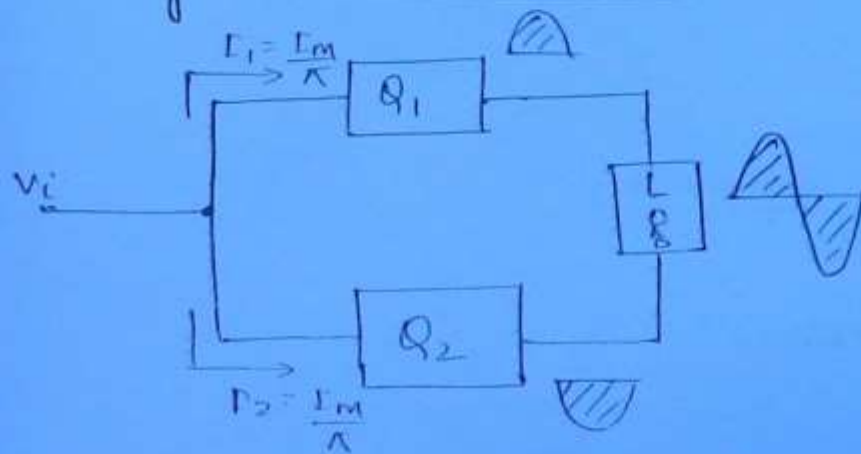

$$P_{DC} = V_{CC} I_{DC}$$


$$= 2 V_{CC} \frac{I_m}{\pi}$$

$$P_{AC} = \frac{V_m I_m}{2}$$

$$\% \eta = \frac{P_{AC}}{P_{DC}}$$

$$= \frac{\frac{V_m I_m}{2}}{2 V_{CC} \frac{I_m}{\pi}}$$

$$= \eta_4 = 78.5\%$$

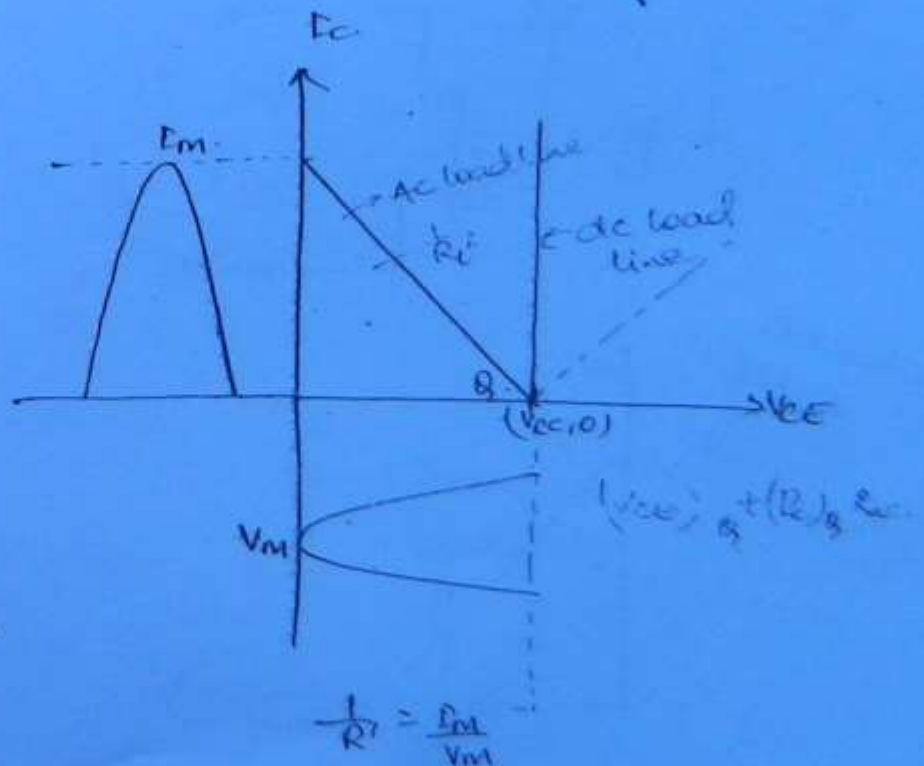

Power dissipation in class B

$$P_D = P_{DC} - P_{AC}$$


$$= \frac{2V_{CC}I_m}{\pi} - \frac{V_m I_m}{2}$$

(274)


At 0 signal conditions

$$P_D = 0$$


Cross over distortion :-

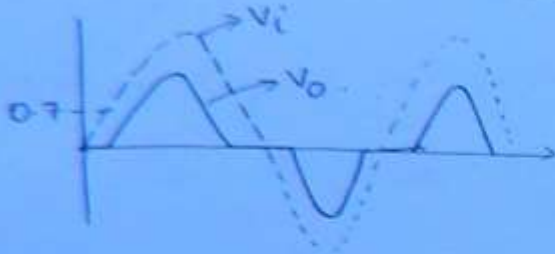

Class B complementary Symmetry :-

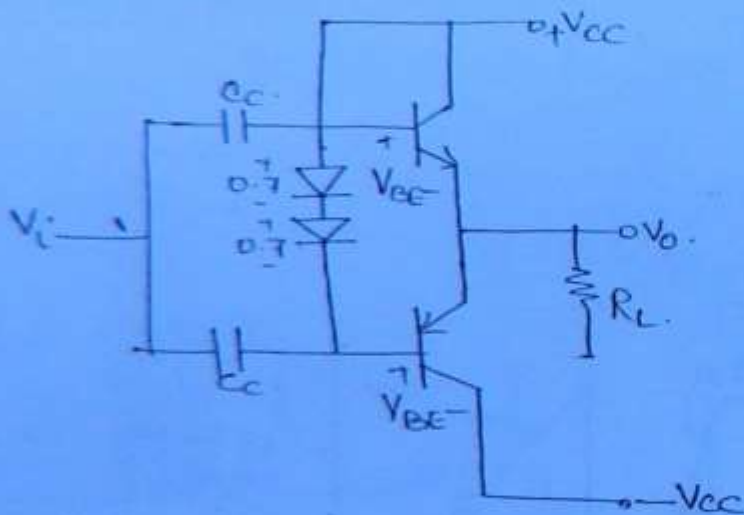

Class AB Amplifier

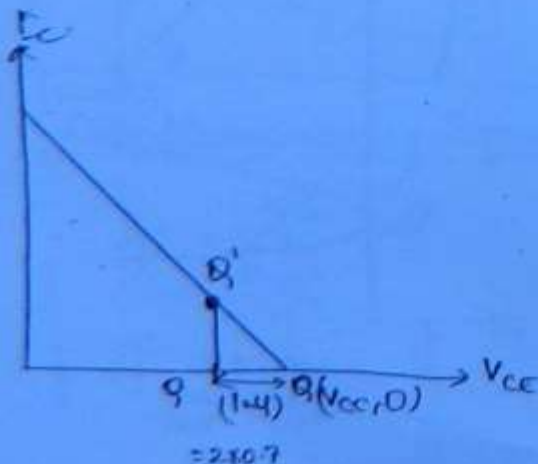




$$= 2 \times 0.7$$

$$(V_{CC} - 1.4)$$

if 1 transistor is there then $(V_{CC} - 0.7)$

LC power amp \rightarrow

225

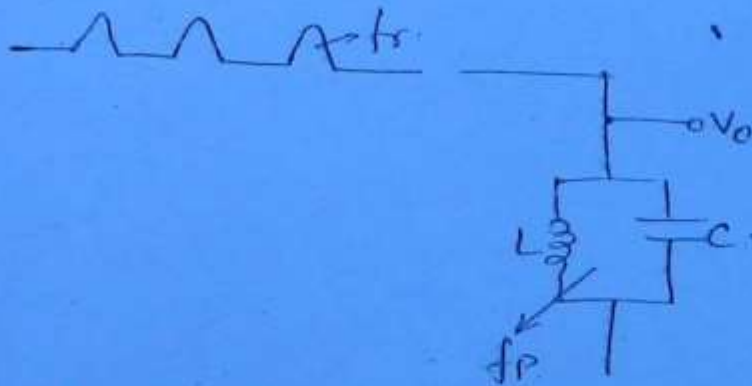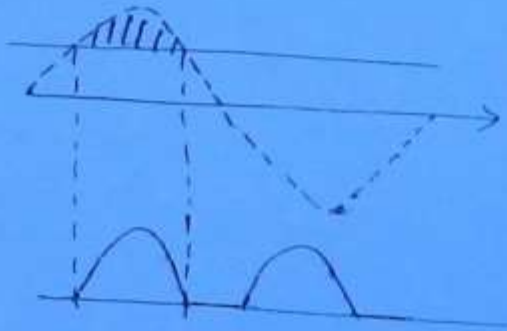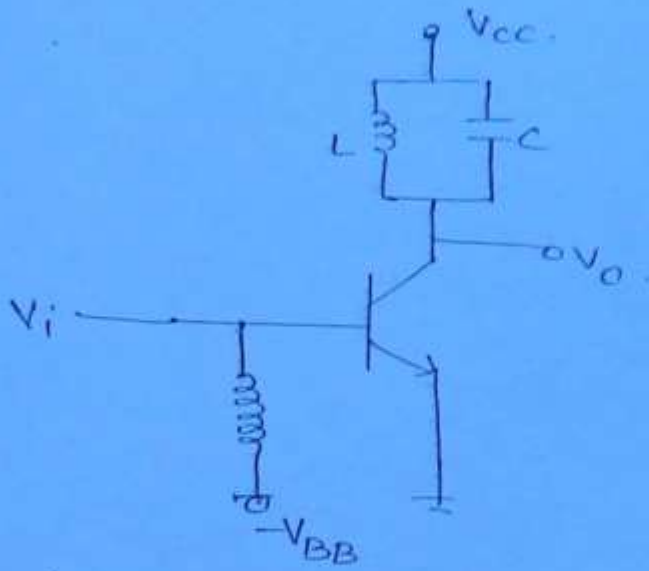

$\rightarrow f_r = f_p$
 $f_r \neq f_p$

} \rightarrow tunner amplifiers.

